

Lab 2
HW 3

Midterm 1: 2 weeks from today, in class


Single pole systems

gain vs. freq
transient step response



or

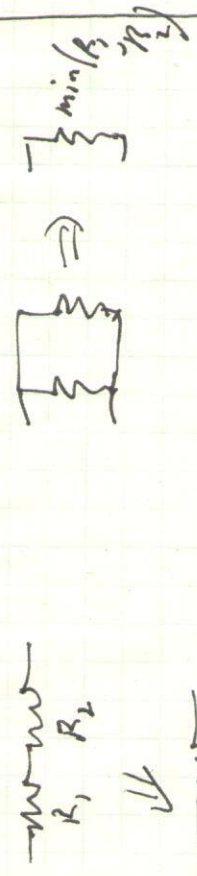
$$v_o = i_x \frac{1}{sC} = i_x \frac{1}{j\omega C}$$




worst case error: ± 1



Max(R_1, R_2)

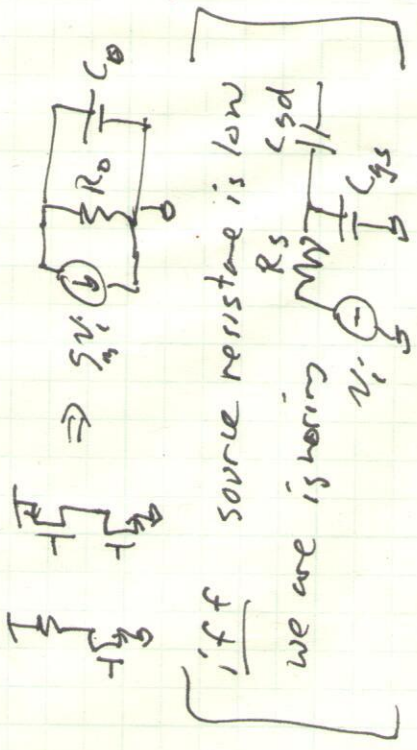Last time: lots of things look like single pole amps



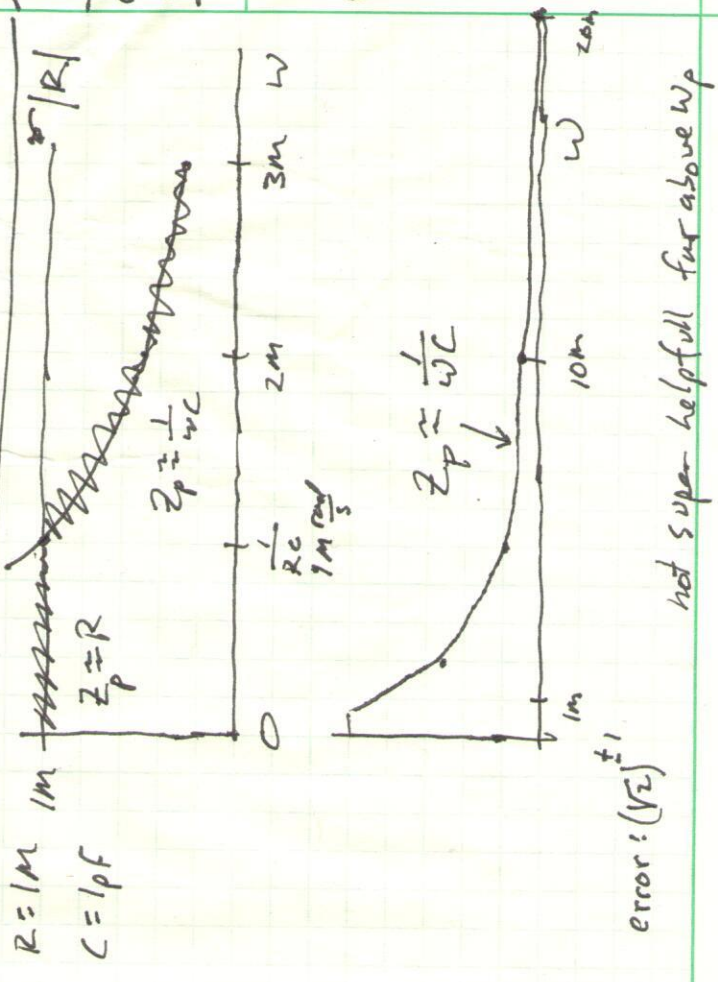so $\frac{v_o}{v_i} = H(s) = \frac{-g_m R_o}{1 + s/\omega_p}$ $\omega_p = \frac{1}{R_o C_o}$



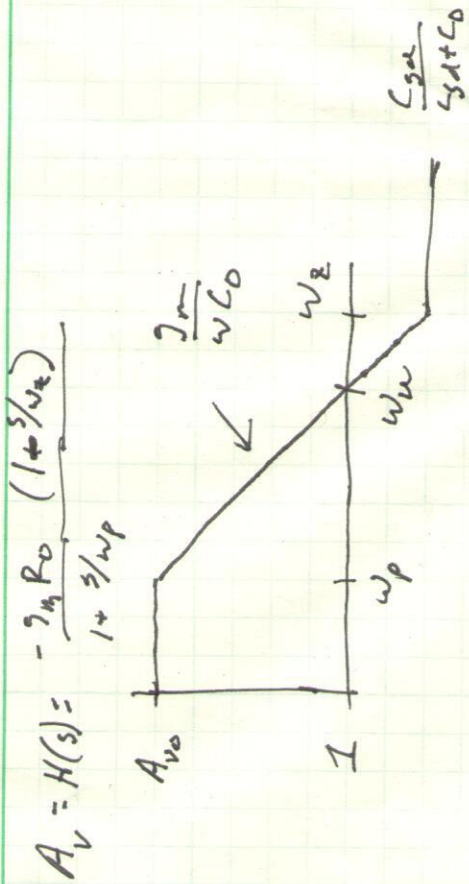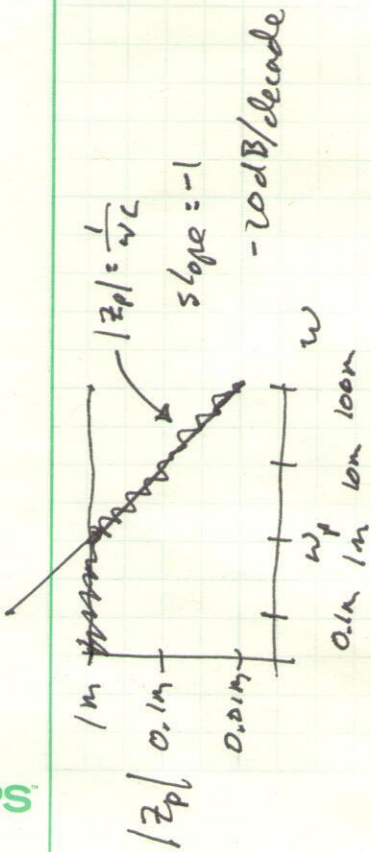


$$|H(j\omega_w)| = 1 \text{ unity gain}$$

$$\left| \frac{g_m R_o}{1 + j\omega/w_p} \right| = \left| \frac{g_m R_o}{w R_o C_o} \right| = \frac{g_m}{w C_o}$$

$$\frac{g_m}{w C_o} = 1 \Rightarrow w = \frac{g_m}{C_o}$$

$$w_w = A_{v0} w_p$$

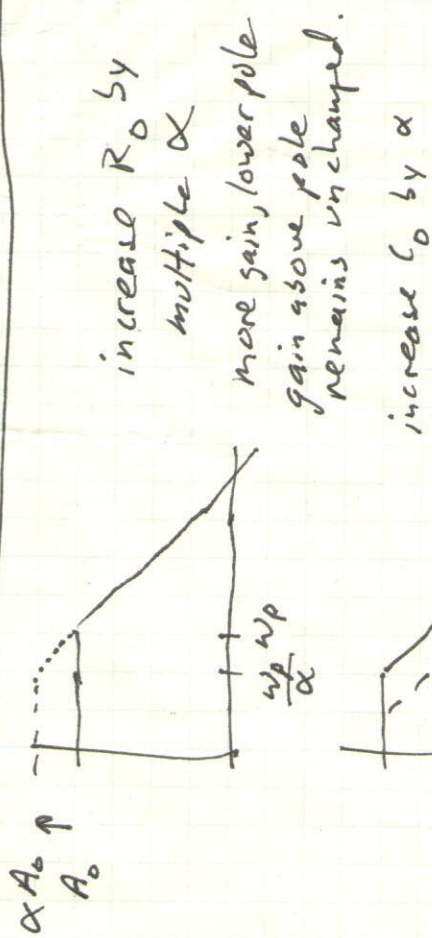$w_w = \frac{g_m}{C_o}$
$w_p = \frac{1}{R_o C_o}$
$ A_{v0} = g_m R_o$



increase g_m by α
 w_p unchanged.
 more gain, more BW good!

EX:

I_m	R_D	C_0	A_{vo}	ω_p	ω_u
$1m5$	$1M\Omega$	$1pF$	10^3	10^6	10^9
		$1pF$	10^3	10^9	10^9

low freq gain is 100. Unity gain is 10^6
 $\omega_p = ?$ gain is 10^5 10^7 10^{10} ?
 500k?

when $\omega_p \ll \omega_u$ $A_v(j\omega) = \frac{\omega_u}{\omega}$

best case, $I_D \geq n V_{TH} g_m = n V_{TH} \omega_u C_0$
 why do anything other than "best case"?

Need to determine region of operation and $SUB-V_t$ correct.


Rough estimate is that $SUB-V_t$ and inversion currents are equal at $V_{OV} = V_{GS} - V_t = 10mV$ and quadratic model looks good above $100mV$

Knowing ω_u and C_0 puts a lower bound on current.

$\omega_u = \frac{g_m}{C_0}$ $g_m = \omega_u C_0$

- $I_m = \left\{ \begin{array}{l} \frac{I_C}{V_{TH}} \\ \frac{I_D}{n V_{TH}} \\ \frac{I_D}{V_{OV}} \\ \frac{I_D}{V_{OV}} \end{array} \right.$
- Bipolar
 - MOS $SUB-V_t$
 - MOS quadratic
 - MOS s.c.l.

Step response

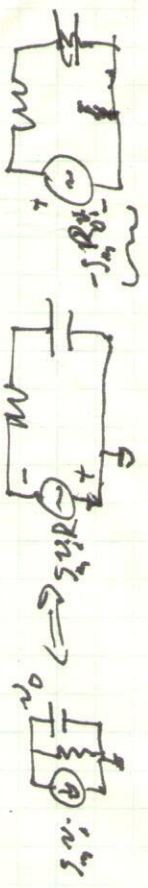

$\frac{dV}{dt} = \frac{i_c}{C}$ $i_c = \frac{v_t}{R}$ $v_r = (v_i - v_o)$
 $\frac{dV}{dt} = \frac{v_i - v_o}{RC} = \frac{v_i - v_o}{\tau}$

