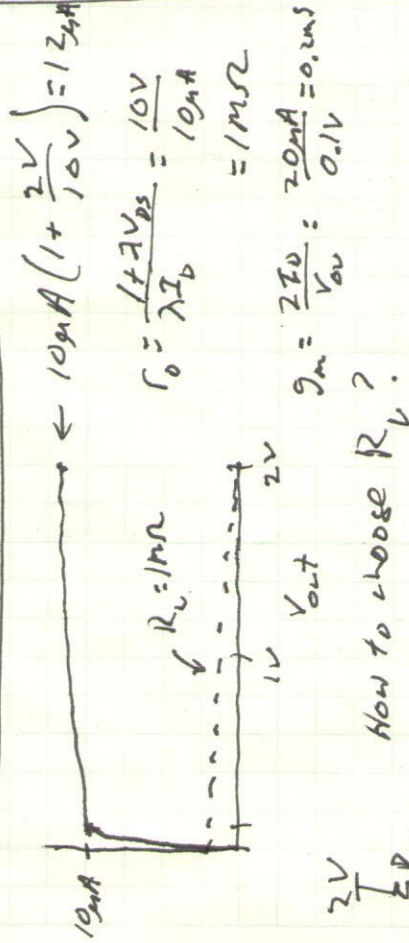


Oh tomorrow
HW3


CS amplifier,
Resistive load
quadratic, low, med bias
Sub- V_E
5CL



How to choose R_L ?
TRY: pick $R_L \gg r_o$ to get close to intrinsic gain
($A_v = -g_m (r_o || R_L) \approx -g_m r_o = \text{int'l gain}$)

possible? NO!
TRY2: $R_L = r_o$? possible? NO.

CS w/ quadratic model

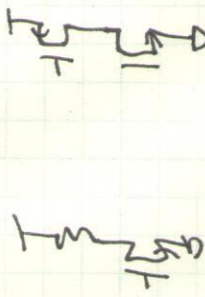

resistive load

active load

Say $M_n \text{ Cox} = 200nA/V^2$
 $M_p \text{ Cox} = 100nA/V^2$
 $\lambda = \frac{1}{10V}$ when $L = 0.5\mu m$
 $-V_{EP} = V_{kn} = 0.5V$
 $V_{DD} = 2V$


$\frac{W}{L} = \frac{5\mu m}{0.5\mu m}$, resistive load, $V_I = 0.6V$

$I_D = \frac{M_n \text{ Cox}}{2} (V_I - V_{kn})^2 (1 + \lambda V_{DS}) = \left(\frac{10nA}{V^2}\right) (0.1V)^2 (1 + \frac{V_{DS}}{10V})$



CMOS active load

Choose $|V_{ovp}| = V_{ovn} = 0.1V$

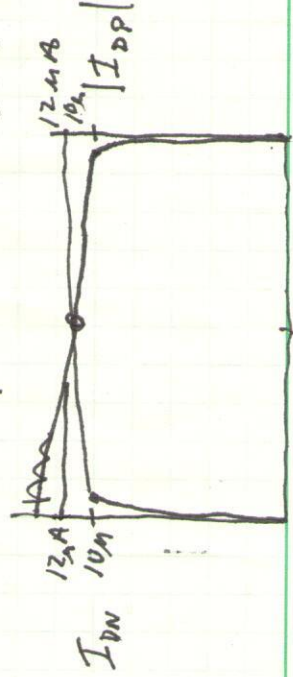Solve for $(\frac{W}{L})_p$ $10\mu A = \frac{M_p \text{ Cox}}{2} (\frac{W}{L})_p (V_{ovp})^2 (1 + \lambda V_{ovp})$
 $10\mu A = \frac{50nA}{V^2} (\frac{W}{L})_p (0.1V)^2 (1 + \lambda V_{ovp})$
 $(\frac{W}{L})_p = 20 = \frac{10\mu A}{0.5\mu m} \leftarrow \text{choose}$



140/240A 185P W4L1

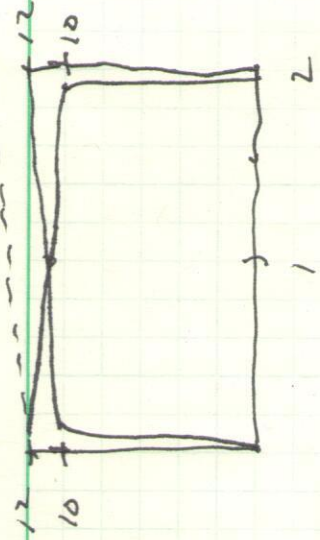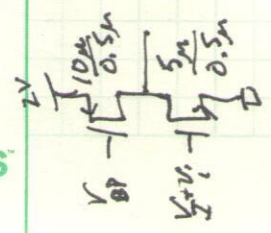

What if I increase V_i by 10mV?


$$i_d = g_m v_i = (200 \mu A/V)(0.01V) = 2 \mu A$$

What if I decrease V_i by 10mV?

$$i_d = -2 \mu A$$

$V_{out} < 0.1V$ NMOS out of saturation
 $V_{out} > 1.9V$ PMOS out of saturation

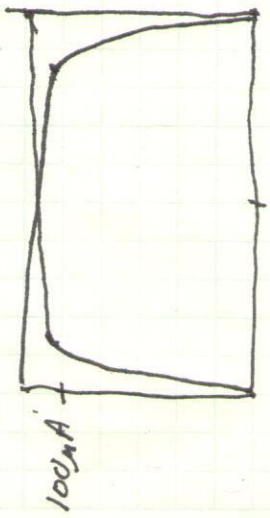What if $V_{I2} = 0.82V$? $V_{ov} = 0.32$ $0.32^2 = 0.1$



$$r_o = 100k$$



$$g_m = \frac{2I_D}{V_{ov}} = \frac{200 \mu A}{0.32V} = 625 \mu A/V$$

$$A_v = g_m \frac{r_o}{2} \approx 332$$

$$V_{BP} = 2V - (V_{cp} + V_{od}) = 2V - 0.82 = 1.18V$$

$I_D \rightarrow 10X$

$g_m \rightarrow 10X$

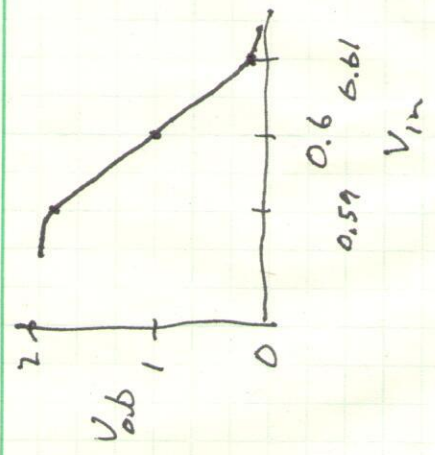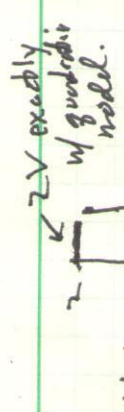

$$A_v = -g_m (r_{o1} || r_{o2}) = -200 \mu A/V (100k || 100k) = -100$$

$$= \frac{2I_D}{V_{ov}} \left(\frac{1}{\lambda I_{D1}} || \frac{1}{\lambda I_{D2}} \right) = \frac{V_A}{V_{ov}} = \frac{V_A}{V_{ov}}$$

What if $V_{I2} = 0.5V$? $S_{US} - V_{I2}$ model

if currents are equal around $V_{ov} = 10mV$
 then $I_{S3} e^{\frac{V_{GS3}}{nV_{TH}}} = 0.1 \mu A$ when $V_{GS3} = 0.510V$
 if $n=1$ $e^{\frac{-10mV}{26mV}} = 0.68$
 if $n=2$ $e^{\frac{-10mV}{52mV}} = 0.82$

SO current is around 0.07 or $0.08 \mu A$

$$r_o = 100k = \frac{1}{\lambda I_D} \leftarrow \text{not a great model}$$

$$g_m = \frac{I_D}{nV_{TH}} = \frac{75 \mu A}{26mV} = 3 \mu S$$

$$A_v = 300$$

What is $V_I \approx 1.5V$?

Scattering limited!

$$I_D = W C_{ox} v_{sat} (1 + \lambda V_{DS}) V_{OV}$$

not a good model

$$r_n = \frac{\partial I_D}{\partial V_{OV}} = \frac{I_D}{V_{OV}}$$

$$I_D = (5 \times 10^{-6} \text{ mm}) \left(5 \frac{\text{ff}}{\text{km}^2} \right) \left(10^5 \frac{\text{cm}}{\text{s}} \right) (1V)$$

$$= 2.5 \times 10^{-10} \frac{\text{C}}{\text{mm}} \frac{\text{m}}{\text{s}}$$

$$= 2.5 \times 10^{-4} \text{ A} = 2.5 \text{ mA}$$

$$V_{OV} = 1V \quad \frac{V_{OV}}{L} = \frac{2V}{\text{mm}}$$

$$g_m = 2.5 \text{ mS}$$

$$r_o = \frac{10V}{2.5 \text{ mA}} = 4 \text{ k}\Omega$$

$$A_v = 10$$

$$w_u = \frac{g_m}{C_L} = \frac{2.5 \text{ mA}}{100 \text{ fF}} = 25 \text{ G rad/sec}$$

$$= 3 \text{ GHz}$$

	Quadratic	Subvt	SC.L.
V_{OV}	100mV	0mV	1V
I_D	100nA	75nA	2.5mA
Swing	0.1-1.7	0.05-1.95	crap.
g_m	$\frac{200 \text{ nA}}{\text{mV}}$	$\frac{3 \text{ nA}}{\text{mV}}$	$\frac{2.5 \text{ mA}}{\text{V}}$
r_o	1M	100k?	4k?
A_v	100	300	10
w_u	$2 \text{ G} \frac{\text{rad}}{\text{s}}$	$30 \text{ M} \frac{\text{rad}}{\text{s}}$	$25 \text{ G} \frac{\text{rad}}{\text{s}}$
	200X	1000X	

Quadratic: $V_{OV} \rightarrow X$
 $I_D \rightarrow X^2$
 $g_m \rightarrow X$
 $r_o \rightarrow \frac{1}{X^2}$
 $A_v \rightarrow X$
 $w_u \rightarrow X$
 power $\rightarrow X^2$

SC.L. is ~ 100x faster than $V_{OV} = 100 \text{ mV}$
 and 2,500 times more power hungry
 and the gain sucks
 Sub-vt is parsimonious w/ power, but slow
 gain is good