

Lab 3  
Lab 2  
HW 4

Midterm in class Friday! 1 page, 2 sides notes

CS amplifier design example

Cascode

Potato model for  $G_m, R_o$

$$A_v \approx 50 = \frac{10V}{V_{ov}} \frac{L}{0.5} \quad \text{pick } \boxed{L_n = L_p = 0.5 \mu m}$$

$$\Rightarrow \boxed{V_{ov} = 0.2V}$$

$$g_m = w_n C_o = (2) \underbrace{\left(10^9 \frac{rad}{s}\right)}_{w_n} (10^{-13} F) = 200 \frac{mA}{V}$$

$$g_m = \mu_n C_{ox} \left(\frac{w}{L}\right)_n V_{ov} = 200 \frac{mA}{V} \left(\frac{w}{L}\right)_n (0.2V)$$

$$\Rightarrow \left(\frac{w}{L}\right)_n = 5 \quad w_n = 2.5 \mu m$$

$$C_{in} = C_{gsn} + (1-A) C_{gdn} = \frac{2}{3} (5 \frac{fF}{\mu m^2}) (1.25 \mu m^2) + 5 / (1.25 \mu m) = 60 fF$$

140/240k

185p

W4L3

CS design example - HW3/4 specs  
 $\mu_n C_{ox} = 200 \frac{mA}{V^2}$   $\mu_p C_{ox} = 100 \frac{mA}{V^2}$

$$\lambda = \frac{1}{10V} \left( \frac{0.5 \mu m}{L} \right) \quad L_{min} = 0.5 \mu m$$

$$C_{ox} = 5 \frac{fF}{\mu m^2}, \quad C_{de} = 0.5 \frac{fF}{\mu m}$$

Design an amp w/ low freq gain  $\approx 50$  (mag)  
gain of 2 at 1G  $\frac{rad}{sec}$  driving 100fF  
input cap less than 1pF


$$|A_v| = g_m (r_{on} || r_{op}) \quad \text{choose pick } L_n = L_p$$

$$A_v = \frac{2I_D}{V_{ov}} \frac{1}{2\lambda I_D} = \frac{1}{\lambda V_{ov}} \Rightarrow r_{on} = r_{op} \quad r_{on} || r_{op} = \frac{1}{2\lambda I_D}$$

pick  $V_{ov} = V_{ovn} = 0.2 \Rightarrow w_p = 2w_n = 5 \mu m$

output parasitic cap:  $C_{gsn} + C_{gdn} = 4fF \ll 100fF$
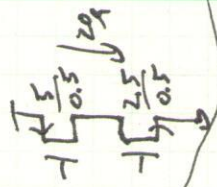
$$I_D = (100 \frac{mA}{V^2}) 5 (0.2V)^2 = 20 \mu A$$



what if  $A_v$  spec were 500?

$$A_v = 500 = \frac{10V}{V_{ov}} \frac{L}{0.5} \quad \text{pick } V_{ov} = 100mV \text{ (minimum allowed)}$$

$$\Rightarrow L_n = L_p = 2.5 \mu m$$

$$g_m = 200 \frac{mA}{V} = 200 \frac{mA}{V} \left(\frac{w}{L}\right)_n (0.1V) \Rightarrow \left(\frac{w}{L}\right)_n = 10$$



$$\Rightarrow L_n = 2.5 \mu m \Rightarrow C_{gdn} = 12.5 fF \Rightarrow C_{in} \approx 60 fF$$

problem!

One of many solutions: cascode

What is  $G_m$ ?  $R_o$ ?

What are  $v_i$ ?

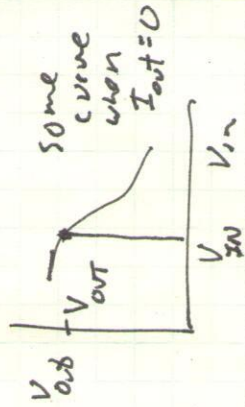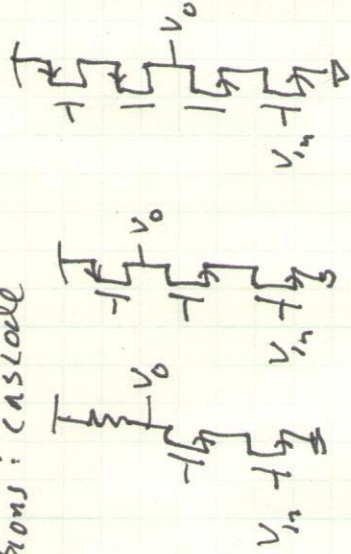

So to find  $R_o$ , we draw small signal model, set  $v_i = 0$

wiggle  $v_o$ , and measure  $i_o$


that's  $\frac{\partial I_{out}}{\partial V_{out}} \bigg|_{v_i=0, V_{in}, V_{out}} = G_o = R_o^{-1}$

to find  $G_m$ , set  $v_o = 0$ , wiggle  $v_i$ , measure  $i_o$

Sometimes people freak out when e.s.

with ideal current source, is

$G_m = 0$ ? NO

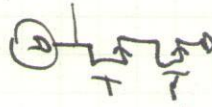

For most real circuits  $I_{out}(v_{in}, v_{out})$  is a continuous function in some neighborhood.


So we use Taylor at a point on the input/output plane

$$I_{out}(v_{in} + v_i, v_{out} + v_o) = I_{out}(v_{in}, v_{out}) +$$

$$\frac{\partial I_{out}}{\partial v_{in}} \bigg|_{v_{in}, v_{out}} v_i + \frac{\partial I_{out}}{\partial v_{out}} \bigg|_{v_{in}, v_{out}} v_o + \text{h.o.t.}$$


If nothing is connected at the output, then  $I_{out} = 0$

and  $G_m v_i + G_o v_o = 0$

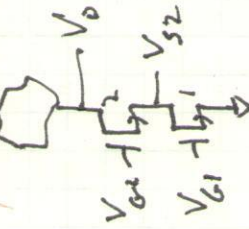

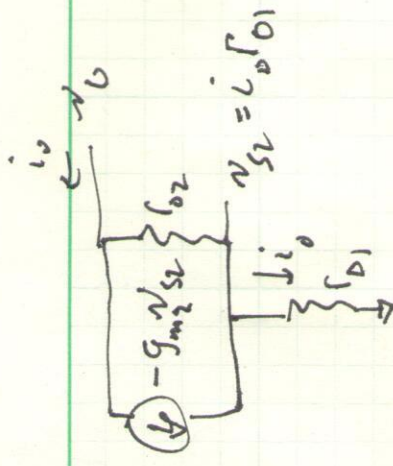4  $G_m, R_o$  pairs ( $Z_{in}, Z_{out}$ ) need to know all of them.





KCL @  $v_o$   $i_o = -g_{m2} i_{o1} + \frac{1}{r_{o2}} (v_o - i_{o1} r_{o1})$

$i_o (1 + g_{m2} r_{o1} + \frac{r_{o1}}{r_{o2}}) = \frac{1}{r_{o2}} v_o$

$R_o = \frac{v_o}{i_o} = r_{o2} (1 + g_{m2} r_{o1} (1 + \frac{1}{g_{m2} r_{o2}})) \approx \frac{g_{m2} r_{o2} r_{o1}}{\text{int gain}}$


KCL @  $v_{s2}$   $i_o = g_{m1} v_i + \frac{1}{r_{o1}} v_{s2}$

$= g_{m1} v_i - \frac{1}{r_o} \frac{i_o}{g_{m2} (1 + \frac{1}{g_{m2} r_{o2}})}$

$g_{m1} v_i = i_o \left[ 1 + \frac{1}{g_{m2} r_{o1} (1 + \frac{1}{g_{m2} r_{o2}})} \right]$

$G_m = \frac{i_o}{v_i} \approx \frac{g_{m1}}{g_{m2}}$

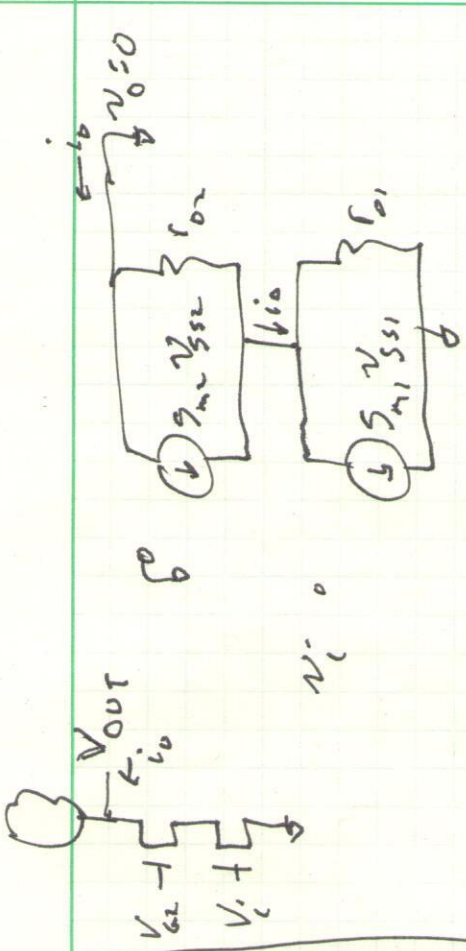
$A_v = -G_m R_o = -g_{m1} r_{o1} g_{m2} r_{o2} \parallel R_{up}$



$i_o = -g_{m2} v_{s2} - \frac{1}{r_{o2}} v_{s2}$

$(0 - v_{s2}) g_{m2} (1 + \frac{1}{g_{m2} r_{o2}}) = i_o$

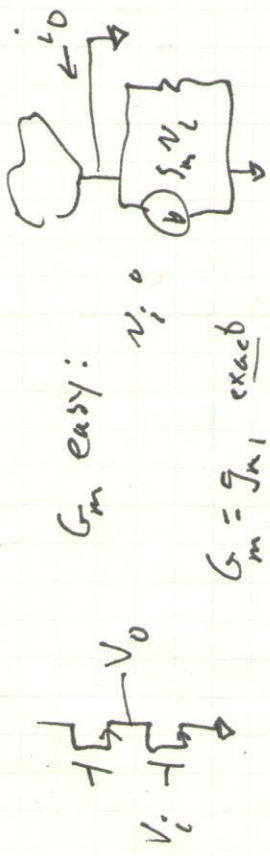for  $C_{in}$ , need gain to  $v_{s2}$  (Miller)




$G_m$  easy:

$v_i = 0$

$G_m = g_{m1}$  exact

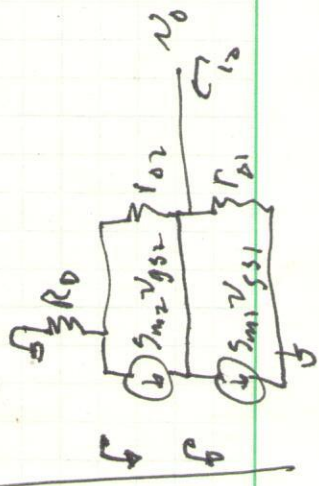$R_o$  harder: depends on  $R_{up}$  or  $R_D$



$r_{o1} \parallel R_{up}$