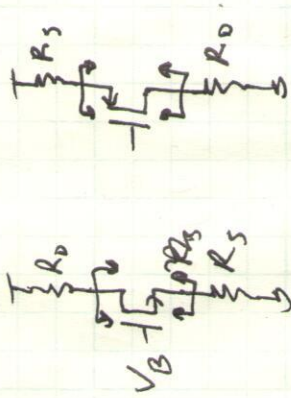


Midterm Friday

Gm

Biasing

Last time




$$R_D = (1 + g_m r_o) R_S + r_o$$

$$= g_m r_o R_S + R_S + r_o$$

$$\approx g_m r_o R_S \quad \text{if } R_S \gg \frac{1}{g_m}$$

$$R_S = \frac{1}{g_m} \left(1 + \frac{R_D}{r_o} \right)$$

Gm for CS w/ degeneration

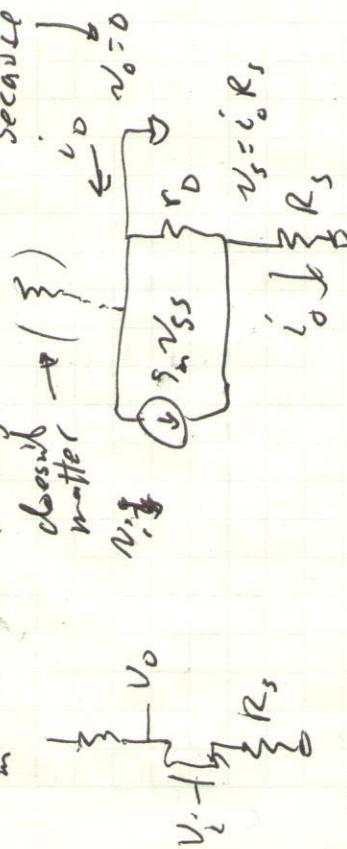

because $v_o = 0$

doesn't matter \rightarrow ()


$$i_o = g_m (v_i - v_s) + \frac{1}{r_o} (0 - v_s)$$

$$i_o \left[1 + g_m R_S + \frac{1}{r_o} R_S \right] = g_m v_i$$

$$G_m = \frac{i_o}{v_i} = \frac{g_m}{1 + g_m R_S \left(1 + \frac{1}{g_m r_o} \right)}$$

$$G_m = \frac{g_m}{1 + g_m R_S} = \frac{g_m}{1 + g_m R_S} \begin{cases} R_S \ll \frac{1}{g_m} \\ R_S = \frac{1}{g_m} \\ R_S \gg \frac{1}{g_m} \end{cases}$$

Gm for CS w/ drain impedance

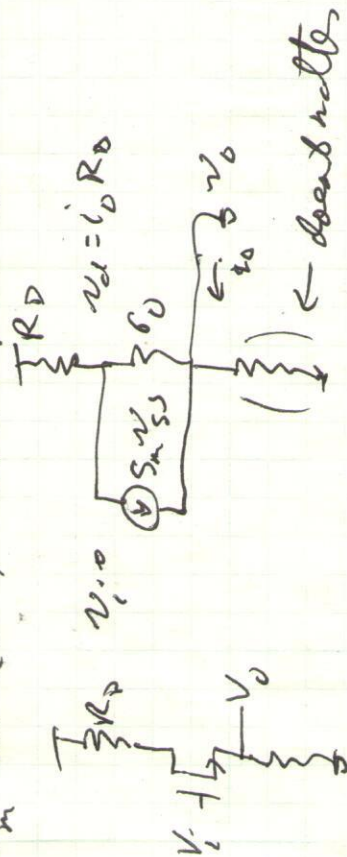



$$KCL @ v_s: i_o + g_m (v_i) + \frac{1}{r_o} (i_o R_D) = 0$$

$$i_o \left[1 + \frac{R_D}{r_o} \right] = -g_m v_i$$

$$G_m = \frac{i_o}{v_i} = \frac{-g_m}{1 + \frac{R_D}{r_o}} = \begin{cases} -g_m & R_D \ll r_o \\ -\frac{g_m}{2} & R_D = r_o \\ -\frac{g_m r_o}{R_D} & R_D \gg r_o \end{cases}$$

Diode connected

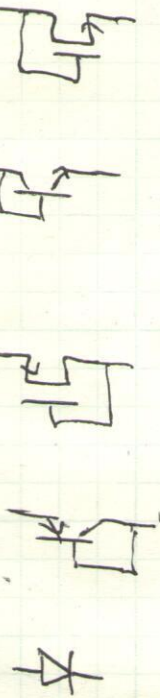

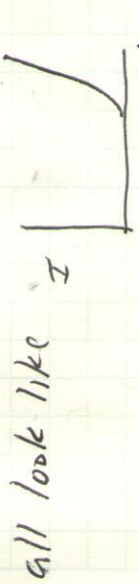all look like I 


turn on depends on scale
for diode, BJTs it's near 0.6, 0.7 almost scales
for MOS, near V_T



$$A_v = -g_m R_o = -g_{m1} \left(r_{o1} \parallel \frac{1}{g_{m2}} \right)$$



$$= -\frac{g_{m1}}{g_{m2}} = -\frac{2I_D}{V_{ov2}} \cdot \frac{V_{ov1}}{2I_D} = -\frac{V_{ov2}}{V_{ov1}}$$

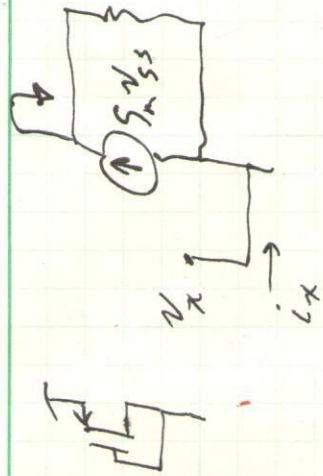if $V_{ov2} = 2V_{ov1}$
and $I_{D2} = I_{D1}$
what is $\left(\frac{A_v}{2}\right)_2 / \left(\frac{A_v}{2}\right)_1$?




$$i_x = g_m (v_x - 0) + \frac{1}{r_o} (v_x - 0) = \left(g_m + \frac{1}{r_o} \right) v_x = g_m r_o \left(1 + \frac{1}{g_m r_o} \right) v_x$$
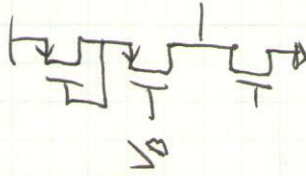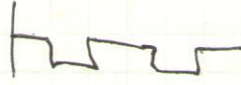
$$R_d = \frac{v_x}{i_x} = \frac{1}{g_m}$$




G_m
 R_o

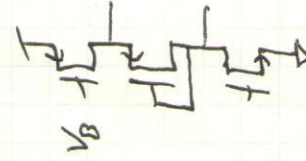

G_m ?
 R_o ?
why?

Biasing

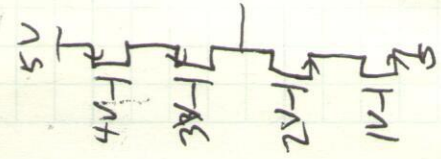

$V_{en} = |V_{tp}| = -0.5$ $M_{n,ox} = 2 \mu p_{lox}$

All have same $\frac{W}{L}$, No gain, why?

Change $(\frac{W}{L})_P = 2 \left(\frac{W}{L}\right)_n$

Bias points? $V_{S2} = 1$
 $V_{S3} = 4$

$V_{out} = 2.5$? very tough to hit exactly

output swing? 1.5 - 3.5

gain? $g_{m1} \left(\frac{g_{m2} r_{o2}}{2}\right) = \frac{1}{2} \left(\frac{2I_D}{V_{ov}} \cdot \frac{1}{\lambda I_{D2}}\right)^2 = 2 \left(\frac{V_A L}{V_{ov} L_{min}}\right)^2$

How low could V_{S2} go?

what if I double W everywhere?

double $\frac{W}{L}$ everywhere?

drop V_{ov} to 0.1V?