

Midterm 1

Midterm 2 Friday March 23

80 minutes

HW 5

Op-amps



e.s.  $V_1$   $V_2$   $V_3$

$$V_o = i_f R_f$$

$$= -i_{in} R_f$$

$$= -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$



$$i_{in} = C \frac{dv_{in}}{dt}$$

$$v_o = -R_f C \frac{dv_{in}}{dt}$$



$$v_o = - \int \frac{v_i}{RC} dt$$

Linear ODEs!  
Apollo!

mathematical operation amplifiers

(e.s. EE128 lab up to ~1980)

before computers, analog computation only

today, still best choice in some situations

we get to decide when to use digital, analog.

Examples: based on virtual ground.



Nonlinear




exp



log

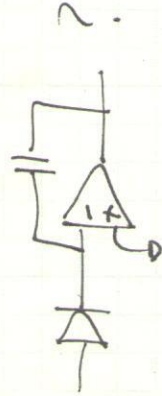With a log table, even Adders can multiply!



How? tubes KZ-W 1951

discrete NPN


integrated NPN  $\Rightarrow$  NPN + PNP

integrated PMOS, NMOS, CMOS

compensator (Miller)



biass network (PVT independent)

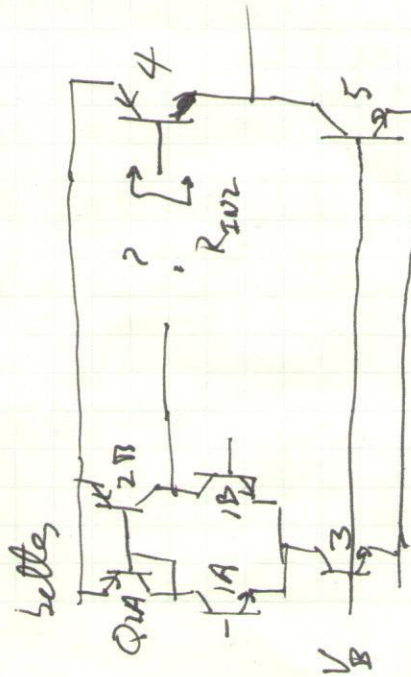

Q3: better common mode rejection

Q2B: better output resistance  $\Rightarrow$  gain

Q1A: easy biasing, 2x better  $G_m$

Q5: better output resistance  $\Rightarrow$  gain

2 stage

simplest:

V<sub>+</sub>


V<sub>-</sub>

d.i.f.f. amp


busx input offset, common mode, etc.

bettes

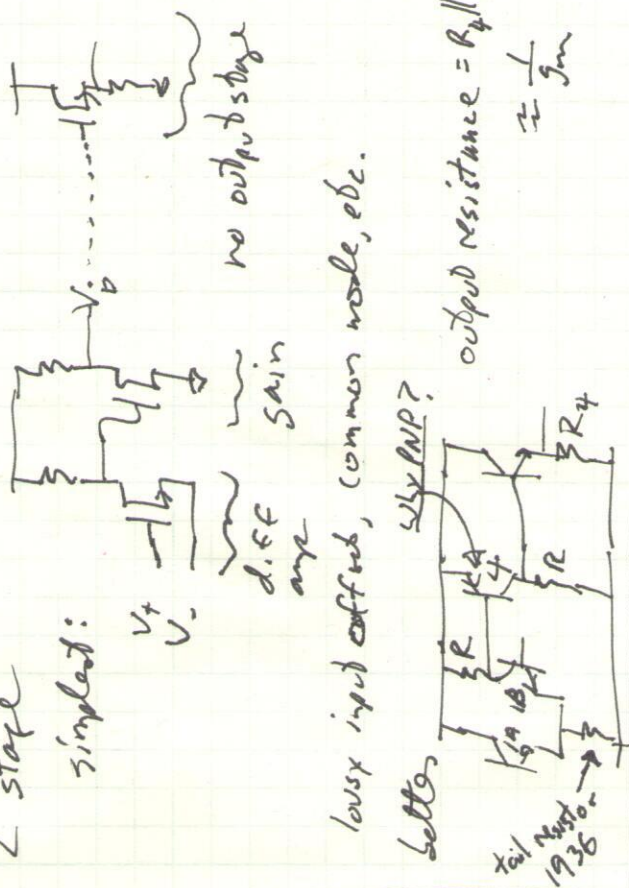output resistance =  $R_4 \parallel g_m$   
 $\approx \frac{1}{g_m}$



increase R<sub>IN2</sub>

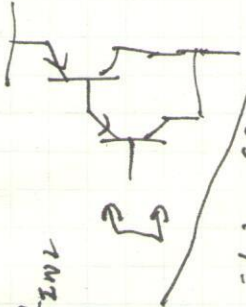

but bias point is off.

2 diodes below the rail

so bring it back



$$R_{E} = \frac{\beta}{g_{m4}}$$

$$\beta R_{E} = \frac{\beta^2 V_{TH}}{g_{m4} I_{C4}}$$


Probably large compared to  $\frac{V_A}{I_{C3}}$

4D Darlington - increase R<sub>in</sub>  
4L level shifting emitter follower (and Darlington)

4LB bias for 4L


TL431

CMOS version

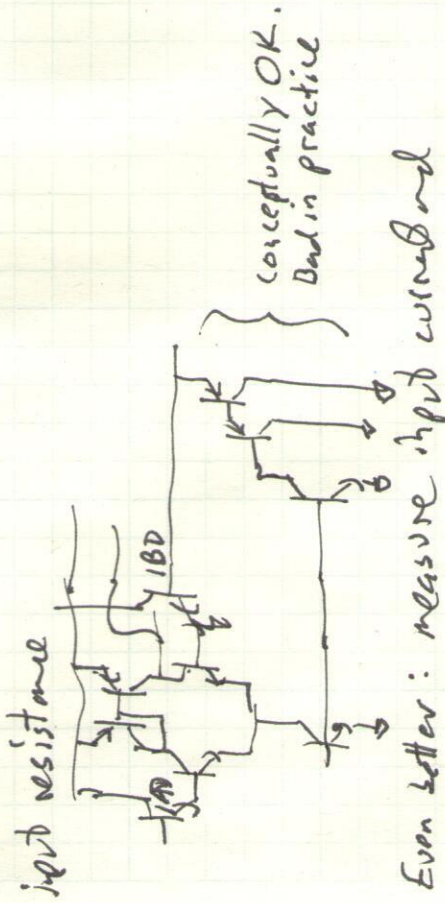

Even better: measure input current and subtract it out

CMOS version - 2 stage (workhorse)

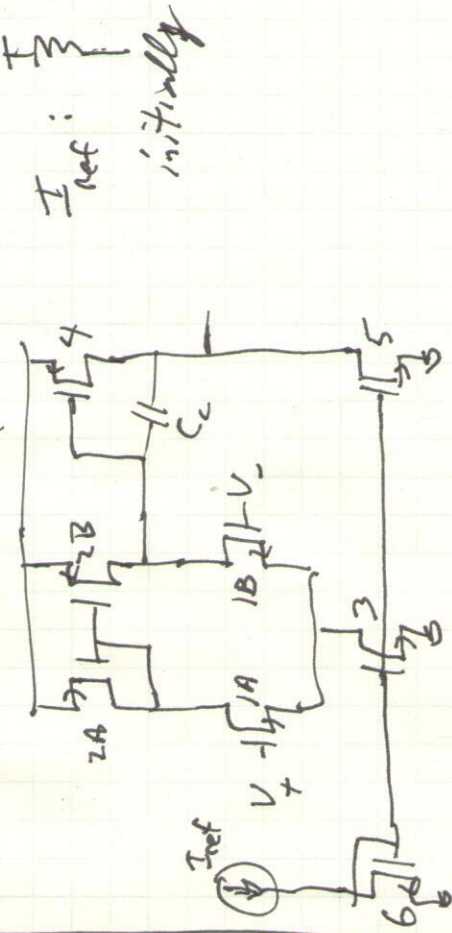

typically no output stage

Diff pair	1, 2, 3	differential gain
Active load	2, 3, 4	Common mode gain
gain stage	4, 5	input offset
Bias network	3, 5, 6	input common mode range
Signal path	1, 2, 4	output swing
		frequency response
		power supply rejection
		noise
		current drive
		slew rate

current mirrors

if A and B have same  $\beta$ ,  $V_t$ ,  $\mu C_{ox}$  and  $\lambda = 0$  how different can the current be if both are in saturation?

A: not at all different  
 What if  $\lambda \neq 0$ ?

$$\frac{\Delta I_D}{I_{D0}} = \lambda \Delta V_D$$

$$\frac{\Delta I_D}{I_{D0}} = \frac{\Delta V_D}{V_D}$$