 


CMOS version


input resistance



conceptually OK.
Bad in practice

Even better: measure input current and subtract it out

CMOS version - 2 stage (workhorse)

 


I_{ref} initially

typically no output stage

- Diff pair 1A, B
- Active load 2A, B
- gain stage 4, 5
- bias network 3, 5, 6
- signal paths 1, 2, 4

 - differential gain
- common mode gain
- input offset
- input common mode range
- output swing
- frequency response
- power supply rejection
- noise
- current drive
- slew rate



if A and B have


Same $\frac{W}{L}$, V_t , μC_{ox} and $\lambda = 0$ how diff'd can the current be if both are in saturation?

A: not at all diff'd


What if $\lambda \neq 0$?

$$\frac{\Delta I_D}{I_{D0}} = \lambda \Delta V_D$$
 
$$\frac{\Delta I_D}{I_{D0}} = \frac{\Delta V_D}{V_D}$$




CMOS op-amp
bias network
current mirrors

 

Feedback & stability

simplest output stage (uncommon)

Bias network

 


establishes V_{GS6} to pass I_{ref} w/ $(\frac{W}{L})_6$ possibly diff'd

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

same for all

If you need sources & sinks (like on homework)

 then mirror the current to opposite supply



$$I_1 = I_{ref} \frac{(W/L)_1}{(W/L)_R}$$

$$I_2 = I_1 \frac{(W/L)_2}{(W/L)_R}$$

$$I_4 = I_1 \frac{(W/L)_4}{(W/L)_R}$$

Always use integer ratios (literally just n copies) in transistor sizing

Always use the same L (easy, if you obey)

1st stage $G_{m1} = g_{m1a} = g_{m1b}$

$$A_{V1} = \frac{g_{m1} r_{O12}}{2}$$

$$R_{O1} = r_{O1B} || r_{O2B}$$



2nd stage

$$G_{m2} = g_{m4}$$

$$A_{V2} = \frac{g_{m4} r_{O45}}{2}$$

$$R_{O2} = r_{O4} || r_{O5}$$

if $C_L = 0$ (impossible) $\omega_{p1} = \frac{1}{R_{O1} C_{O1}}$ $\omega_{p2} = \frac{1}{R_{O2} C_{O2}}$

Why use feedback?

- stable gain based on ratios of passive component values
- improved input/output impedance
- reduced nonlinearities
- etc.

op-amp




$V_o = 100 V_i$ but how accurate?

Resistor & capacitor

matching pretty good ~0.1%

How much gain do we need to get 0.1% accuracy?

 How do you get a gain of, say, 100? $\pm 1\%$?




design so that $g_{m,fo} = 100$
 but these models are terrible
 output resistance varies w/ V_o
 g_m varies w/ V_o

everything varies w/ Temp, Process
 and supply voltage

not possible

EE128 view

 

$$y = Ae$$

$$= A(u - fy)$$

$$= Au - Afy$$

$$(1 + Af)y = Au$$

$$N(s) = \frac{y}{u} = \frac{A}{1 + Af} = \frac{A}{Af} \frac{1}{1 + \frac{1}{Af}} \approx \frac{1}{f} \left(1 - \frac{1}{Af}\right)$$

$$\approx \frac{1}{f} \text{ if } Af \gg 1$$

gain error

need $\frac{1}{Af} < \text{gain error spec, e.g. } 0.1\%$