

CMOS op-amp
 2 stage output swing
 2 stage sizing
 poles & time response
 poles & time response
 poles move in feedback

Linear Time Invariant
 $\sin(\omega t) \rightarrow [H(s)] \rightarrow |H(j\omega)| \sin(\omega t + \angle H(j\omega))$
 $\sum A_i \sin(\omega_i t + \phi_i) \rightarrow \sum |H(j\omega_i)| A_i \sin(\omega_i t + \angle H(j\omega_i))$
 changes magnitude and phase

hence, Bode plots
 $|H(j\omega)|$
 $\angle H(j\omega)$

$$\sum_{i=0}^n a_i \frac{d^i v_o}{dt^i} = \sum_{i=0}^m b_i \frac{d^i v_i}{dt^i}$$

ODEs $RC \frac{dv_o}{dt} + v_o = v_i$ $v_i = m \frac{v_i}{B}$
 Heaviside $(sRC + 1)v_o = v_i$ $C \frac{dv_o}{dt} = \frac{1}{R}(v_i - v_o)$

$$H(s) = \frac{1}{1 + sRC} = \frac{1}{1 + s/\omega_p}$$

when is $H(s) = \infty$? when $s = -\omega_p$ pole

Shorted to ODEs: $\frac{1}{s} \Rightarrow Z = \frac{1}{sL}$


$$m \frac{v_o}{B} \Leftrightarrow \lim_{s \rightarrow 0} \frac{Z_c}{R + Z_c} = \frac{1}{1 + s/\omega_p}$$

time response $(\sum_{i=0}^n a_i s^i) v_o = (\sum_{i=0}^m b_i s^i) v_i$

$H(s) = \frac{\sum b_i s^i}{\sum a_i s^i} \leftarrow$ characteristic polynomial


roots of $a(s) = 0$ are poles
 Poles $\sigma_i \pm j\omega_i$

impulse response: $e^{p_i t}$

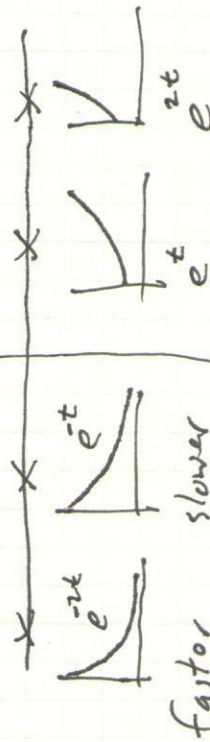

Complex conjugate poles
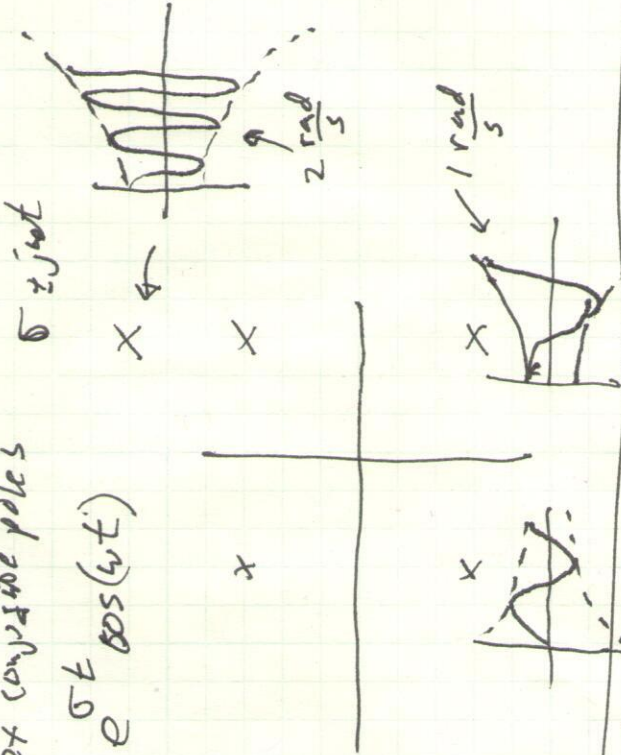
$$\Rightarrow e^{\sigma t} \cos(\omega t)$$



Poles move in feedback

$$A(s) = \frac{A_0}{1 + s/\omega_p}$$

where $A_0 = 10^5$

$\omega_p = 10 \text{ rad/sec}$




$$A_{LL} = \frac{A_0}{1 + Af} = \frac{A_0}{1 + s/\omega_p} = \frac{A_0}{1 + A_0 f + s/\omega_p}$$

$$= \frac{A_0}{1 + A_0 f} \frac{1}{1 + \frac{s}{\omega_{pCL}}}$$

DC

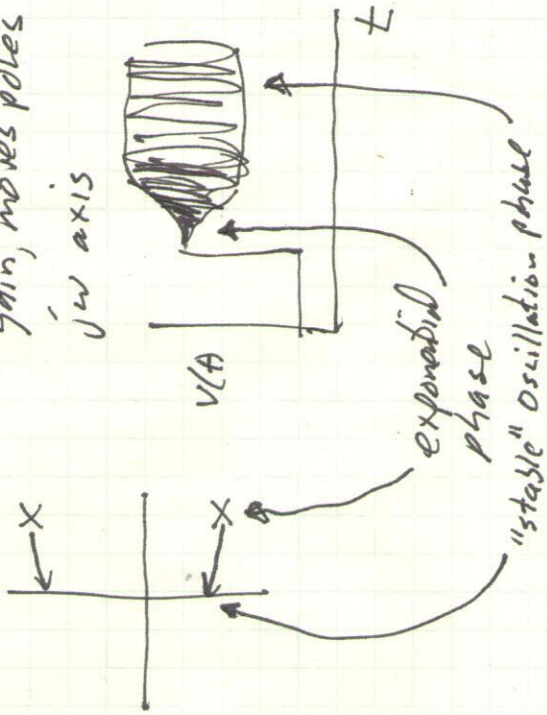
nonlinear effects: growth of oscillation reduces gain, moves poles toward $j\omega$ axis



f increasing


$f=0$, open loop pole

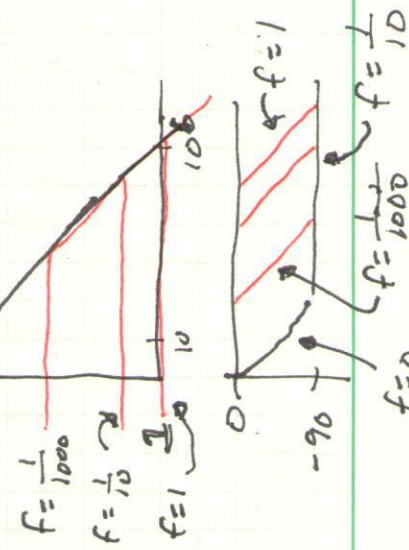unity gain; $\omega_{p,CL} = (1+A_0)\omega_p = \text{unity gain BW}$





feedback is good for lots of reasons, but
risk of instability

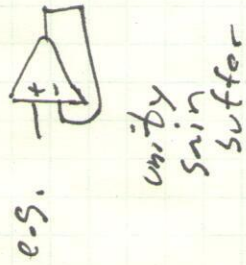Negative feedback good
positive feedback (usually) dangerous/bad



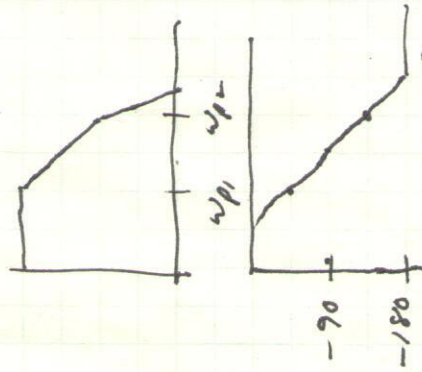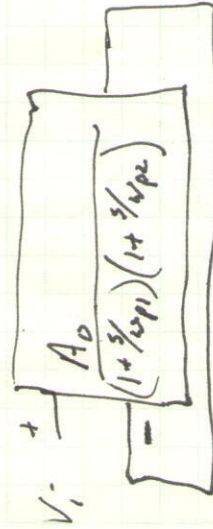each pole gives -90 phase shift above $\approx 10\omega_p$
so 2 poles give -180



at high frequency, -180
phase shift +/- swap!

~~notes~~ ~~more~~ ~~in~~

consider the effect of phase


single pole:



$$\frac{V_o}{V_i} = \frac{-g_m r_o}{1 + s/\omega_p} \quad \omega_p = \frac{1}{r_o C}$$

$$|H(j\omega)| = \begin{cases} g_m r_o & \omega \ll \omega_p \\ g_m r_o / \sqrt{2} & \omega = \omega_p \\ \frac{g_m}{\omega C} & \omega \gg \omega_p \end{cases} \quad \angle H(j\omega) = \begin{cases} -180 & \\ -225 & \\ -270 & \end{cases}$$

1mV signal
Vi:

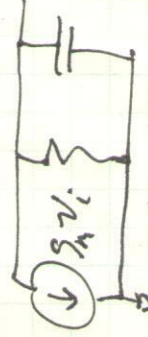

$$g_m V_i = 10^{-6} \text{ A } \sin(\omega t)$$

at low freq, $v_o = -1 \text{ V } \sin(\omega t)$

above ω_p $Z_o \approx \frac{1}{j\omega C}$

$$i_c = C \frac{dv_o}{dt} = -1 \mu\text{A } \sin(\omega t) = i_{gm}$$

$$\frac{dv_o}{dt} = -10 \frac{6 \text{ V}}{5} \sin(\omega t)$$

$$V_o = 10 \frac{6 \text{ V}}{5} \cos(\omega t) = \frac{10 \frac{6 \text{ V}}{5} / \omega_p}{\omega / \omega_p} \sin(\omega t - 2.7\pi)$$

$$= 1 \text{ V } \left(\frac{\omega_p}{\omega} \right) \sin(\omega t - 2.7\pi)$$

$$\begin{aligned} r_m &= 1 \text{ m}\Omega \\ r_o &= 1 \text{ M}\Omega \\ C_o &= 1 \text{ pF} \\ \omega_p &= \frac{1}{10^6 \cdot 10^{-12}} = 10^6 \\ &= \frac{1 \text{ V } \sin(\omega t - \pi)}{1 \text{ V } \sin(\omega t - 180^\circ)} \end{aligned}$$