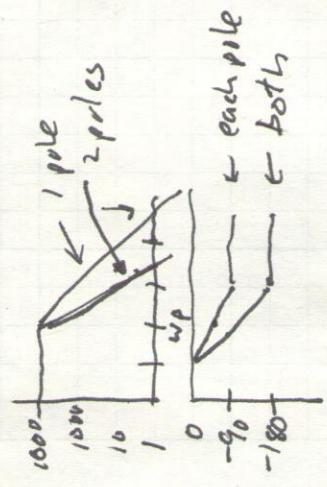


Some examples


co-located poles, gain of 1000



$w_h = \sqrt{1000} w_p$

$\angle A(jw_h) = -180$
 $PM = 0$ BAD!

co-located, gain of 10

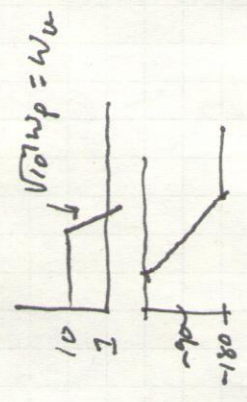

$\angle A(jw_h) = -135$

$PM = 45$ OK!

Always want at least 45° PM, so must

choose $w_p \geq w_h$


$w_p = w_h$



$\angle A(jw_h) = -135$

$PM = 45$ OK

$w_p = 3w_h$

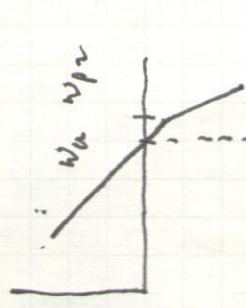


$\angle A(jw_h) \approx -90 - 22.5$


$PM \approx 67$ good!

Big gain

2 well separated poles

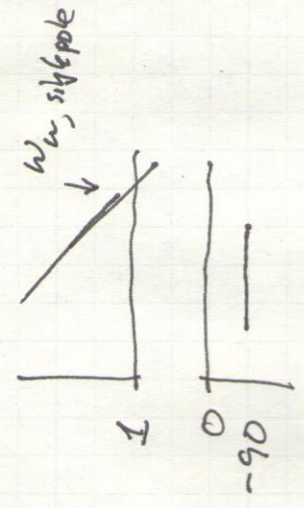

effect of low freq pole

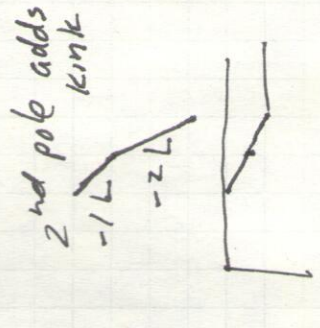

and another -45

compensation changing the freq response of the open loop amplifier (typically by adding capacitance) so that the closed loop amplifier is stable (phase margin)

How to compensate

single stage: doesn't need it (only 1 pole, $\omega_{p1} > \omega_{p2}$)

2 stage:

3 natural points: output of 1st stage

output of 2nd stage

→ across 2nd stage ←

Miller compensation

moves ω_{p1} lower w/ smaller cap
moves ω_{p2} higher!





$$C_{Miller} = (-A_{v2}) C_c$$



$$Z'_{Miller} = \frac{1}{j\omega C_{Miller}}$$

$$= \frac{1}{j\omega(1-A_{v2})C_c}$$

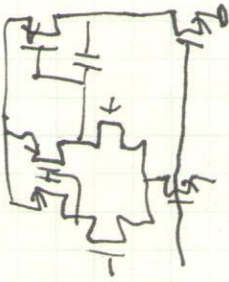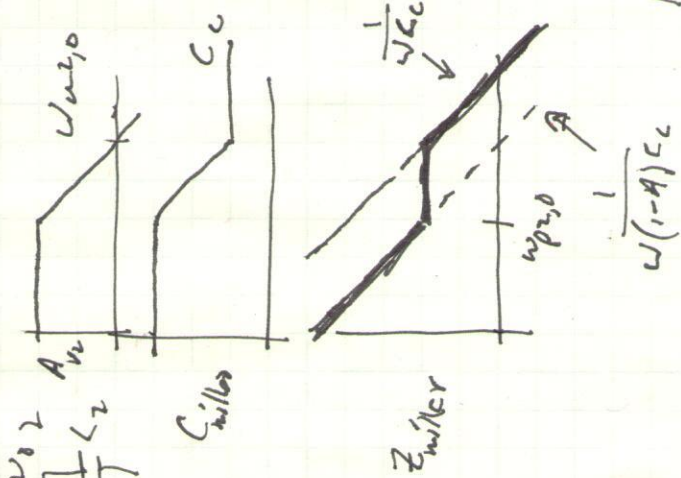where $A_{v2} = \frac{-A_{v20}}{1 + s/\omega_{p20}}$



with no C_c

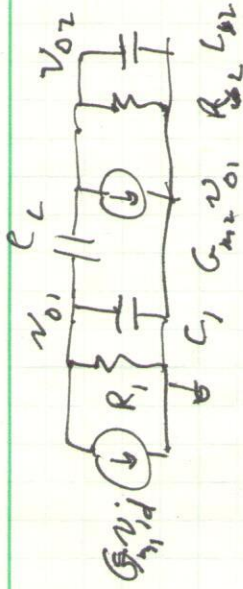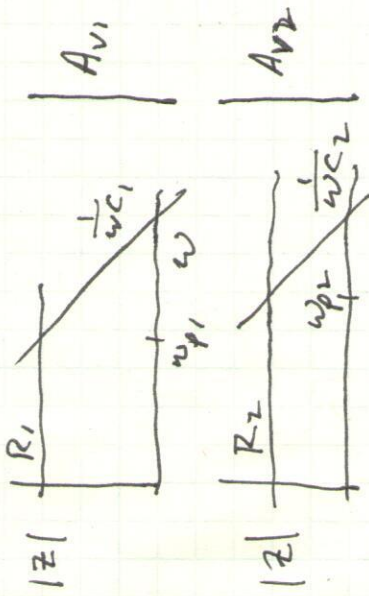

$$Z_{Miller} = \frac{1}{s(1 - \frac{-A_{v20}}{1 + s/\omega_{p20}})C_c}$$

$$= \frac{1 + s/\omega_{p20}}{s(1 + \frac{s}{\omega_{p20}} + A_{v20})C_c}$$

$$= \frac{1 + s/\omega_{p20}}{s(1 + A_{v20})C_c(1 + \frac{s}{(1 + A_{v20})\omega_{p20}})}$$

$$\approx \omega_{p20}$$

low freq $s = j\omega$ $\omega < \omega_{p20}$

$$Z_{\text{Miller}} \approx \frac{1}{s(1+A_{v30})C_c} = \frac{1}{j\omega C_{\text{Miller}}}$$

mid freq $\omega_{p20} < \omega < \omega_{u20}$

$$Z_{\text{Miller}} \approx \frac{\cancel{s/\omega_{p20}}}{s(1+A_{v30})C_c} = \frac{1}{\omega_{p20} C_{\text{Miller}}}$$

constant real! $A_v \sim \frac{1}{\omega}$

capacitance $\sim \frac{1}{\omega A_v}$

high freq $\omega_{u20} < \omega$

$$Z_{\text{Miller}} = \frac{\cancel{s/\omega_{p20}}}{s(1+A_{v30})C_c} \left(\frac{\cancel{1+s}}{(1+A_{v30})\omega_{p20}} \right)$$

$$= \frac{1}{sC_c}$$