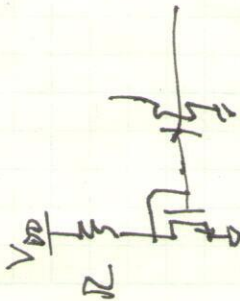


2 stage wrap up

Supply indep. biasing

Need a reference current/voltage



$$I_{ref} = \frac{V_{DD} - (V_{tn} + V_{ov})}{R}$$

would like I_{ref} to be independent of

Process

n_{ox} , V_{tn} , μ

Voltage

Batteries $n_{ox} \approx 1.6 \rightarrow 0.8V$

Temperature

V_{tn} temp $-2mV/K$

consumer $0-70C$

industrial $-40-+85C$

auto/mil $-55-+125C$

2-stage review


uncompensated

$$\omega_{p1} = \frac{1}{R_1 C_1}$$

$$\omega_{p2} = \frac{1}{R_2 C_2}$$

$$\omega_{pm} = \frac{g_{m2}}{2 C_{gs}}$$

$$\omega_{zm} = 2 \omega_{pm}$$

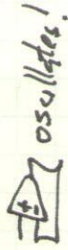

C_L



$$\omega_{pk} = \frac{1}{R_1 C_{m2} C_L}$$

$$\omega_{pc} = \frac{g_{m2}}{C_1 + C_2 + C_L}$$

$$\omega_{uc} = \frac{g_{m1}}{C_L}$$

$$\omega_{zc} = \frac{g_{m2}}{C_L}$$



stable



$$A = \frac{1}{F}$$

$$\text{error} = \frac{1}{AF}$$

$$\omega_{FB} = f \omega_{uc}$$

$$\omega_{yFB} = \frac{\omega_{uc}}{A_{CL}}$$

Like to also have a reference voltage

what is $1V$?

How much charge left in battery?

~~Is~~

Like to have a temperature sensor


Const S_m bias circuit



$$I_1 = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{ov1})^2$$

$$I_2 = \mu_n C_{ox} K \left(\frac{W}{L}\right) (V_{ov1} - I_2 R)^2$$

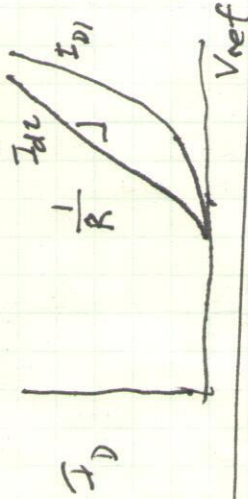If $I_2 R \ll V_{ov1}$, then $I_{D2} \approx K I_{D1}$



$$\frac{V_{ov1}}{\sqrt{K}} + I_2 R = V_{ov1}$$


$$I_2 R = \left(1 - \frac{1}{\sqrt{K}}\right) V_{ov1}$$

pick $K=4 \Rightarrow I_2 R = \frac{1}{2} V_{ov1}$

$$V_{ov2} = V_{ov1} - I_2 R = \frac{1}{2} V_{ov1}$$

$$g_{m1} = \frac{2 I_{D1}}{V_{ov1}} = \frac{2 I_{D2}}{I_{D2} R} = \frac{1}{R}$$

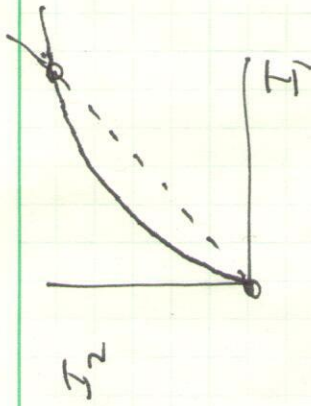"constant S_m " biasing indep $\mu_n C_{ox}$, V_t , V_{DD}




$I_{D1} = I_{D2}$ at $2 S_m$
bias points
so enforce

$$V_{ov1}^2 = K (V_{ov1} - I_2 R)^2$$

$$V_{ov1} = \sqrt{K} (V_{ov1} - I_2 R)$$

$$I_2 R = \frac{V_{ov1}}{\sqrt{K}}$$

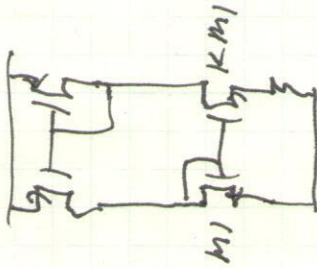

- use long-channel devices

- often cascode to improve supply rejection.
(we ignored $(1 + \lambda V_{DS})$)