

Midterm 2 Friday 80 minutes, either

2:30-4
or
4-5:30

HW8 - 3 midterms online - lots of similarity!

Guest lecture Monday: Prof. Nguyen

~~Both diodes are kept at constant temp,~~

$$\begin{aligned} \Delta V_x &= V_{D1} - V_{D2} = V_{TH} \ln 10 = \frac{k_B}{q} \ln 10 T \\ &= 60 \text{ mV} @ 300 \text{ K} = (0.2 \text{ mV/K})(300 \text{ K}) \\ &= 40 \text{ mV} @ 200 \text{ K} \\ &= 80 \text{ mV} @ 400 \text{ K} \end{aligned}$$



What if both diode currents are increased

by a factor of 2.7

impact on $\Delta V = ?$, no impact

impact on $V_{D1} = ?$

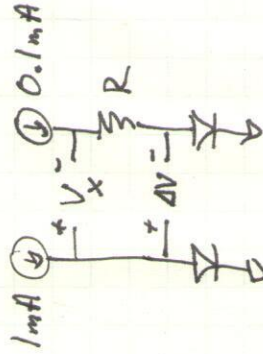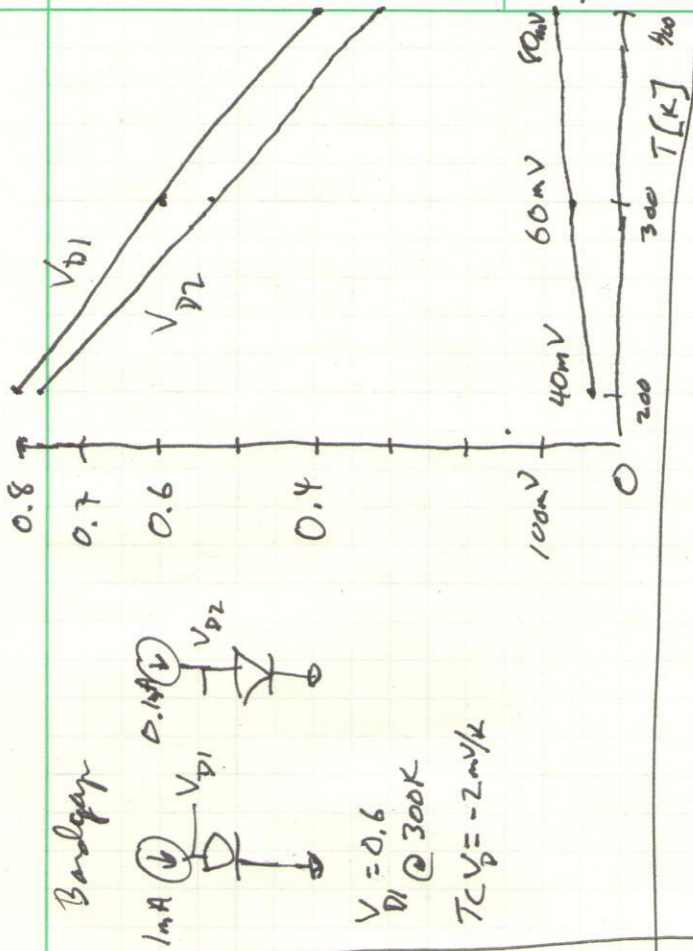increase V_D by 26 mV @ 300 K
 $\frac{2}{3}$ as much at 200 K
 $\frac{4}{3}$ as much at 400 K



if $R = 600 \Omega$

What is voltage drop? 60 mV

What is V_x at R.T.? 0

What is V_x at 400 K?

$$V_x = \Delta V - I_{D2} R = 80 \text{ mV} - 60 \text{ mV} = 20 \text{ mV}$$

To set $V_x = 0$

need to increase current by $\frac{1}{3} \Rightarrow 0.13 \text{ mA} = I_{D1}$

$$V_x = \Delta V - I_{D2} R = 80 \text{ mV} - 80 \text{ mV} = 0 \text{ mV}$$


What will happen? - what will happen $V_x = 0$ @ 200 K?

0.086
n. 1.1


1/40/240A

18 SP

W9L3

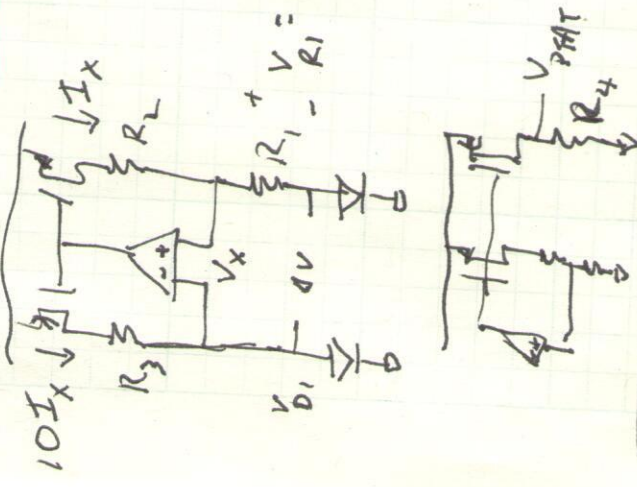

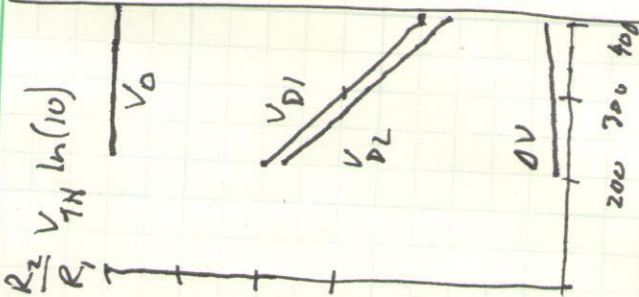$V_{R2} = I_x R_2 = \frac{R_2}{R_1} V_{TH} \ln(10)$
 1.2
 1.0
 0.8
 0.6




$I_{1a} = I_{2a}$
 $I_{1b} = I_{2b}$ same voltage, same R_x
 $I_1 = I_2, I_{1b} = I_{2b}$
 $\Delta V = V_{D1} - V_{D2} = V_{TH} \ln(n)$
 $V_{R4} = \Delta V = V_{TH} \ln(n)$

$I_{2a} = \frac{\Delta V}{R_1}$
 $I_{2b} = I_{1b} = \frac{V_{D1}}{R_x}$

$I_{2a} = I_{2a} + I_{2b} = \frac{\Delta V}{R_1} + \frac{V_{D1}}{R_x}$
 $V_0 = R_2 \left(\frac{V_{TH} \ln(n)}{R_1} + \frac{V_{D1}}{R_x} \right) = \frac{R_2}{R_x} \left(\frac{R_1}{R_1} V_{TH} \ln(n) + V_{D1} \right)$

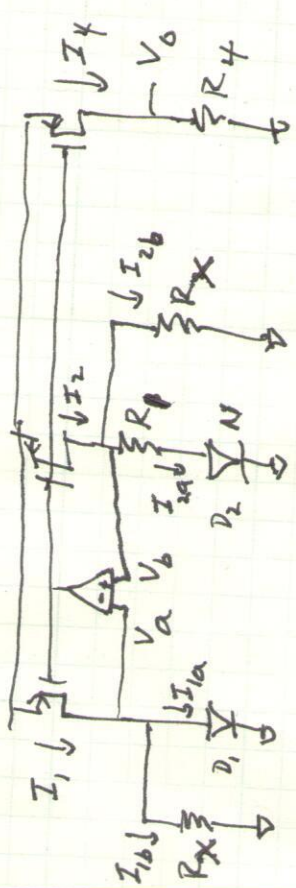Great! But how to make it work from 0.8V?
Banba, 1999



Assume $V_a = V_b$ (op-amp)
 $I_1 = I_2 = I_3$ (long channels)

choose $\frac{R_x}{R_1}$ to match temp coefficients
 e.s. 10:1
 choose $\frac{R_4}{R_x}$ to scale output, e.s. 1:2

$V_0 = \frac{1}{2} \left(10 \left(\frac{0.2mV}{K} \right) (T) + 0.6 + \left(-\frac{2mV}{K} \right) (T - 300K) \right) V_{D1}$
 $= \frac{1}{2} \left(0.6 + 0.6 \right) + \left(+\frac{2mV}{K} - \frac{2mV}{K} \right) (T - 300K)$
 $= 0.6$

Back to 2 stage.

$$A_v = A_{v0} \left(1 + \frac{s}{\omega_{pm}}\right) \left(1 - \frac{s}{\omega_{zc}}\right)$$

$$\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \left(1 + \frac{s}{\omega_{pm}}\right)$$

RHP zero: push higher w/ R_Z or other trick

Mirror doublet: usually not too much trouble
design for a bit higher PM to address

would be much easier w/ that 2nd pole, but we'd like more gain than just (g_mr_o)²

Problem Headroom


Benefit: single pole? well no, but close

$$\omega_{p1} = \frac{1}{R_0 C_0} \quad R_0 = \frac{1}{2} g_m r_o^2$$

others: ω_{pm}, ω_{zm}

w/ cascode

What is freq response of a common gate?

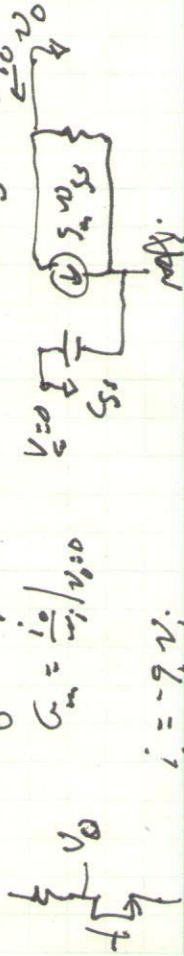


$$i_o = -g_m v_i$$

$$G_m = -g_m$$

Solution: cascode

① telescopic

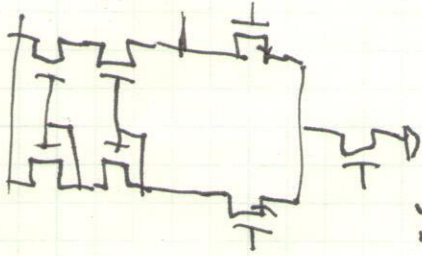

$$G_m = g_{m1}$$

$$R_0 = r_{o1b} \leftarrow 2X$$

$$\text{but } Z_i = \frac{V_i}{I_i} = \frac{1}{g_m + sC_{gs}} = \frac{1}{g_m} \left(1 + \frac{s}{\omega_p}\right)$$

$$\omega_p = \frac{g_m}{C_{gs}}$$



$$i_o = -g_{m1} \left(\frac{1}{g_{m2}} \left(1 + \frac{s}{\omega_{pm}}\right) \right) (-g_{m2})$$

N_{SR}

$$= g_{m1} \frac{1}{1 + \frac{s}{\omega_{pm}}}$$