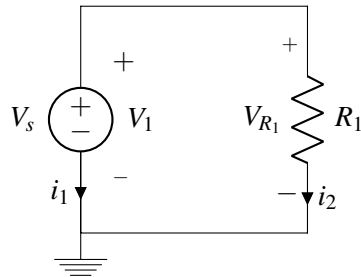



EECS 16A Designing Information Devices and Systems I Discussion 7B

1. Passive Sign Convention and Power

- (a) Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5\text{ V}$ and let $R_1 = 5\ \Omega$.




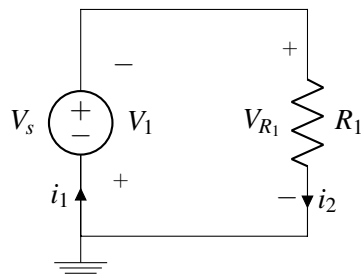- (b) Suppose we change the label of the currents in the circuit to be as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5\text{ V}$ and let $R_1 = 5\ \Omega$.



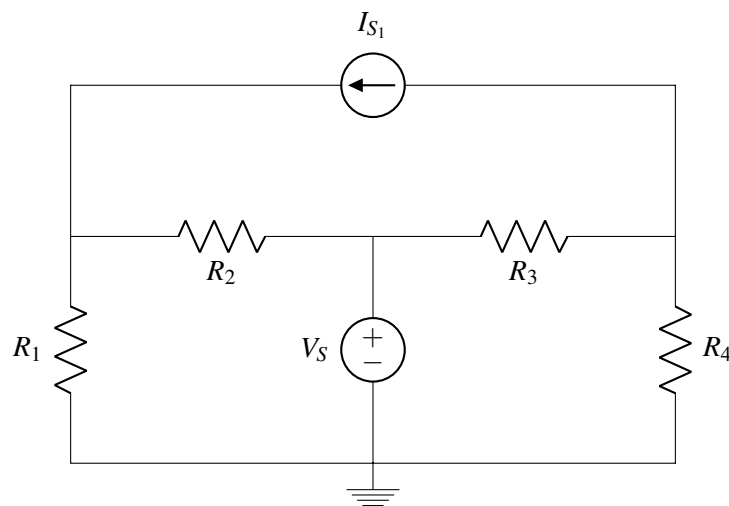2. Circuit Analysis

Setup the matrix to solve for the voltages across and the currents flowing through each component.



3. Resist the Touch

In this question, we will be re-examining the 2-dimensional resistive touchscreen previously discussed in both lecture and lab. The general touch screen is shown in Figure 1 (a). The touchscreen has length L and width W and is composed of a rigid bottom layer and a flexible upper layer. The strips of a single layer are all connected by an ideal conducting plate on each side. The upper left corner is position $(1, 1)$.

The top layer has N vertical strips denoted by y_1, y_2, \dots, y_N . These vertical strips all have cross sectional area A , and resistivity ρ_y .

The bottom layer has N horizontal strips denoted by x_1, x_2, \dots, x_N . These horizontal strips all have cross sectional area A as well, and resistivity ρ_x .

Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally. Also assume that all resistive strips are rectangular as shown by Figure 1 (b).

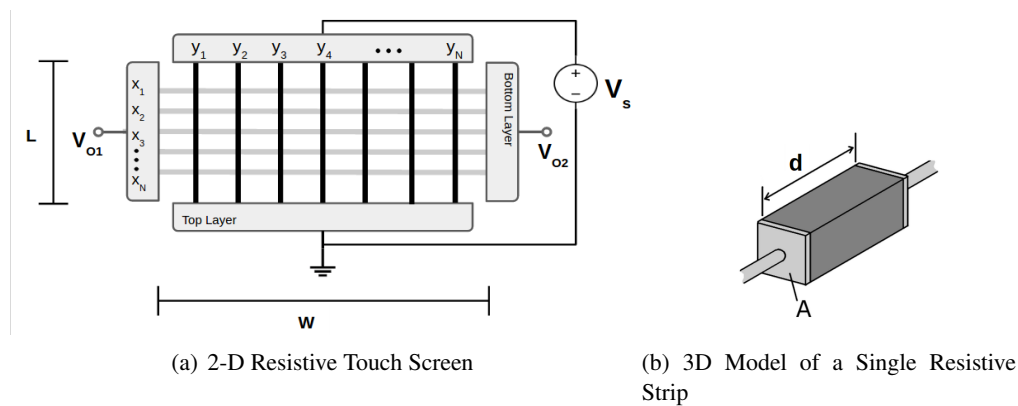
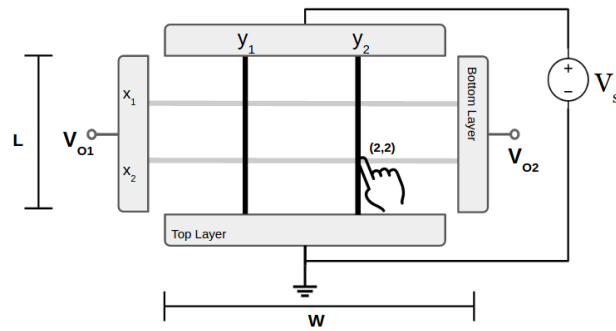


Figure 1:

(a) (3 points) Figure 1(b) shows a model for a single resistive strip. Find the equivalent resistance R_y for the vertical strips and R_x for the horizontal strips, as a function of the screen dimensions W and L , the respective resistivities, and the cross-sectional area A .

(b) (5 points) Consider a 2×2 example for the touchscreen circuit.

Given that $V_s = 3\text{V}$, $R_x = 2000\Omega$, and $R_y = 2000\Omega$, draw the equivalent circuit for when the point $(2, 2)$ is pressed and solve for the voltage at terminal V_{o2} with respect to ground.

Figure 2: 2×2 Case of the Resistive Touchscreen

- (c) (8 points) Suppose a touch occurs at coordinates (i, j) in Figure 1(a). Find an expression for V_{O2} as a function of V_s , N , i , and j . The upper left corner is the coordinate $(1, 1)$ and the upper right coordinate is $(N, 1)$.