

---

# EECS 16A    Designing Information Devices and Systems I


## Fall 2018    Discussion 8A

---


### 1. Equivalence

Find the Thévenin and Norton equivalents across terminals  $a$  and  $b$  for the circuits given below.


(a)

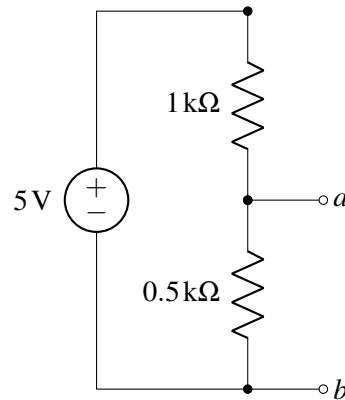


(b)

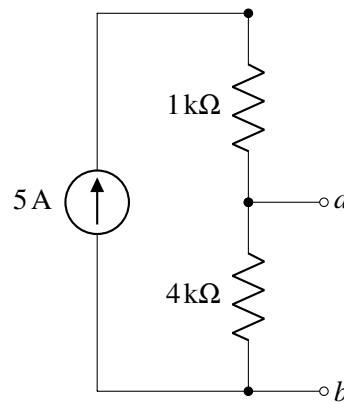


(c)

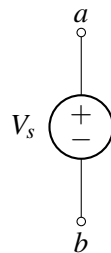


(d)

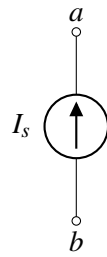

(e) (Practice)

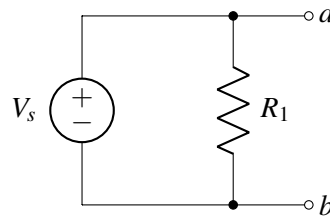

(f) (Practice)

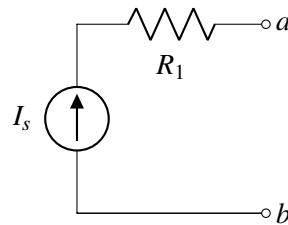


## 2. Super-power


For the following circuits:

- i. Use the superposition theorem to solve for the voltages across the resistors.
- ii. For parts (a) and (b) only, find the power dissipated/generated by all components. Is power conserved?


(a)

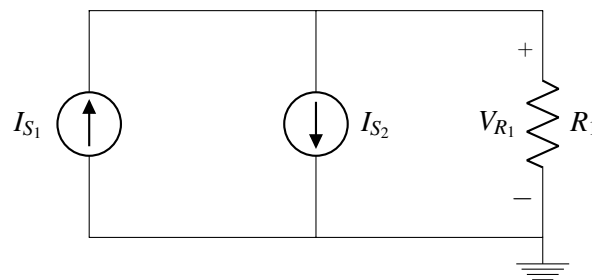

(b)

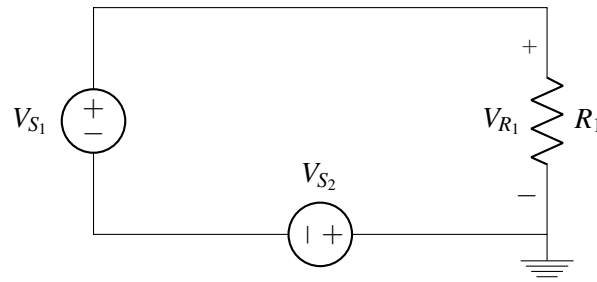


(c)

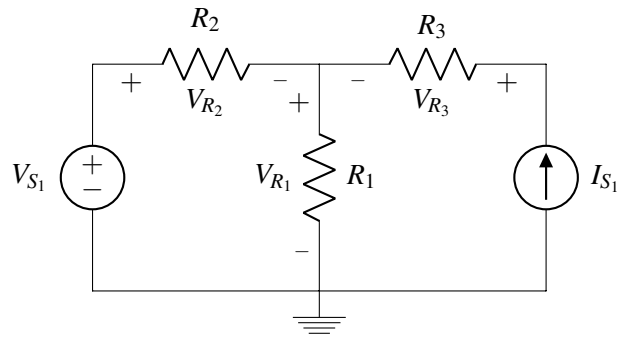
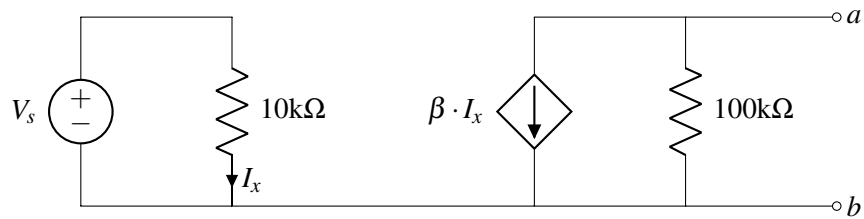
### 3. Equivalence

Find the Norton equivalent of the following circuit across the terminals  $a$  and  $b$  (in terms of  $V_s$  and  $\beta$ ). Note that the current source is dependent on the current  $I_x$ .



### 4. Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals  $A$  and  $B$  using the resistor combination rules for series and parallel resistors.

