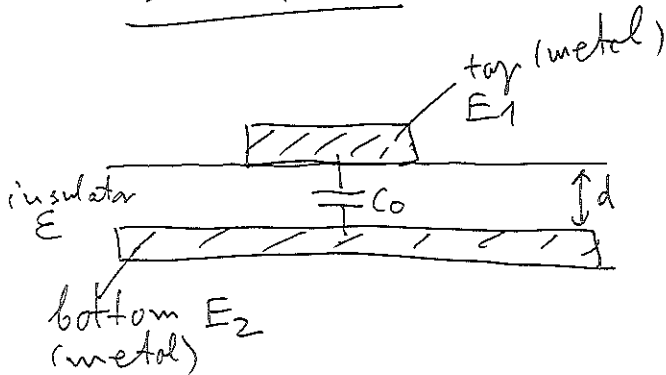



Today:  
Note 17

- \* 2D touchscreen (capacitive)
- \* sensing capacitor
- \* capacitance measurement circuit
- \* comparator (op-amp)

Side view:




Top view:

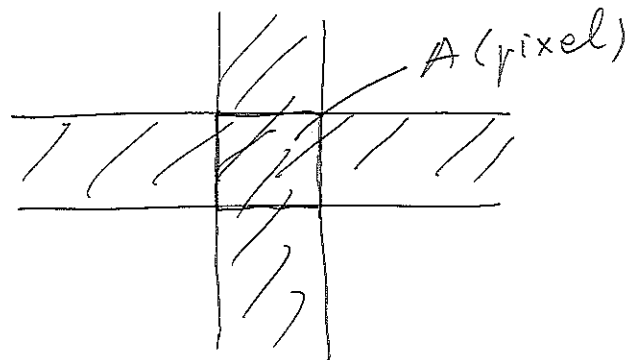


Model w/o touch:

$$\begin{array}{c} | \\ E_1 \\ \hline C_0 \\ \hline | \\ E_2 \end{array} = \epsilon \cdot \frac{A}{d}$$

add insulator:

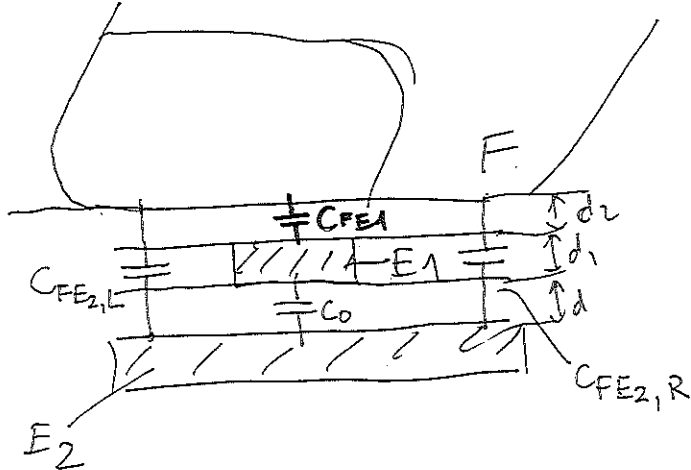


Model with touch:

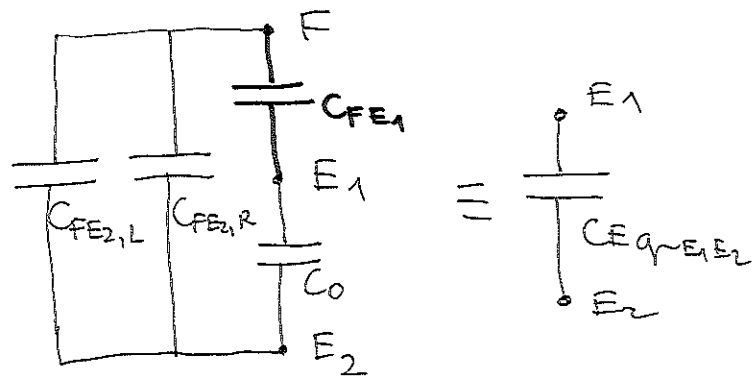


$$C_{eq_{FE_1E_2}} = C_0 + C_{FE_1} \parallel (C_{FE_{2,L}} + C_{FE_{2,R}})$$


(b2)

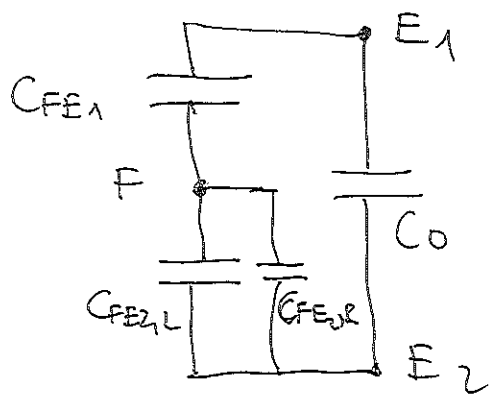

=>

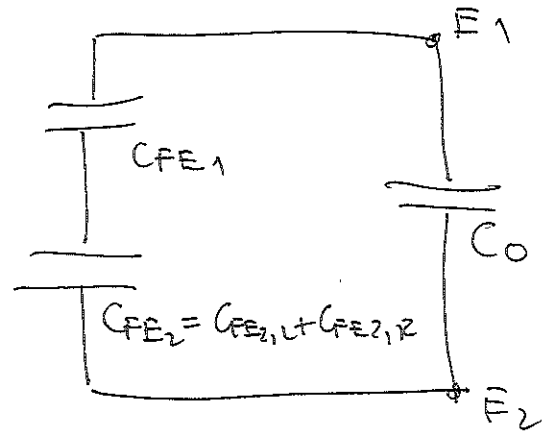


⇓


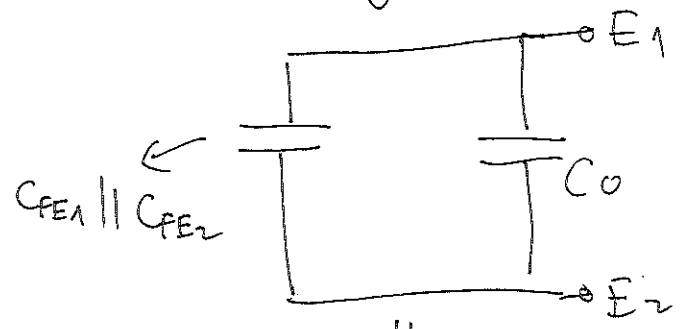


⇓



$C_0 + C_{FE1} \parallel C_{FE2}$

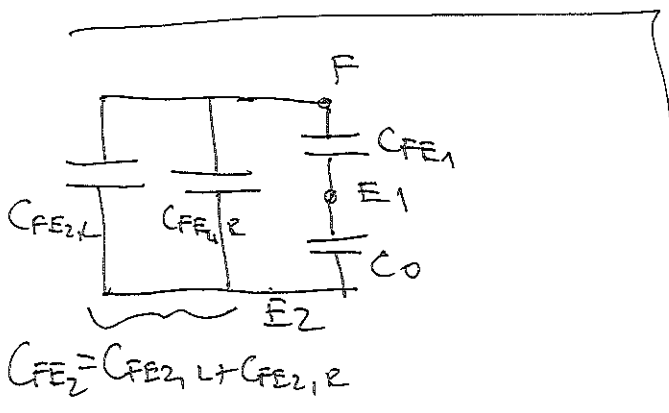

$C_{FE2} = C_{FE2,L} + C_{FE2,R}$

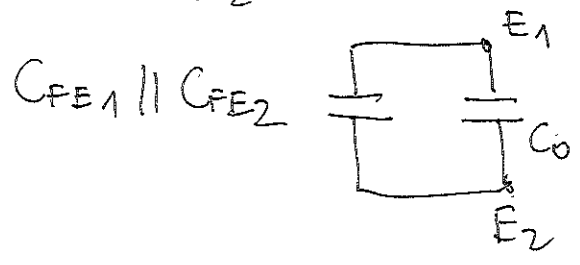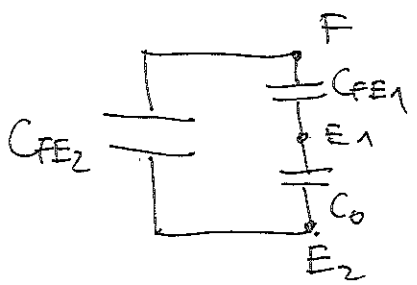

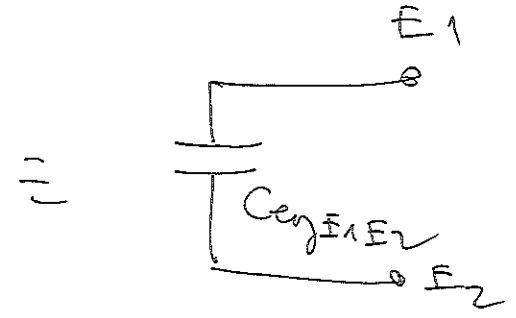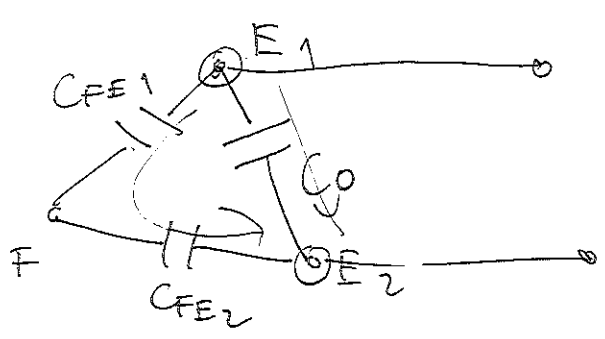$C_{FE1} \parallel C_{FE2} \equiv C_{eq_{E1E2}} = C_0 + C_{FE1} \parallel C_{FE2}$




Touch :

$C_{eq_{E1E2}} = C_0 + \Delta C$

$C_{FE1} \parallel C_{FE2} > 0$

(23)


2D view :

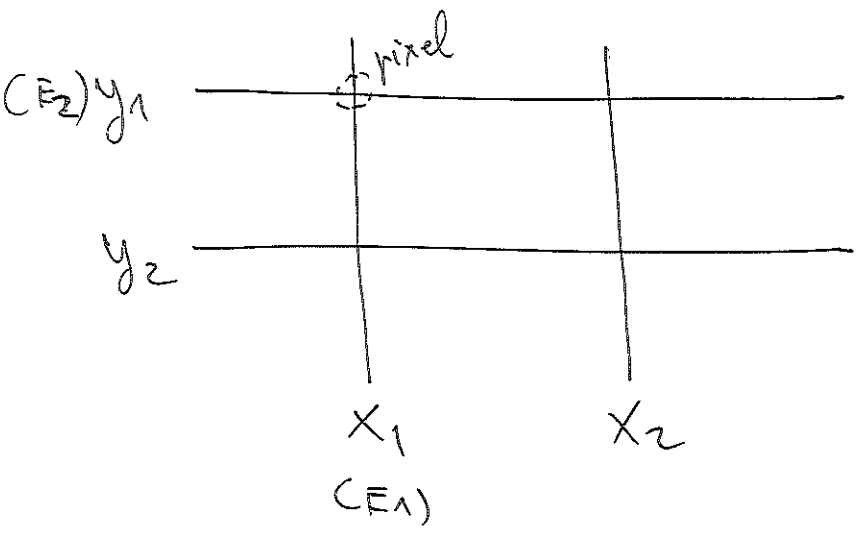


upper left  $(x_1, y_1)$   
⋮

How do we measure the capacitance?

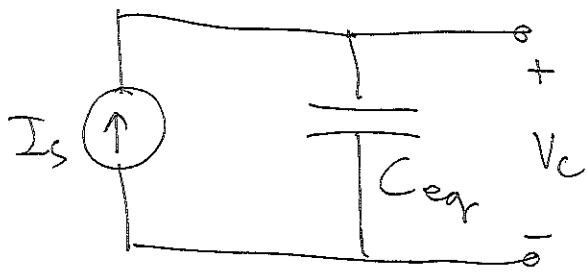Attempt 1: Want to convert capacitance value to voltage:


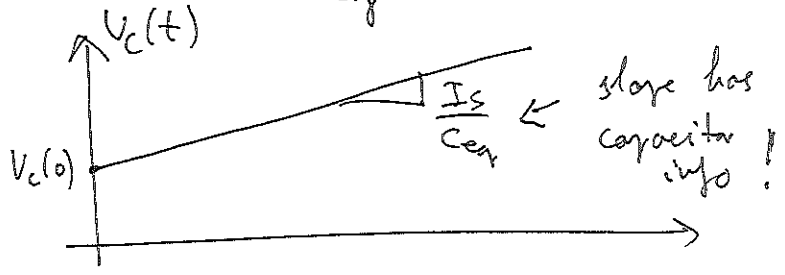
$$V_c(t) = \frac{I_s}{C_{cap}} \cdot t + V_c(0)$$





$V_c(t)$  grows indefinitely  $\Rightarrow$  problem for practical implementation.

In general, for constant  $I_s$  from  $t_0$  to  $t$

$$V_c(t) = \frac{I_s}{C_{cap}} \cdot (t - t_0) + V_c(t_0)$$

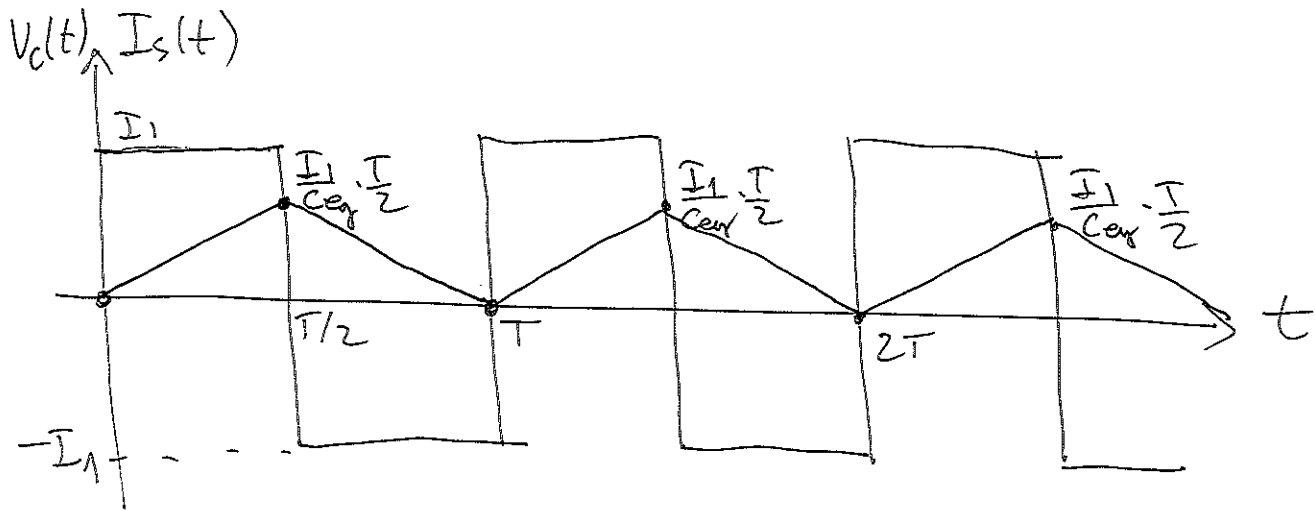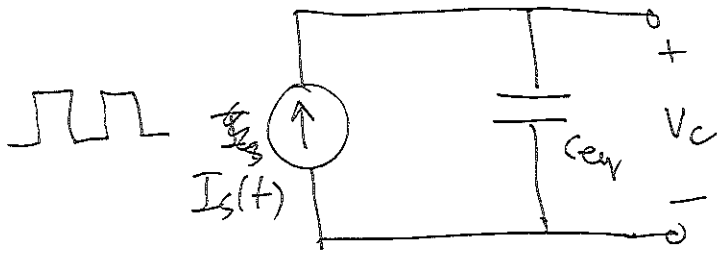(24) Attempt #2: Make current source periodic to limit  $V_c(t)$



$$t \in [0, \frac{T}{2}] : I_s(t) = I_1 \Rightarrow V_c(t) = \frac{I_1}{C_{eq}} \cdot t + V_c(0)$$

$$t \in [\frac{T}{2}, T] : I_s(t) = -I_1 \Rightarrow V_c(t) = -\frac{I_1}{C_{eq}} \cdot (t - \frac{T}{2}) + V_c(\frac{T}{2})$$

$$V_c(\frac{T}{2}) = \frac{I_1}{C_{eq}} \cdot \frac{T}{2}$$

$$V_c(t) = -\frac{I_1}{C_{eq}} \cdot (t - \frac{T}{2}) + \frac{I_1 T}{2 C_{eq}}$$


$$V_c(T) = 0$$

$$\max(V_c(t)) = \frac{I_1}{C_{eq}} \cdot \frac{T}{2}$$

$\Leftarrow$  Cap. info.



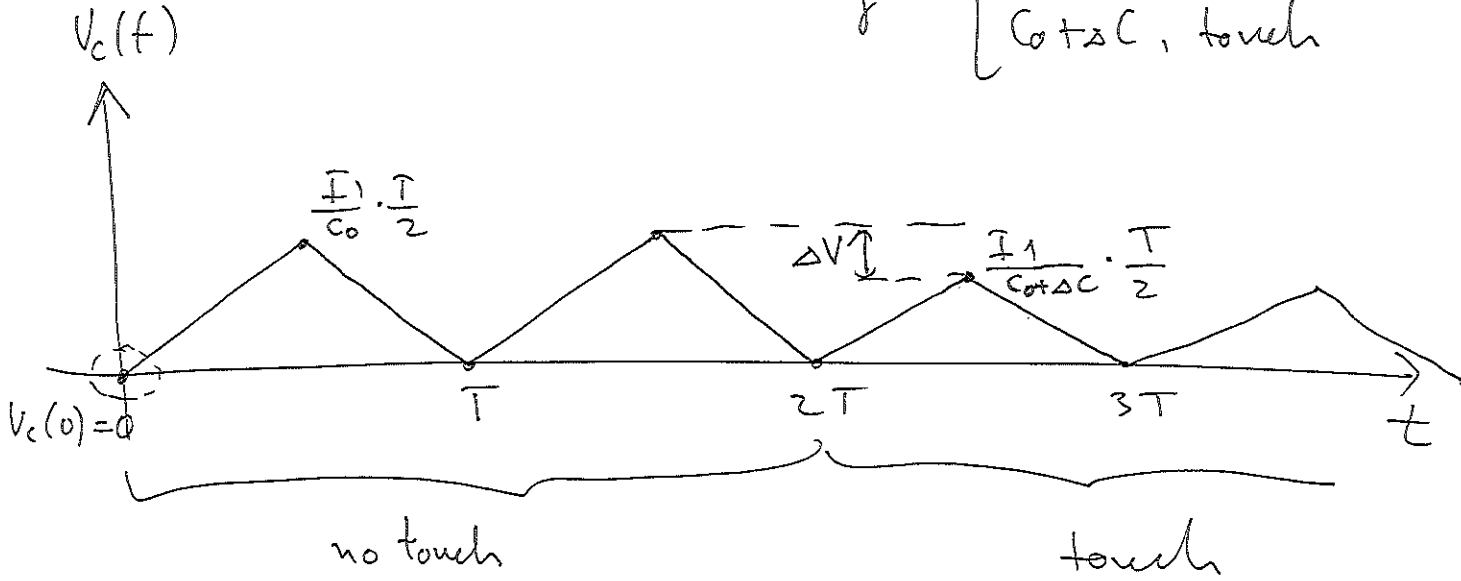
(25)

$$C_{eq} = \begin{cases} C_0, & \text{no touch} \\ C_0 + \Delta C, & \text{touch} \end{cases}$$




small change in  $(V_c(t))_{max} = \left( \frac{I_1}{C_0} - \frac{I_1}{C_0 + \Delta C} \right) \frac{T}{2}$

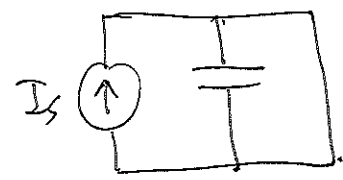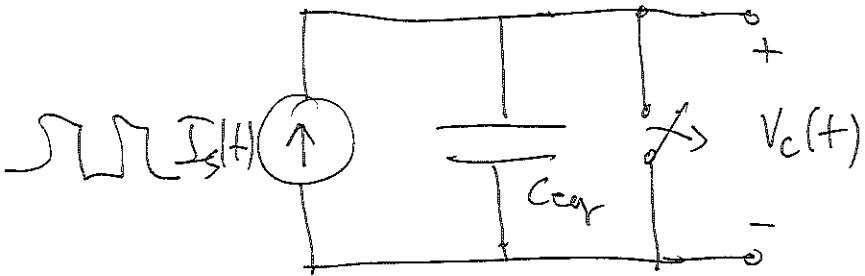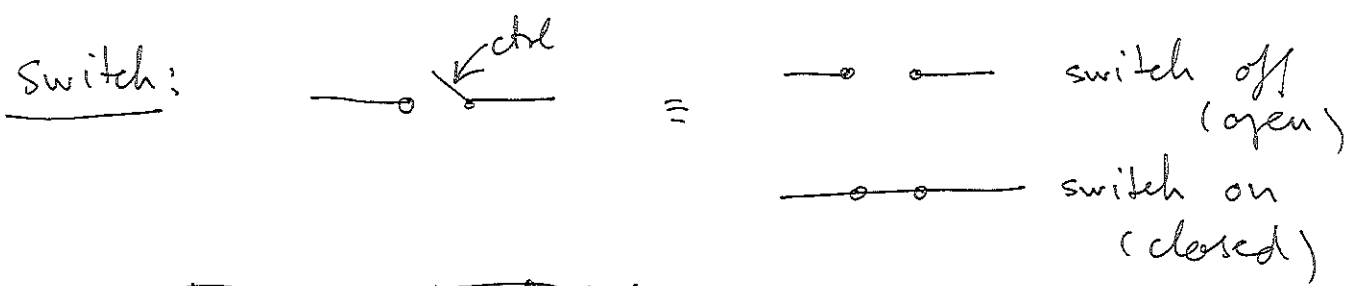
How do we get a bigger charge in voltage?




26a

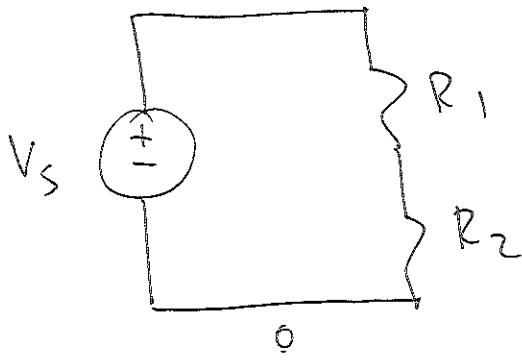

$\equiv$

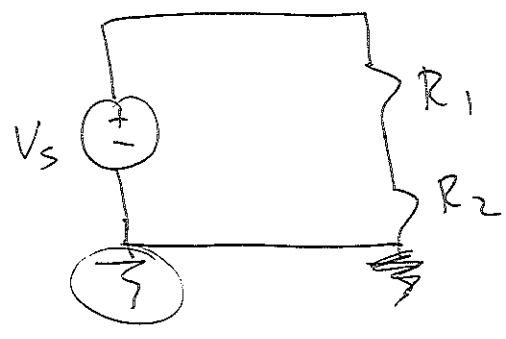


$\equiv$

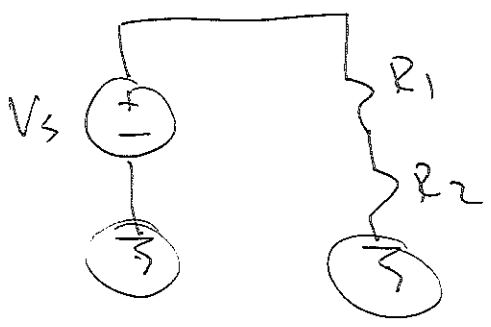


(26) New element: Op-amp

(can be used as a comparator - compare two potentials and determines which one is larger)

Symbol:

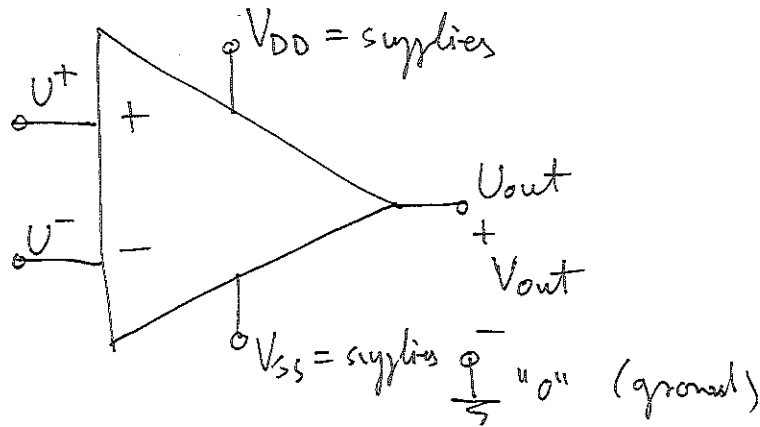

Model:

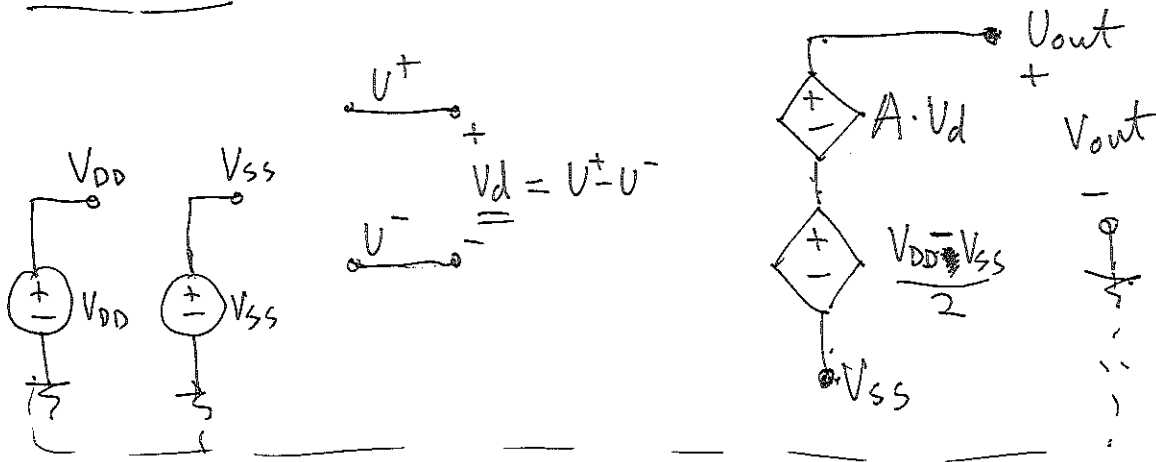

In ideal op-amp  $A \rightarrow \infty$

KVL: 
$$V_{out} = \begin{cases} V_{DD}, & V^* > V_{DD} \\ V_{SS} + \frac{V_{DD} - V_{SS}}{2} + A \cdot V_d, & \text{when } V_{SS} \leq \frac{V_{SS} + V_{DD}}{2} + A \cdot V_d \leq V_{DD} \\ V_{SS}, & V^* < V_{SS} \end{cases} = V^*$$