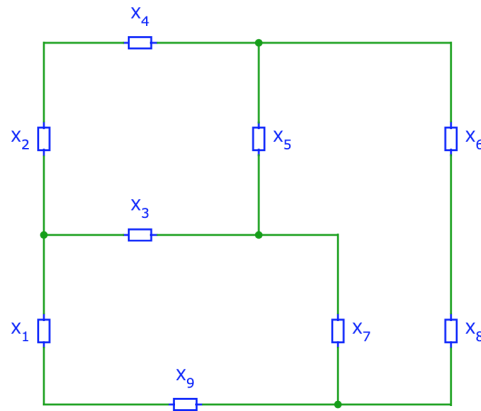


EECS 16A Designing Information Devices and Systems I

Fall 2019 Discussion 6B

1. Nodes and Branches

In the circuit shown below, identify and count all nodes and branches.



Answer: There are seven nodes and nine branches.

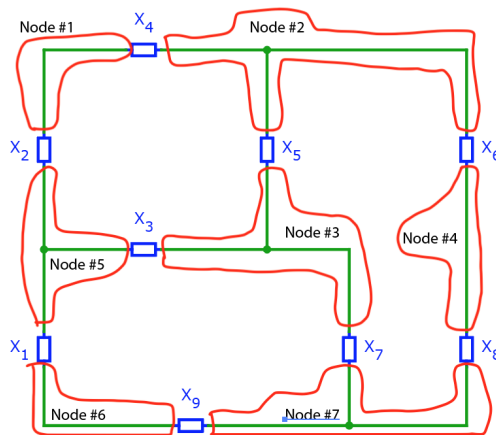


Figure 1: Labeled Nodes


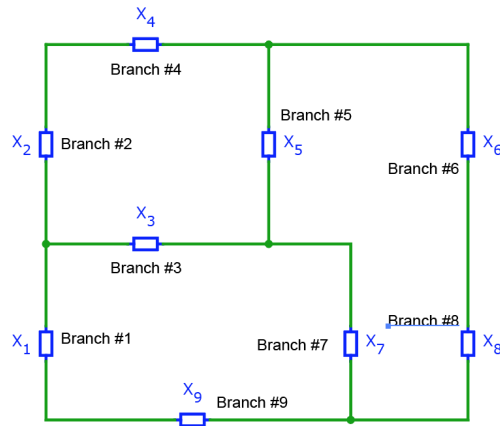


Figure 2: Labeled branches

2. A Simple Circuit

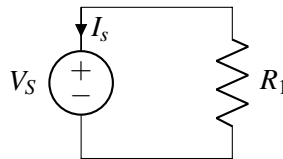- (a) For this problem assume $V_S = 1V$ and $R_1 = 1k\Omega$. Find the current flowing through the voltage source, I_S .



Answer:

Based on Ohms law,

$$I_1 = \frac{V_S}{R_1} \tag{1}$$

Then based on KCL at the top node,


$$I_1 + I_S = 0 \tag{2}$$

$$I_S = -\frac{V_S}{R_1} \tag{3}$$

Plugging in,

$$I_S = -1mA \tag{4}$$

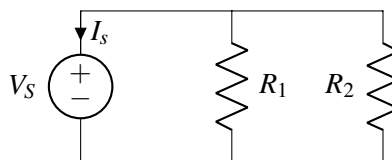- (b) For this problem assume $V_S = 1V$, $R_1 = 2k\Omega$, and $R_2 = 2k\Omega$. Find the current flowing through the voltage source, I_S .



Answer:

Based on Ohms law,

$$I_1 = \frac{V_S}{R_1} \quad (5)$$

$$I_2 = \frac{V_S}{R_2} \quad (6)$$

$$(7)$$

Then based on KCL at the top node,

$$I_1 + I_2 + I_S = 0 \quad (8)$$

$$\frac{V_S}{R_1} + \frac{V_S}{R_2} + I_S = 0 \quad (9)$$


$$I_S = -\left(\frac{V_S}{R_1} + \frac{V_S}{R_2}\right) \quad (10)$$

Plugging in,


$$I_S = -1mA \quad (11)$$

3. (Optional) Divider

For the circuit below, find the voltage V_{out} in terms of the resistances R_1 , R_2 , and V_S .

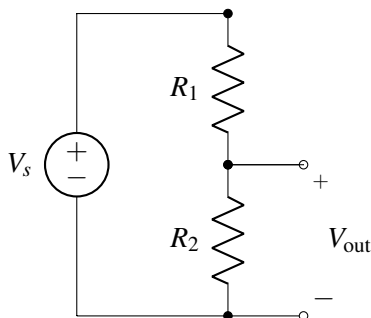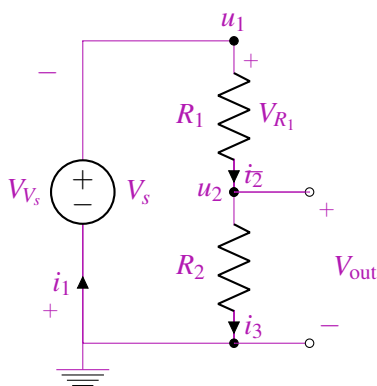**Answer:**

We start by selecting a ground node and labeling all the node potentials and branch currents.



Next we write KCL equations for all the nodes, except for the ground node:

$$i_1 - i_2 = 0$$

$$i_2 - i_3 = 0$$

$$i_3 - i_1 = 0$$

Notice the above equations imply that $i_1 = i_2 = i_3$. We will remove some of the variables and just set $i_x = i_1 = i_2 = i_3$.

Next we write element equations:

$$0 - u_1 = V_{V_s} = -V_s$$

$$u_1 - u_2 = V_{R_1}, V_{R_1} = i_x R_1 \implies u_1 - u_2 = i_x R_1$$

$$u_2 - 0 = V_{R_2}, V_{R_2} = i_x R_2 \implies u_2 - u_0 = i_x R_2$$

We can again remove an extra variable by setting u_1 to V_s . The above equations then become:

$$V_s - u_2 = i_x R_1$$

$$u_2 = i_x R_2$$

Now we have two unknowns, i_x and u_2 , and two equations. We can solve them directly for u_2 . Notice that $V_{\text{out}} = u_2 - 0 = u_2$

$$V_{\text{out}} = u_2 = \frac{R_2}{R_1 + R_2} V_s$$