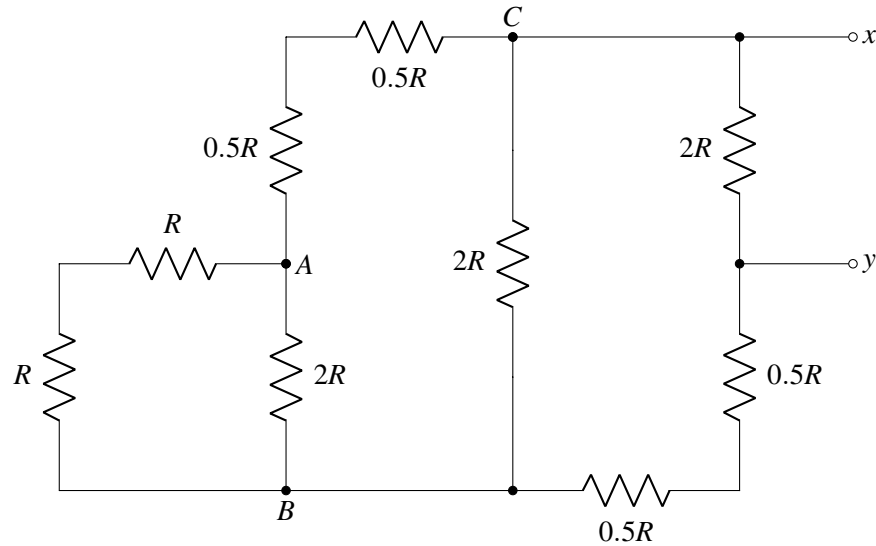


EECS 16A Designing Information Devices and Systems I

Fall 2019 Discussion 8A

1. Equivalence

For the circuit shown below, find the equivalent resistance looking in from points x and y .




2. Superposition


For the following circuits:

- Use the superposition theorem to solve for the voltages across the resistors.
- For parts (a) and (b) only, find the power dissipated/generated by all components. Is power conserved?


(a)

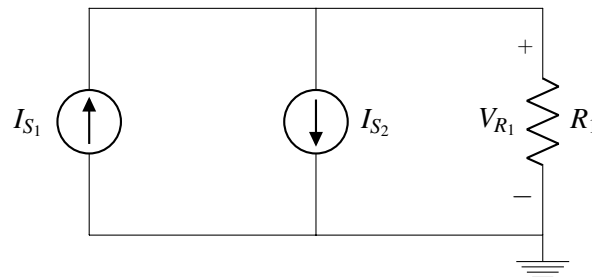

(b)

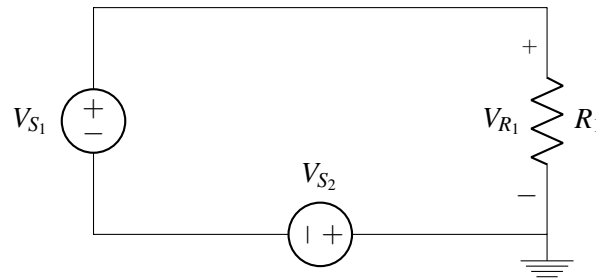

(c)

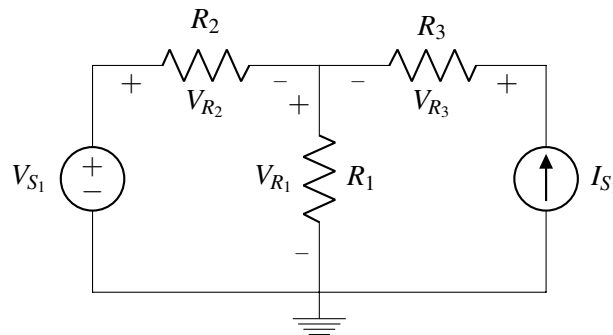

3. Resist the Touch

In this question, we will be re-examining the 2-dimensional resistive touchscreen previously discussed in both lecture and lab. The general touch screen is shown in Figure 1 (a). The touchscreen has length L and width W and is composed of a rigid bottom layer and a flexible upper layer. The strips of a single layer are all connected by an ideal conducting plate on each side. The upper left corner is position $(1, 1)$.


The top layer has N vertical strips denoted by x_1, x_2, \dots, x_N . These vertical strips all have cross sectional area A , and resistivity ρ_x .

The bottom layer has N horizontal strips denoted by y_1, y_2, \dots, y_N . These horizontal strips all have cross sectional area A as well, and resistivity ρ_y .


Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally. Also assume that all resistive strips are rectangular as shown by Figure 1 (b).

(a) (3 points) Figure 1(b) shows a model for a single resistive strip. Find the equivalent resistance R_x for the vertical strips and R_y for the horizontal strips, as a function of the screen dimensions W and L , the respective resistivities, and the cross-sectional area A .

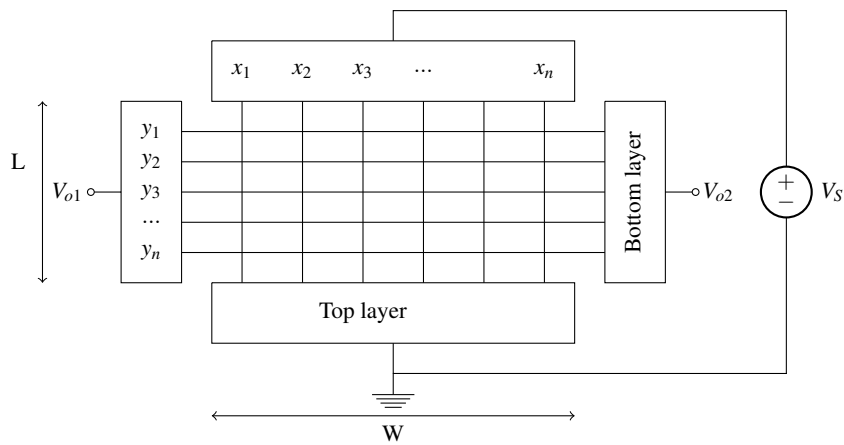(b) (5 points) Consider a 2×2 example for the touchscreen circuit.



(a) 2-D Resistive Touch Screen

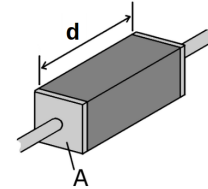

(b) 3D Model of a Single Resistive Strip

Figure 1:

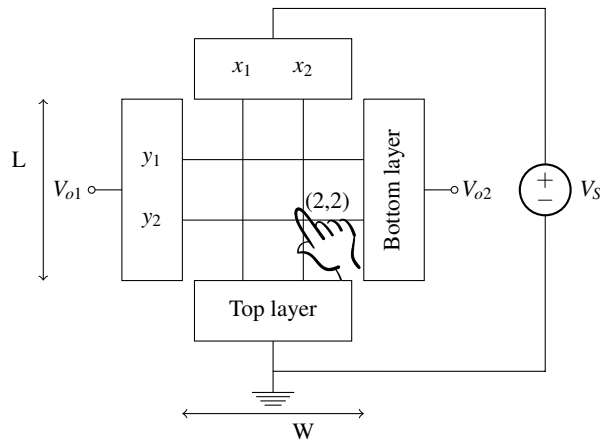


Figure 2: 2 × 2 Case of the Resistive Touchscreen

Given that $V_s = 3\text{V}$, $R_x = 2000\Omega$, and $R_y = 2000\Omega$, draw the equivalent circuit for when the point (2,2) is pressed and solve for the voltage at terminal V_{O2} with respect to ground.

(c) (8 points) Suppose a touch occurs at coordinates (i, j) in Figure 1(a). Find an expression for V_{O2} as a function of V_s , N , i , and j . The upper left corner is the coordinate $(1, 1)$ and the upper right coordinate is $(N, 1)$.