

---

EECS 16A    Designing Information Devices and Systems I  
 Fall 2019    Practice Handout

---


**This handout contains a selection of problems that will serve as preparation for Midterm 2.**

### 1. Charge Sharing

In the circuit below, switch  $S_1$  is initially open. Capacitor  $C_1 = 10^{-3}\text{F}$  is initially charged to  $V_1 = 3\text{V}$  and capacitor  $C_2 = 3 \times 10^{-3}\text{F}$  is initially charged to  $V_2 = 2\text{V}$ .


Now  $S_1$  is closed. Calculate the new value of  $V_2$ .

*Hint:* Charge is conserved.

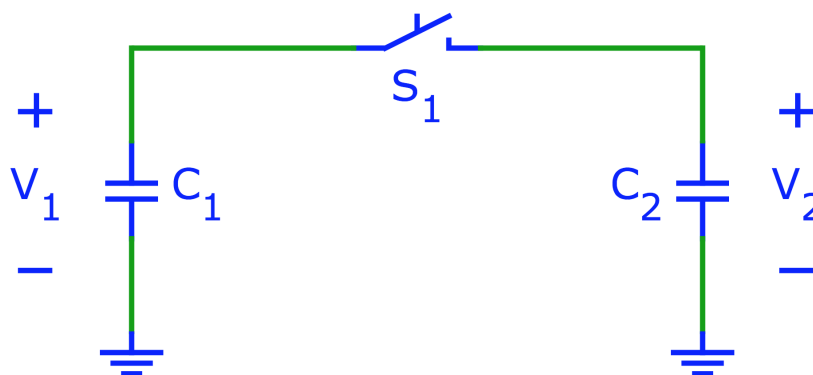
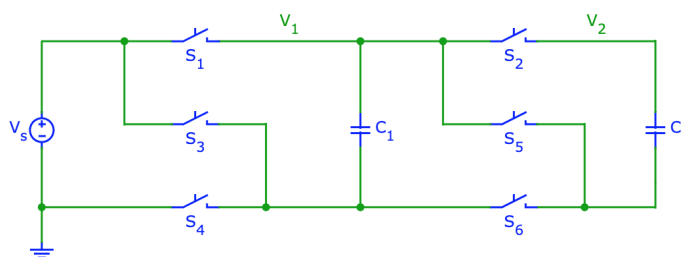
### 2. Voltage Booster


We have made extensive use of resistive voltage dividers to reduce voltage. What about a circuit that boosts voltage to a value greater than the supply  $V_S = 5\text{V}$ ? We can do this with capacitors!




- In the circuit above switches  $S_1$ ,  $S_2$ ,  $S_4$  and  $S_6$  are initially closed and switches  $S_3$  and  $S_5$  open. Calculate voltages  $V_1$  and  $V_2$ .
- Now, after the capacitors are charged, switches  $S_1$ ,  $S_2$ ,  $S_4$  and  $S_6$  are opened and switches  $S_3$  and  $S_5$  closed. Calculate the new voltages  $V_1$  and  $V_2$ .
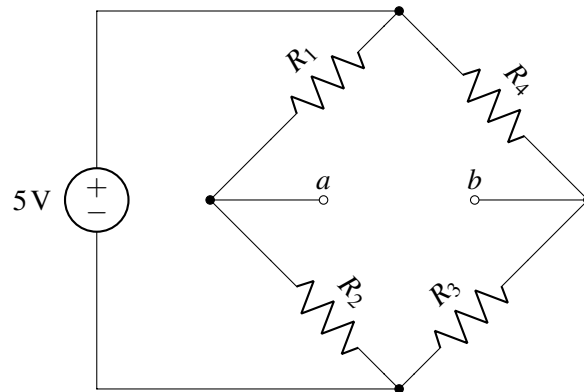
### 3. Wheatstone Bridge

Thévenin equivalence is a powerful technique we can use to analyze the Wheatstone bridge circuit shown below. This circuit is used in many sensor applications where resistors  $R_1 - R_4$  are varying with respect to some external actuation. For example, it can be used to build a strain gauge or a scale (remember Fruity Fred from HW 7). In that case the resistors  $R_1 - R_4$  would vary with respect to a strain caused by a force, and the Wheatstone Bridge circuit would translate that variation into a voltage difference across the “bridge” terminals  $a$  and  $b$ . Assume that  $R_1 = 2\text{ k}\Omega$ ,  $R_2 = 2\text{ k}\Omega$ ,  $R_3 = 1\text{ k}\Omega$ ,  $R_4 = 4\text{ k}\Omega$



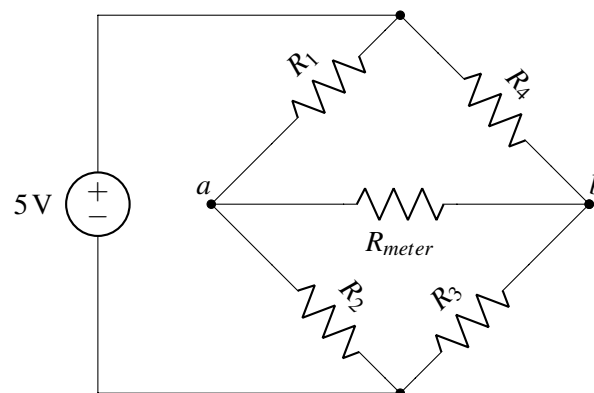- Calculate the voltage  $V_{ab}$  between the two terminals  $a$  and  $b$ .
- Next, draw the Thévenin equivalent of the Wheatstone bridge circuit.
- Now assume that you are trying to measure the voltage  $V_{ab}$  using a voltmeter, whose resistance is  $R_{meter}$ , so you end up with the circuit below.



Unfortunately, your voltmeter is far from ideal, so  $R_{meter} = 4\text{ k}\Omega$ . Is the voltage  $V_{ab}$  you found in part (a) equal to the new voltage  $V_{R_{meter}}$  across the voltmeter resistor? Why or why not? Calculate the current  $I_{R_{meter}}$  through the voltmeter resistor and the voltage  $V_{R_{meter}}$  across the meter resistor.

### 4. Digital to Analog Converter (DAC)


For some outputs, such as audio applications, we need to produce an analog output, or a continuous voltage from 0 to  $V_s$ . These analog voltages must be produced from digital voltages, that is sources, that can only be  $V_s$  or 0. A circuit that does this is known as a Digital to Analog Converter. It takes a binary representation of a number and turns it into an analog voltage.

The output of a DAC can be represented with the equation shown below:


$$V_{\text{out}} = V_s \sum_{n=0}^N \frac{1}{2^n} \cdot b_n$$

where each binary digit  $b_n$  is multiplied by  $\frac{1}{2^n}$ .

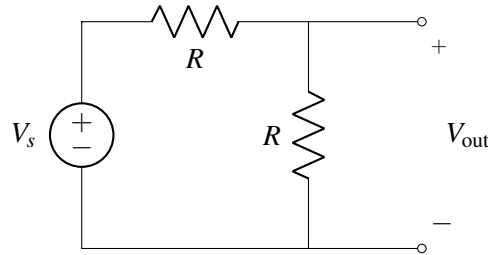(a) We know how to take an input voltage and divide it by 2:



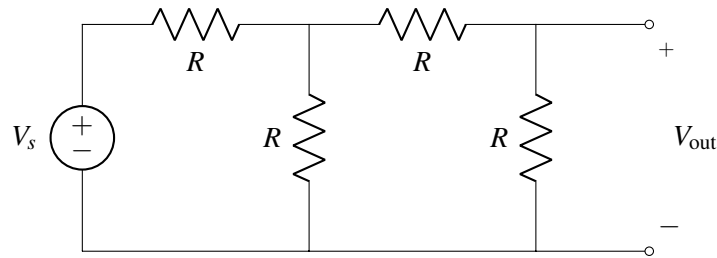
To divide by larger powers of two, we might hope to just “cascade” the above voltage divider. For example, consider:




Calculate  $V_{\text{out}}$  in the above circuit. Is  $V_{\text{out}} = \frac{1}{4}V_s$ ?

(b) The  $R$ - $2R$  ladder, shown below, has a very nice property. For each of the circuits shown below, find the equivalent resistance looking in from points  $a$  and  $b$ . Do you see a pattern?


i.

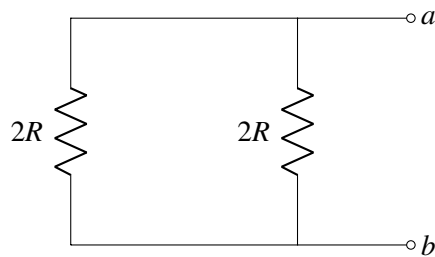


ii.

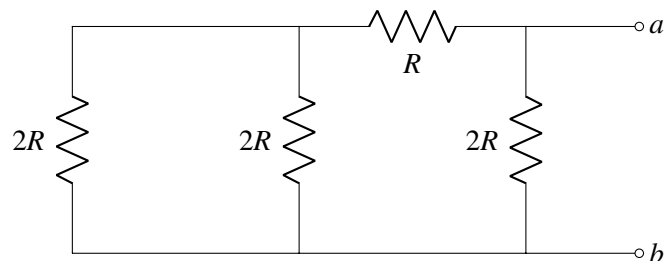


iii.

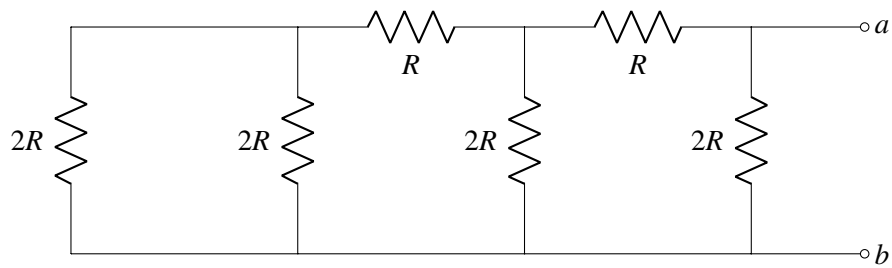

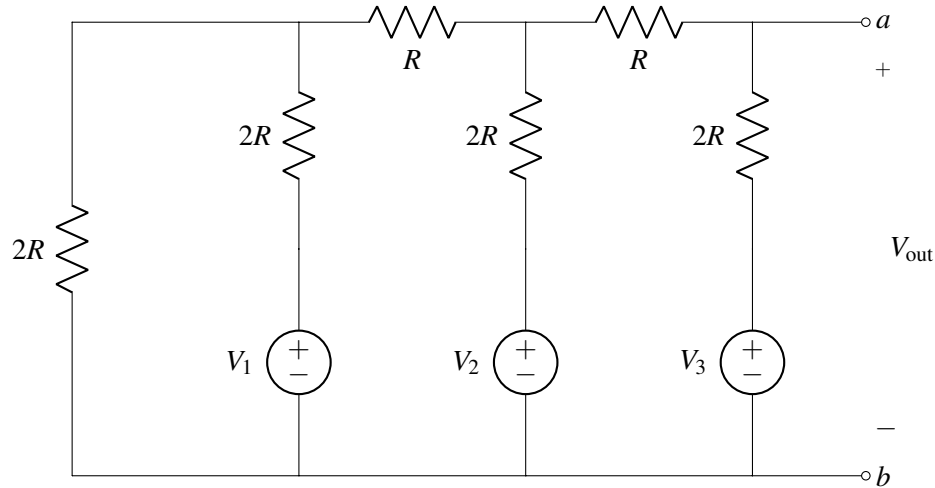(c) The following circuit is an  $R$ - $2R$  DAC. To understand its functionality, use superposition to find  $V_{out}$  in terms of each  $V_k$  in the circuit.



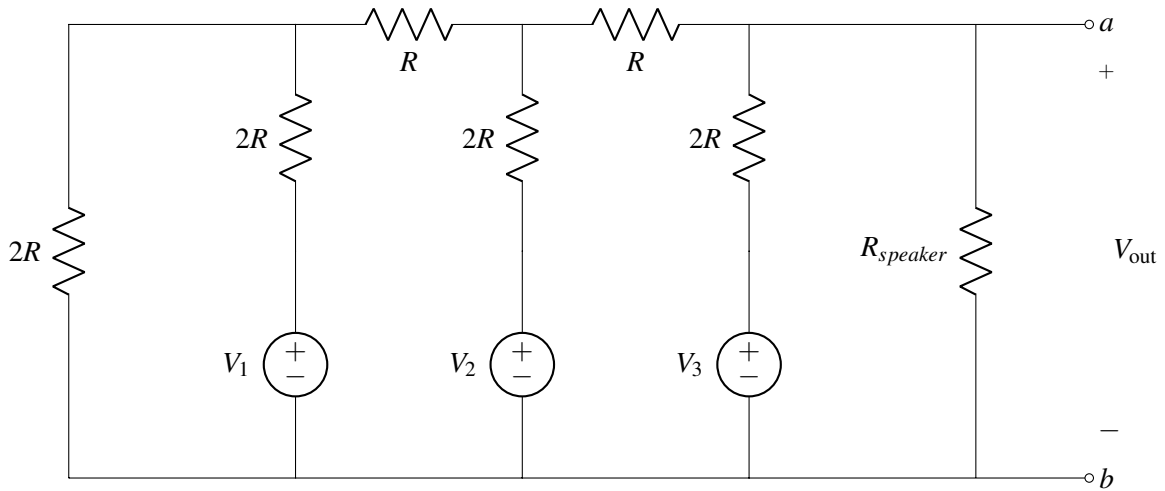- (d) We've now designed a 3-bit  $R$ - $2R$  DAC. What is the output voltage  $V_{out}$  if  $V_2 = 1\text{ V}$  and  $V_1 = V_3 = 0\text{ V}$ ?
- (e) Draw the Thévenin equivalent of the above circuit, looking in from the terminals  $a$  and  $b$  with  $V_2 = 1\text{ V}$  and  $V_1 = V_3 = 0\text{ V}$ .
- (f) Suppose that we now attach a speaker to the DAC with a resistance of  $R_{speaker} = 50\Omega$  as shown in the figure below. Assume also, that the value of  $R$  is  $50\Omega$  as well. What is the voltage across the speaker and the power dissipated by the speaker? *Hint:* Use the Thevenin equivalent circuit to calculate the above.



- (g) Repeat part (f) now assuming that the speaker resistance is  $100\Omega$ . The value of  $R$  remains  $50\Omega$ . How do the power and voltage values you found in the two parts compare? Why is the voltage across the speaker in both cases lower than  $V_{th}$ ?

**5. Challenge Problem: Average**

The circuit in Figure 1 below operates in time steps  $k$ , as illustrated in Figure 2. Each step is of duration  $T$ . During each step, switch  $S_2$  is opened, and then switch  $S_1$  is closed immediately afterwards. Then, after time  $T/2$ , switch  $S_1$  is opened just before switch  $S_2$  is closed.

At the end of each time step the input  $V_{in}(kT)$  changes and the process repeats.

Derive an expression for  $V_2(kT)$  as a function of  $V_{in}(kT)$ . Use  $C_1 = pC_0$  and  $C_2 = (1 - p)C_0$ .

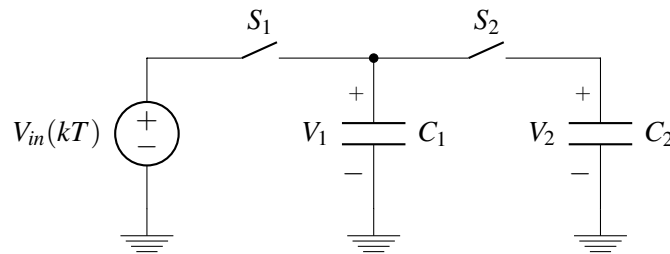


Figure 1: Averaging circuit

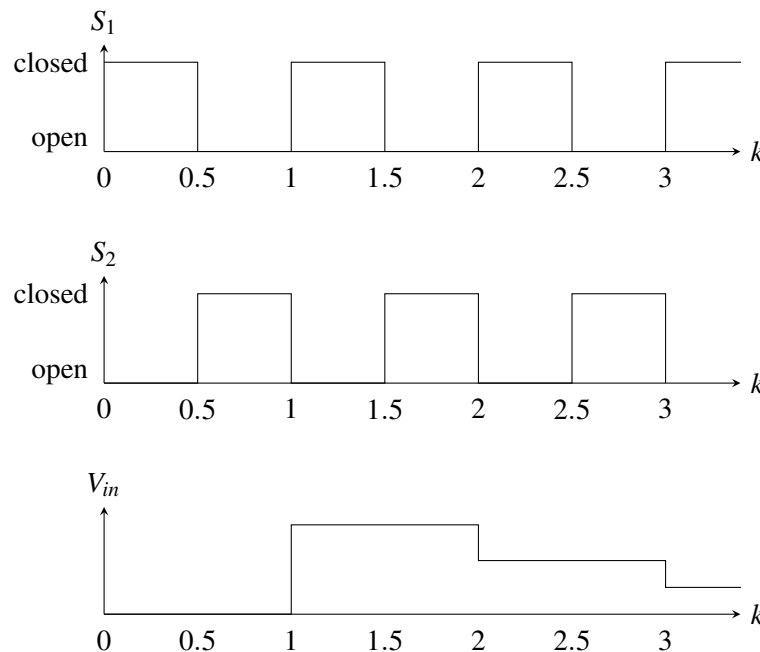


Figure 2: Timing diagram