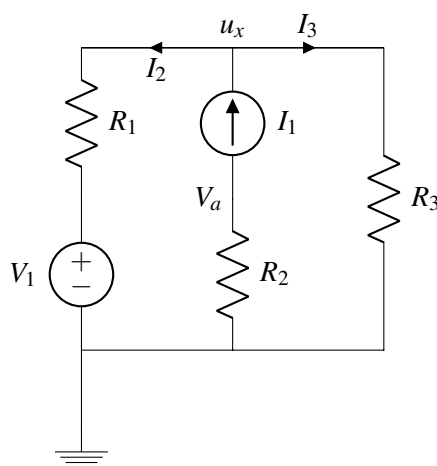


1. Superposition

Learning Goal: This problem aims to make students familiar with the technique of superposition. It will also show how to nullify different types of sources in the process.

Relevant Notes: [Note 15: Section 15.3](#) goes over the principle of superposition.

Solve the following circuit for u_x using superposition. Let $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 2\Omega$, $V_1 = 12V$, and $I_1 = 3A$.



(a) Find u_x when only V_1 is active.

(b) Find u_x when only I_1 is active.

(c) Use your results from the last two parts to find u_x when all the sources are active.


2. Equivalence in Capacitive Networks

Learning Goal: This objective of this problem is to practice finding equivalent capacitance for series/parallel network of capacitors.


Relevant Notes: [Note 16](#) derives the equivalent capacitance formula for series/ parallel capacitors.

For all of the following networks find an expression or a numerical value for the equivalent capacitance between terminals A and B.

(a)

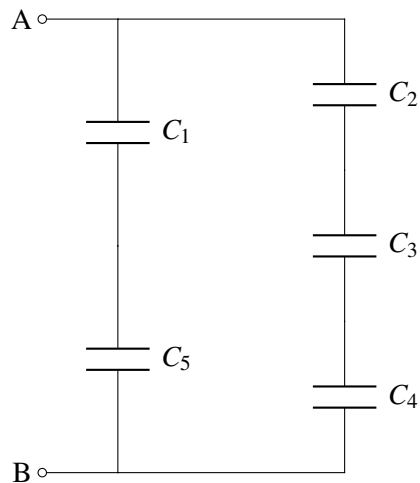

(b)

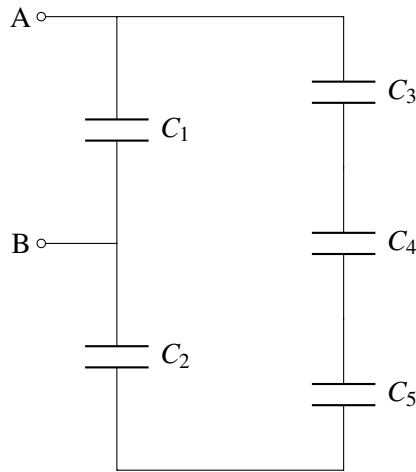


3. Capacitor with a Periodic Current Source


Learning Goal: This problem aims to make students familiar with the charging/ discharging response of a capacitor.

Relevant Notes: [Note 17](#) covers capacitive behavior in the presence of difference types of current sources.

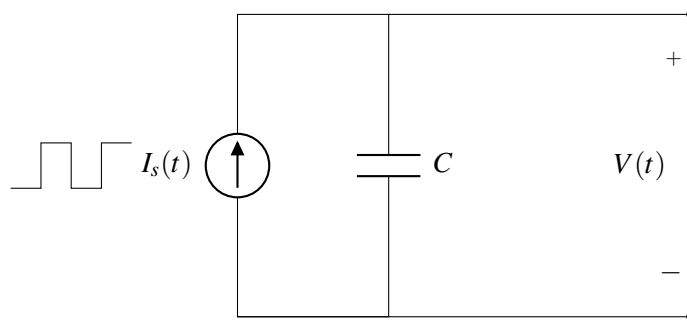Capacitive touchscreen requires detection of capacitance change due to touch. If we connect a known current source I_s to the capacitor and measure the voltage across the capacitor V , we will be able to solve for the capacitance C . So we build the following circuit to measure with a periodic current source:




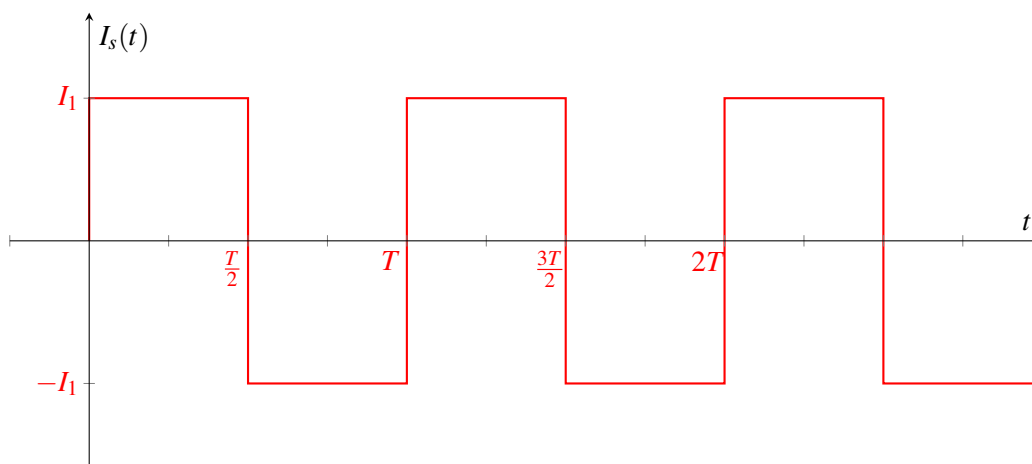(a) Let us assume the current I_s is a function of time as follows:



What does the voltage V look like with this current source? Let's assume that the capacitor is initially uncharged (i.e. $Q = 0$). Since $Q = CV$, this means that at time $t = 0$ the voltage $V = 0$.

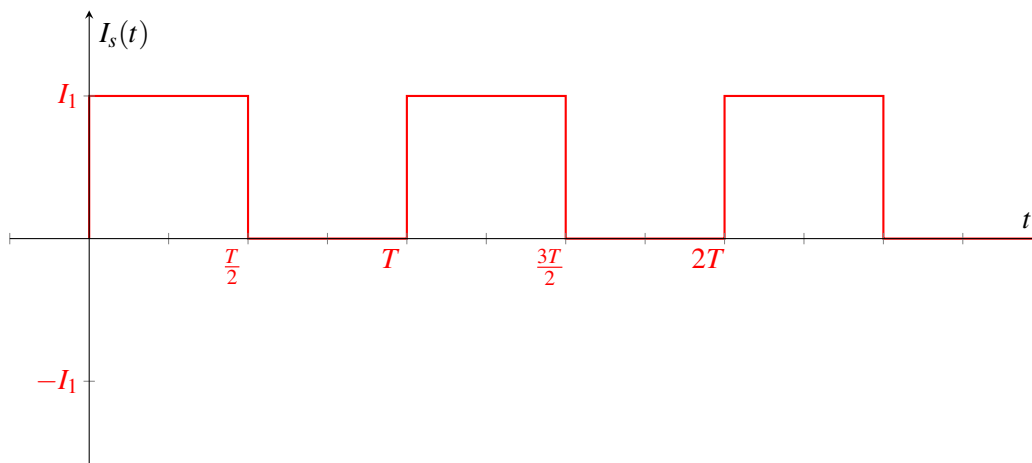(b) Now let us assume the current I_s is a function of time as follows:



What does the voltage V qualitatively look like with this current source? Draw out on the above graph how the voltage changes over time, starting at time $t = 0$. Let's assume that the capacitor is initially uncharged (i.e. $Q = 0$). Since $Q = CV$, this means that at time $t = 0$ the voltage $V = 0$.