

# EECS 16A Designing Information Devices and Systems I Discussion 8A

## 1. Resist the Touch

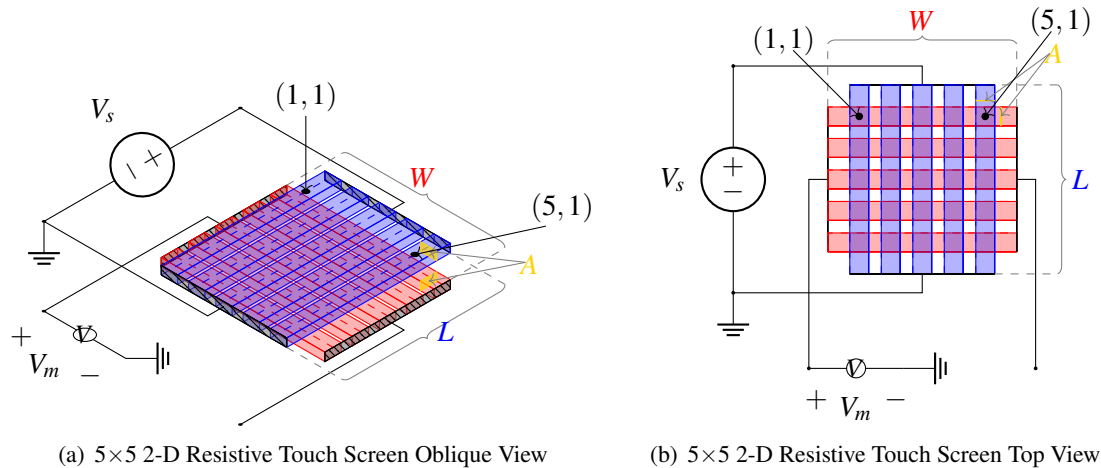


Figure 1:  $N \times N$  Resistive Touch Screen,  $N = 5$

In this question we will be re-examining the 2-dimensional resistive touchscreen. This touchscreen, is slightly different to the one shown in lecture and more like the one we will be examining in lab.

The touchscreen has length  $L$  and width  $W$  and is composed of a rigid bottom-layer and a flexible top-layer. Instead of having two continuous resistive sheets on the top and bottom layers, this is a simpler implementation with  $N$  vertical strips of conductive material in the top layer and  $N$  horizontal strips of conductive material in the bottom layer. The strips of a single layer are all connected by an ideal conducting plate on each side. All strips have resistivity,  $\rho$ , and cross-sectional area,  $A$ .

Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point in Figure 1(b) is position  $(1,1)$ , and the upper right touch point is  $(N,1)$ . The spacing between the strips in the top layer is  $\frac{W}{N+1}$ , and the spacing between the strips in the bottom layer is  $\frac{L}{N+1}$ .

- (a) Find the resistance  $R_y$  for a single vertical blue strip and  $R_x$  for a single horizontal red strip, as a function of the screen dimensions  $W$  and  $L$ , the strip resistivity  $\rho$ , and the cross-sectional area  $A$ .

**Answer:** The equation for resistance is  $R = \frac{\rho l}{A}$

Therefore for the bottom red horizontal resistive strips we have,  $R_x = \frac{\rho W}{A}$ .

For the top blue vertical resistive strips,  $R_y = \frac{\rho L}{A}$ .

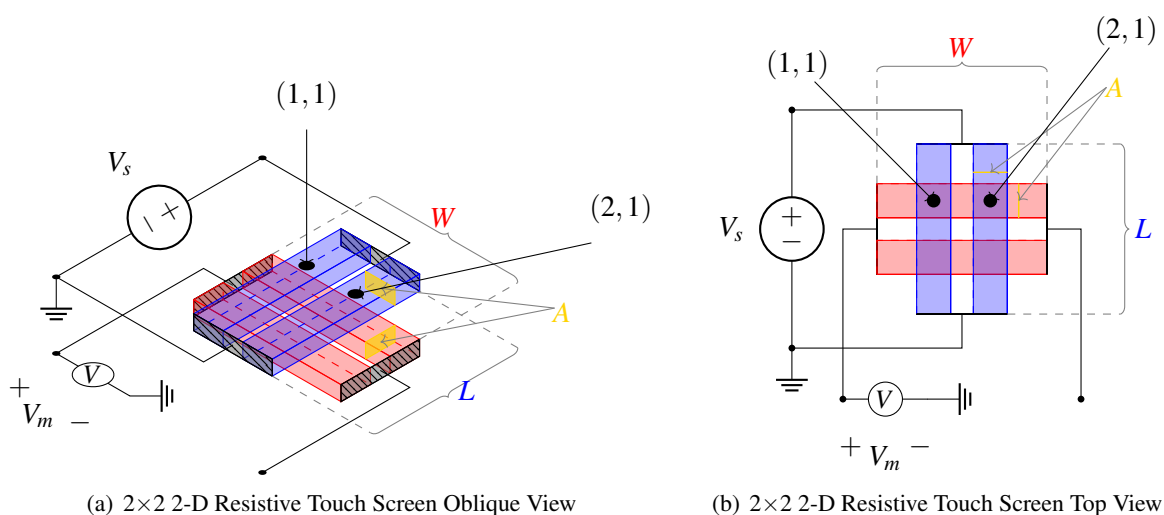


Figure 2:  $2 \times 2$  Resistive Touch Screen

(b) Consider a  $2 \times 2$  example for the touchscreen circuit, shown in Figure 2.

Assume that we connect a voltage source  $V_s$ , between the top and bottom terminals of the blue strips, and a voltmeter  $V_m$  to one of the left or right terminals as depicted in the diagram.


If  $V_s = 3\text{ V}$ ,  $R_x = 2000\Omega$ , and  $R_y = 2000\Omega$ , draw the equivalent circuit for when the point  $(2, 2)$  is pressed and solve for the measured voltage,  $V_m$ , with respect to ground.

Reminder: all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point is position  $(1, 1)$ . The spacing between the strips in the top layer is  $\frac{W}{N+1}$ , and the spacing between the strips in the bottom layer is  $\frac{L}{N+1}$ .

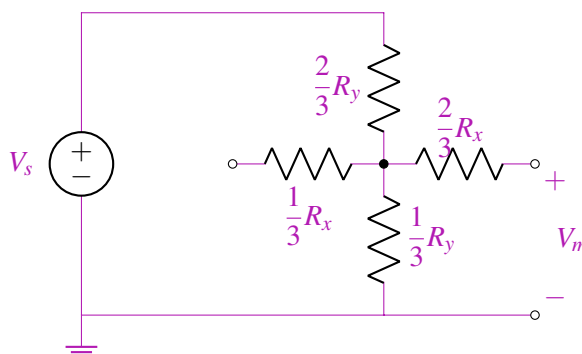**Answer:**

Since all of the resistive strips are equally spaced, the resistor above point  $(2, 2)$  on the vertical blue strip becomes  $\rho \frac{2L}{A} = \frac{2}{3}\rho \frac{L}{A} = \frac{2}{3}R_y$ , and the resistor below point  $(2, 2)$  on the vertical strip becomes  $\rho \frac{L}{3A} = \frac{1}{3}\rho \frac{L}{A} = \frac{1}{3}R_y$ .

The bottom layer red resistors, although they must be drawn in the equivalent circuit, do not affect the measured voltage,  $V_m$ , as there are open circuits, leading to no currents through those resistors, and therefore no voltage drops over either of them.



Observing that the rightmost top layer blue resistive strip forms a voltage divider, and remembering that there is no voltage drop across the dangling  $R_x$  resistors, we can determine  $V_m$  using the voltage divider equation.

$$\text{Therefore, } V_m = V_{(2,2)} = V_s \frac{\frac{1}{3}R_y}{\frac{1}{3}R_y + \frac{2}{3}R_y} = \frac{1}{3}V_s = 1\text{V.}$$

- (c) Suppose a touch occurs at coordinates  $(i, j)$  for an arbitrary  $N \times N$  touchscreen, and the voltage source and meter are connected as in the figures. A  $5 \times 5$  example is shown in Figure 1(b). Find an expression for  $V_m$  as a function of  $V_s$ ,  $N$ ,  $i$ , and  $j$ . Again, the upper left corner is the coordinate  $(1, 1)$  and the upper right coordinate is  $(N, 1)$

**Answer:** The voltage does not depend on the  $x$  coordinate, as the meter is connected to the red dangling resistors along the horizontal. We will only be able to detect changes in the  $y$  coordinate. If the touch point occurs at  $(i, j)$ , the  $i$ -th blue vertical bar from the left will be split into lengths of  $L_{top} = \frac{j}{N+1}L$  and  $L_{bottom} = \frac{N+1-j}{N+1}L$  at the  $j$ -th touch point from the top. The voltage divider takes the voltage over the bottom resistor, so we will see  $V_m = \frac{L_{bottom}}{L}V_s = \frac{N+1-j}{N+1}V_s = \frac{N+1-j}{N+1}V_s$


- (d) Optional / Fun: Experiment with the TinkerCad models below to validate the theoretical results you just derived.

TinkerCad model of  $2 \times 2$  equivalent circuit: <https://www.tinkercad.com/things/0wIXz3MkD7B>

TinkerCad model of  $3 \times 2$  equivalent circuit: <https://www.tinkercad.com/things/k5oolj2tUEN>
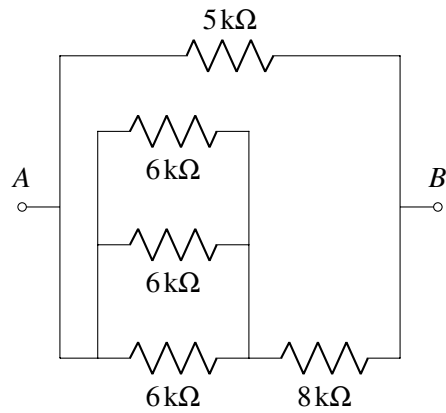
## 2. Practice: Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals  $A$  and  $B$  using the resistor combination rules for series and parallel resistors.



**Answer:**

$$5\text{ k}\Omega \parallel ((6\text{ k}\Omega \parallel 6\text{ k}\Omega \parallel 6\text{ k}\Omega) + 8\text{ k}\Omega) = 5\text{ k}\Omega \parallel (2\text{ k}\Omega + 8\text{ k}\Omega) = 5\text{ k}\Omega \parallel 10\text{ k}\Omega = 3.33\text{ k}\Omega$$