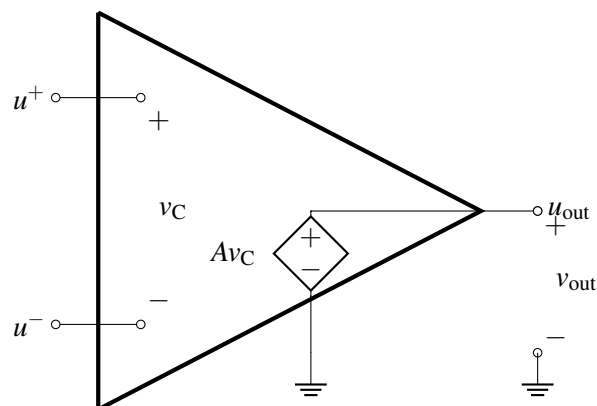


**1. Op-Amp Rules and Negative Feedback Rules**

Here is an equivalent circuit of an op-amp (where we are assuming that  $V_{SS} = -V_{DD}$ ) for reference:



- (a) What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are  $I^+$  and  $I^-$ )? Based on this answer, what are some of the advantages of using an op-amp in your circuit designs?

**Answer:**


The  $u^+$  and  $u^-$  terminals have no closed circuit connection between them, and therefore no current can flow into or out of them. This is very good because we can connect an op-amp to any other circuit, and the op-amp will not disturb that circuit in any way because it does not load the circuit (it is an open circuit).

- (b) Suppose we add a resistor of value  $R_L$  between  $u_{out}$  and ground. What is the value of  $v_{out}$ ? Does your answer depend on  $R_L$ ? In other words, how does  $R_L$  affect  $Av_C$ ? What are the implications of this with respect to using op-amps in circuit design?

**Answer:**

Notice that  $u_{out}$  is connected directly to a controlled/dependent voltage source, and therefore  $v_{out}$  will always have to be equal to  $Av_C$  regardless of what  $R_L$  is connected to the op-amp. This is very advantageous because it means that the output of the op-amp can be connected to any other circuit (except a voltage source), and we will always get the desired/expected voltage out of the op-amp.

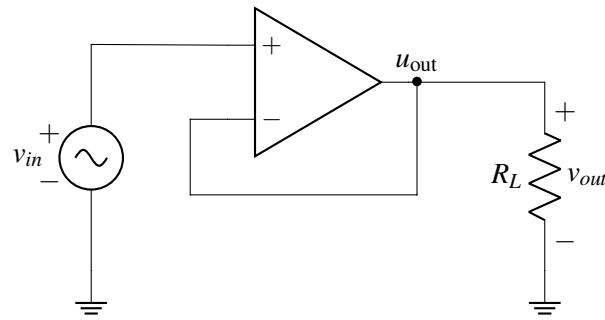**For the rest of the problem, consider the following op-amp circuit in negative feedback:**



- (c) Assuming that this is an ideal op-amp, what is  $v_{out}$ ?

**Answer:**

Recall for an ideal op-amp in negative feedback, we know from the negative feedback rule that  $u^+ = u^-$ . In this case,  $u^- = u_{out} = u^+$ .

- (d) Draw the equivalent circuit for this op-amp and calculate  $v_{out}$  in terms of  $A$ ,  $v_{in}$ , and  $R_L$  for the circuit in negative feedback. Does  $v_{out}$  depend on  $R_L$ ? What is  $v_{out}$  in the limit as  $A \rightarrow \infty$ ?

**Answer:**

Notice that the op-amp can be modeled as a voltage-controlled voltage source. Thus, we have the following equation:

$$\begin{aligned} v_{out} &= A(v_{in} - v_{out}) \\ v_{out} + Av_{out} &= Av_{in} \\ v_{out} &= v_{in} \frac{A}{1+A} \end{aligned}$$


Thus, as  $A \rightarrow \infty$ ,  $v_{out} \rightarrow v_{in}$ . This is the same as what we get after applying the op-amp rule.

Notice that output voltage does not depend on  $R$ . Thus, this circuit acts like a voltage source that provides the same voltage read at  $u^+$  without drawing any current from the terminal at  $u^+$ . This is why the circuit is often referred to as a “unity gain buffer,” “voltage follower,” or just “buffer.”

## 2. Comparators


For each of the circuits shown below, plot  $V_{out}$  for  $V_{in}$  ranging from  $-10\text{V}$  to  $10\text{V}$  for part (a) and from  $0\text{V}$  to  $10\text{V}$  for part (b).

(a)

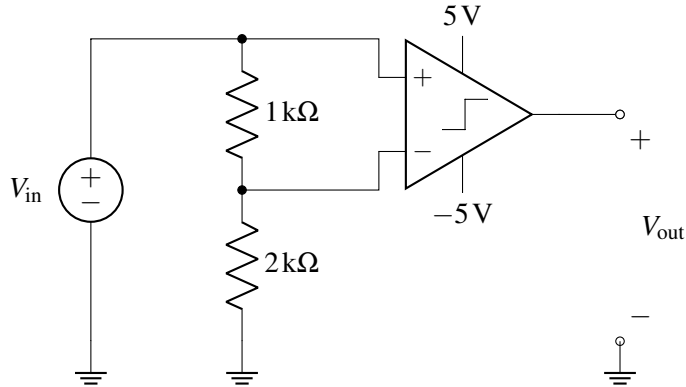

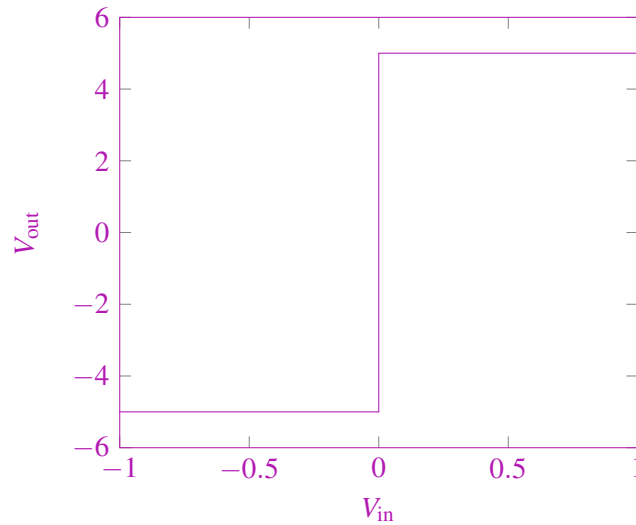
### Answer:

When the positive terminal's voltage,  $V_+$ , is greater than the negative terminal's voltage,  $V_-$ , the value at the positive supply rail,  $V_{DD}$ , will be output. Likewise, if the negative terminal's voltage,  $V_-$ , has a higher voltage then the value at the negative supply rail,  $V_{SS}$ , will be output. Since  $V_-$  is just the output of a voltage divider with the source  $V_{in} = V_+$ , it will always have lower absolute value and same polarity as the positive terminal. Thus, the comparator's output will depend only on the sign of the source  $V_{in}$ .



(b)

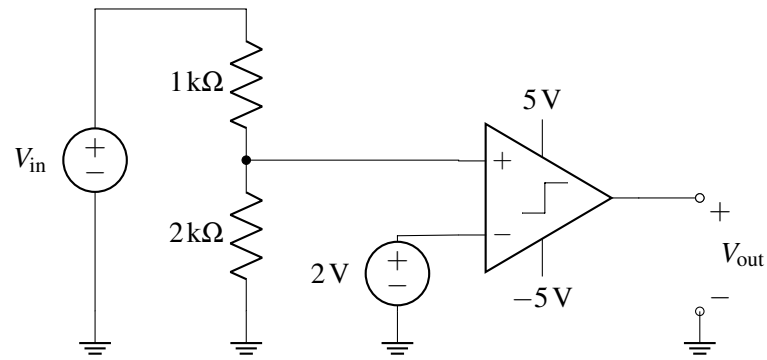**Answer:**

$$V_+ = \frac{2\text{k}\Omega}{1\text{k}\Omega + 2\text{k}\Omega} V_{\text{in}} = \frac{2}{3} V_{\text{in}}$$

$$V_- = 2\text{V}$$

The comparator will output positive 5V when the voltage divider's output  $V_+ > 2\text{V}$  and thus when  $V_{\text{in}} > 3\text{V}$ . Otherwise, it will output -5V.

