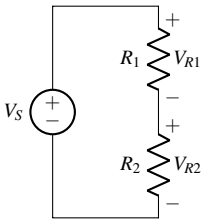
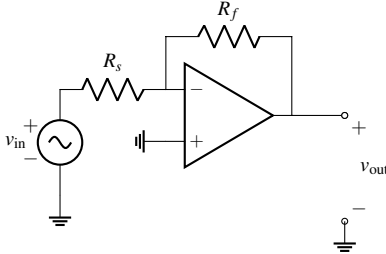
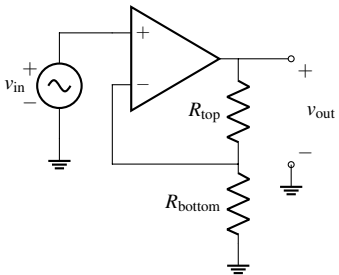
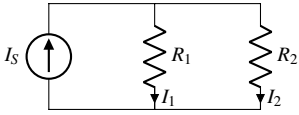
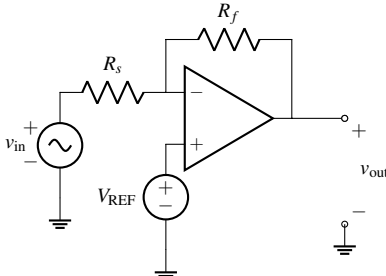
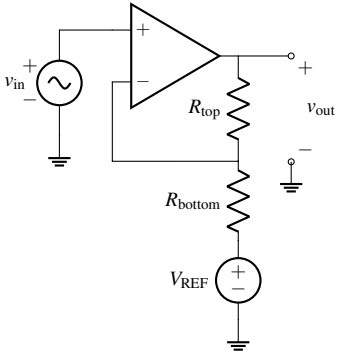
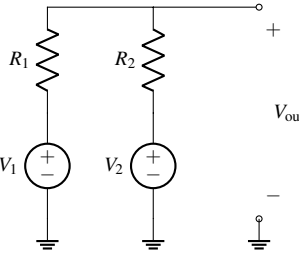
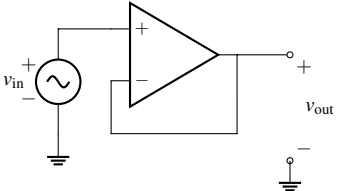


EECS 16A Designing Information Devices and Systems I


Fall 2020 Discussion 11A

Reference: Op-Amp Example Circuits

| | | |
|--|--|---|
| <p style="text-align: center;">Voltage Divider</p>  $V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$ | <p style="text-align: center;">Inverting Amplifier</p>  $v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right)$ | <p style="text-align: center;">Noninverting Amplifier</p>  $v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right)$ |
| <p style="text-align: center;">Current Divider</p>  $I_1 = I_S \left(\frac{R_2}{R_1 + R_2} \right)$ | <p style="text-align: center;">Inverting Amplifier with Reference</p>  $v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right) + V_{REF} \left(\frac{R_f}{R_s} + 1 \right)$ | <p style="text-align: center;">Noninverting Amplifier with Reference</p>  $v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$ |
| <p style="text-align: center;">Voltage Summer</p>  $V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$ | <p style="text-align: center;">Unity Gain Buffer</p>  $v_{out} = v_{in}$ | |

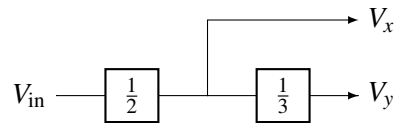1. Modular Circuit Buffer

Let's try designing circuits that perform a set of mathematical operations using op-amps. While voltage dividers on their own cannot be combined without altering their behavior, op-amps can preserve their behavior when combined and thus are a perfect tool for modular circuit design. We would like to implement the block diagram shown below:



In other words, create a circuit with two outputs V_x and V_y , where $V_x = \frac{1}{2}V_{in}$ and $V_y = \frac{1}{3}V_x = \frac{1}{6}V_{in}$.

- (a) Draw two voltage dividers, one for each operation (the $1/2$ and $1/3$ scalings). What relationships hold for the resistor values for the $1/2$ divider, and for the resistor values for the $1/3$ divider?

Answer: Recall our voltage divider consists of V_{in} connected to two resistors (R_1, R_2) in series with the output voltage between ground and the central node. This yields the formula


$$V_{out} = \left(\frac{R_2}{R_1 + R_2} \right) V_{in}.$$

For the $1/2$ operation (V_x output) we recognize

$$\frac{1}{2} = \left(\frac{R_2}{R_1 + R_2} \right) \rightarrow R_1 + R_2 = 2R_2 \rightarrow R_1 = R_2 \equiv R_x.$$


For the $1/3$ operation (V_y output) we recognize
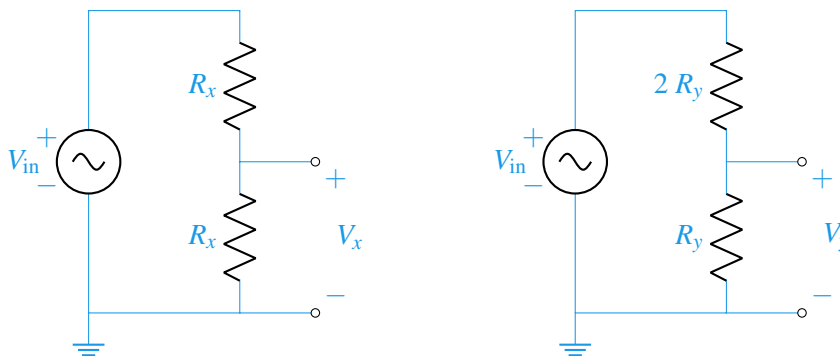
$$\frac{1}{3} = \left(\frac{R_2}{R_1 + R_2} \right) \rightarrow R_1 + R_2 = 3R_2 \rightarrow \frac{R_1}{2} = R_2 \equiv R_y.$$




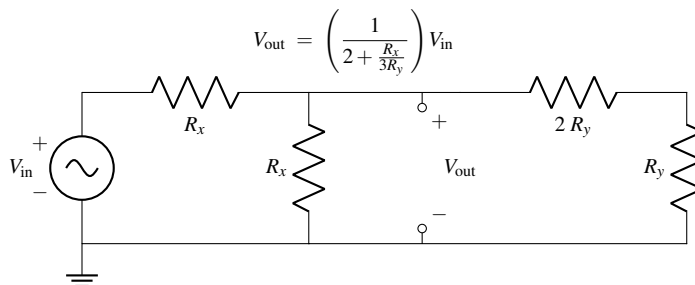- (b) If you combine the voltage dividers, made in part (a), as shown by the block diagram (output of the $1/2$ voltage divider becomes the source for the $1/3$ voltage divider circuit), do they behave as we hope (meaning $6V_{in} = 3V_x = V_y$)?

HINT: The following circuit and formula may be handy:



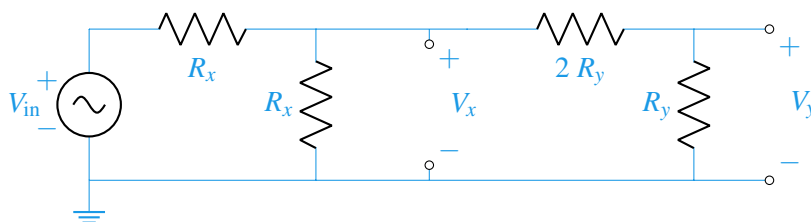Answer: Combining the voltage divider circuits yield



To quickly access this combined system, we may identify V_x as the result of a new equivalent voltage divider (recognizing the R_y resistors in series and that series is in parallel with R_x). The load resistor becomes $R_{eq} = \frac{3R_x R_y}{R_x + 3R_y}$. This yields

$$V_x = \left(\frac{R_{eq}}{R_x + R_{eq}} \right) V_{in} = \left(\frac{1}{2 + \frac{R_x}{3R_y}} \right) V_{in} \quad V_y = \frac{1}{3} V_x = \left(\frac{1}{6 + \frac{R_x}{R_y}} \right) V_{in}$$

From this stage it is evident that combining our dividers changes their behavior (although they preserve behavior in the limit $R_y \gg R_x$).

The new values for V_x, V_y are dependent on values from both dividers, which means they can't be treated independently! □.


(c) Perhaps we could use an op-amp (in negative-feedback) to achieve our desired behavior.

Modify the implementation you tried in part (b) using a negative feedback op-amp in order to achieve the desired V_x, V_y relations $V_x = (1/2)V_{in}$ and $V_y = (1/3)V_x = (1/6)V_{in}$.

HINT: Place the op-amp in between the dividers such that the V_x node is an input into the op-amp, while the source of the 2nd divider is the output of the op-amp!

Answer: Use the op-amp as a voltage buffer.

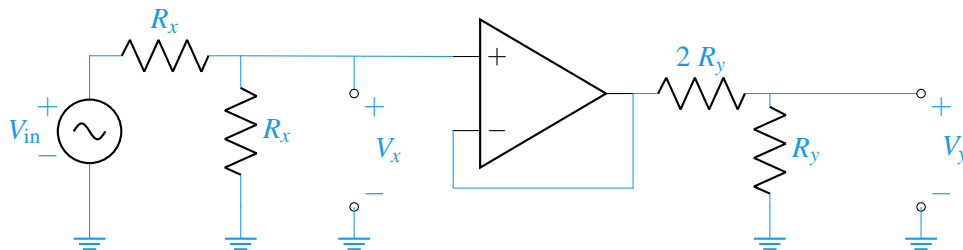This means we short the op-amp's negative input to its output, since the positive input must now match its output (by the golden rules).



Since no current flow into the positive op-amp input, we've successfully isolated the dividers so they can be used in a modular fashion! □

NOTE: The V_x, V_y outputs from this configuration would change with the addition of a load on either terminal. As a follow-up, think about ways to make each output agnostic to the loads attached!

2. Modular Op-Amp Circuits

Let's expand our toolbox of op-amp circuits that perform mathematical operations by designing blocks that implement the following operations


- Scale the input voltage so that: $V_{\text{out}} = +5 V_{\text{in}}$
- Scale and invert the input voltage so that: $V_{\text{out}} = -2 V_{\text{in}}$
- Sum two input voltages together so that: $V_{\text{out}} = V_{\text{in}_1} + V_{\text{in}_2}$

Use the reference above for help!


Would connecting any of these blocks together modify their intended functionality?

Answer:

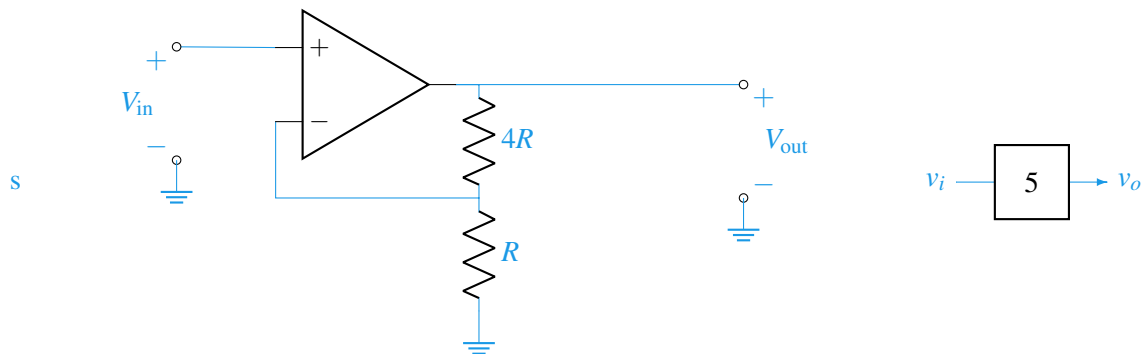- Since our scaling of $+5$ is positive, we employ a non-inverting amplifier without a V_{REF} supply:



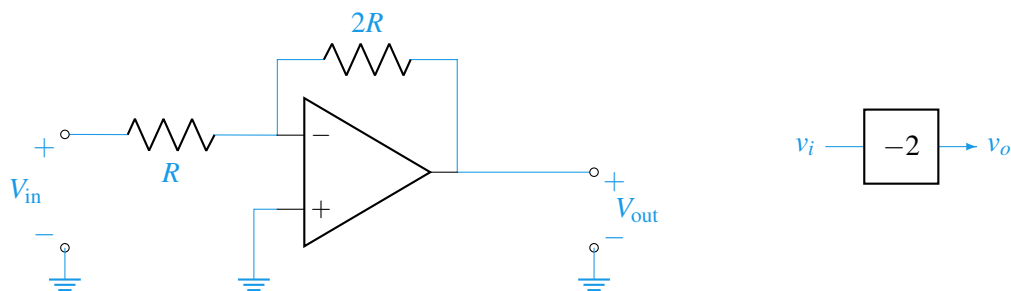- To scale the input by -2 we must use the inverting amplifier configuration:




- This one is tricky!

The voltage summing circuit (in the reference) can get us close, but the resulting voltage still must be scaled by $+2$ using a non-inverting amplifier. Further, we need an op-amp in the circuit anyway to serve as a buffer! The best mindset for this problem is to think:

can we use a voltage divider involving the two input voltages as an input for a non-inverting amplifier?

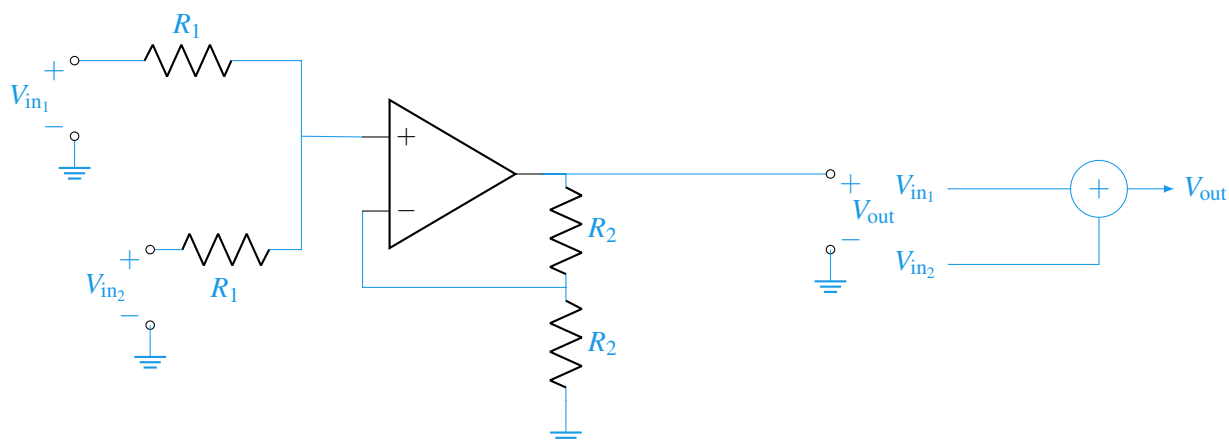Conceptually we can imagine a $1/2$ voltage divider where the usual ground node is replaced by a source, say V_{in2} . Then our divider equation becomes $V_{out} = \frac{1}{2}(V_{in1} + V_{in2})$. Next we can feed that input into a non-inverting amplifier circuit:



We check if our circuit modules can be combined together by examining how the circuit output voltages change with an attached load resistor. Since every circuit has at least 1 fixed input (a node that is isolated from V_{out} entirely), and the golden rules ($u_+ = u_-$) apply for negative-feedback circuits, the circuits' functionalities are unimpeded by the load.