


---

EECS 16A    Designing Information Devices and Systems I    Discussion 7B  
 Fall 2020


---

### 1. Passive Sign Convention and Power

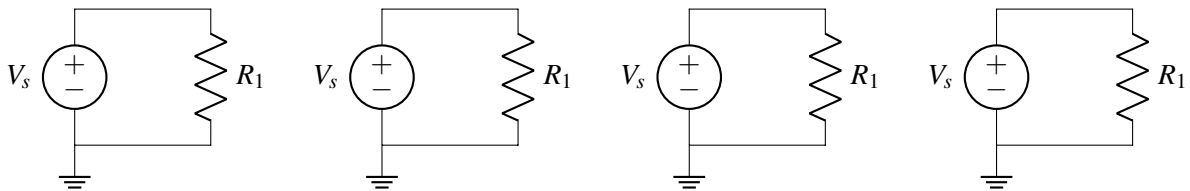
- (a) We have made four copies of a circuit below. Following passive sign convention, there are four different possible labelings of current directions and voltage polarities for the circuit. For each copy, label each circuit's voltage source and resistor with current direction and voltage polarity labelings, keeping with passive sign convention.



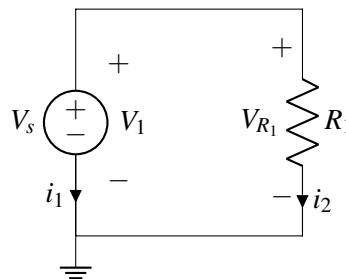- (b) Suppose we consider one of the possible labelings you have found above. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$  and let  $R_1 = 5\Omega$ .



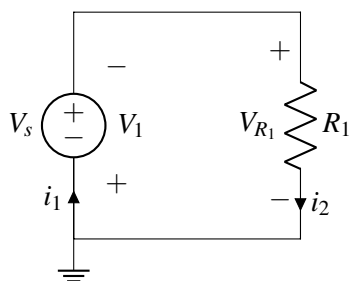- (c) Suppose we choose a second labeling of the circuit as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$  and let  $R_1 = 5\ \Omega$ .



- (d) Did the values of the element voltages and element currents change with the different labeling? Did the power for each circuit element change? Did the node voltages change? If a quantity didn't change with a difference in labeling, discuss what would have to change for quantity to change.

## 2. Volt and ammeter

Consider the following circuit below. We have also included relevant NVA equations below it.

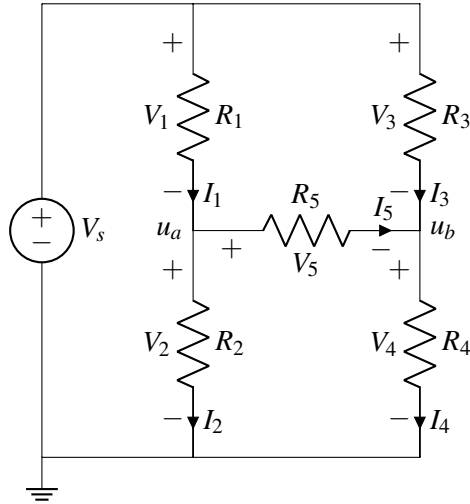


Figure 1: Circuit consisting of a voltage source  $V_s$  and five resistors  $R_1$  to  $R_5$ .

$I_1 = I_2 + I_5$ $I_5 + I_3 = I_4$	$I_1 = \frac{V_1}{R_1} = \frac{V_s - u_a}{R_1}$ $I_2 = \frac{V_2}{R_2} = \frac{u_a - 0}{R_2}$ $I_3 = \frac{V_3}{R_3} = \frac{V_s - u_b}{R_3}$ $I_4 = \frac{V_4}{R_4} = \frac{u_b - 0}{R_4}$ $I_5 = \frac{V_5}{R_5} = \frac{u_a - u_b}{R_5}$	$\frac{V_s - u_a}{R_1} = \frac{u_a - 0}{R_2} + \frac{u_a - u_b}{R_5}$ $\frac{u_a - u_b}{R_5} + \frac{V_s - u_b}{R_3} = \frac{u_b - 0}{R_4}$
KCL	Ohm's law in terms of node voltages	Substitute Ohm's into KCL

- (a) The circuit diagram shown in Figure 1 has been redrawn in Figure 2 by adding a voltmeter (letter  $V$  in a circle and plus and minus signs indicating direction) to measure voltage  $V_{ab} = u_a - u_b$ . Assume that the voltmeter is ideal. Are the values of  $V_{ab}$  before adding the voltmeter and after adding the voltmeter different? If so, which of the given equations change when doing NVA?

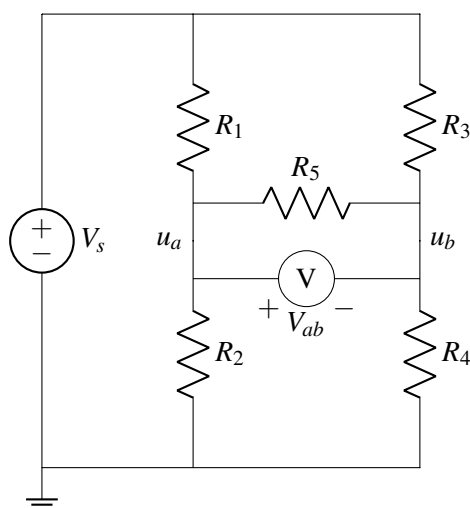


Figure 2: Circuit with voltmeter.

- (b) Suppose you accidentally connect an ideal ammeter in part (a) to nodes  $u_a$  and  $u_b$  instead of an ideal voltmeter. Does the value of  $V_{ab}$  with the ammeter connected differ from the value of  $V_{ab}$  without the ammeter connected? If so, what equations change when doing NVA?

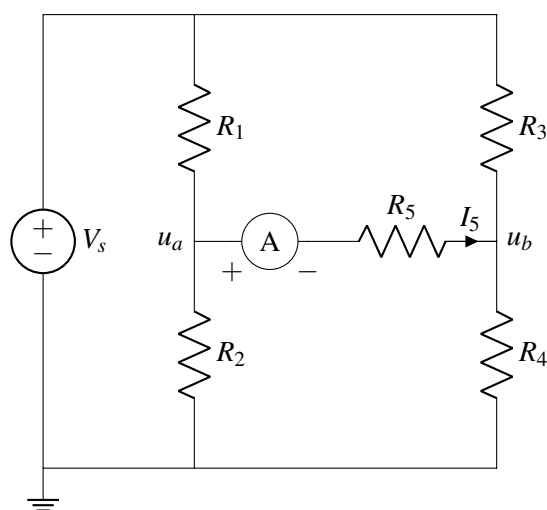


Figure 3: Circuit with ammeter.

- (c) The circuit diagram shown in Figure 1 has been redrawn in Figure 3 by adding an ideal ammeter (letter  $A$  in a circle and plus and minus signs indicating direction) in series with resistor  $R_5$ . This will measure the current  $I_5$  through  $R_5$ . Are the values of  $I_5$  before adding the ammeter and after adding the ammeter different? If so, what equations change when doing NVA?
- (d) Your friend accidentally connects a voltmeter in part (c) above, rather than an ammeter. Are the values of  $I_5$  before adding the ammeter and after adding the ammeter different? If so, what equations change when doing NVA?



(d) Suppose PG&E charges \$0.12 per kWh. Every day, you completely discharge the battery (meaning more than typical usage) and you recharge it every night. How much will recharging cost you for the month of October (31 days)?

(e) The battery has internal circuitry that prevents it from getting overcharged (and possibly exploding!). We will model the battery and its internal circuitry as a resistor  $R_{\text{bat}}$ . We now wish to charge the battery by plugging into a wall plug. The wall plug can be modeled as a 5 V voltage source and 200 m $\Omega$  resistor, as pictured in Figure 4. What is the power dissipated across  $R_{\text{bat}}$  for  $R_{\text{bat}} = 1 \text{ m}\Omega$ ,  $1 \Omega$ , and  $10 \text{ k}\Omega$ ? (i.e. how much power is being supplied to the phone battery as it is charging?). How long will the battery take to charge for each of those values of  $R_{\text{bat}}$ ?

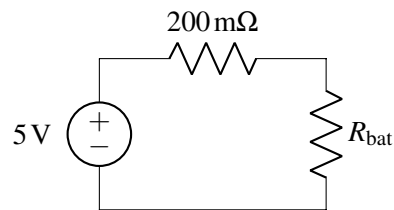


Figure 4: Model of wall plug, wire, and battery.