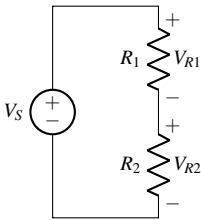
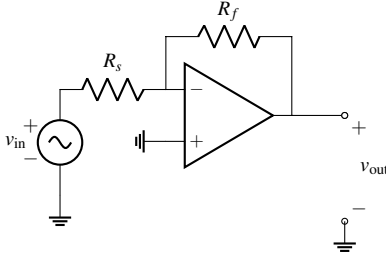
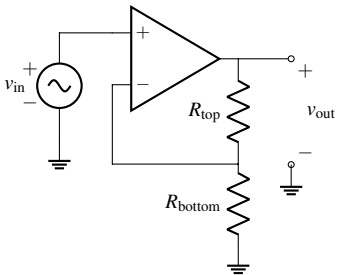
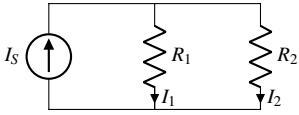
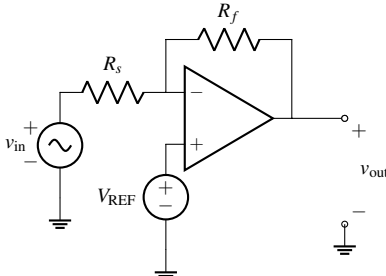
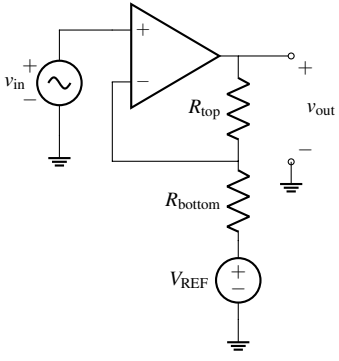
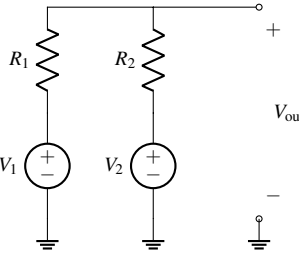
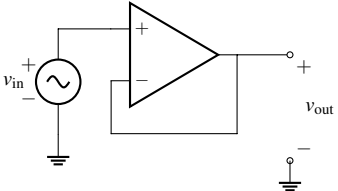


EECS 16A Designing Information Devices and Systems I


Discussion 11A

Reference: Op-Amp Example Circuits

<p style="text-align: center;">Voltage Divider</p>  <p style="text-align: center;">$V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$</p>	<p style="text-align: center;">Inverting Amplifier</p>  <p style="text-align: center;">$v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right)$</p>	<p style="text-align: center;">Noninverting Amplifier</p>  <p style="text-align: center;">$v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right)$</p>
<p style="text-align: center;">Current Divider</p>  <p style="text-align: center;">$I_1 = I_S \left(\frac{R_2}{R_1 + R_2} \right)$</p>	<p style="text-align: center;">Inverting Amplifier with Reference</p>  <p style="text-align: center;">$v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right) + V_{REF} \left(\frac{R_f}{R_s} + 1 \right)$</p>	<p style="text-align: center;">Noninverting Amplifier with Reference</p>  <p style="text-align: center;">$v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$</p>
<p style="text-align: center;">Voltage Summer</p>  <p style="text-align: center;">$V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$</p>	<p style="text-align: center;">Unity Gain Buffer</p>  <p style="text-align: center;">$v_{out} = v_{in}$</p>	

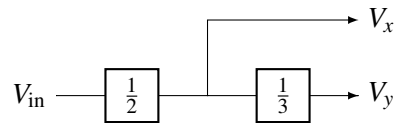1. Modular Circuit Buffer

Let's try designing circuits that perform a set of mathematical operations using op-amps. While voltage dividers on their own cannot be combined without altering their behavior, op-amps can preserve their behavior when combined and thus are a perfect tool for modular circuit design. We would like to implement the block diagram shown below:




In other words, create a circuit with two outputs V_x and V_y , where $V_x = \frac{1}{2}V_{in}$ and $V_y = \frac{1}{3}V_x = \frac{1}{6}V_{in}$.

- (a) Draw two voltage dividers, one for each operation (the $1/2$ and $1/3$ scalings). What relationships hold for the resistor values for the $1/2$ divider, and for the resistor values for the $1/3$ divider?

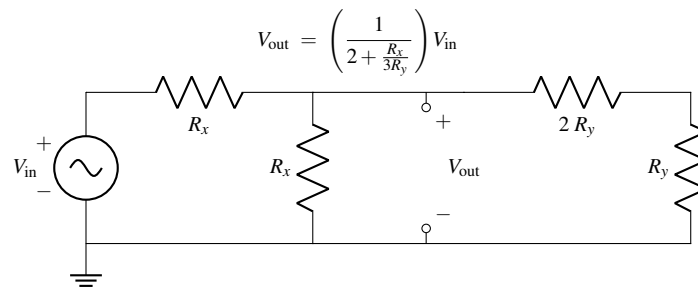- (b) If you combine the voltage dividers, made in part (a), as shown by the block diagram (output of the $1/2$ voltage divider becomes the source for the $1/3$ voltage divider circuit), do they behave as we hope (meaning $6V_{in} = 3V_x = V_y$)?

HINT: The following circuit and formula may be handy:



- (c) Perhaps we could use an op-amp (in negative-feedback) to achieve our desired behavior. Modify the implementation you tried in part (b) using a negative feedback op-amp in order to achieve the desired V_x, V_y relations $V_x = (1/2)V_{in}$ and $V_y = (1/3)V_x = (1/6)V_{in}$.

HINT: Place the op-amp in between the dividers such that the V_x node is an input into the op-amp, while the source of the 2nd divider is the output of the op-amp!

2. Modular Op-Amp Circuits

Let's expand our toolbox of op-amp circuits that perform mathematical operations by designing blocks that implement the following operations

- (a) Scale the input voltage so that: $V_{\text{out}} = +5 V_{\text{in}}$
- (b) Scale and invert the input voltage so that: $V_{\text{out}} = -2 V_{\text{in}}$
- (c) Sum two input voltages together so that: $V_{\text{out}} = V_{\text{in}_1} + V_{\text{in}_2}$

Use the reference above for help!

Would connecting any of these blocks together modify their intended functionality?