

EECS16A DIS10A

"New" (old) setup. Technical issues. I won't be able to hear, so type in chat!

email: moseswon@

OH: W 10AM-12PM (HWP)


Logistics

MT2 Today! Good luck.



Learning Objectives

- 25/120 ① Voltage dividers - how to choose resistors to get a design (analysis, design)
- 44/120 ② Charge sharing example → Voltage doubler
- ③ General Q & A

[2] Voltage booster

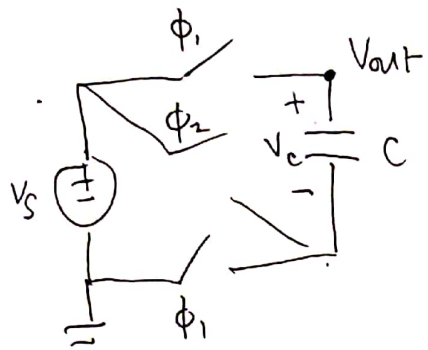

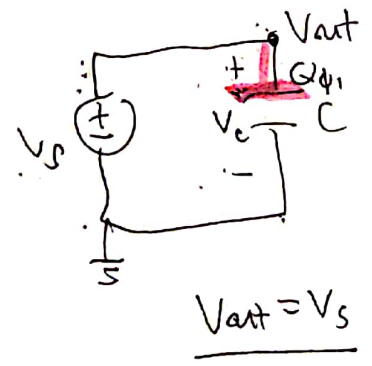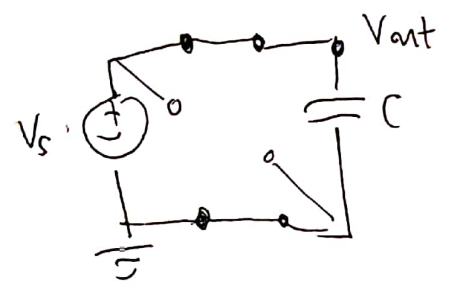a) Find V_{out} in phase ϕ_1
 (ϕ_1 switches closed)
 ϕ_2 switch open




$$Q_{\phi_1} = CV_c = CV_s$$



How to determine charges for charge cons.

- ① Look @ a floating node in phase 2
- ② Compute the sum of charges on that node as a function of node voltages
- ③ Look at charges as they started in phase 1

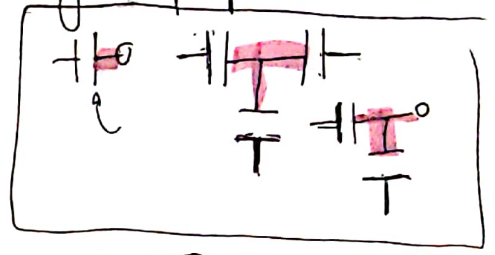Floating node: node connected to only cap. plates or open circuits



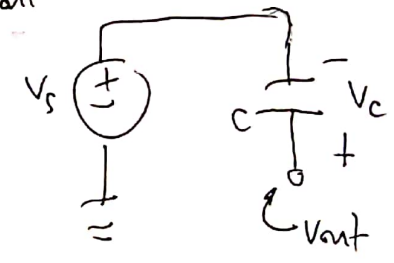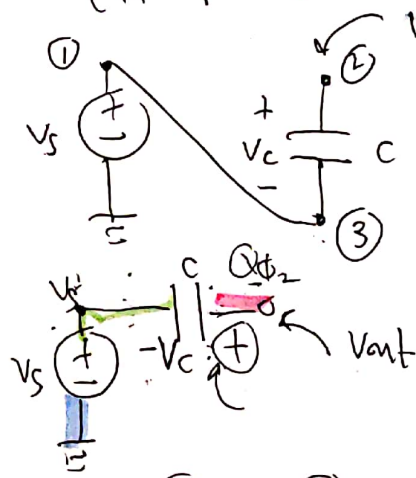b) Find V_{out} in phase ϕ_2
 (ϕ_1 open, ϕ_2 closed)



$$Q_{\phi_2} = +CV_c$$



$$V_c = V_{out} - V_s$$

$$Q_{\phi_1} = Q_{\phi_2} \text{ (cons. of charge)}$$

$$CV_s = C(V_{out} - V_s)$$

$$V_{out} = 2V_s$$

$$V_s = V_{out} - V_s$$

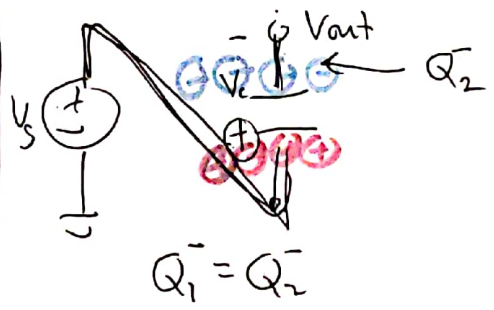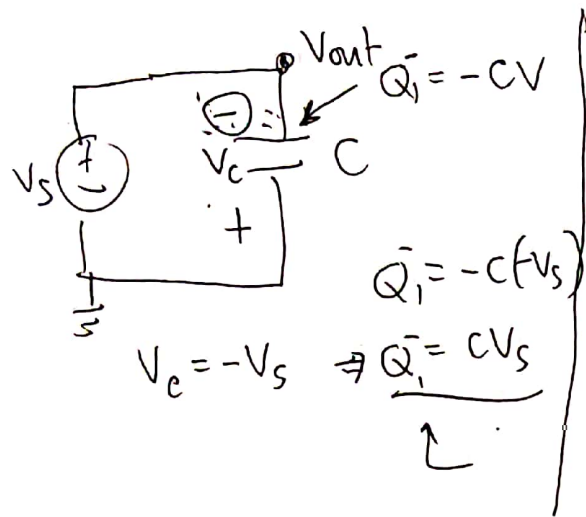

$$CV_s = -CV_c$$





$$CV_s = -C(V_s - V_{out})$$

$$V_s = -V_s + V_{out}$$

$$V_{out} = 2V_s$$

element voltage =
 node voltage on + - node voltage on -


Q: How to redraw

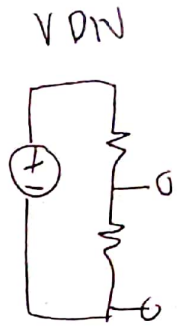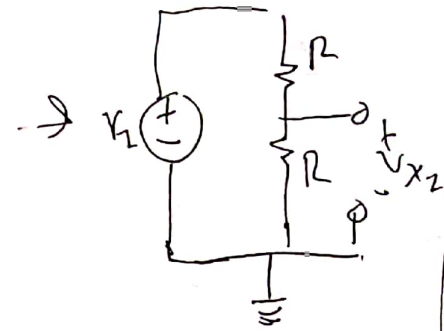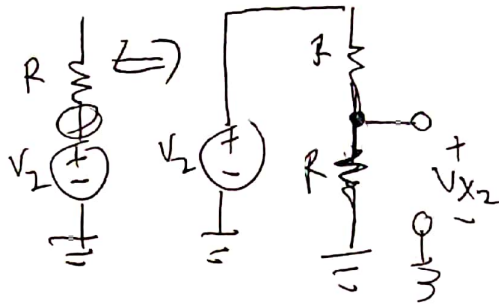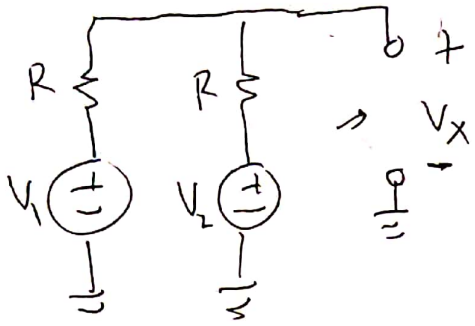

a) Find V_x


① Superposition

V_1 on, V_2 off

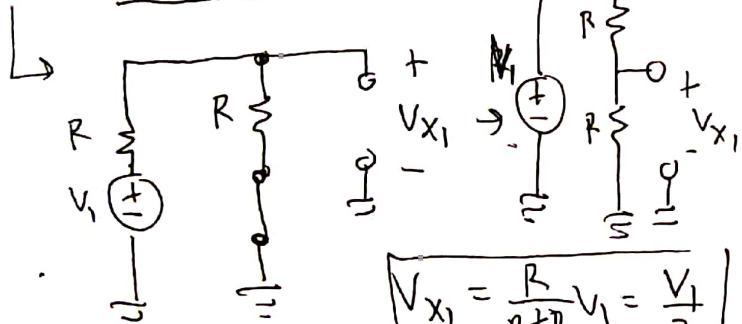

$$V_{x1} = \frac{R}{R+R} V_1 = \frac{V_1}{2}$$


V_2 on, V_1 off

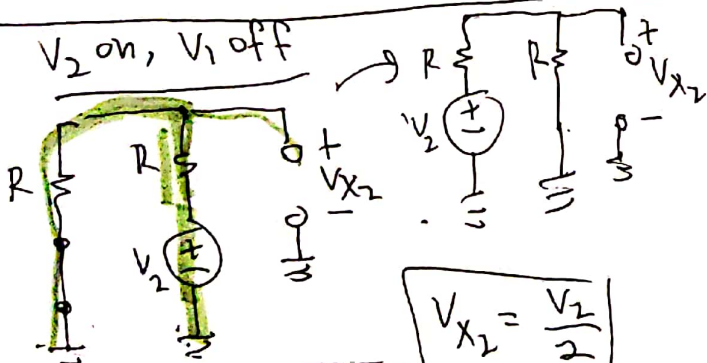

$$V_{x2} = \frac{V_2}{2}$$

$$V_x = V_{x1} + V_{x2} = \frac{V_1 + V_2}{2}$$

② NVA

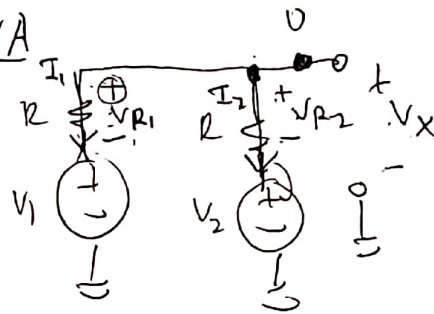

$$V_x = u - 0$$

$$V_x = u$$

$$I_1 + I_2 = 0$$

$$\frac{u - V_1}{R} + \frac{u - V_2}{R} = 0$$



$$u - V_1 + u - V_2 = 0$$

$$2u = V_1 + V_2$$


$$u = \frac{V_1 + V_2}{2}$$

$$V_x = \frac{V_1 + V_2}{2}$$

If two things are in parallel

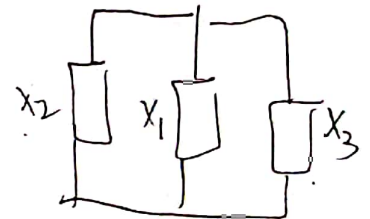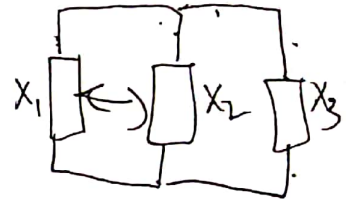


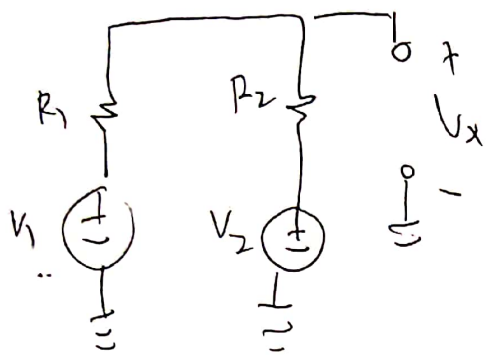Can switch elements, doesn't change circuit



Goal: $V_x = \frac{1}{3}V_1 + \frac{2}{3}V_2$

$\frac{V_1 \text{ on}}{V_2 \text{ off}}$

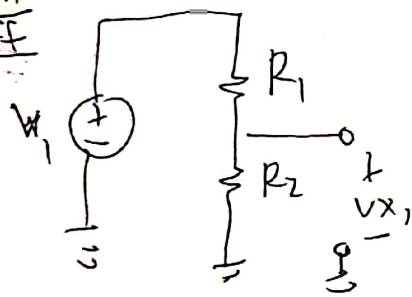


$$V_{x1} = \frac{R_2}{R_1 + R_2} V_1$$

$$V_{x2} = \frac{R_1}{R_1 + R_2} V_2$$

$$V_x = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2 = \boxed{\frac{1}{3}V_1 + \frac{2}{3}V_2}$$

$\frac{V_2 \text{ on}}{V_1 \text{ off}}$

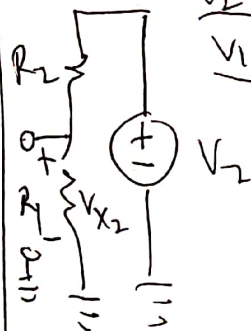

$$\frac{R_2}{R_1 + R_2} = \frac{1}{3}, \quad \frac{R_1}{R_1 + R_2} = \frac{2}{3}$$

$$R_2 = \frac{1}{3}R_1 + \frac{1}{3}R_2$$

$$0 = \frac{1}{3}R_1 - \frac{2}{3}R_2$$

$$\rightarrow R_1 = 2R_2$$

$$R_1 = 1k\Omega$$

$$R_2 = 500\Omega$$

$$R_1 = \frac{2}{3}R_1 + \frac{2}{3}R_2$$

$$\frac{1}{3}R_1 - \frac{2}{3}R_2 = 0$$


$$\frac{1}{3}R_1 = \frac{2}{3}R_2$$

$$R_1 = 2R_2$$

Power:


$$P = IV$$

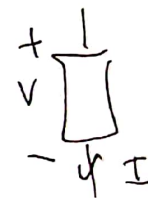\uparrow element current
 \nwarrow element voltage






Have:

(c)

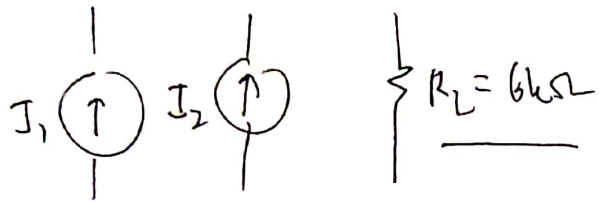
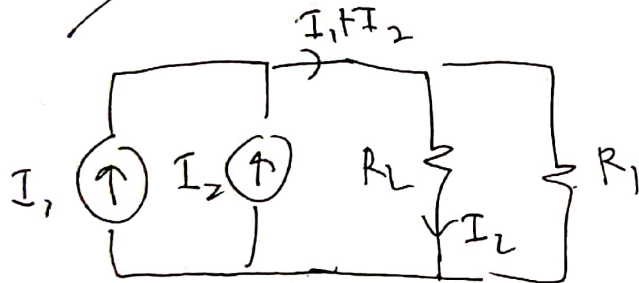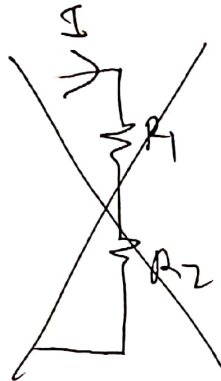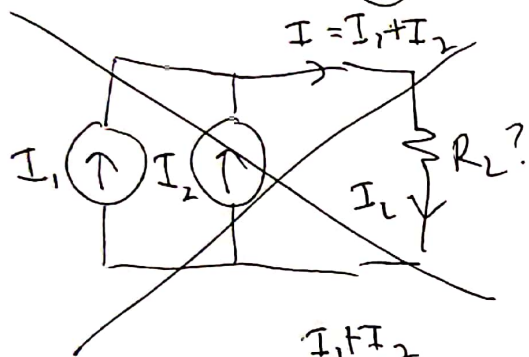
$$I_L \text{ (through } R_L) = \left(\frac{2}{5}\right)(I_1 + I_2)$$



$$I_L = \left(\frac{R_1}{R_1 + R_L}\right)(I_1 + I_2)$$

$$\Rightarrow \frac{R_1}{R_1 + R_L} = \frac{2}{5}$$

$$R_1 = \frac{2}{5}R_1 + \frac{2}{5}R_L$$



$$\frac{3}{5}R_1 = \frac{2}{5}R_L$$

$$R_1 = \frac{2}{3}R_L = 4k\Omega$$


Equivalence in caps / resistors

Find all voltages + charges (assume intially all discharged)

$$Q = C_1 V_1$$

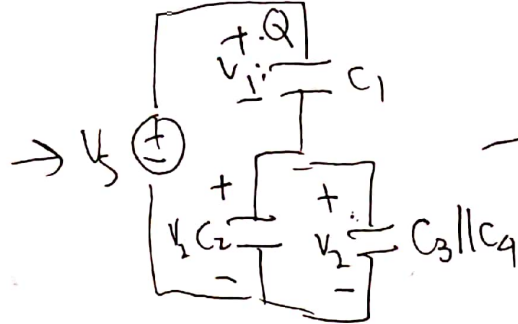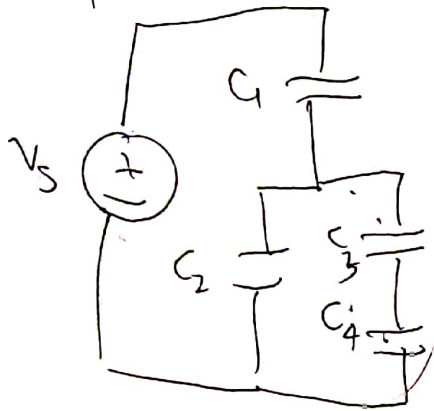


$$A \parallel B = \frac{AB}{A+B}$$

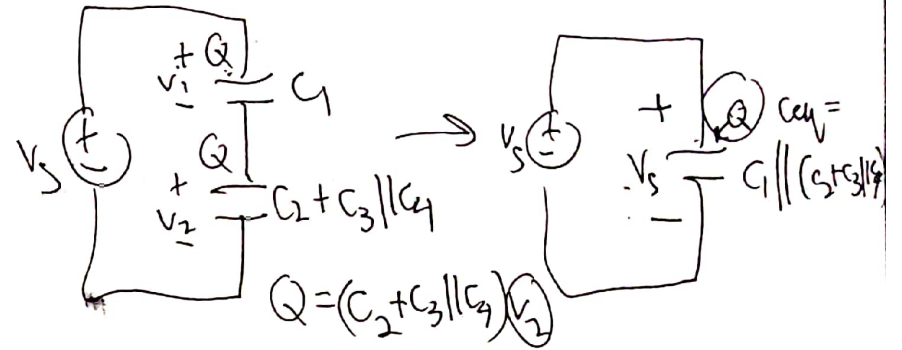


$$Q = (C_2 + C_3 \parallel C_4) V_2$$

Find all currents + voltages


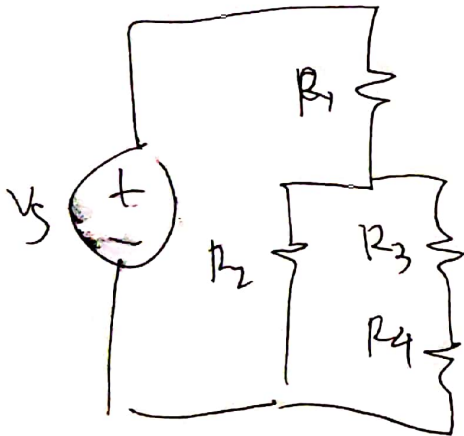


Charge on cap

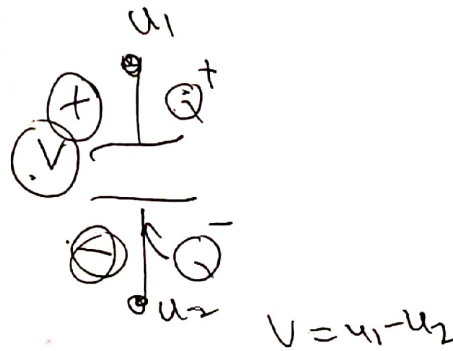

$$Q^+ = CV = C(u_1 - u_2)$$

$$Q^- = -CV = -C(u_1 - u_2)$$

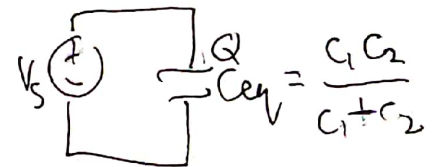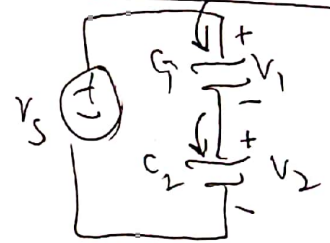

$$Q = \frac{C_1 C_2}{C_1 + C_2} V_s$$

$$V_1 = \frac{Q}{C_1} = \frac{C_2}{C_1 + C_2} V_s$$

$$V_2 = \frac{Q}{C_2} = \frac{C_1}{C_1 + C_2} V_s$$