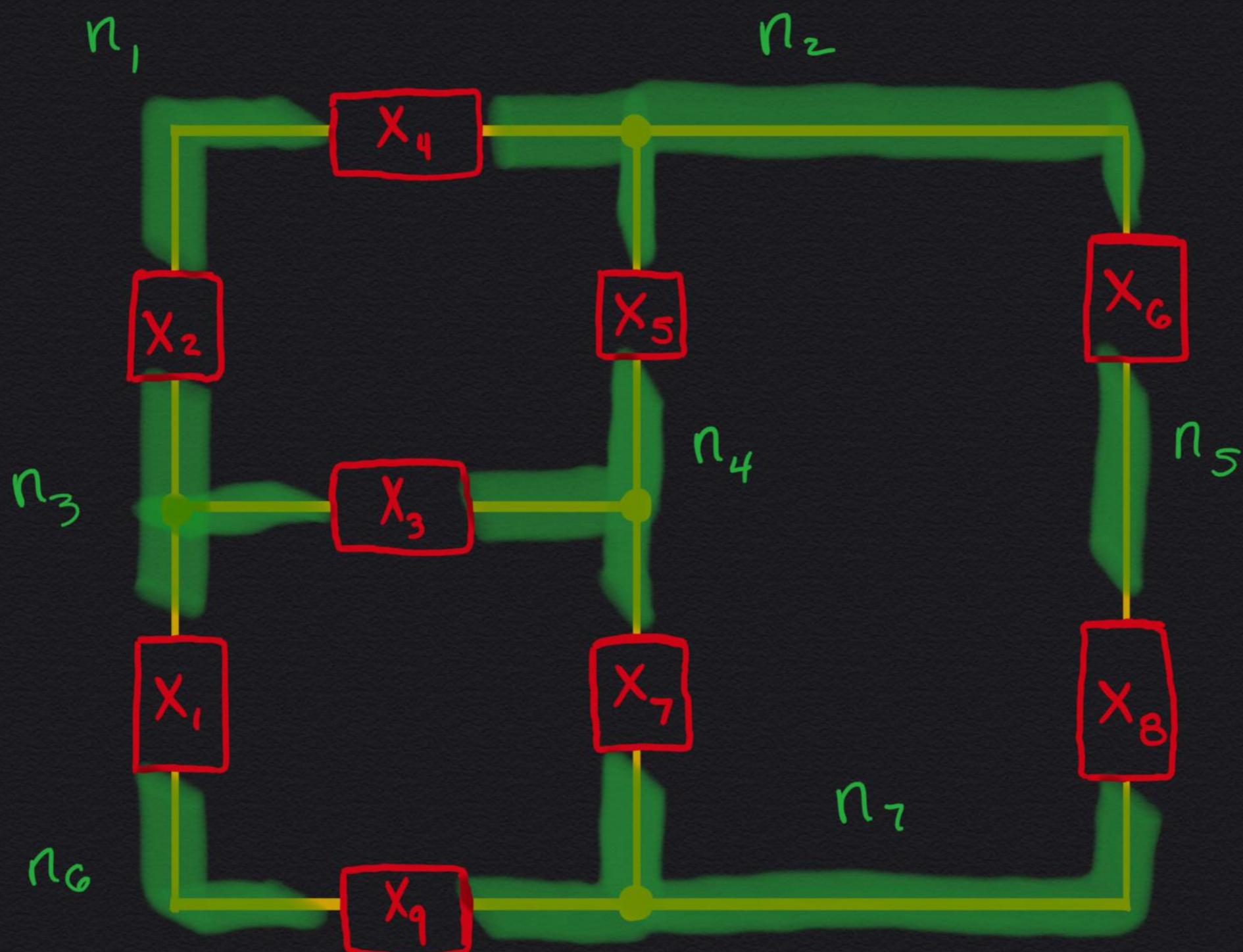


- ① In the circuit below, label & count all nodes and branches:

↳ Nontrivial Circuit Elements

↳ Regions of "equi-potential"


↳ Basically all connected wiring which is all at the same voltage.



There are 7 nodes.

There are 9 branches.

② Voltage Divider! (Re-run)

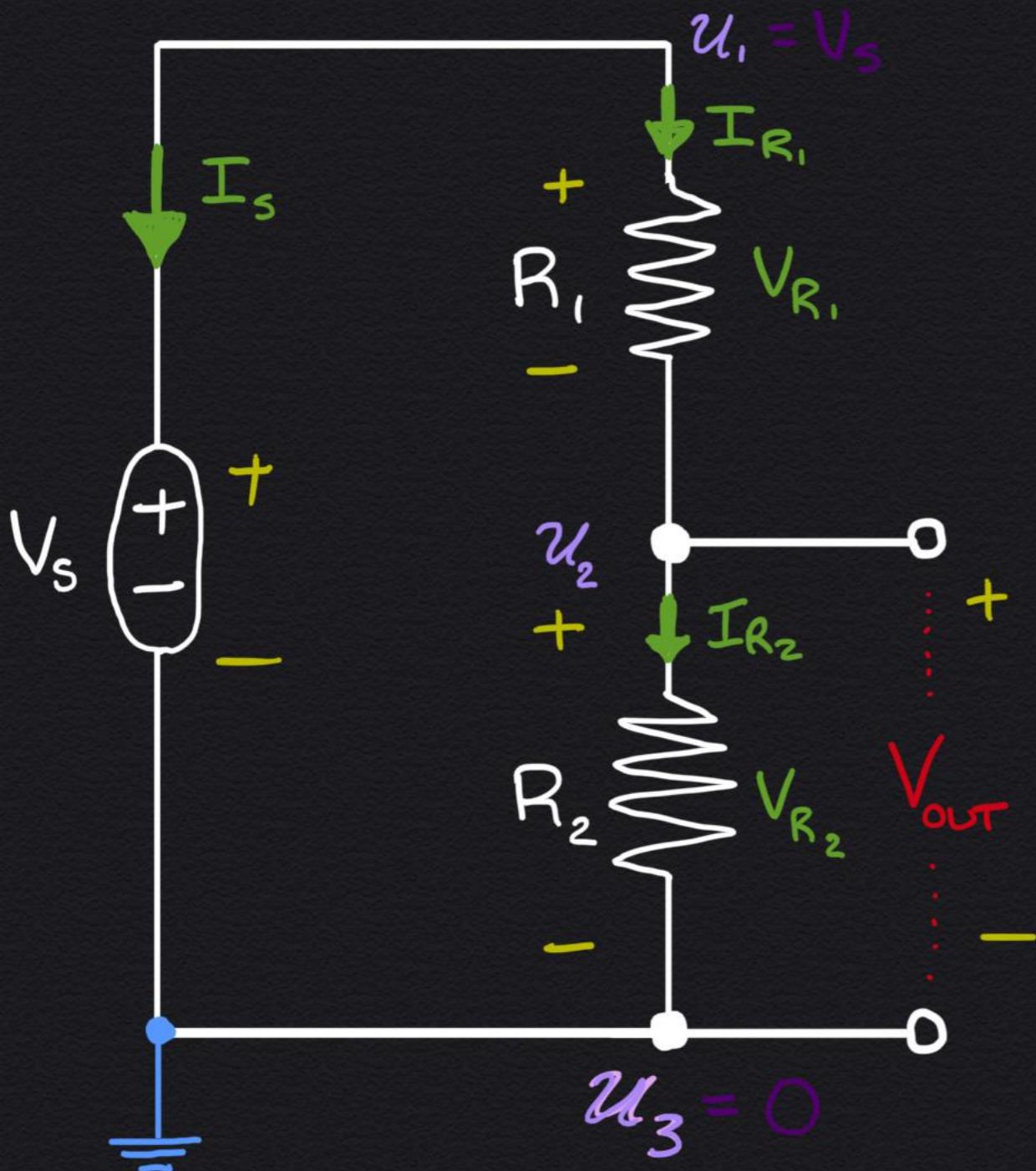

Step 0: Knowns (except V_{OUT})

Step 1: Set ground

Step 2/3: Label node voltages

Step 4: Label element voltages and currents, including passive sign convention.

Note: Only the things in red and white on the circuit are known/mandatory/unambiguous. The rest is the engineer's choice, but make sure YOUR CHOICES ARE CONSISTENT!

5] Write the KCL equations:

$$-\mathbf{I}_{R_1} - \mathbf{I}_S = 0 \rightarrow \mathbf{I}_{R_1} = -\mathbf{I}_S$$
$$+\mathbf{I}_{R_1} - \mathbf{I}_{R_2} = 0 \rightarrow \mathbf{I}_{R_1} = \mathbf{I}_{R_2}$$

Sum of the currents in/out
of each junction, + sign for
'in', and - sign for out.

KCL says this sum must be
zero at all junctions

Note this another independent convention choice, since multiplying both
sides of each equation would change nothing!!

6] Write currents in terms of element voltages &
characteristics, using Ohm's law $V = IR$.


$$\mathbf{I}_{R_1} \cdot R_1 = V_{R_1}$$

$$\mathbf{I}_{R_2} \cdot R_2 = V_{R_2}$$

7] Substitute in for known voltages

$$\underline{U_1}, \underline{U_2}, \underline{U_3}$$
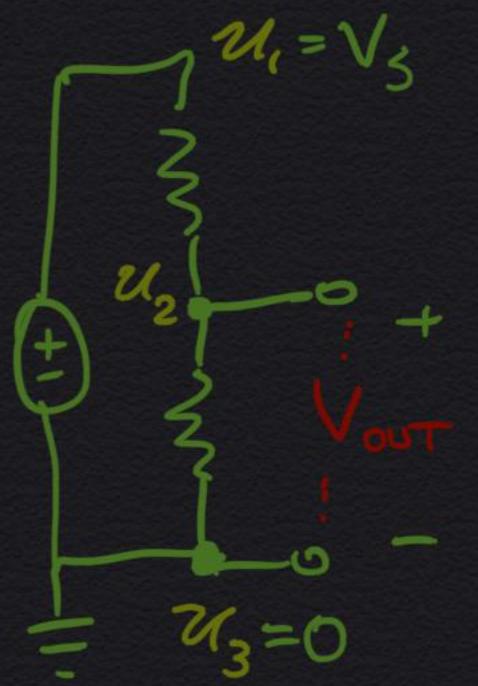
$$\underline{V_S} \quad \underline{V_{OUT}} \quad 0$$



$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{\underline{U_1} - \underline{U_2}}{R_1} = \frac{V_S - V_{OUT}}{R_1}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{\underline{U_2} - \underline{U_3}}{R_2} = \frac{V_{OUT}}{R_2}$$

Everything here in this color of green is technically step 9.

$$V_{OUT} = \underline{U_2} - \cancel{\underline{U_3}}$$

8] Plug into KCL equations

$$I_{R_1} = \frac{\underline{U_1} - \underline{U_2}}{R_1} = -I_S$$

$$I_{R_1} = I_{R_2}$$



$$\frac{\underline{U_1} - \underline{U_2}}{R_1} = \frac{\underline{U_2} - \underline{U_3}}{R_2}$$

9] Solve for our node voltages U_j $j=1,2,3$ from known circuit variables:

$$\frac{U_1 - U_2}{R_1} = \frac{V_{\text{OUT}} - 0}{R_2}$$

$$\frac{V_s}{R_1} = V_{\text{OUT}} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_s = V_{\text{OUT}} \left(1 + \frac{R_1}{R_2} \right)$$

$$V_{\text{OUT}} = V_s \left(\frac{1}{1 + R_1/R_2} \cdot \frac{R_2}{R_2} \right)$$

multiply by $1 = \frac{R_2}{R_2}$

$$V_{\text{OUT}} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

Notes:

1. If $R_2 = 0$, then
 $V_{\text{OUT}} = 0$

2. If $R_1 = 0$, then
 $V_{\text{OUT}} = V_s$

3. If $R_1 = R_2 = 0$, then you've blown up the battery!

Luiz, actually most batteries have a tiny resistance inside, so you'd probably notice the battery get really hot, and die.

- Some fancy power supplies will be designed to have a device inside that sets a limit to the current through it.

4. If $R_1 < 0$ or $R_2 < 0$, then you've broken the laws of physics...