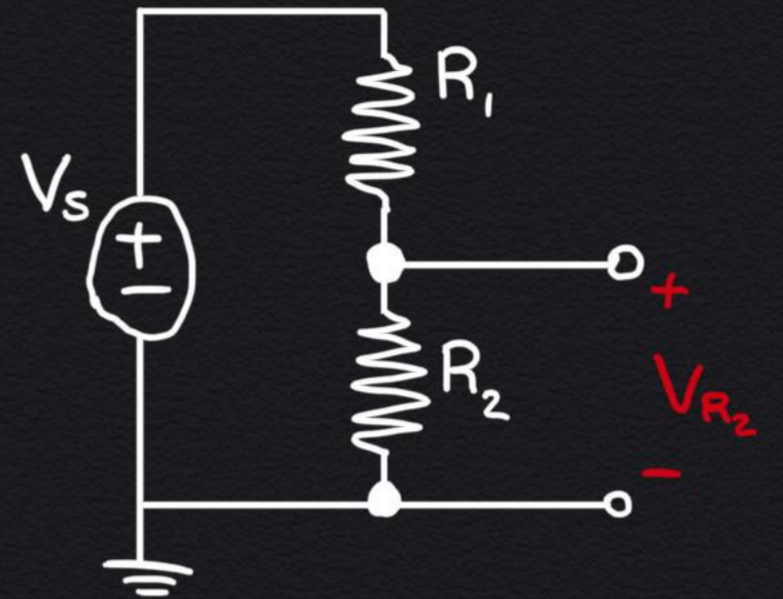



1 Current Divider

Previously we played with the voltage divider (shown right) and found the relationship

$$V_{R_2} = \left(\frac{R_2}{R_1 + R_2} \right) V_s$$



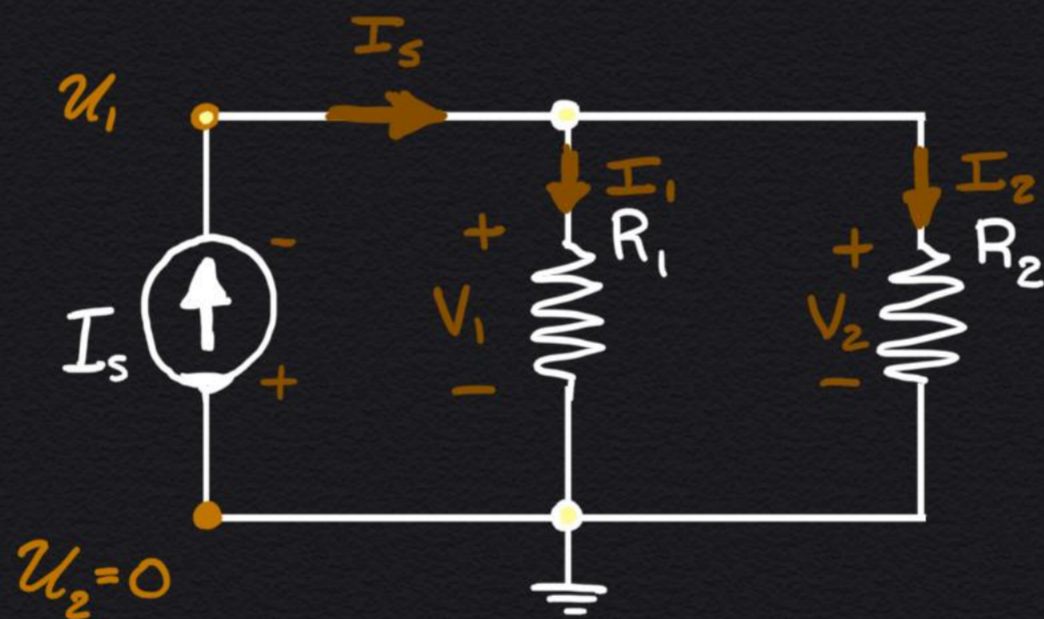Now we are going to make a similar derivation for a current divider. For the diagram below, find the current I_2 through R_2 as a function of I_s :



Step 1: Set ground ✓

Step 2/3: Label nodes


Step 4: Label currents and element voltages

Step 5: Using KCL

$$+I_s - I_1 - I_2 = 0$$

Step 6: Substitute in element voltages (using Ohm's law)
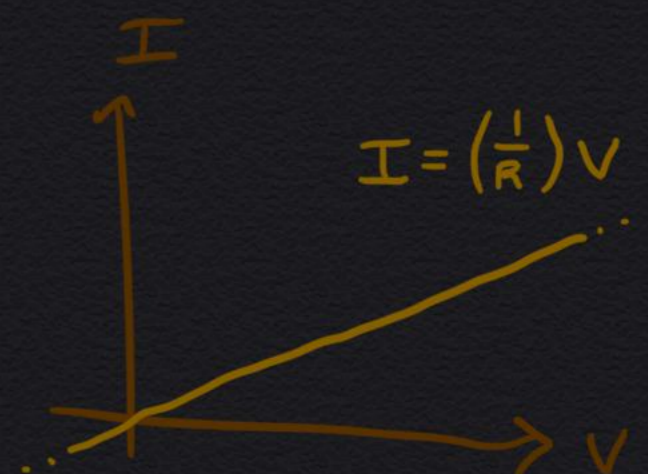
$$I_1 = \frac{V_1}{R_1} \quad I_2 = \frac{V_2}{R_2}$$



Step 7: Plug in node voltages (might use KVL):

$$V_1 = u_1 - u_2$$

$$V_2 = u_1 - u_2$$

$$I_1 = \frac{u_1 - u_2}{R_1} = \frac{u_1}{R_1}$$

$$I_2 = \frac{u_1 - u_2}{R_2} = \frac{u_1}{R_2}$$

$$u_2 = 0$$

$$\underline{\text{KVL}}: +V_1 - V_2 = 0 \checkmark$$

Step 8/9: Plug step 7 into KCL.

Solve for any unknown nodes, and currents.

$$I_s - \frac{u_1}{R_1} - \frac{u_1}{R_2} = 0 \rightarrow I_s = u_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$
$$= u_1 \left(\frac{R_2 + R_1}{R_1 R_2} \right)$$

$$u_1 = I_s \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$I_2 = \frac{u_1}{R_2}$$


$$I_2 = I_s \left(\frac{R_1}{R_1 + R_2} \right)$$

$$I_1 = \frac{u_1}{R_1}$$

$$I_1 = I_s \left(\frac{R_2}{R_1 + R_2} \right)$$

② Circuit Practice

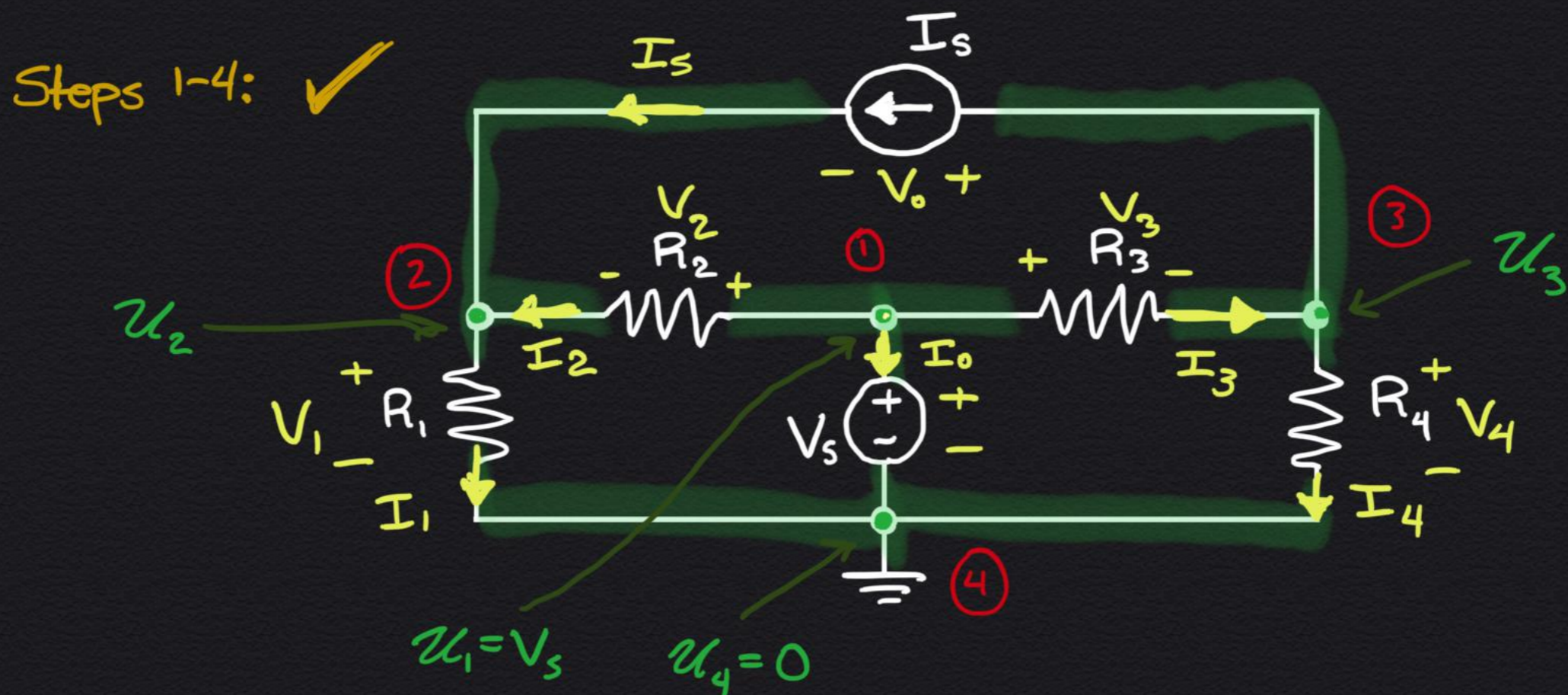Given the circuit below, solve for (a) all node voltages and (b) find I_3 through R_2 (from V_s):



Step 5: KCL

$$\textcircled{1} \quad -I_0 - I_2 - I_3 = 0$$

$$\textcircled{2} \quad I_2 + I_s - I_1 = 0$$

$$\textcircled{3} \quad I_3 - I_s - I_4 = 0$$

$$\textcircled{4} \quad I_1 + I_4 + I_0 = 0$$

Step 6/7: Voltage Plug-in

$$I_1 = \frac{V_1}{R_1} = \frac{u_2 - u_4}{R_1} = \frac{u_2}{R_1}$$

$$I_2 = \frac{V_2}{R_2} = \frac{u_1 - u_2}{R_2} = \frac{V_s - u_2}{R_2}$$

$$I_3 = \frac{V_3}{R_3} = \frac{u_1 - u_3}{R_3} = \frac{V_s - u_3}{R_3}$$

$$I_4 = \frac{V_4}{R_4} = \frac{u_3 - u_4}{R_4} = \frac{u_3}{R_4}$$

Step 8/9: Solve by plugging into KCL

$$\frac{u_2}{R_1} + \frac{u_3}{R_4} + I_0 = 0$$

$$\frac{u_2}{R_1} + \frac{u_3}{R_4} - I_2 - I_3 = 0$$

$$\frac{u_2}{R_1} + \frac{u_3}{R_4} - \frac{V_s - u_2}{R_2} - \frac{V_s - u_3}{R_3} = 0$$

$$u_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + u_3 \left(\frac{1}{R_4} + \frac{1}{R_3} \right) - V_s \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = 0$$

This was all good work, but it will be easier instead to use the other KCL expressions.

$$\frac{V_s - u_2}{R_2} + I_5 - \frac{u_2}{R_1} = 0$$

$$\left(\frac{V_s}{R_2} + I_5 \right) - u_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = 0$$

$$u_2 = \left(\frac{V_s}{R_2} + I_5 \right) \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$-I_0 - I_2 - I_3 = 0$$

$$I_2 + I_5 - I_1 = 0$$

$$I_3 - I_5 - I_4 = 0$$

$$I_1 + I_4 + I_0 = 0$$

$$\frac{V_s - \mathcal{U}_3}{R_3} - I_s - \frac{\mathcal{U}_3}{R_4} = 0$$

$$\left(\frac{V_s}{R_3} - I_s \right) - \mathcal{U}_3 \left(\frac{1}{R_3} + \frac{1}{R_4} \right) = 0 \Rightarrow \mathcal{U}_3 = \left(\frac{V_s}{R_3} - I_s \right) \left(\frac{R_3 R_4}{R_3 + R_4} \right)$$

• Plug in \mathcal{U}_3 to get I_3 , this can be tough!

$$I_3 = \frac{V_s - \mathcal{U}_3}{R_3} = \frac{1}{R_3} \left[V_s - \left(\frac{V_s}{R_3} - I_s \right) \left(\frac{R_3 R_4}{R_3 + R_4} \right) \right]$$

$$= \frac{V_s}{R_3} - \frac{V_s}{R_3} \left(\frac{R_4}{R_3 + R_4} \right) + I_s \left(\frac{R_4}{R_3 + R_4} \right)$$

$$= \frac{V_s R_3 + \cancel{V_s R_4} - \cancel{V_s R_4} + I_s R_3 R_4}{R_3 (R_3 + R_4)}$$

$$I_3 = \frac{V_s + I_s R_4}{R_3 + R_4}$$