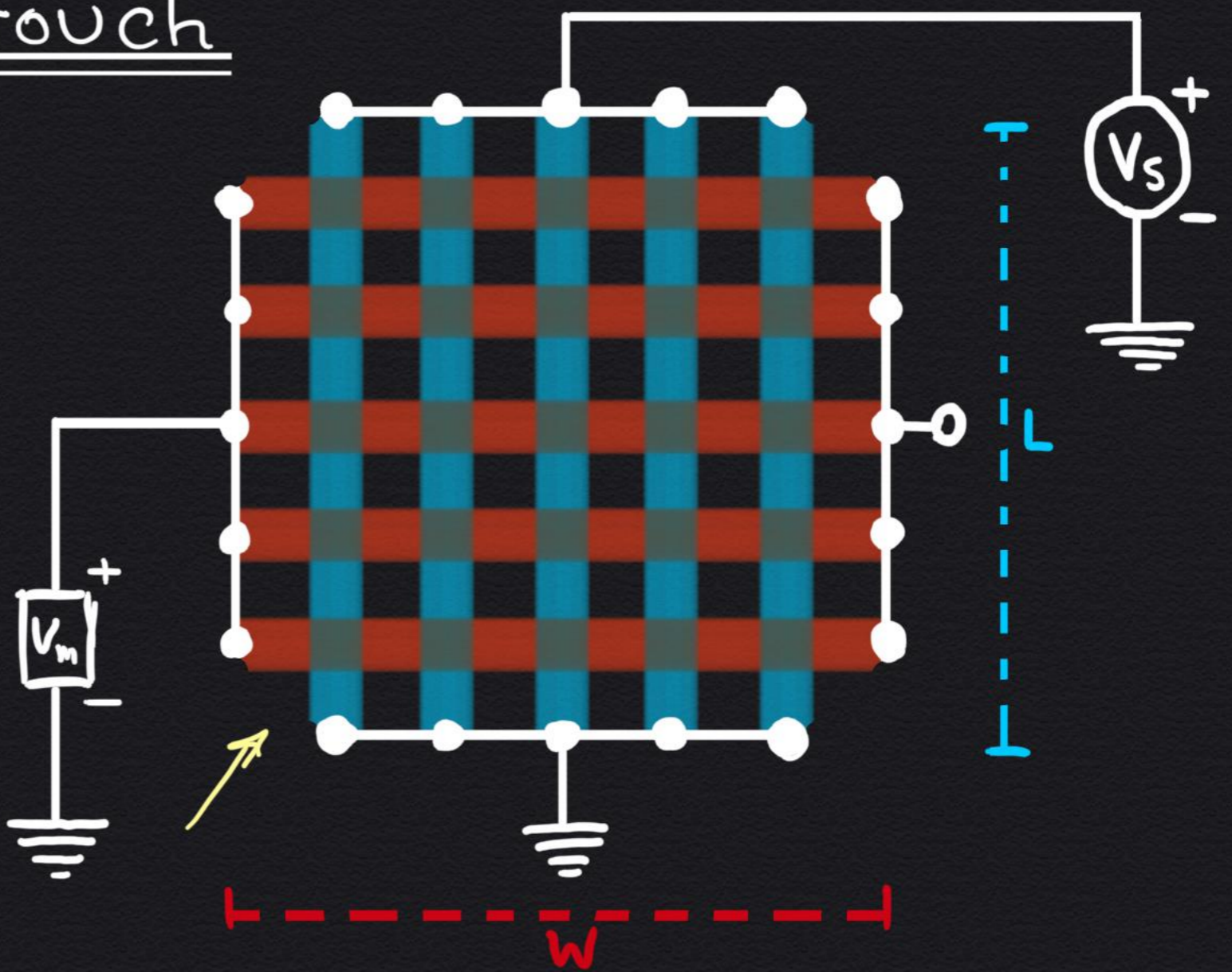



① Resist the touch

- Length L , width w .
- $N \times N$ strips (discretized)
- All strips have cross A , and resistivity ρ .
- Strips are split into $N+1$ segments.



(a) Find the resistance for a single blue strip R_y , and a red strip R_x .

$$R_x = \rho \frac{w}{A} \quad || \quad R_y = \rho \frac{L}{A}$$


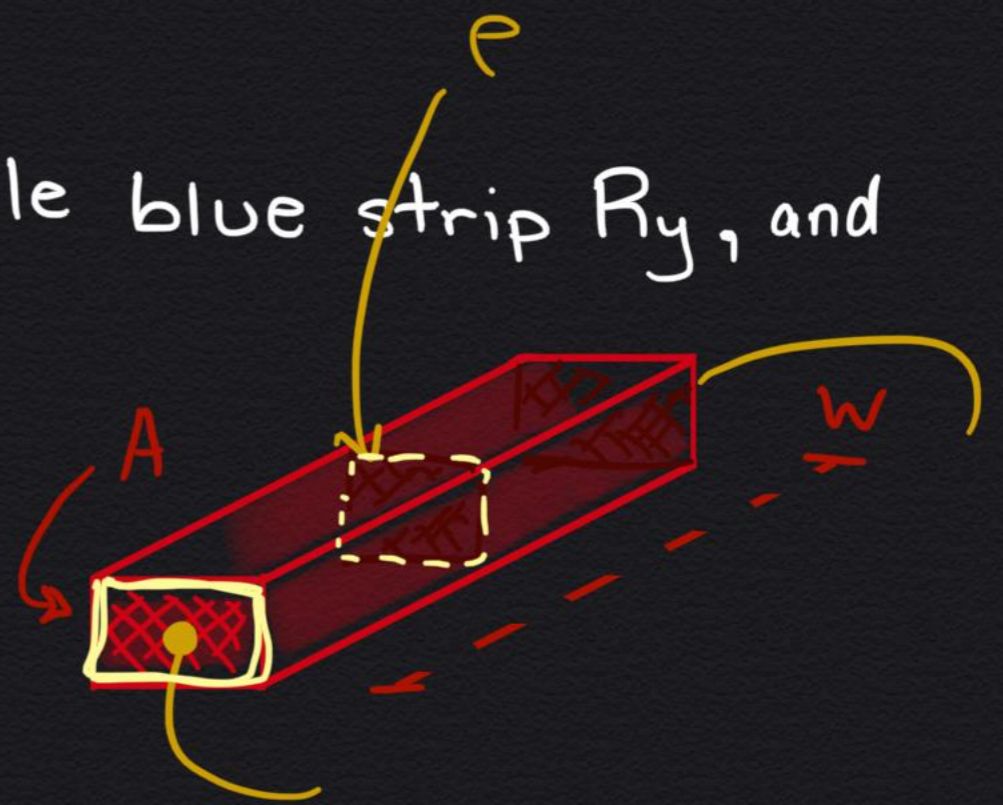


'A' ~ upping the cross-sectional area is like "opening more high-ways"
 'L' ~ upping the length adds more resistor to go through.

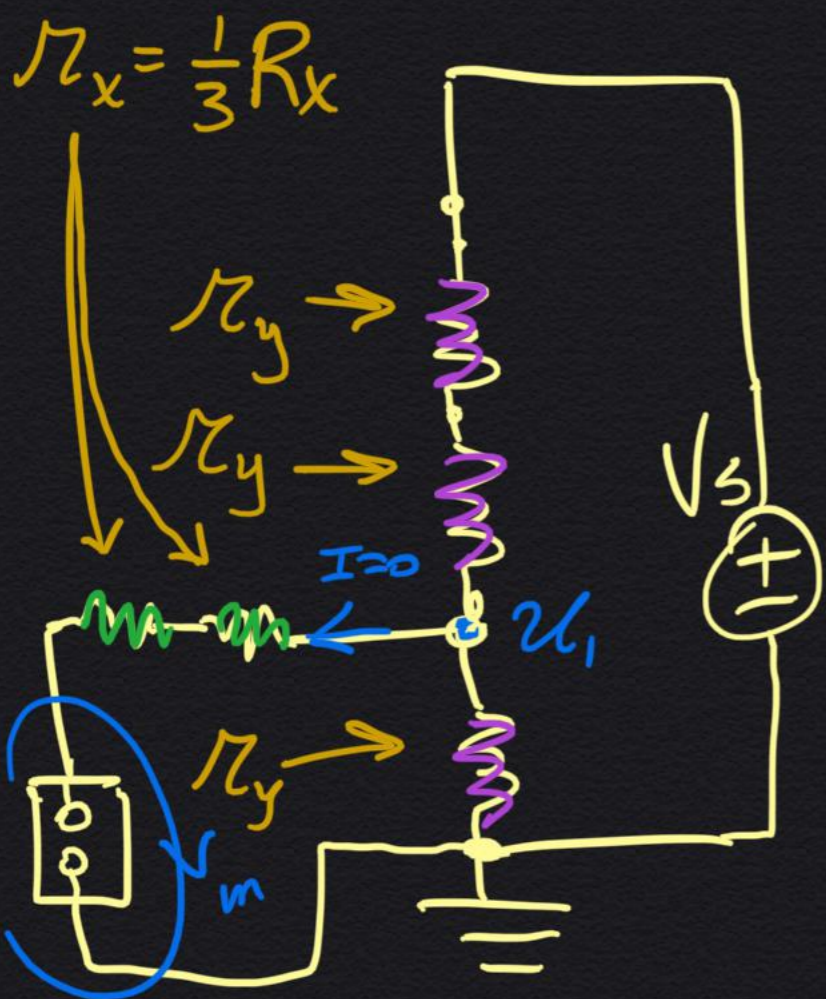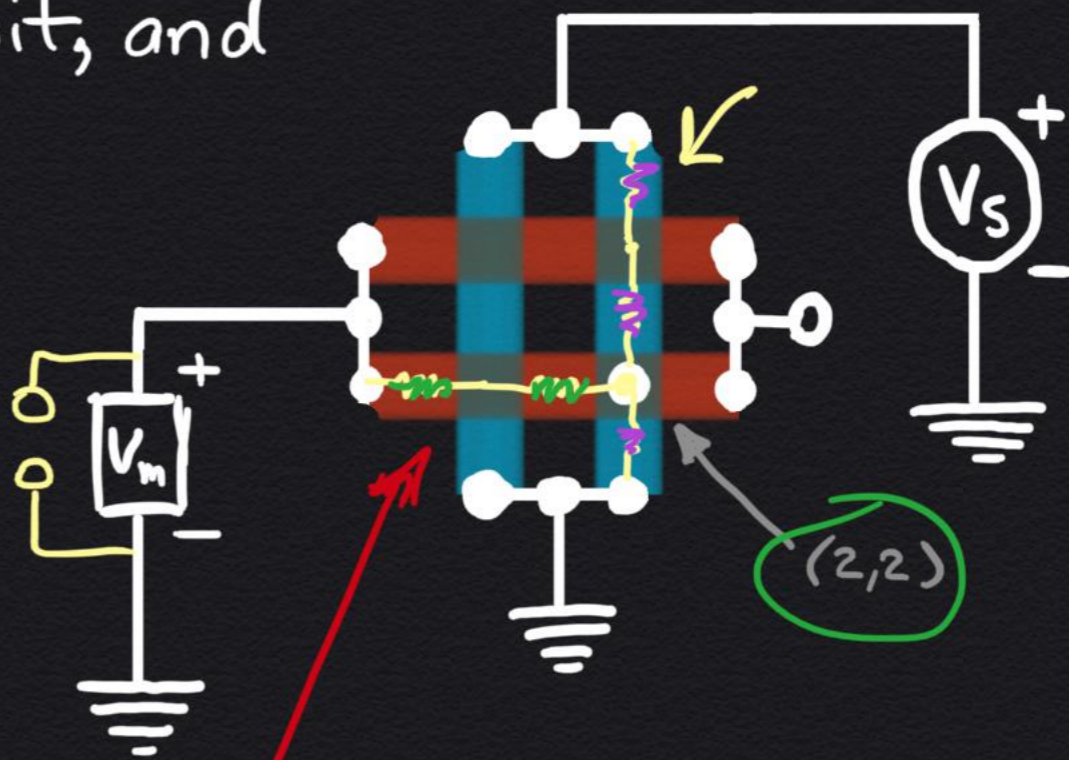(b) Now suppose our touchscreen has $N=2$, and R_x, R_y are given so $V_s = 3V$, $R_x = 2k\Omega$, and $R_y = \underline{\underline{2k\Omega}}$.

Draw an equivalent circuit, and find V_m :

R_y $\pi_y = \frac{R_y}{2+1} = \frac{1}{3}R_y$




$\pi_x = \frac{1}{3}R_x$

$\pi_x = \frac{R_x}{N+1} = \frac{1}{3}R_x$

$$U_1 = V_s \frac{\pi_y}{2\pi_y + \pi_x} = V_s \frac{\frac{1}{3}R_y}{(\frac{2}{3}R_y) + (\frac{1}{3}R_x)}$$

$$= \frac{1}{3}V_s$$

$$V_m = U_1 = 1V$$

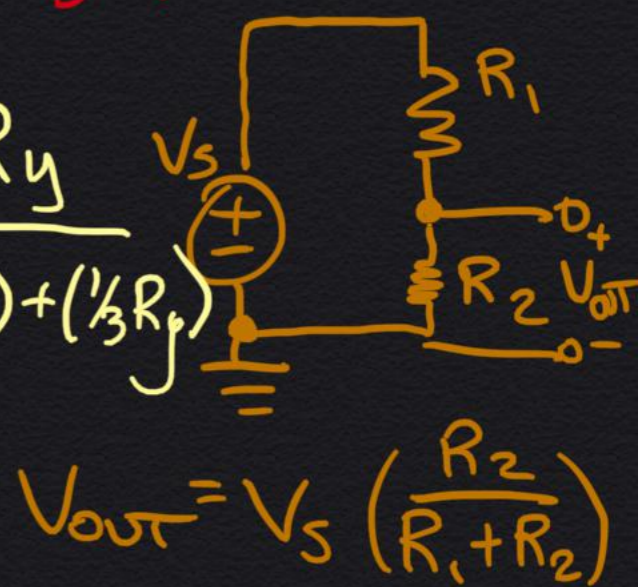


Voltmeter is like an open circuit, so no current and no voltage drop across green resistors.


$$V_{out} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

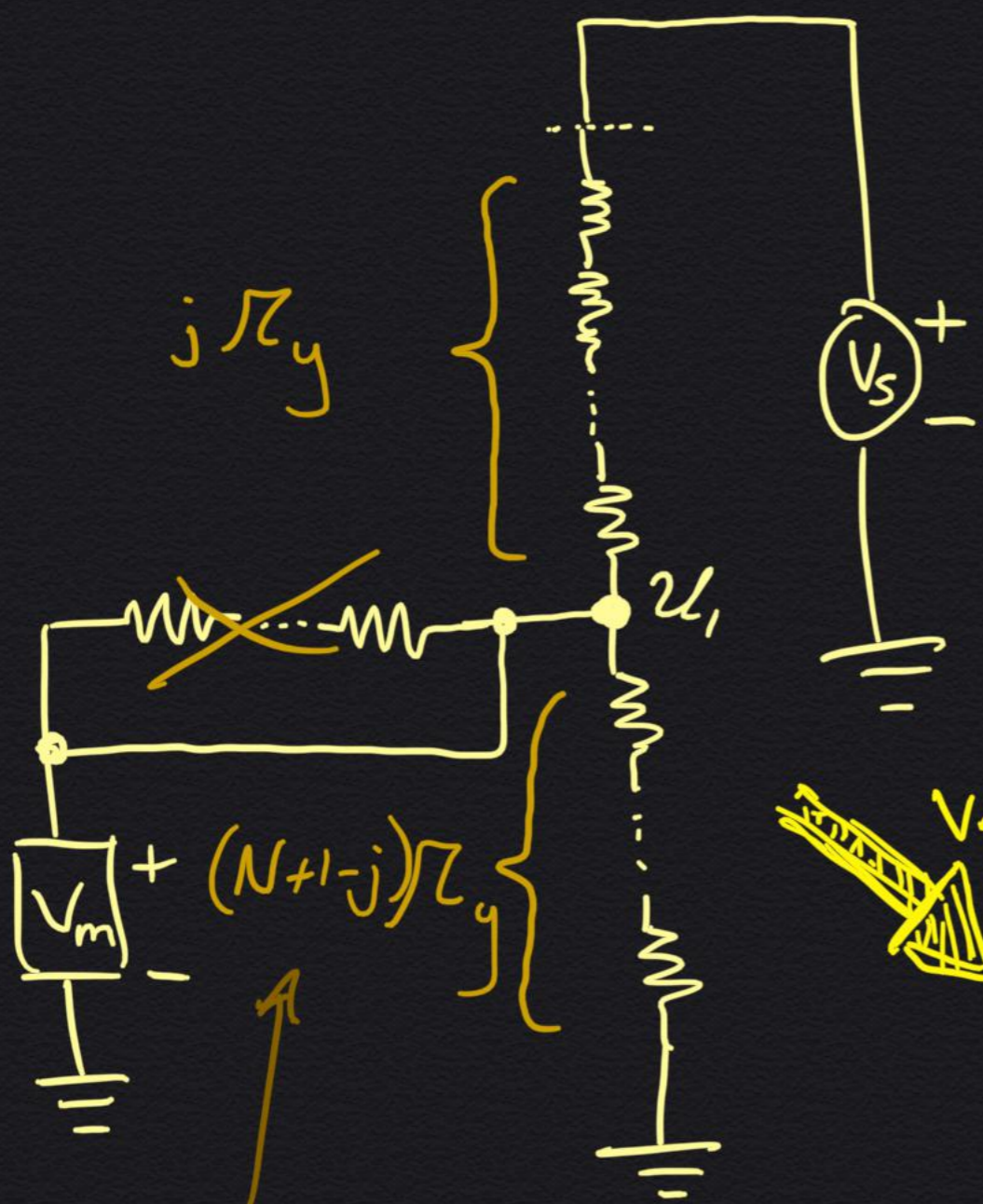(c) Let's generalize to the arbitrary $N \times N$ with node (i, j) . Find V_m in terms of $V_s, N, i, j, \rho, L, W, A$.


$$R_y = \rho \cdot \frac{L}{A} \quad \cancel{R_y} = \frac{R_y}{N+1}$$



Voltage Divider!

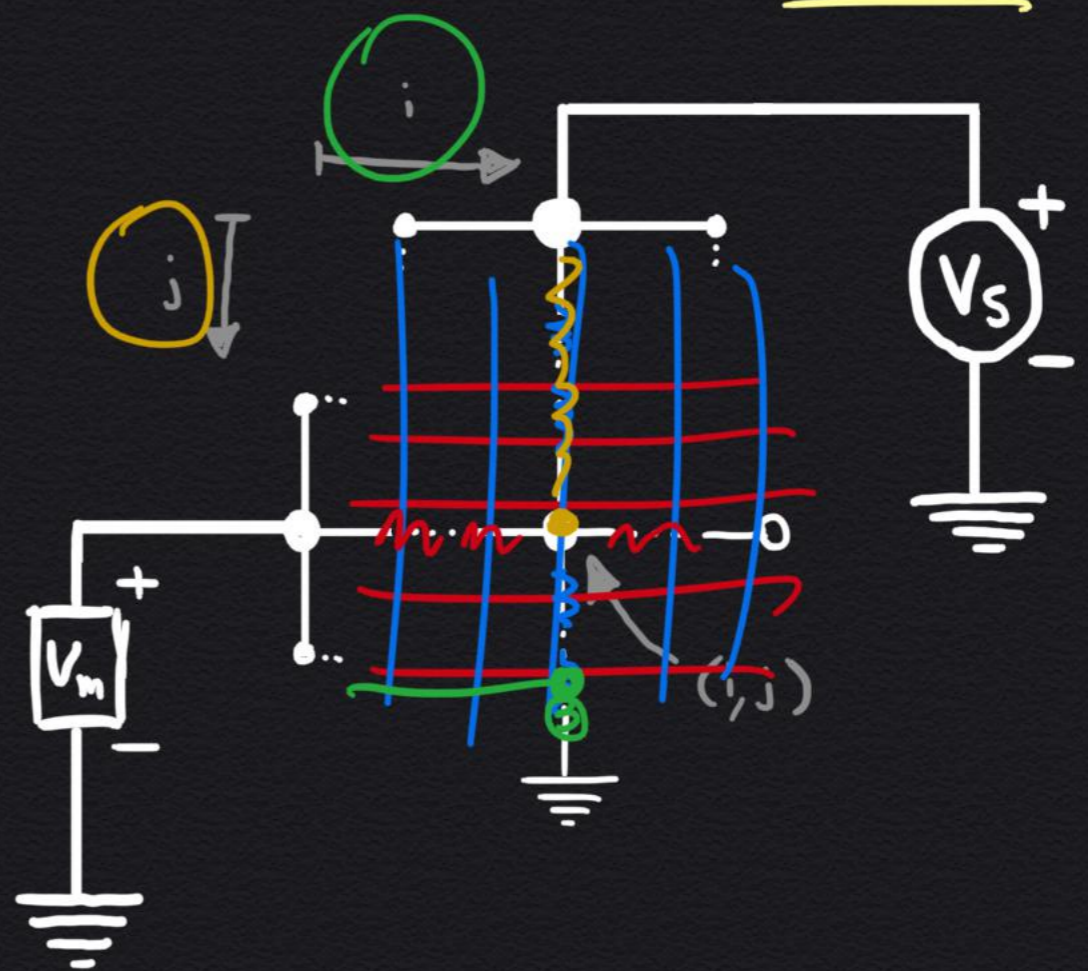

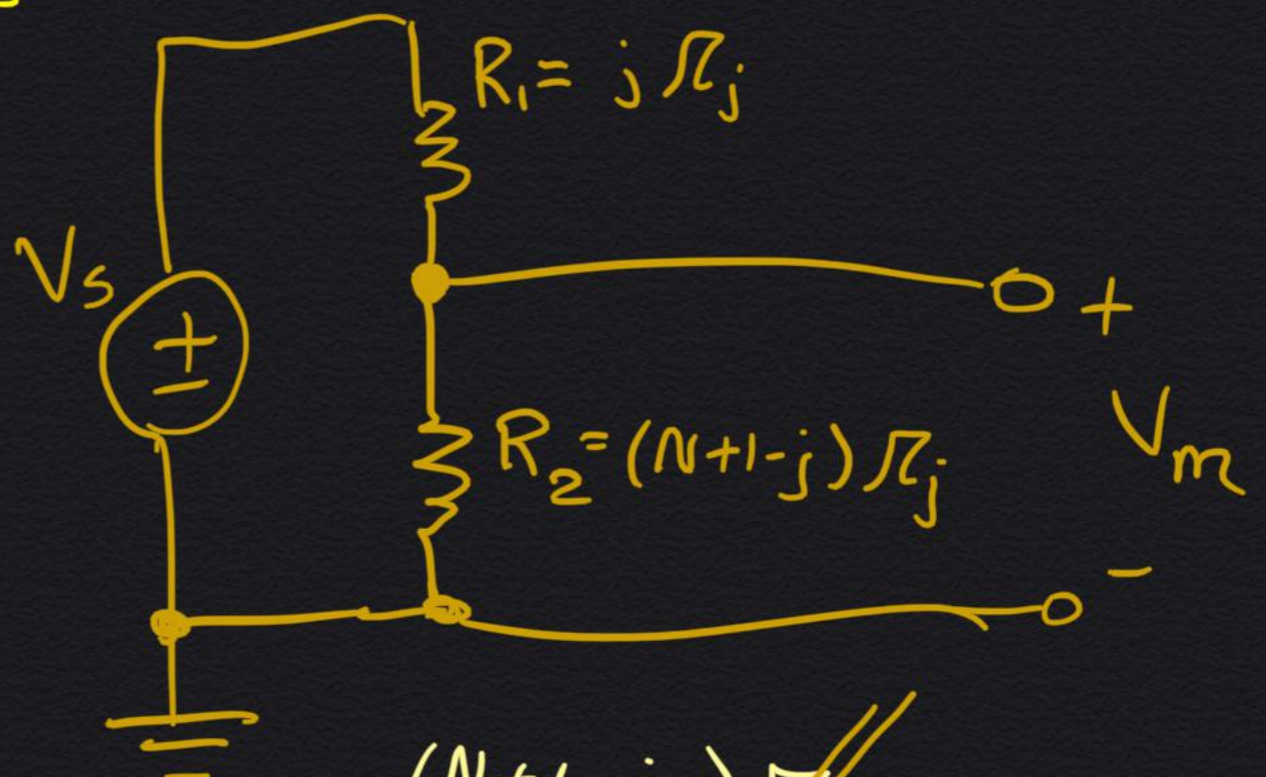Since $jR_y + (N+1-j)R_y = (N+1)R_y = R_y \checkmark$



$$V_m = V_s \cdot \left(\frac{R_2}{R_1 + R_2} \right) = V_s \cdot \frac{(N+1-j)R_j}{(N+1-j+j)R_j}$$

$$= V_s \cdot \frac{N+1-j}{N+1} = V_s \left(\frac{N+1}{N+1} - \frac{j}{N+1} \right)$$

$$V_m = V_s \left(1 - \frac{j}{N+1} \right)$$



Yay! Check $j=1$ & $j=N$, should always be $0 < V_m < V_s$



$$R_{EQ} = \left(\frac{1}{5} + \frac{1}{10} \right)^{-1}$$

$$= \left(\frac{3}{10} \right)^{-1}$$

~~$$= \frac{10}{3} \text{ k}\Omega$$~~

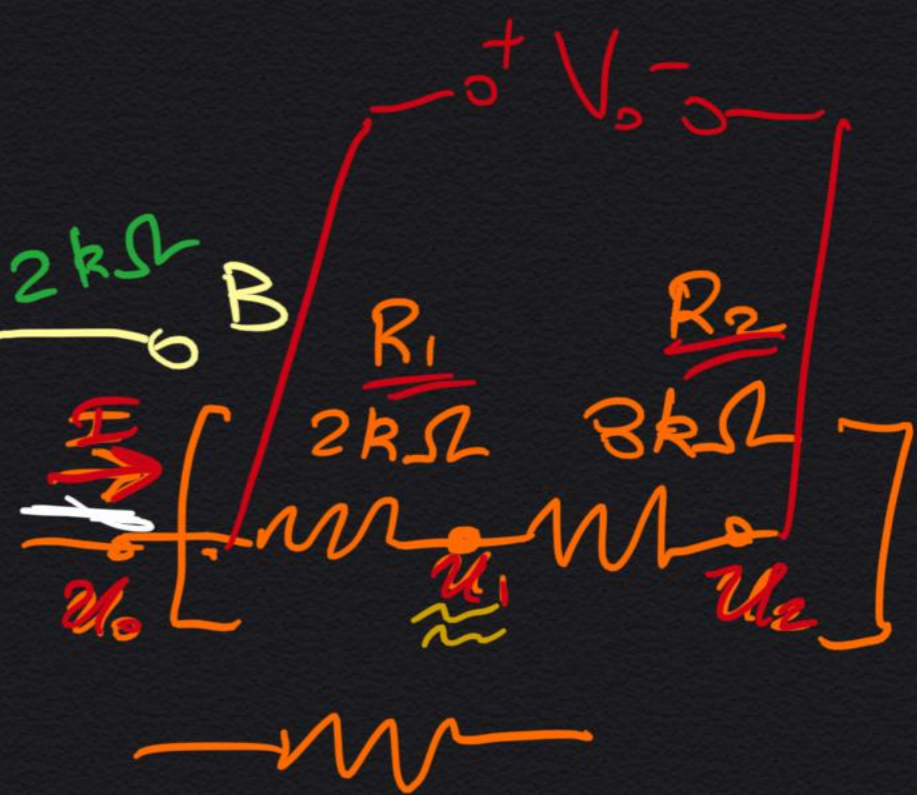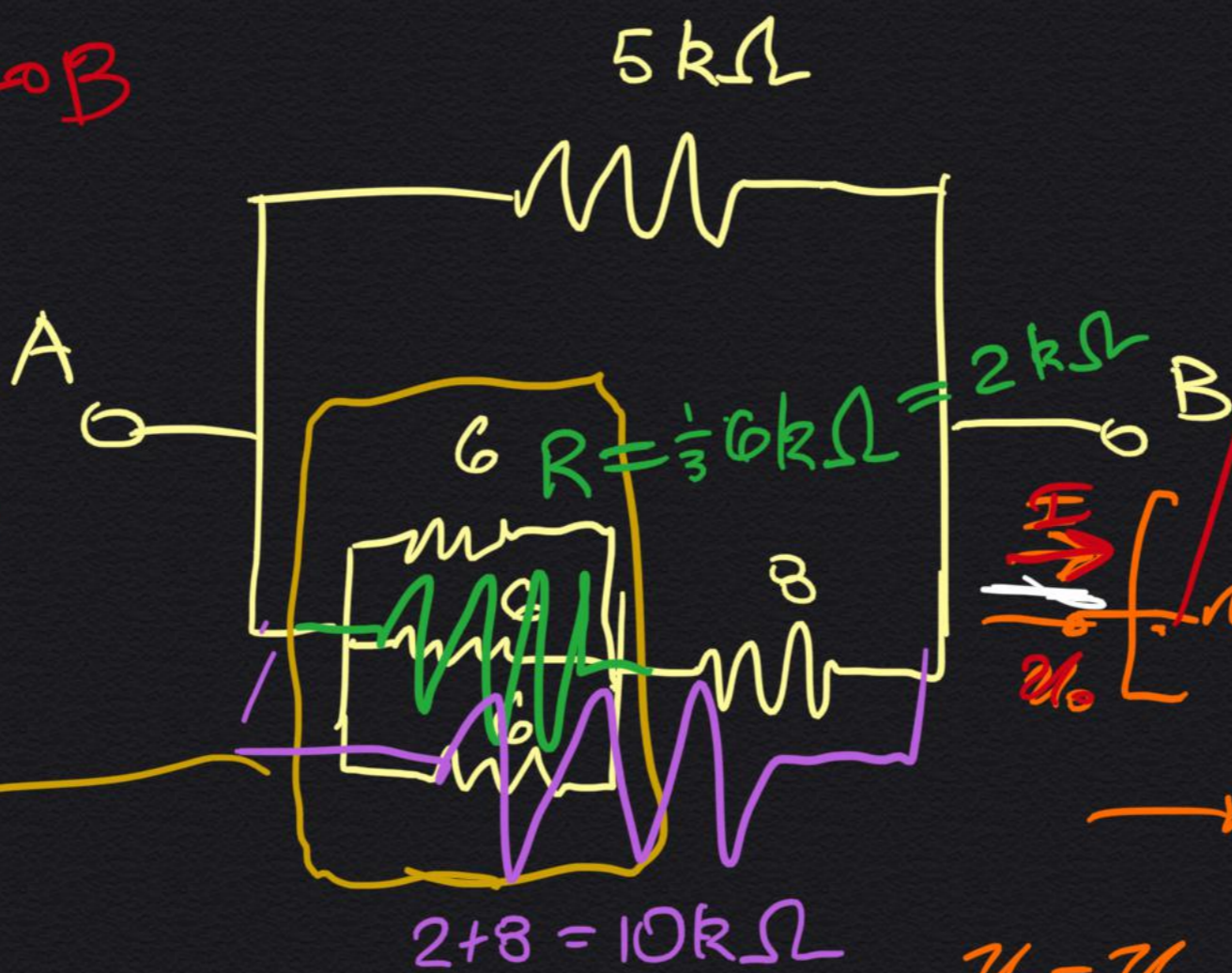


$$u_0 - u_1 = I R_1$$

$$u_1 - u_2 = I R_2$$

$$V_0 = u_0 - u_2$$

$$= I (R_1 + R_2)$$

R_{EQ}

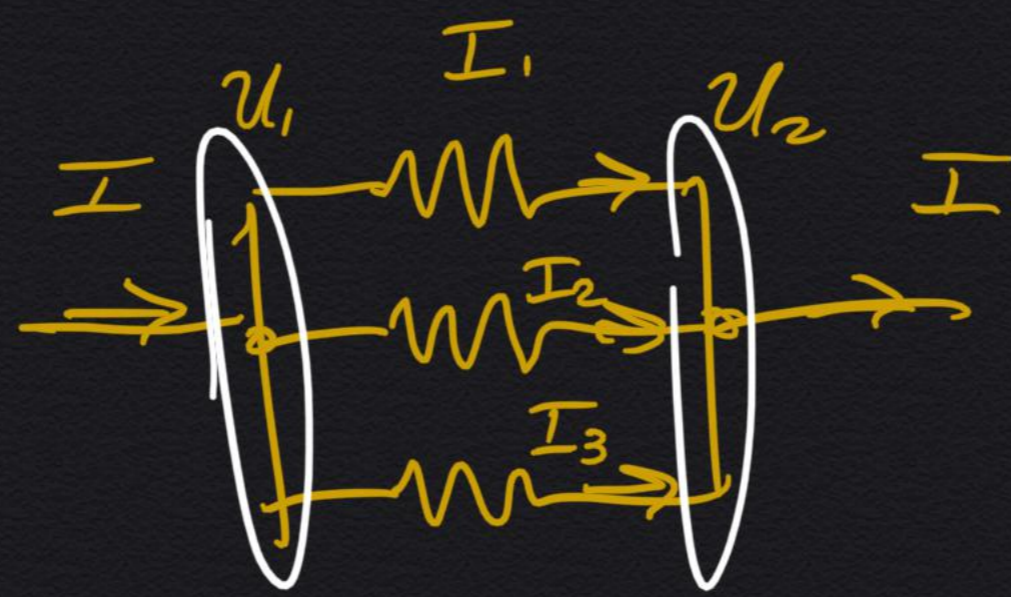

$$V_0 = U_1 - U_2 = \underbrace{I_1 R_1} = \underbrace{I_2 R_2} = \underbrace{I_3 R_3}$$

$$I = I_1 + I_2 + I_3$$

$$= \left(\frac{V_0}{R_1} + \frac{V_0}{R_2} + \frac{V_0}{R_3} \right) = V_0 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{V_0}{R_{EQ}} = I = V_0 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$R_{EQ} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

when $R_1 = R_2 = R_3 \dots$

$$= \left(\frac{3}{R_1} \right)^{-1} = \frac{R_1}{3} = \frac{1}{3} R_1$$