

# ① Charge conservation



Consider this circuit with  $C_1 = C_2 = 1 \mu\text{F}$ .

Before  $\phi_1$  is closed,  $C_1$  is charged with +1V and  $C_2$  with +2V.



a) What are the initial charges on  $C_1$  &  $C_2$ ?

$$\left[ C = \frac{Q}{V} \right]$$

$$Q_1 = C_1 V_1 = (1 \mu\text{F})(1\text{V}) = 1 \mu\text{C} \equiv 1 \times 10^{-6} \text{C}$$

$$Q_2 = C_2 V_2 = (1 \mu\text{F})(2\text{V}) = 2 \mu\text{C} \quad \checkmark$$

b) After closing  $\phi_1$ , what are the charges and voltages across  $C_1$  &  $C_2$ ?

$$Q_{\text{Tot}} = Q_1^{(\phi_1)} + Q_2^{(\phi_1)} = 3 \mu\text{C} = Q_1 + Q_2$$

$$V = \frac{Q}{C} = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$\left[ \begin{array}{l} Q_1 = 3 \mu\text{C} - Q_2 \\ Q_1 = \left( \frac{C_1}{C_2} \right) Q_2 \end{array} \right]$$

$$Q_1 = Q_2 = 1.5 \mu\text{C}$$


$$2Q_1 = 3 \mu\text{C}$$


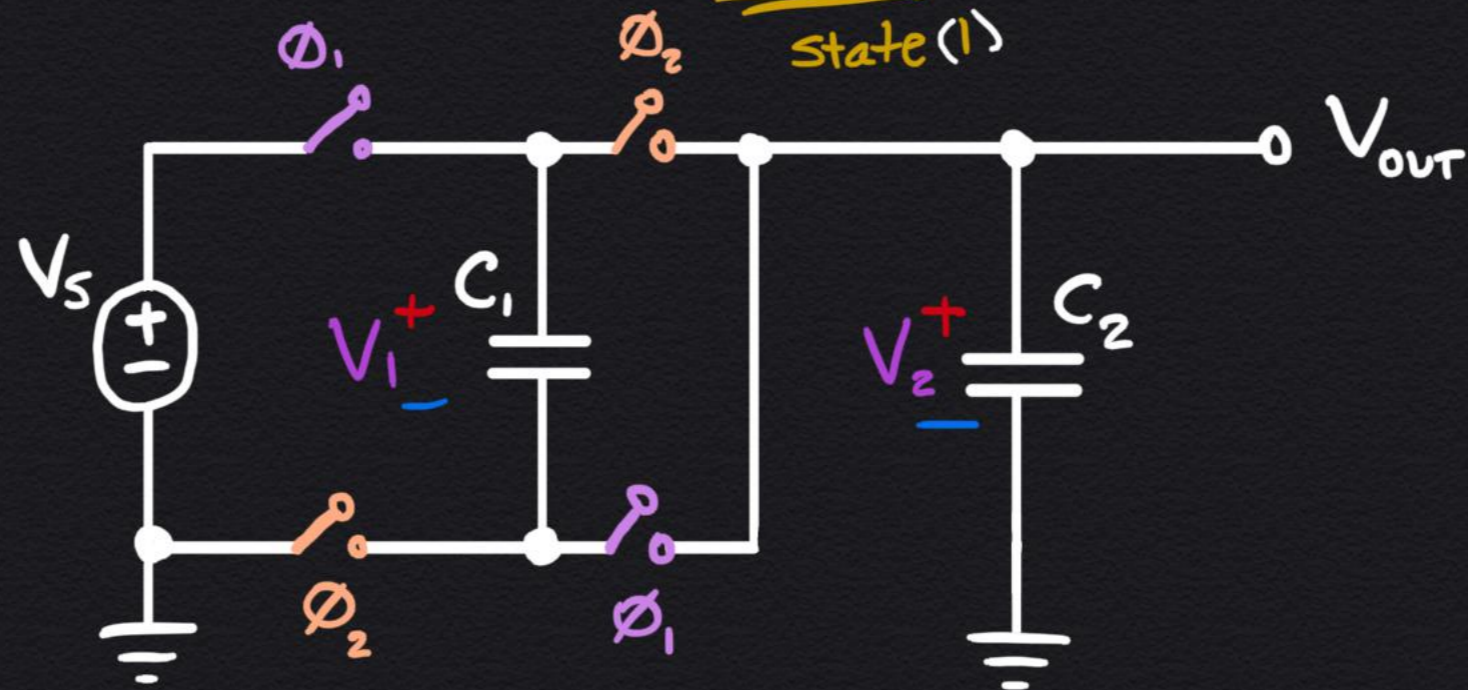
# ② Charge sharing

Consider the following circuit.


(We will go :  $\phi_1$  open  $\phi_2$  open  $\rightarrow$   $\phi_1$  closed  $\phi_2$  open  $\rightarrow$   $\phi_1$  open  $\phi_2$  open  $\rightarrow$   $\phi_1$  open  $\phi_2$  closed )




a) Draw voltage polarities on each capacitor:  
(Make sure to stay consistent btwn phases!)

b) Draw the equivalent circuits for  $\phi_1$  &  $\phi_2$ :


State 1

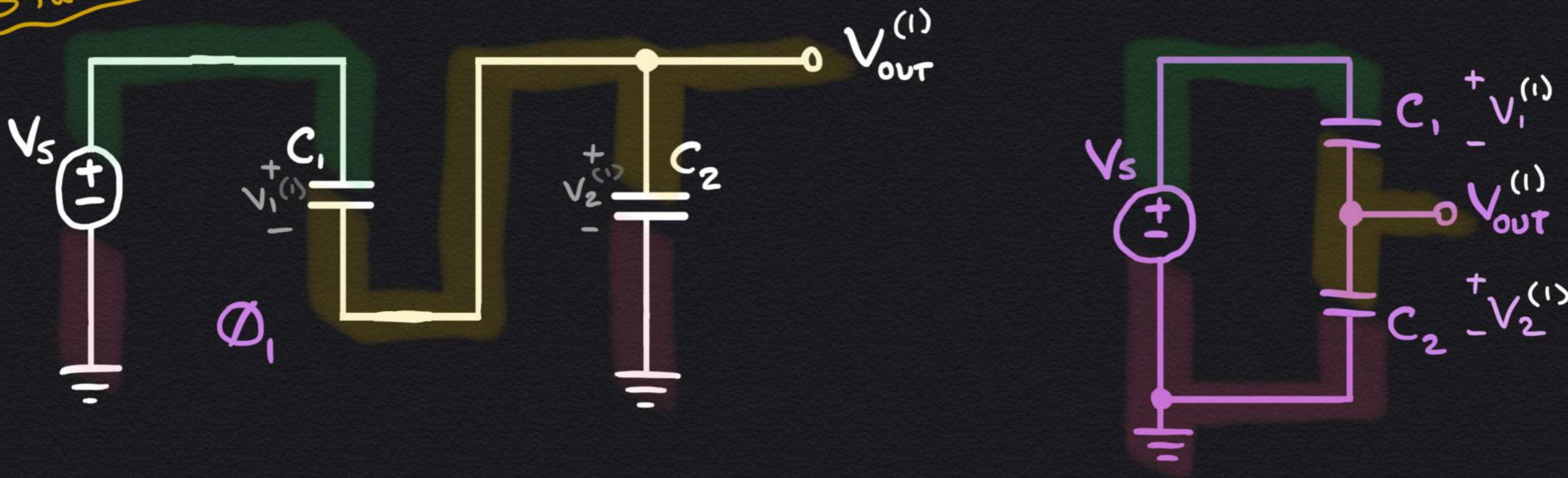


State 2

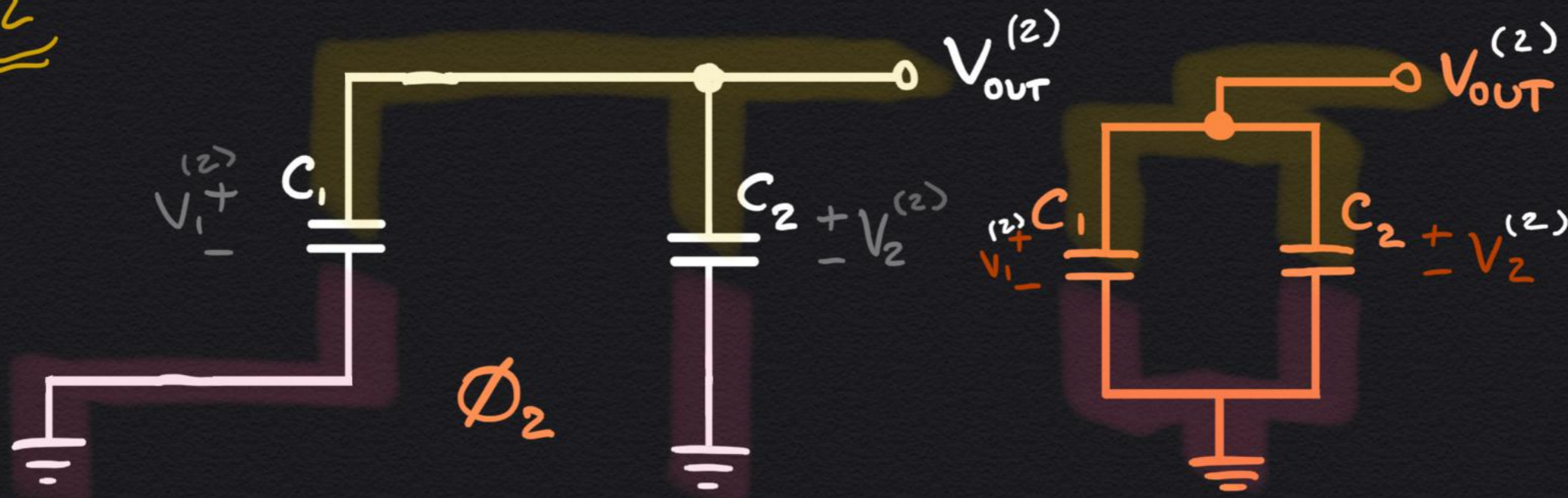

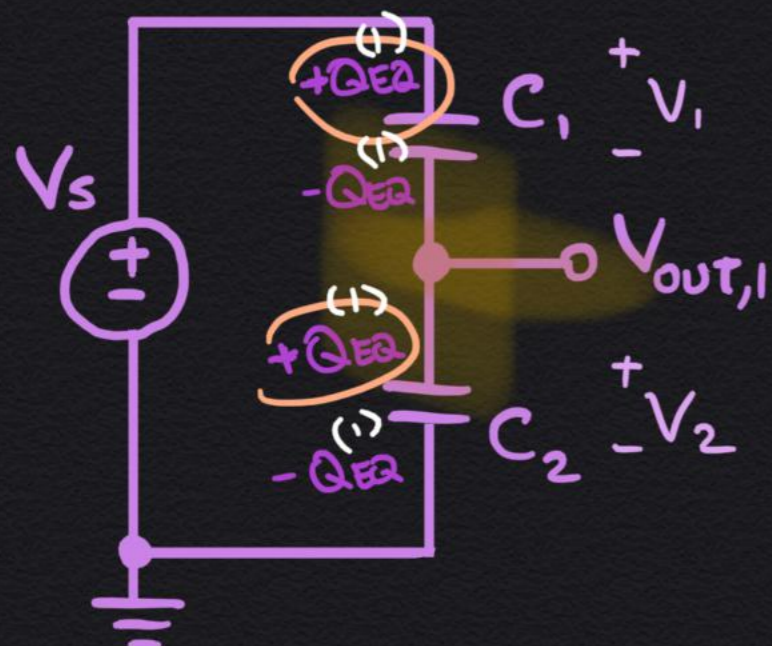c) Find  $V_{OUT}$  in  $\phi_2$  as a function of  $V_s$ ,  $C_1$ , and  $C_2$ :



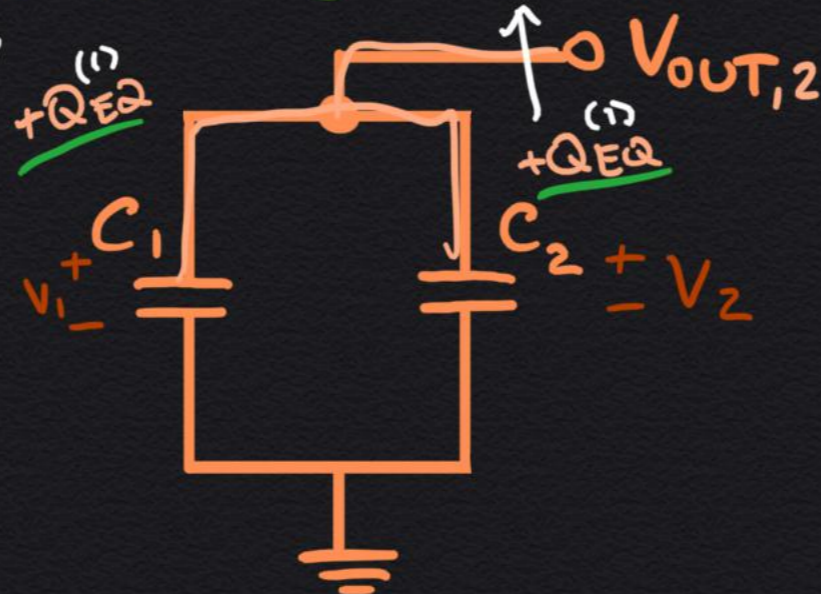The floating node has  $Q_{EQ}^{(1)} + Q_{EQ}^{(2)}$  in total.



$$Q_{EQ}^{(2)} = 2Q_{EQ}^{(1)} = V_s \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{EQ}^{(1)} = \left( \frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \left( \frac{C_2}{C_1 C_2} + \frac{C_1}{C_1 C_2} \right)^{-1} = \left( \frac{C_1 + C_2}{C_1 C_2} \right)^{-1} = \frac{C_1 C_2}{C_1 + C_2}$$

$$Q_{EQ}^{(1)} = C_{EQ} V_s = \frac{C_1 C_2}{C_1 + C_2} V_s$$

$$V_{OUT}^{(2)} = \frac{Q_1^{(2)}}{C_1} = \frac{Q_2^{(2)}}{C_2}$$

$$C_{EQ}^{(2)} = C_1 + C_2$$

$$V_{OUT}^{(2)} = \frac{Q_{EQ}^{(2)}}{C_{EQ}^{(2)}} = \frac{2Q_{EQ}^{(1)}}{C_1 + C_2}$$

$$V_{OUT}^{(2)} = 2V_s \frac{C_1 C_2}{(C_1 + C_2)^2}$$

d) How are the charges distributed when  $C_1 \gg C_2$ ?

Since  $C_1 \gg C_2$

$$Q_2^{(2)} = \left[ \frac{C_2}{C_1} \right] Q_1^{(2)} \approx 0$$

All charge goes to the much bigger capacitor.

We can also solve this formally using the charge sum:

$$Q_1^{(2)} + Q_2^{(2)} = 2V_s \left( \frac{C_1 C_2}{C_1 + C_2} \right)$$

$$2V_s \left( \frac{C_1 C_2}{C_1 + C_2} \right) - Q_1^{(2)} = Q_2^{(2)} = \left( \frac{C_2}{C_1} \right) Q_1^{(1)}$$

$$2V_s \left( \frac{C_1 C_2}{C_1 + C_2} \right) = Q_1^{(1)} \left( \frac{C_2}{C_1} + 1 \right) \frac{C_1 + C_2}{C_1}$$

$$2V_s \left( \frac{C_1^2 C_2}{(C_1 + C_2)^2} \right) = Q_1^{(1)}$$

$$Q_1^{(2)} = 2V_s C_2 \frac{1}{\left(1 + \frac{C_2}{C_1}\right)^2} \approx 2V_s C_2$$

$$Q_2^{(2)} = 2V_s C_2 \frac{C_2/C_1}{\left(1 + \frac{C_2}{C_1}\right)^2} \approx 0$$