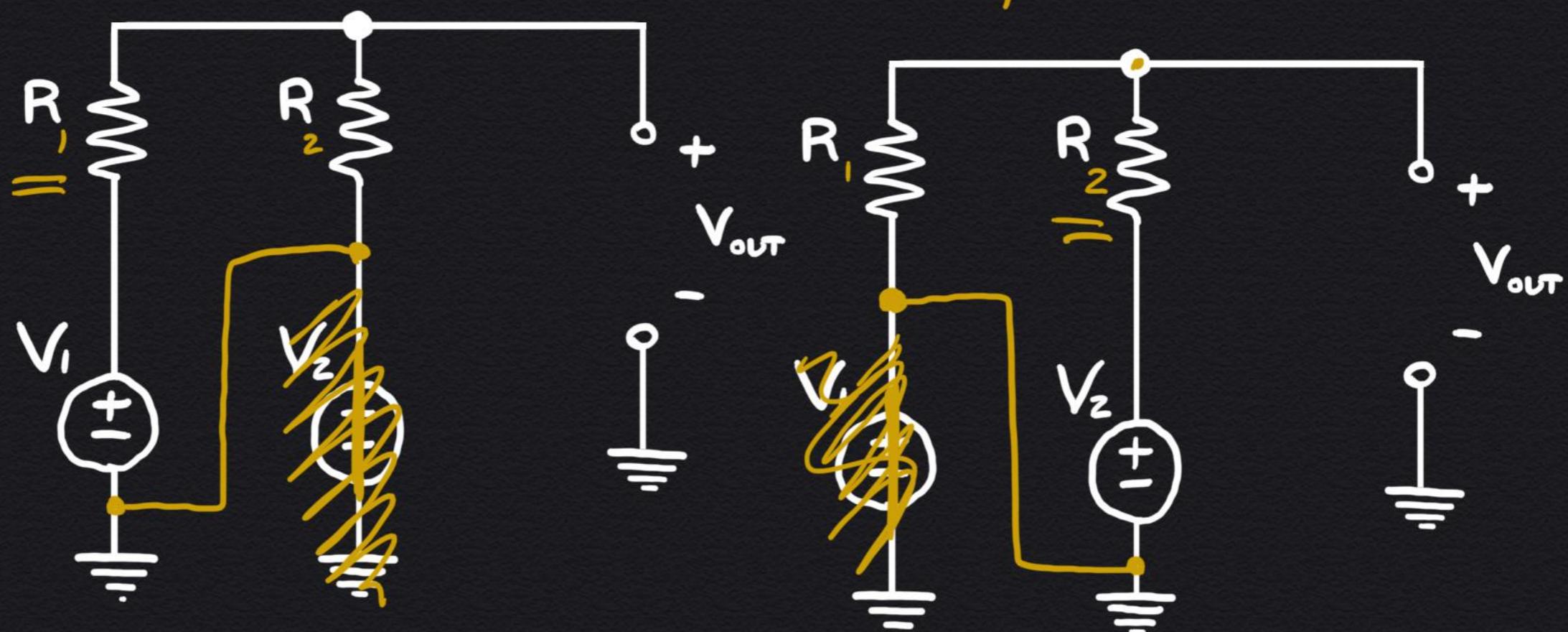


"Casual Pre-midterm Session"

- Super position:

$$V_{\text{OUT}} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$$

I Dividers for Days:




a] Find V_{out} :

$$V_{out} = \frac{1}{2} V_1 + \frac{1}{2} V_2$$

b] Can you identify new resistors for the circuit so that $V_{out} = \frac{1}{3} V_1 + \frac{2}{3} V_2$?
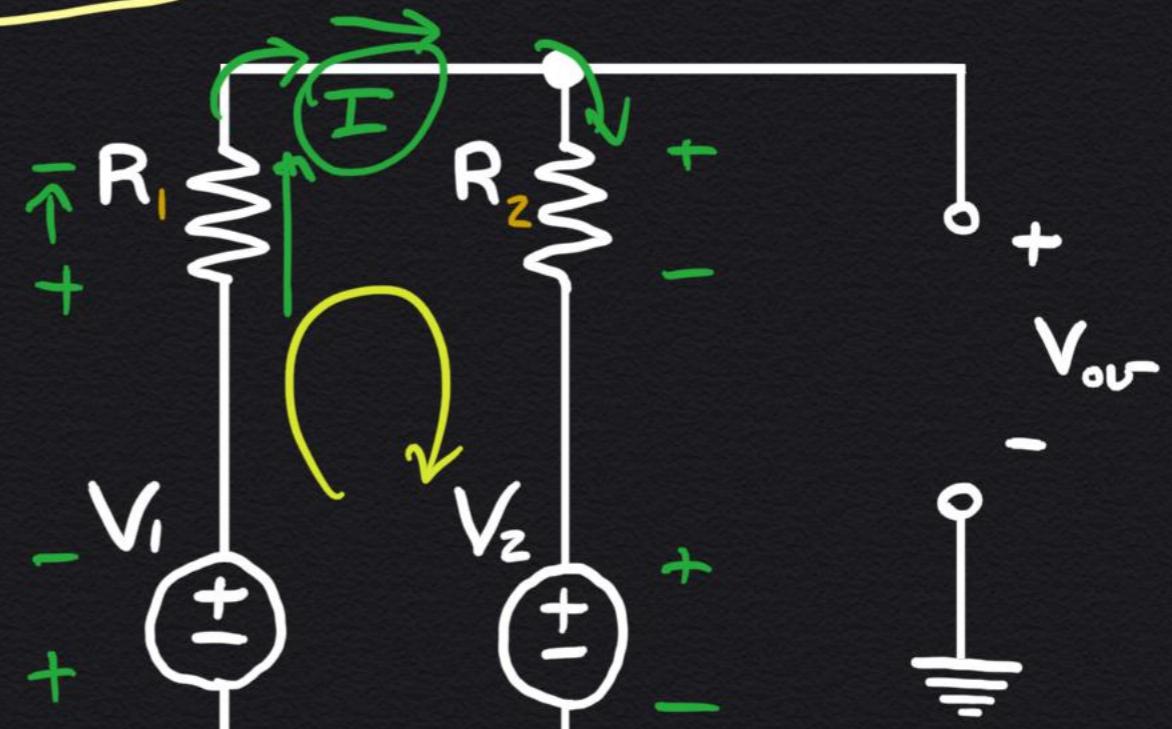
$$V_{out} = V_1 \underbrace{\left(\frac{R_2}{R_1+R_2} \right)}_{1/3} + V_2 \underbrace{\left(\frac{R_1}{R_1+R_2} \right)}_{2/3}$$



$$R_1 + R_2 = 3k\Omega$$

$$R_1 = 2k\Omega$$

$$R_2 = 1k\Omega$$

Technically any values work provided $R_1 = 2R_2$!!
(2 unknowns, but each eqn is identical to each other)

* Green is NVA approach:

$$I = \frac{V_1 - V_2}{(R_1 + R_2)}$$

$$V_{out} = V_1 - IR_1 = V_1 \left(1 - \frac{R_1}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$$

~OR~

$$V_{out} = V_2 - IR_2 = V_1 \left(\frac{R_1}{R_1 + R_2} \right) + V_2 \left(1 - \frac{R_1}{R_1 + R_2} \right)$$




$$V_1 - IR_1 - IR_2 - V_2 = 0$$

$$V_1 - V_2 = I(R_1 + R_2)$$

Consider this new circuit:

- Select R_3 & R_L such that

$$I_L = \frac{2}{5} (I_1 + I_2)$$

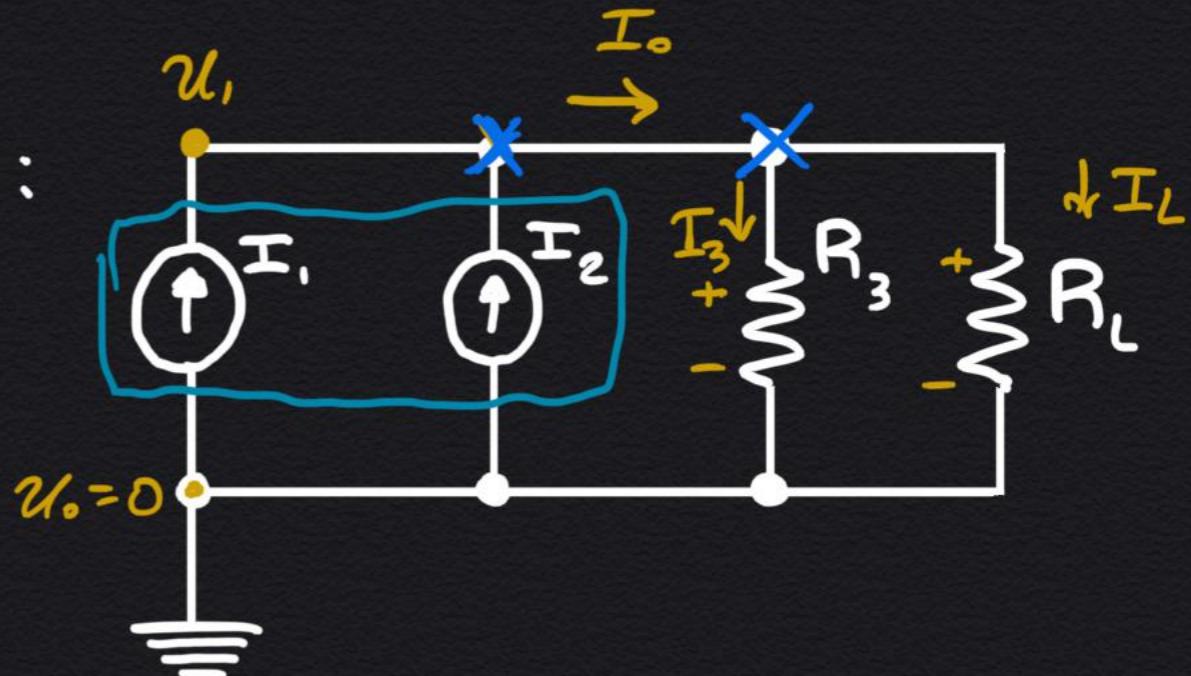

$$u_1 = (I_1 + I_2) \left(\frac{R_L R_3}{R_L + R_3} \right) \Leftarrow$$

$$(I_1 + I_2) = I_L + I_3 = u_1 \left(\frac{R_3}{R_L R_3 + R_3 R_L} + \frac{R_L}{R_3 R_L} \right)$$


$$I_L = \frac{u_1}{R_L} = (I_1 + I_2) \left(\frac{R_3}{R_3 + R_L} \right)$$

$$\frac{u_1}{R_L}$$

$$\frac{u_1}{R_3}$$

$$\frac{R_3 + R_L}{R_3 R_L}$$


② Voltage Booster:
[$V_s = 5V$]

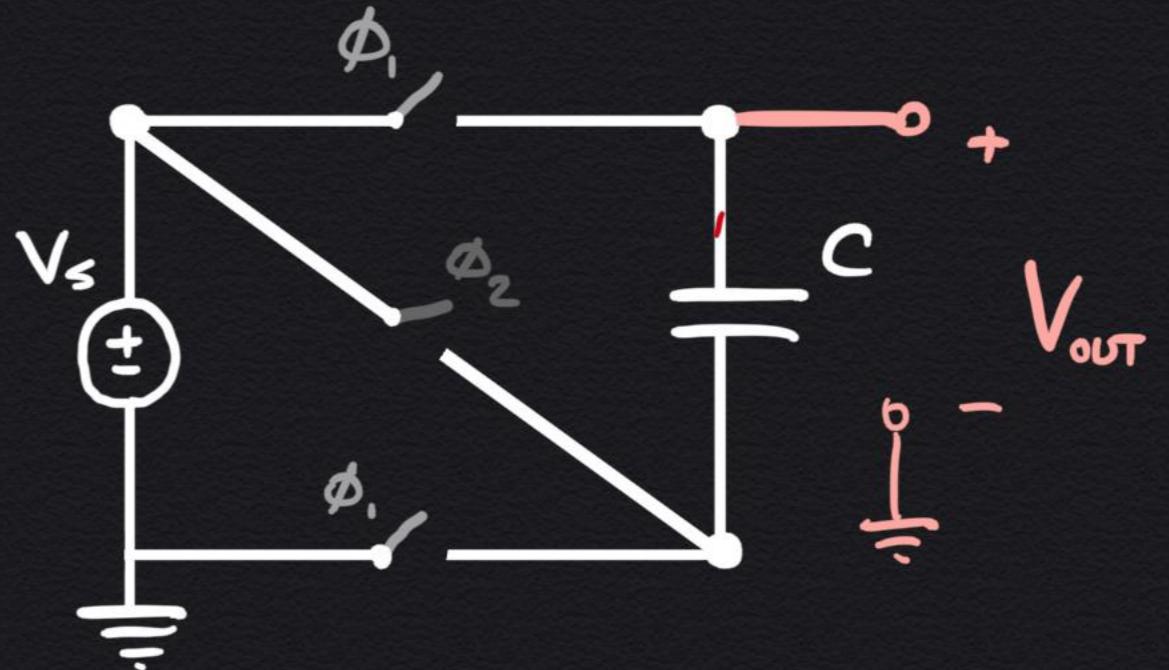

a) Identify Q and V_{out} in phase 1 (ϕ_1):

$$V_{out} = V_s$$

$$Q'' = C V_s$$

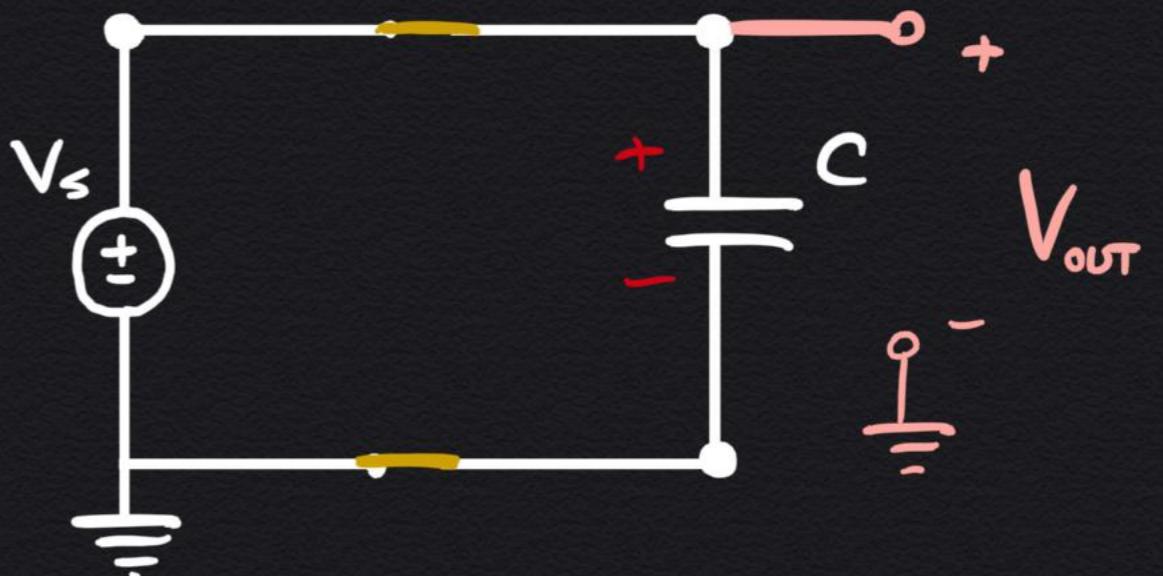

b) Determine V_{out} in phase 2 (ϕ_2):

$$Q^{(2)} = CV \rightarrow V_c = \frac{Q^{(2)}}{C}$$

$$V_{out} = V_s + V_c$$

$$= V_s + \frac{1}{C} (CV_s)$$

$$= 2V_s = 10V$$

