

EECS 16A Module 2

Today

Op-Amps

Negative Feedback


Unreasonable effectiveness of mathematics.

↳ AI, Robotics, feedback, economics, social justice, biology.

"The loading effect" "Digitally" 0, 1, ... "bits"


DAC

Digital to Analog Converter.

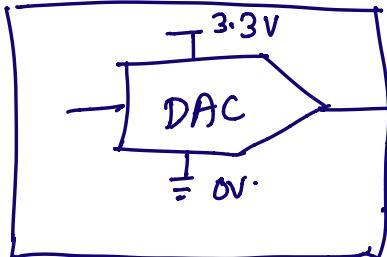


Equivalent

+
- Vout, DAC

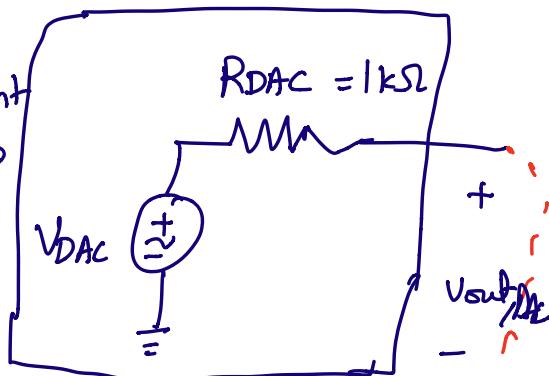



Speaker:

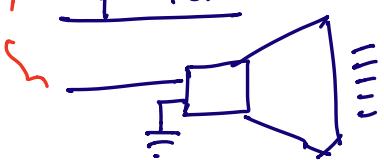

Equivalent

↔

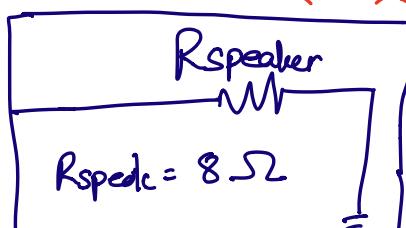

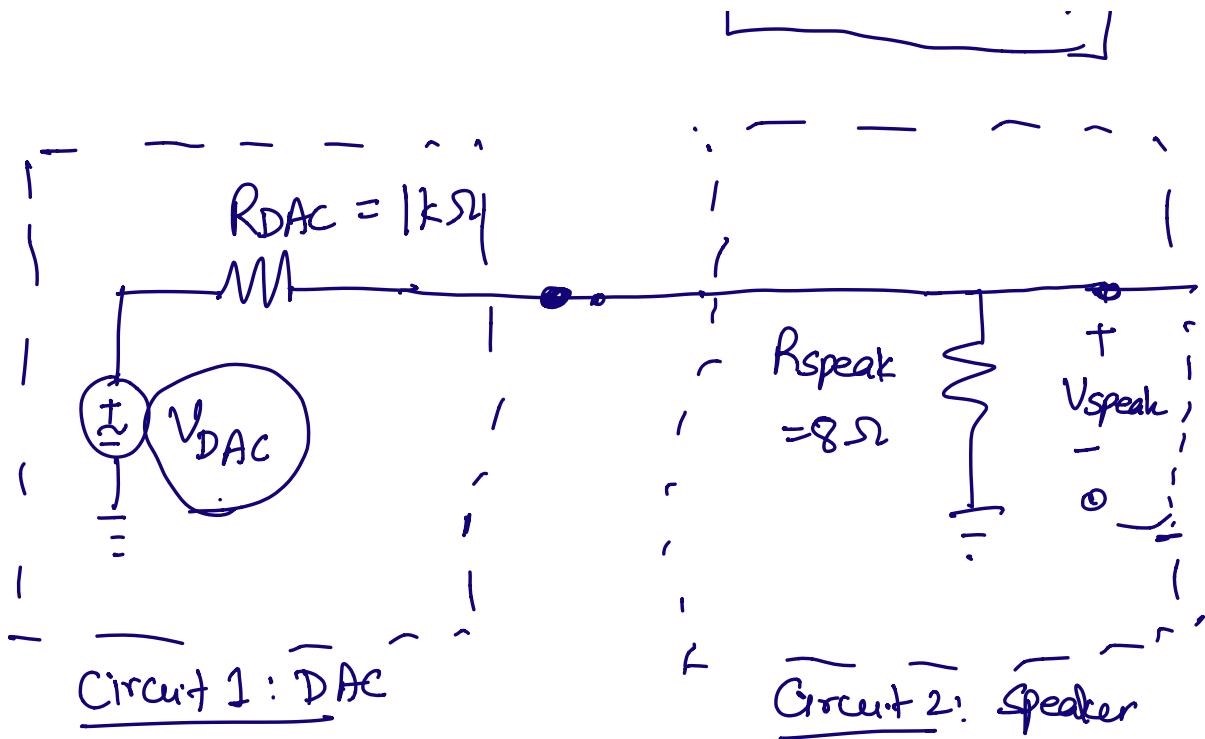

$$V_{speaker} = \frac{R_{speaker}}{R_{speaker} + R_{DAC}} \cdot V_{DAC}$$


$$= \frac{8\Omega}{8 + 1000\Omega} \cdot V_{DAC}$$

$$= \frac{8}{1008} \cdot V_{DAC}$$

$$V_{speaker} = \frac{1}{126} V_{DAC}$$

"Loading effect"

Op-Amps + Negative feedback

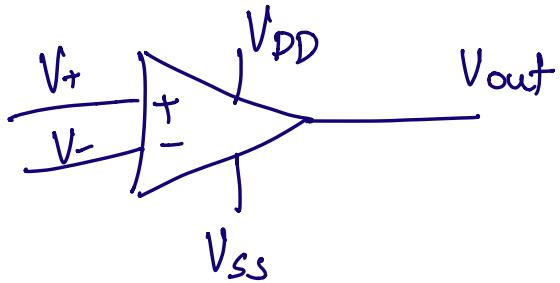


$$\begin{aligned}
 V_{\text{out}} &= V_{\text{ss}} + \underbrace{\frac{V_{\text{DD}} - V_{\text{ss}}}{2}}_{2} + A(V_+ - V_-) \\
 &= \underbrace{\frac{V_{\text{DD}} + V_{\text{ss}}}{2}}_{2} + A(V_+ - V_-)
 \end{aligned}$$

If $V_{\text{DD}} = -V_{\text{ss}}$ = 0

then, $V_{\text{out}} = A(V_+ - V_-)$

Negative feedback:

$$x \xrightarrow{A} Ax$$

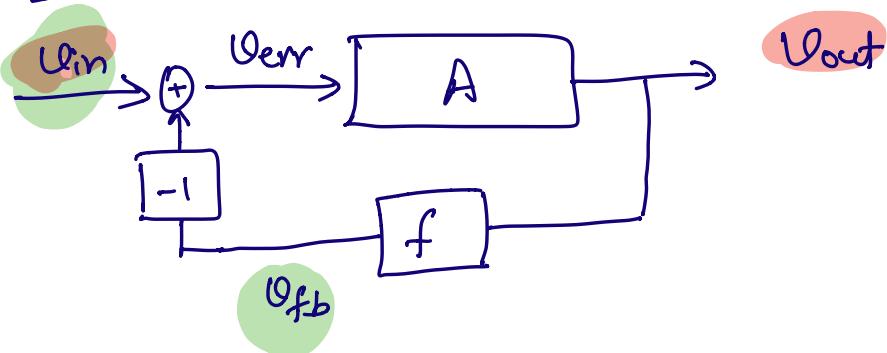

$$V_{in} - V_{fb} = V_{err} \quad ①$$

$$V_{out} = A \cdot V_{err} \quad ②$$

$$V_{fb} = f \cdot V_{out} \quad ③$$

$$V_{out} = A \cdot V_{err}$$

$$V_{out} = A(V_{in} - f \cdot V_{out}) \quad \text{using } ①, ③$$

$$V_{out} + Af \cdot V_{out} = A V_{in}$$

$$(1 + Af) V_{out} = A \cdot V_{in}$$

$$\Rightarrow V_{out} = \frac{A}{1 + Af} \cdot V_{in}$$

$A \rightarrow \infty$ very large gain

$$V_{out} = \frac{1}{\frac{1}{A} + f} \cdot V_{in}$$

$\frac{1}{A} \rightarrow 0$
as $A \rightarrow \infty$

$$A \rightarrow \infty, \quad V_{out} = \frac{1}{f} \cdot V_{in}$$

U_{in}, U_{fb}

$$U_{in} = f \cdot U_{out}$$

$$U_{fb} = f \cdot U_{out}$$


As $A \rightarrow \infty$, in negative feedback

$$U_{fb} = U_{in}$$

"Golden Rules of Op Amps"

Op-Amp in Negative feedback.

$$V_{DD} = -V_{SS}$$

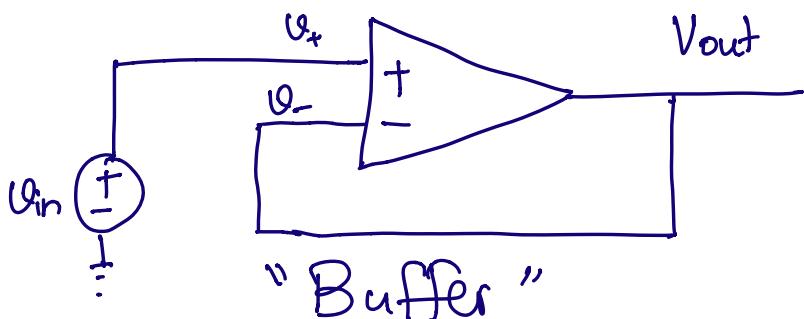


$$V_{out} = A(V_+ - V_-)$$

$\underbrace{V_+ - V_-}_{V_{err}}$

How to check if op-amp is in negative feedback?

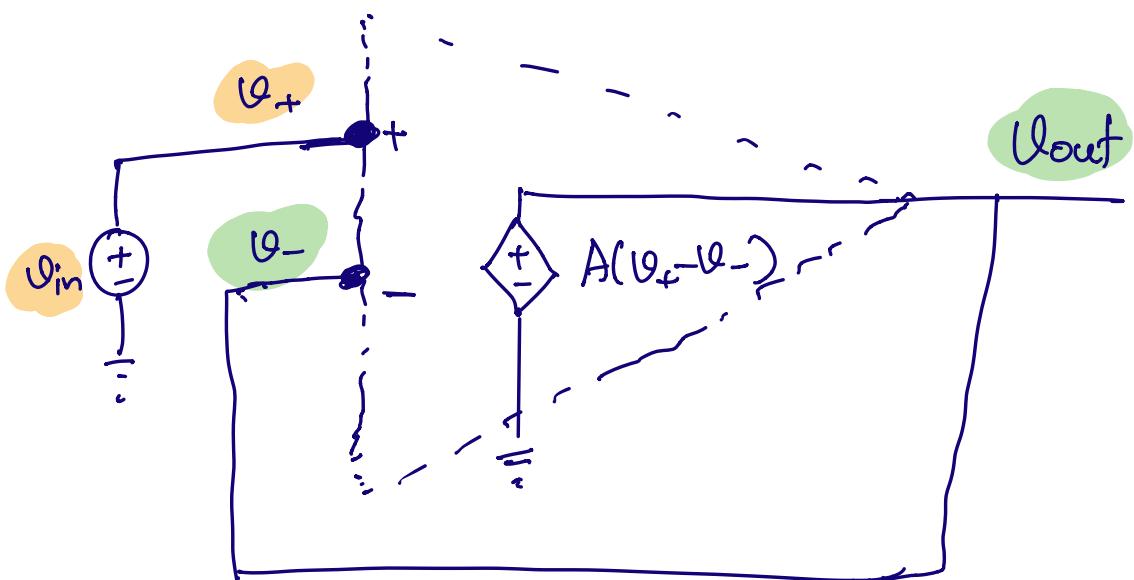- If V_{out} goes \uparrow and your input goes \downarrow then $(V_+ - V_-)$ decreases \downarrow then you are in negative feedback.



$$V_- = V_{out} \quad ; \quad V_{out} = A(V_+ - V_-)$$

$$V_+ = V_{in}$$

$$V_{out} = A(V_+ - V_{out})$$


$$\Rightarrow V_{out}(1+A) = A \cdot V_+ = A \cdot V_{in}$$

$$V_{out} = \frac{A}{1+A} \cdot V_{in}$$

$A \rightarrow \infty \text{ large}$

$V_{out} = V_{in}$

Golden-Rules of Op-Amps

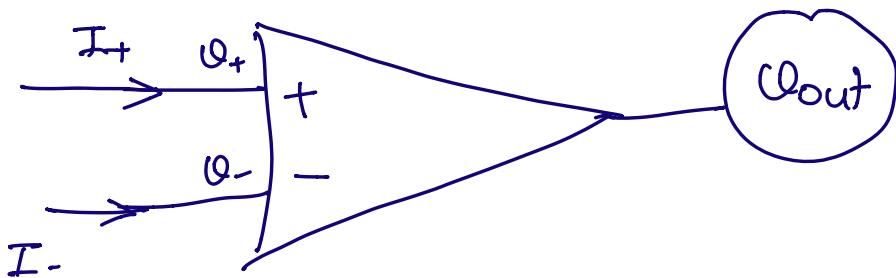

① $I_+ = 0, I_- = 0$

② Only if you are in negative feedback

$$V_+ = V_-$$

"Input to the op-amp":

$$\boxed{V_+ - V_-}$$

$$V_{out} = A(V_+ - V_-)$$


Negative feedback:

If V_{out} goes ↑.

then $(V_+ - V_-)$ goes down.

$$V_{out} = A(V_+ - V_-).$$

⇒ V_{out} goes ↓

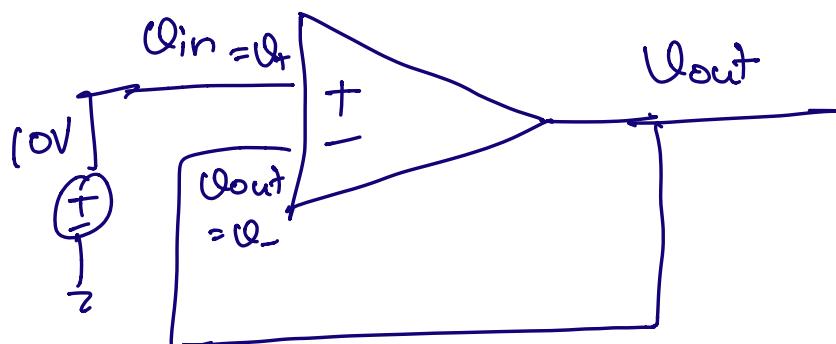

$$V_{out} \rightarrow 2V_{out}$$

$$V_{in} = V_+ = 10V$$

$$V_{out} = V_-$$

$$V_{out} = A(V_+ - V_-)$$

V_{out} doubles


$$\Rightarrow \text{need to be } \frac{(10V - V_{out})}{1}$$

does $(V_+ - V_-)$ decrease?

$$(V_+ - V_-) = \underline{\underline{(10V - 2V_{out})}}$$

$$V_{out} = A(V_+ - V_-)$$

decreased

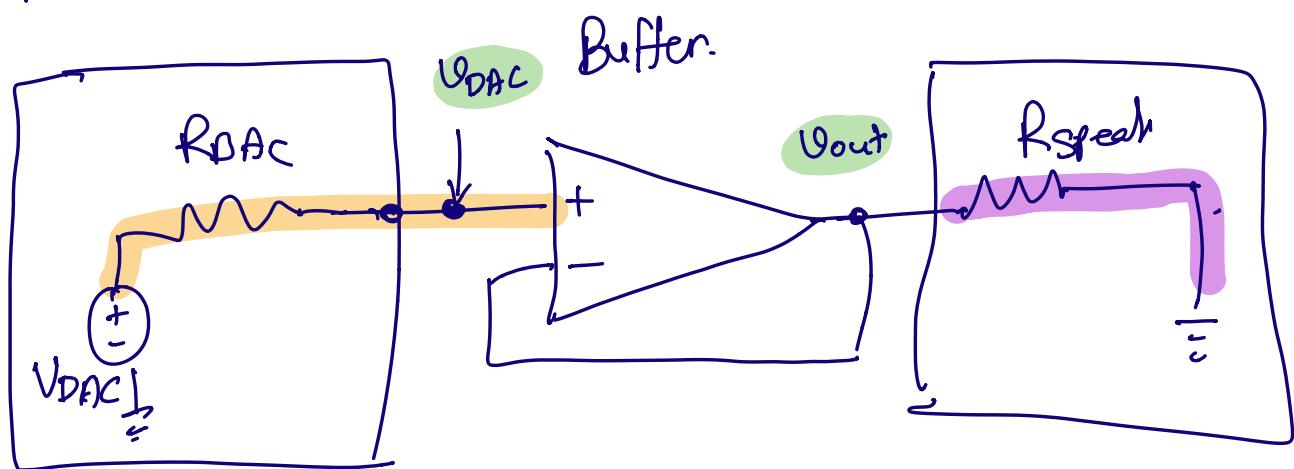


$$V_{out} = V_{DAC} !$$

"Design using Op-Amps"

Buffers are a way to have a feedback gain = 1.

What if I want to multiply by 1000?

Non-inverting op-amp

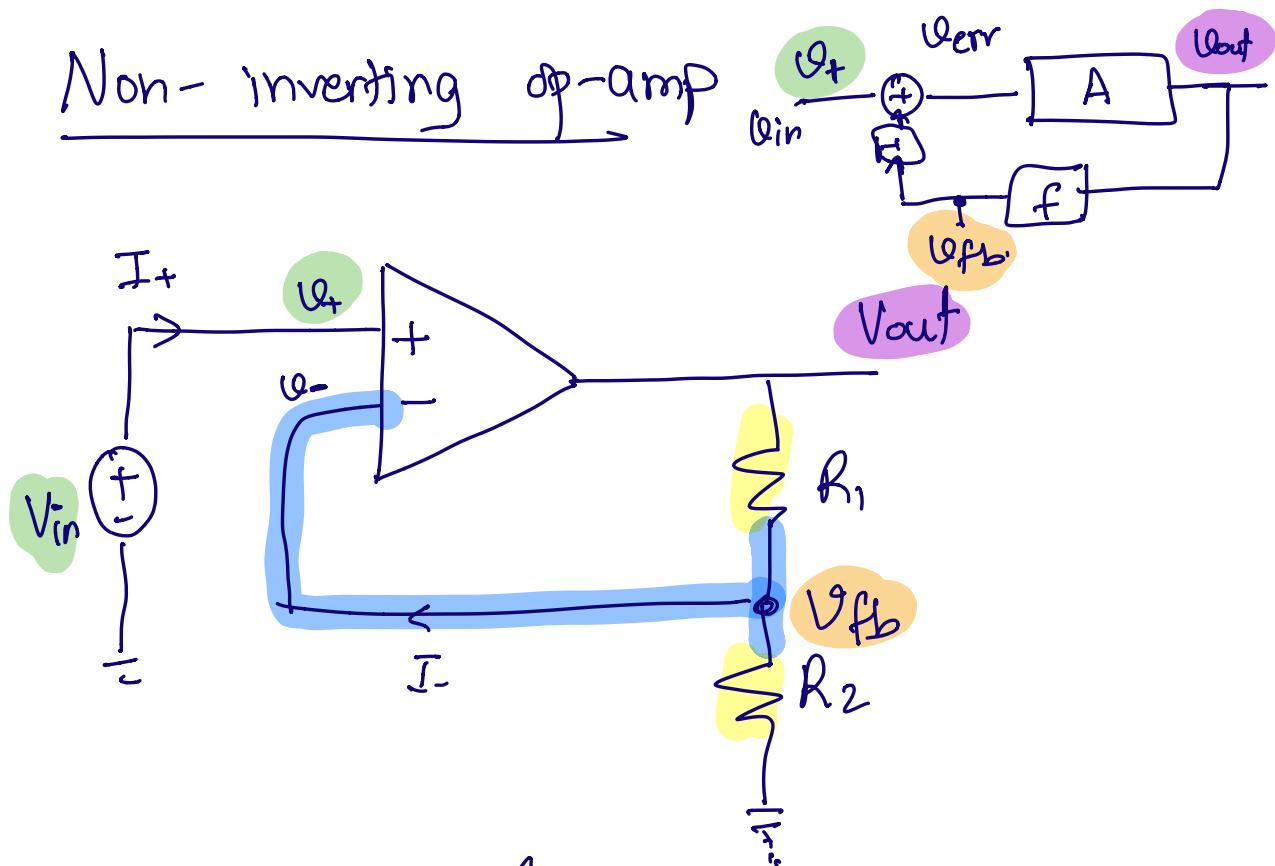

$$V_{fb} = V_{out} \cdot \left(\frac{R_2}{R_1 + R_2} \right)$$

$$U_- = U_{fb}$$

$$U_{out} = A (U_+ - U_-)$$

$$U_{out} = A \left(U_{in} - \frac{R_2}{R_1 + R_2} \cdot U_{out} \right)$$

$$U_{out} + A \cdot \frac{R_2}{R_1 + R_2} \cdot U_{out} = A U_{in}$$

$$U_{out} = \frac{A}{1 + A \frac{R_2}{R_1 + R_2}} \cdot U_{in}$$

$$\frac{R_2}{R_1 + R_2} = f$$

$$A \rightarrow \infty$$

$$U_{out} = \frac{1}{f} \cdot U_{in}$$

$$V_{out} = \frac{\frac{1}{R_L}}{\frac{R_1+R_2}{R_2}} V_{in}$$

$$V_{out} = \frac{R_1 + R_2}{R_2} \cdot V_{in}$$

"Non-inverting amplifier"