


## EECS 16A - Module 2

Today:   
 \* Quick Review   
 \* Inverting Amplifier   
 \* Cascading Ckt Blocks   
 \* Design Example

### Logistics

- OH right after lecture (Panoc) - same link as Prof. Ranade
- No extension for M+2 Rebo


## Review: Op-Amp Golden Rules

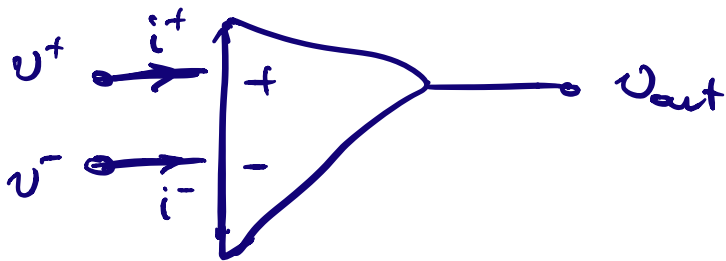

GR #1:  $i^+ = i^- = 0$  Always


GR #2:  $v^+ = v^-$  For an Op-Amp in **Negative Feedback** and with **infinite gain A**

## Non-Inverting Amplifier

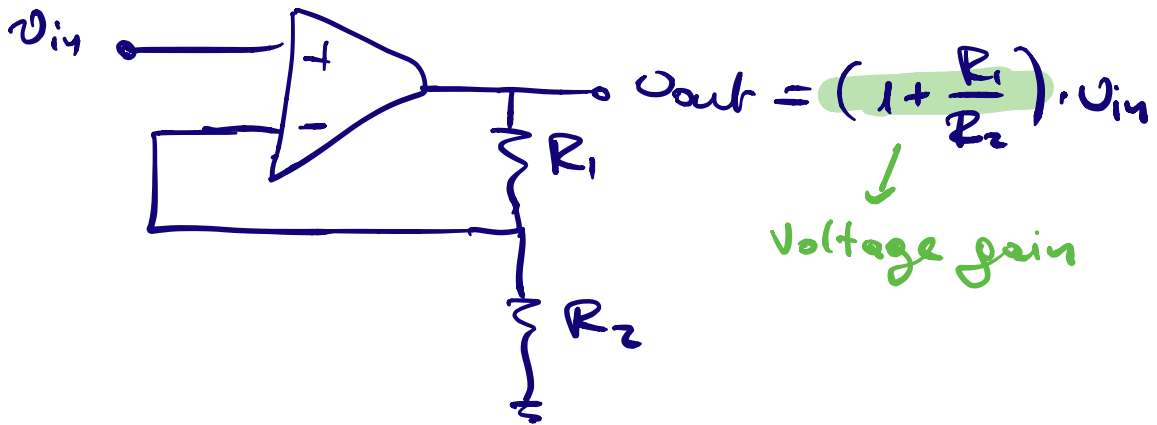


Non-inverting because the voltage gain is always  $> 0$

## Inverting Amplifier

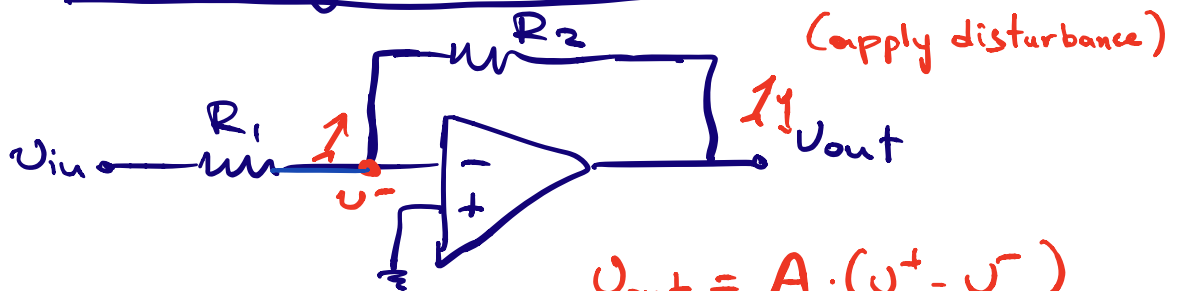

if  $V_{out} \uparrow \Rightarrow V^- \uparrow \Rightarrow V_{out} \downarrow$   
Established Negative Feedback!

Let's analyze this circuit:

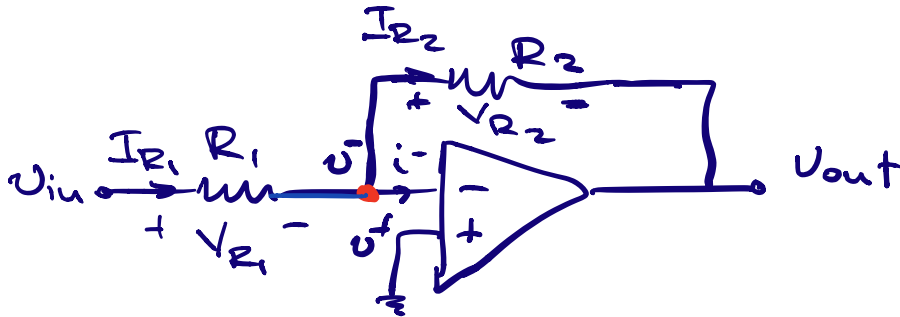

KCL on  $u^-$ :  $I_{R_1} = I_{R_2} + i^-$  (GR #1)

Ohm's law  $\Rightarrow \frac{V_{R_1}}{R_1} = \frac{V_{R_2}}{R_2}$

$\Rightarrow \frac{u_{in} - u^-}{R_1} = \frac{u^- - u_{out}}{R_2}$  (1)

GR #2:  $u^- = u^+ = 0$  (2)

(1)  $\stackrel{(2)}{\Rightarrow} \frac{u_{in}}{R_1} = - \frac{u_{out}}{R_2}$

$\Rightarrow u_{out} = - \frac{R_2}{R_1} u_{in}$

$\Delta$  Voltage gain



Why negative coefficients?

$$V_{out} = a V_{in_1} + b V_{in_2} + c V_{in_3} + \dots$$

↓  
want  $b < 0$

Inversion is a very useful operation in general (for signal processing, sensing, matrix-matrix mult)


## Cascading Circuit Blocks

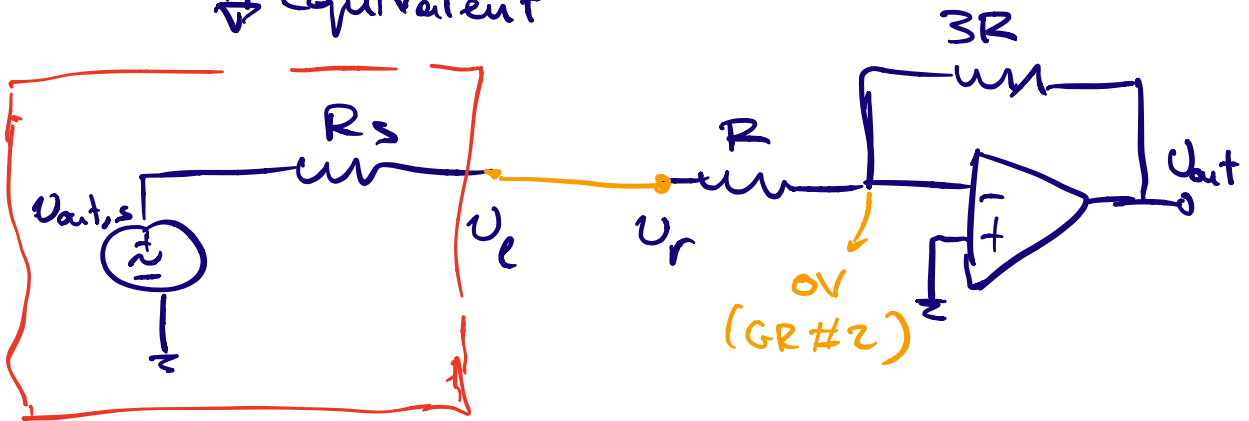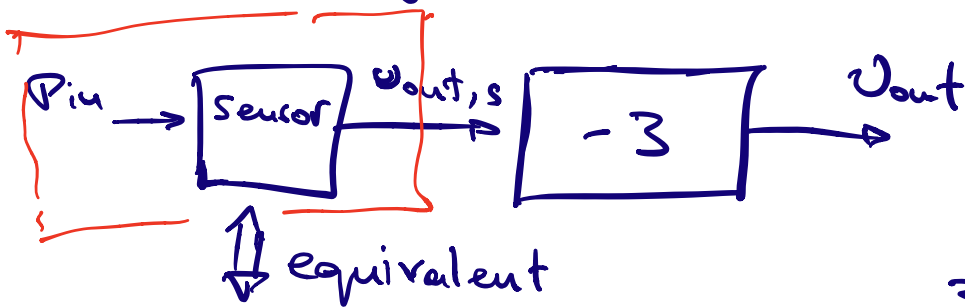

Before connection:  $V_e = V_{out,s}$  ✓

$$\text{After connection: } V_e = V_r = \frac{R}{R + R_s} V_{out,s}$$
$$\neq V_{out,s} \checkmark$$

Solution: Add a buffer!

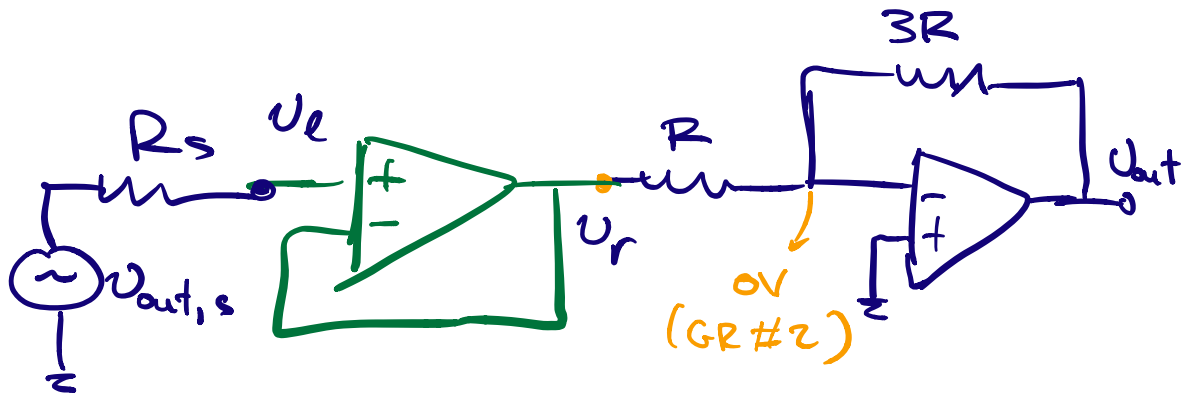


(GR #2)

$$V_r = V_- = V_+ = V_e = V_{out,s} \quad \checkmark$$

Takeaway: Safe way to connect  
ckt blocks is by  
adding buffers in-between

# DESIGN EXAMPLE

## Countdown Timer Circuit

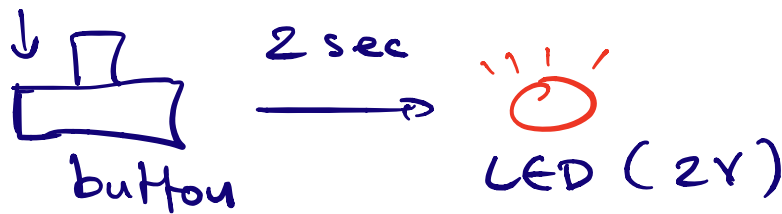


### Step 1 : (Specification)

Build a circuit that after a button is pushed measures 2s and then applies 2V on an LED.


Assumption: You can only press the button once.

### Step 2 : (Strategy)

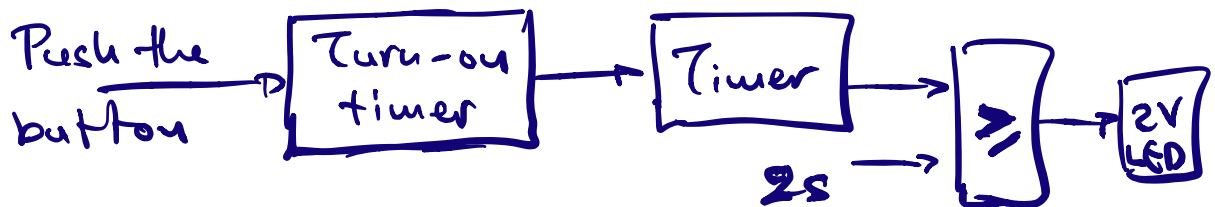


### Step 3 : (Implementation)


Turn-on ckt :  (switch)

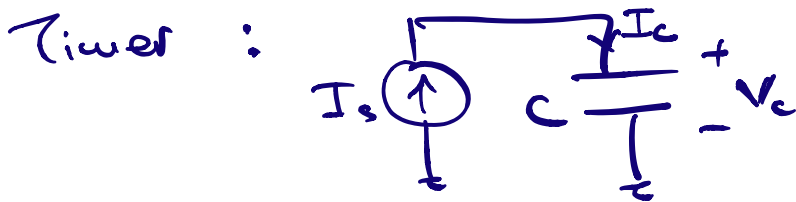
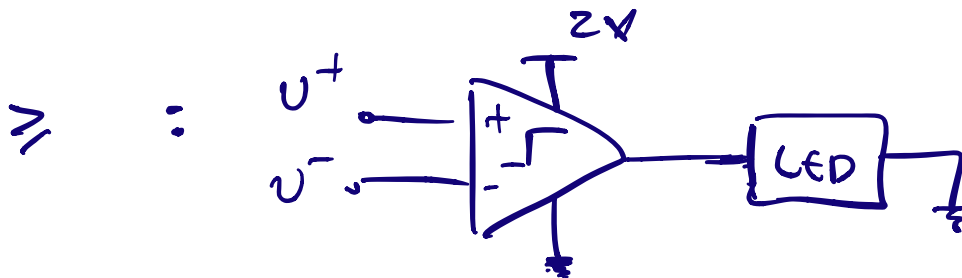
$$I_c = C \cdot \frac{dV_c}{dt} \Rightarrow V_c(t) = \frac{I_s}{C} t + V_c(0)$$



Putting it all together:

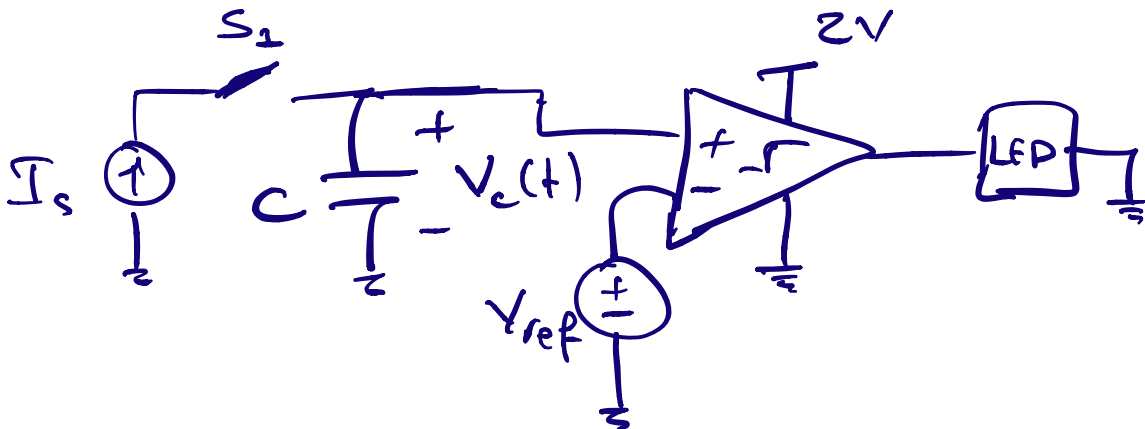

Set  $V_{ref} = V_c(z)$


Step 4: (Verify)

$$V_c(t) = \frac{I_s}{C} t + \underline{V_c(0)}$$

Prob. #1

↳ ? unknown!

Before button pushed:

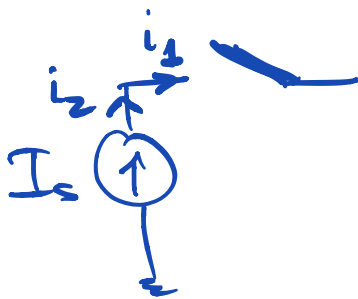

$$\text{KCL: } \begin{cases} i_1 = i_2 \\ i_1 = 0 \text{ (open-ckt definition)} \\ i_2 = I_s \neq 0 \end{cases}$$


$I_s = 0$ : contradiction  
inconsistency

Prob. #2

Solution: Connect the switch  
to ground.




## Revisit Step 3:

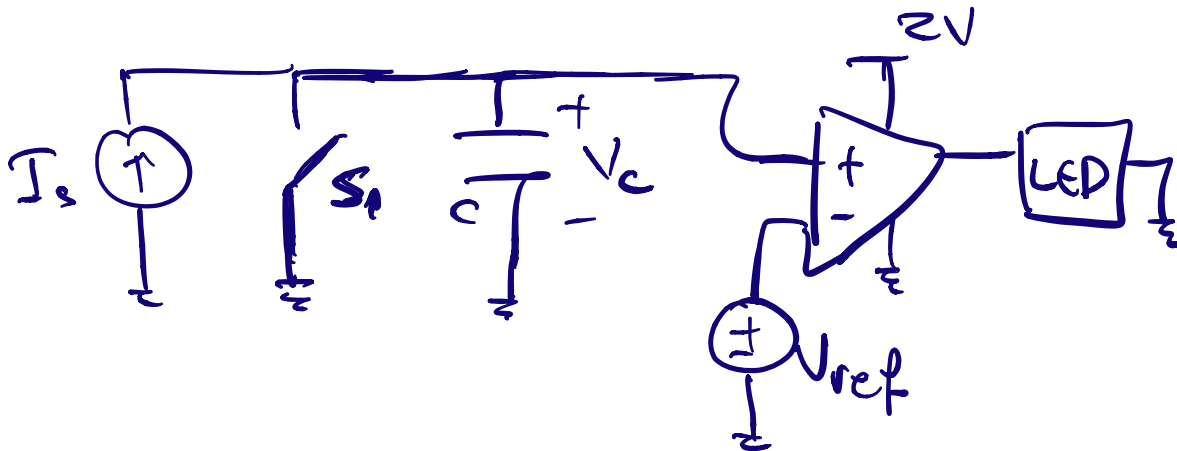

NOTE: Now the switch is CLOSED BEFORE the button is pushed and OPEN after it is pushed

Before the button is pushed:

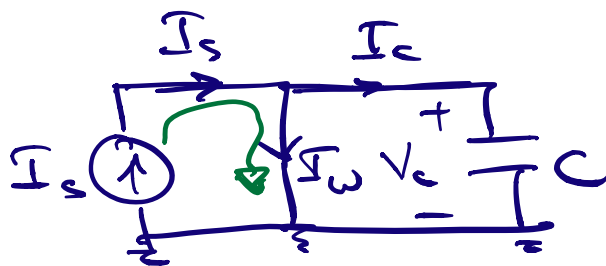

$$V_c = 0 = \text{constant}$$


$$I_c = C \cdot \frac{dV_c}{dt} \rightarrow 0$$

KCL:

$$I_s = I_w + I_c, \text{ but } I_c = 0$$

$$\Rightarrow I_w = I_s \text{ (path of least resistance)}$$

After the button is pushed

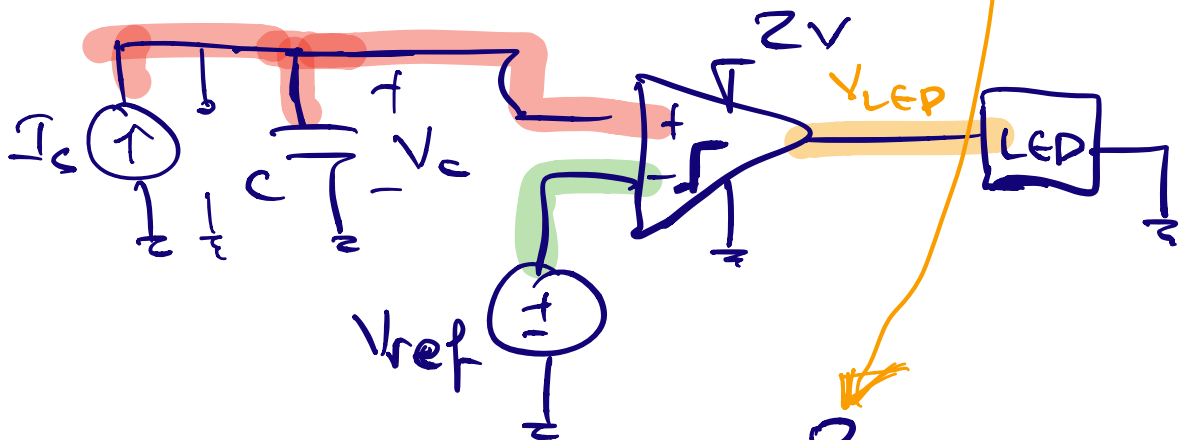

$$V_c(t) = \frac{I_s}{C} t + V_c(0)$$

$$V_{ref} = V_c(2) = \frac{I_s}{C} \cdot 2$$

