

EECS 16A


Module 2 Lecture 1

Introduction to Circuit Analysis

Module 1: How to model


- Tomography.
- Page Rank
- Imaging.
- Traffic example.
- Communications
- Speech processing.
- Segway / Control / Robotics.

Module 2: Get into one model:

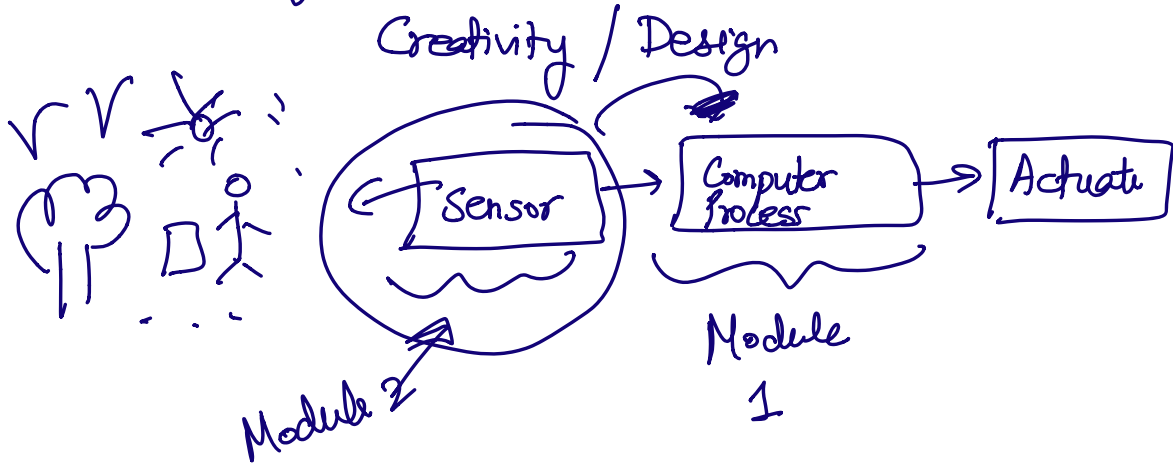

This module : Circuit Analysis

Notation / Conventions

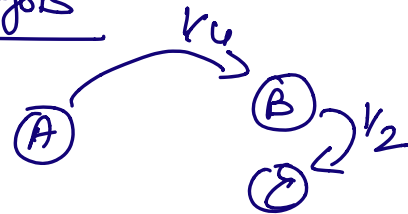

Logistics

- ① Google docs test.
- ② Office hours.
- ③ Review tonight.
- ④ HW 5 solutions released
- ⑤ Intro to research
↳ Tue after midterm.
Oct 6th, 5-6 pm.

Electrical Quantities

		Units	Symbol
①	Voltage "Across"	Volts (V)	V
②	Current	Amperes (A)	I
③	Resistance	Ohm (Ω)	R

Circuit Diagrams


Equations : Linear

Circuit Elements

$$V_{el} = V_{element}$$

① Wire

Voltage: across
Current: through.

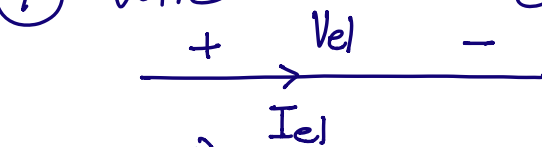




Current (I)

$$V_{el} = 0$$

$$I_{el} = \text{arbitrary}$$



Voltage (V)

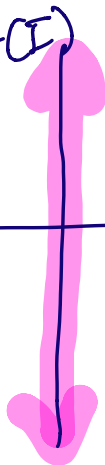

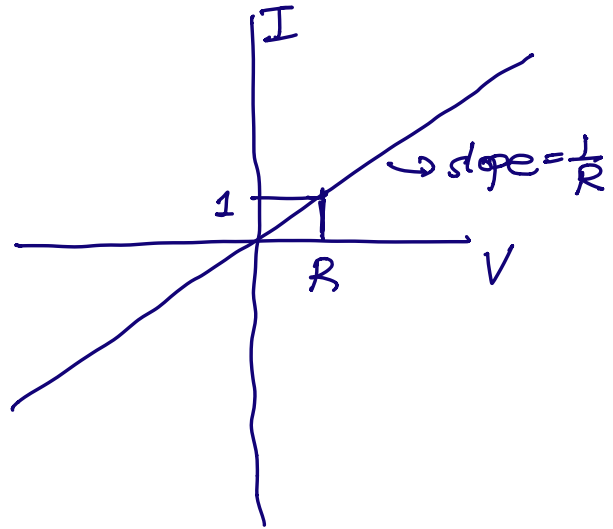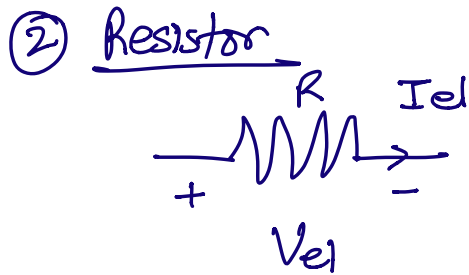

Ohm's Law


$$V_{el} = R \cdot I_{el}$$

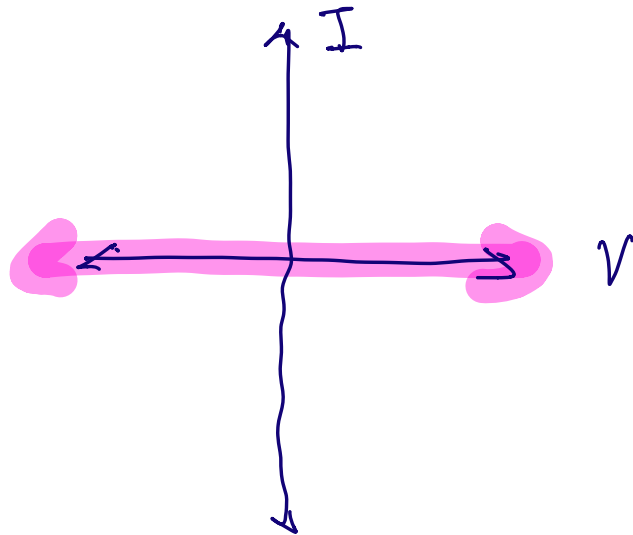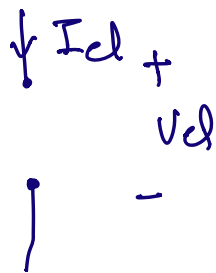


Maintains a potential difference across its terminals

↗ voltage





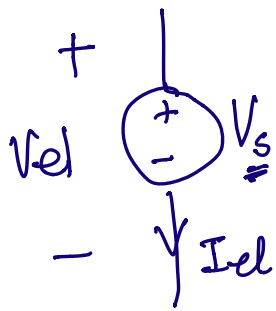

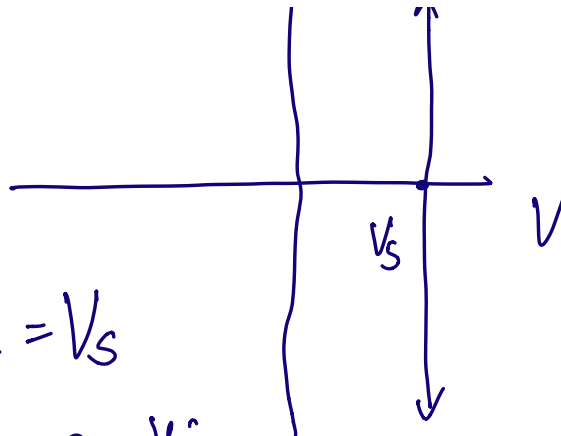$V_{el} = V_s$
 $I_{el} = \text{anything}$



⑤ Current Source

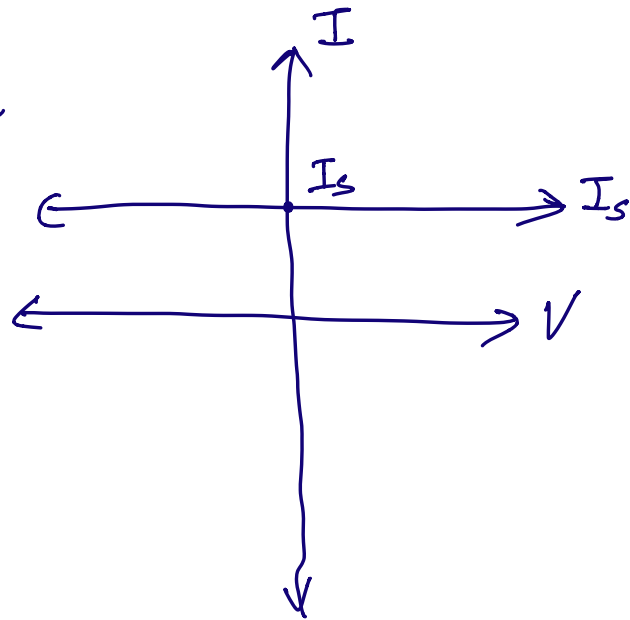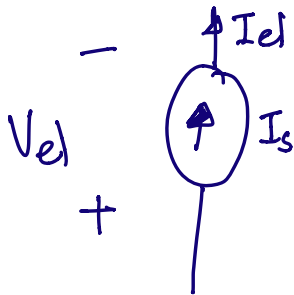

⑥ Ground Node


Mt Rainier: 4000 mts



Define voltage as 0.
 Measure voltage with respect to this point.

How to draw circuits


"Generic" circuit element

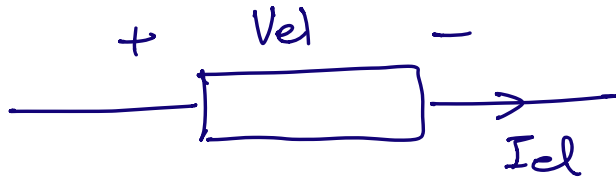

"Passive Sign Convention"

Current goes in to the + sign of the voltage and out of the negative sign.

Nodes, Branches

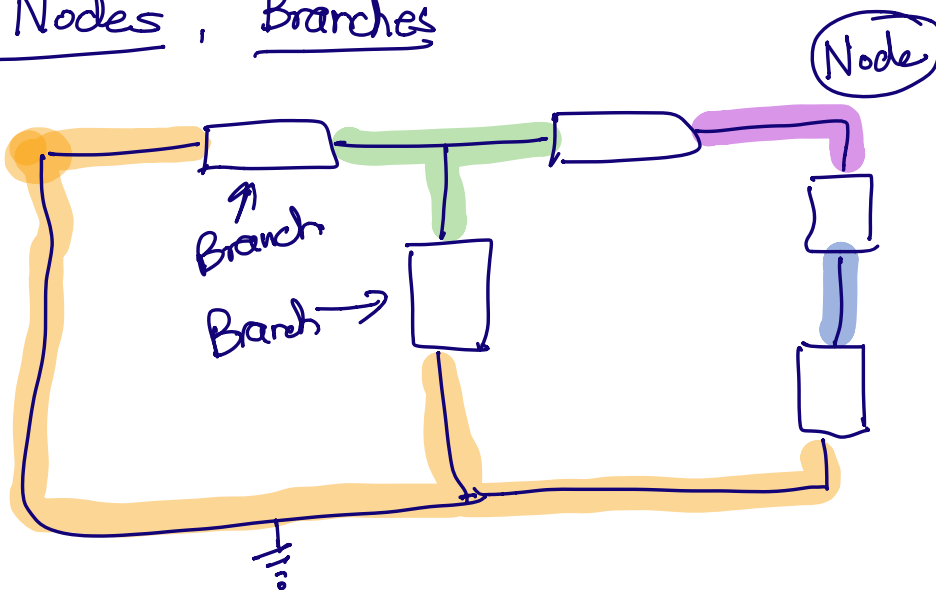


Branches: connections between nodes.

• The unreasonable effectiveness of mathematics.

• Kirchhoff's Laws

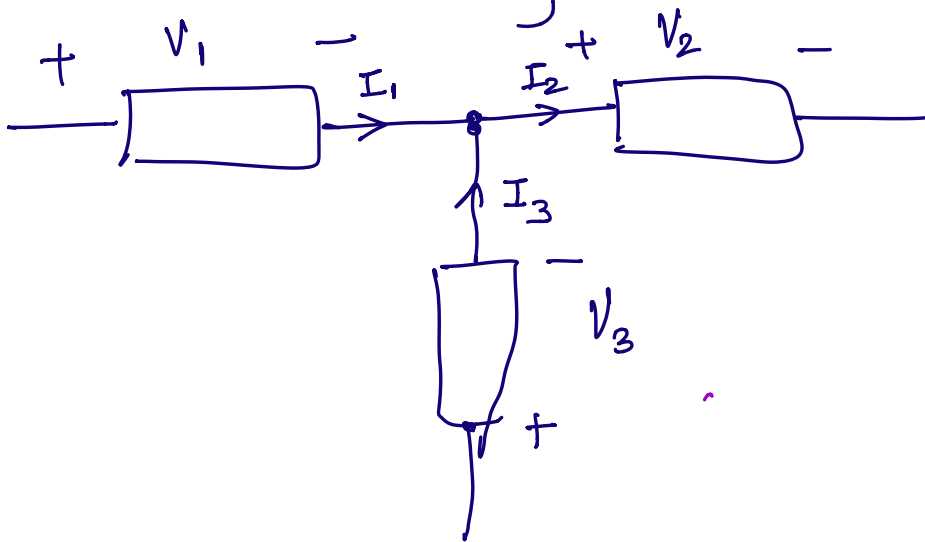
• KCL : The sum of all currents entering a node equals the sum of all currents exiting a node.



$$I_1 + I_3 = I_2$$

$$I_1 + I_3 - I_2 = 0$$

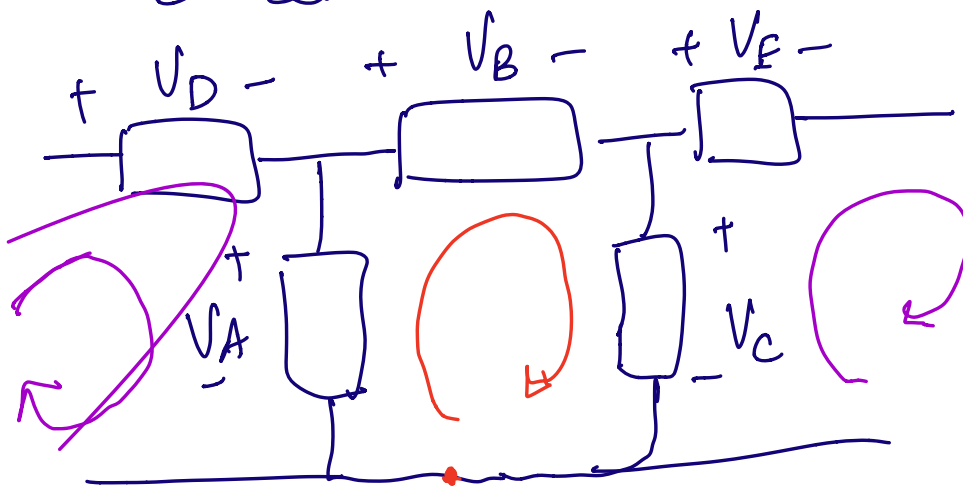KVL : The sum of the voltages across the elements of a connected loop must be zero



$$-V_A + V_B + V_C = 0$$

6.02) Quantitative Physiology
