
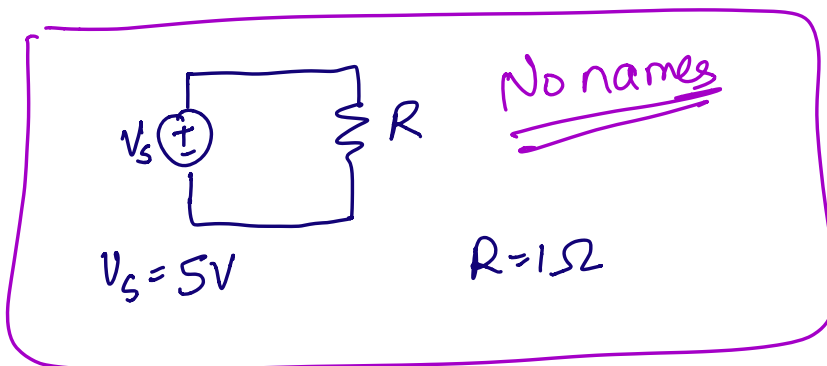


EECS 16A Module 2, Lecture 2

- Logistics :
- Introduction to Research (Today) 5pm.
 - Trivia Game Night (Saturday) 7pm
 - ~~Sheet~~ HW 6 tonight
 - Midterm redo - due Monday.

Module 2: ① Node Voltage Analysis

Analyse / Solve a circuit:

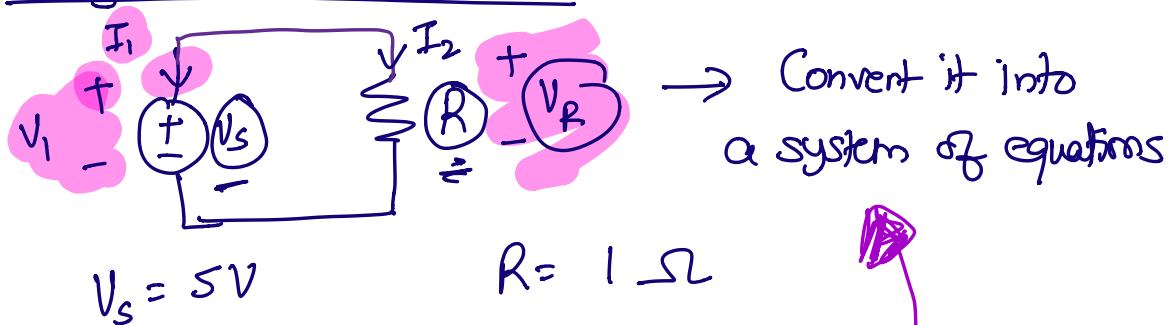

Two main parts of analysing a circuit

- ① Picture → System of linear equations.
- Giving labels

② KVL, KCL, Ohm's Law

③ Solve. ✓

Node Voltage Analysis Example

V_s, R_1, R_2 are known.

Challenge: No labels.

Solve: Systematic labeling.

① Select your reference



② What are the nodes?

Which node voltages do we know?

Label node voltages that you know


③ Mark the unknown nodes.

← Label unknown voltages.

④ Mark element currents

• Passive sign convention to mark element voltages.


→ voltage source. — (⊕)

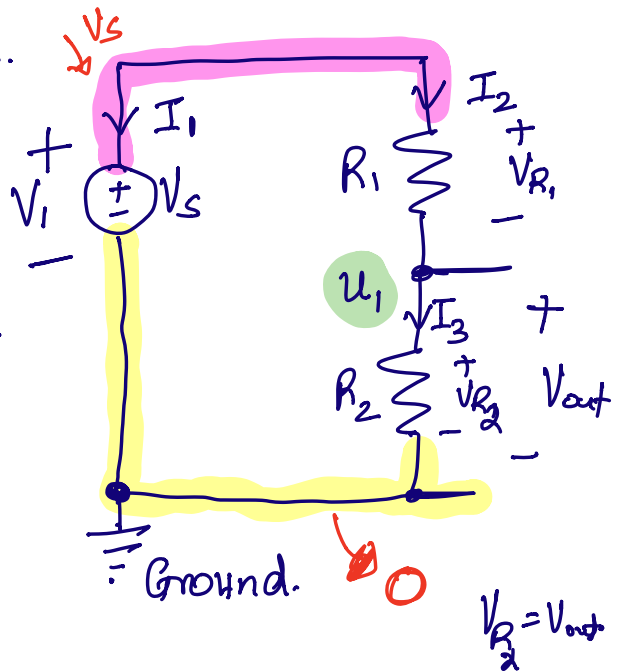

⑤ Write out the KCL equations for all nodes with an unknown voltage.

$$I_2 = I_3$$


$$I_2 - I_3 = 0$$

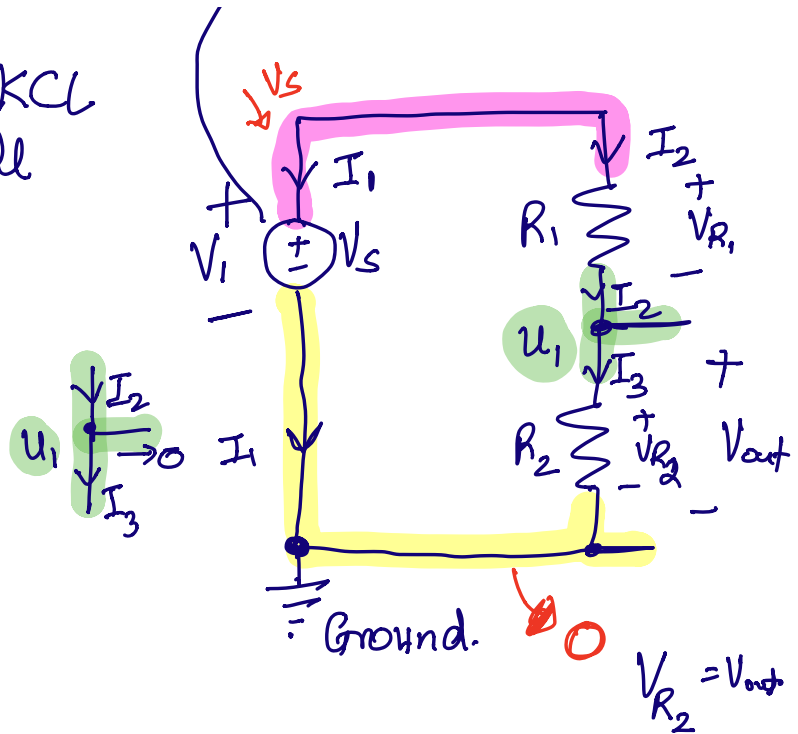

⑥ Use Ohm's law (other component eqⁿ) to express currents in terms of voltages.

$$V_{R_1} = I_2 \cdot R_1 \Rightarrow I_2 = \frac{V_{R_1}}{R_1}$$


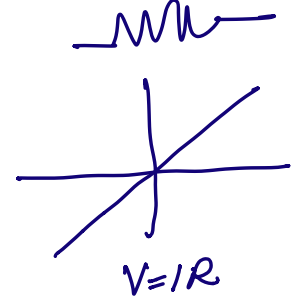
$$V_{R_2} = I_3 \cdot R_2 \Rightarrow I_3 = \frac{V_{R_2}}{R_2}$$



⑦ Replace element voltages with node voltages V_{R_1}, V_{R_2} with known things and u_1

$$V_{R_1} = V_s - u_1$$

$$V_{R_2} = u_1 - 0$$

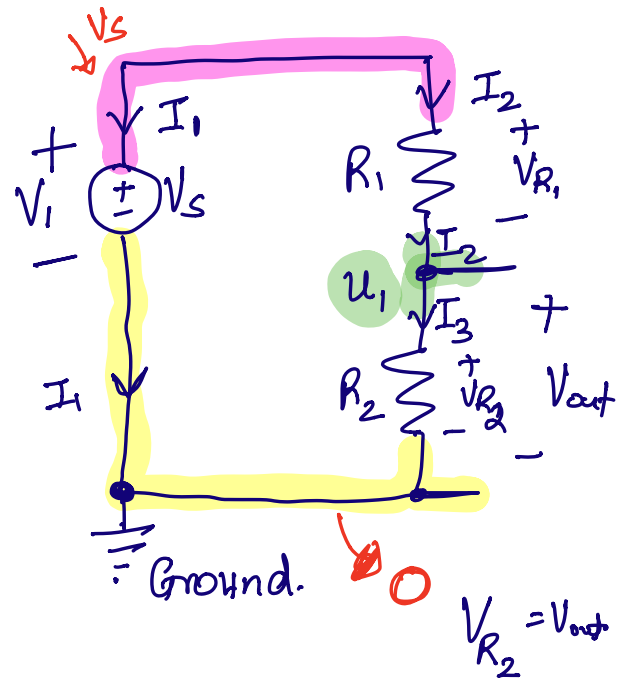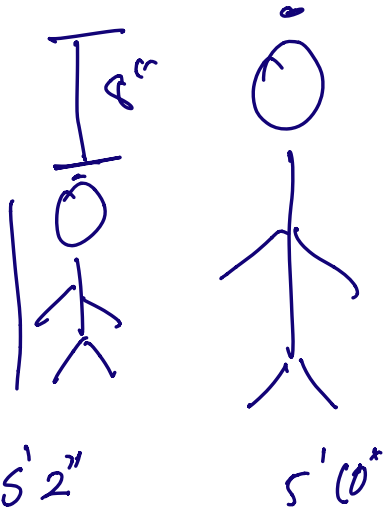

$$\left(\begin{aligned} I_2 &= \frac{V_{R_1}}{R_1} = \frac{V_S - u_1}{R_1} \\ I_3 &= \frac{V_{R_2}}{R_2} = \frac{u_1 - 0}{R_2} = \frac{u_1}{R_2} \end{aligned} \right.$$

⑧ Substitute into KCL ⑤



$$\frac{V_S - u_1}{R_1} = \frac{u_1}{R_2} \quad \text{Using KCL from step ⑤}$$

$$\frac{V_s}{R_1} = U_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = U_1 \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

$$\textcircled{a} \quad U_1 = \frac{V_s}{R_1} \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$U_1 = \frac{V_s \cdot R_2}{R_1 + R_2}$$


Voltage
Dividers

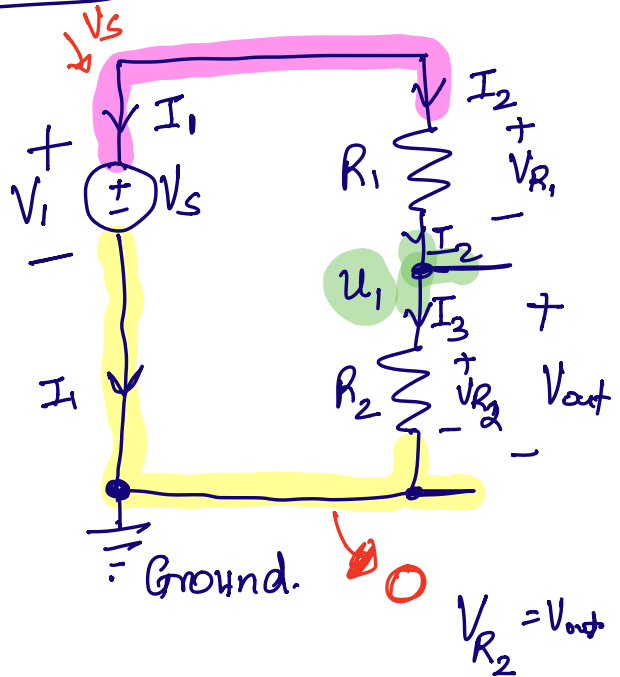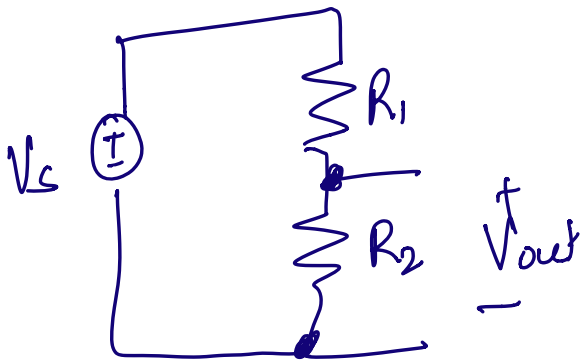

Thinking like an engineer

Say I told you, V_{out} , V_s , $R_1 + R_2$.

$$R_2 = \frac{U_1 (R_1 + R_2)}{V_s}$$

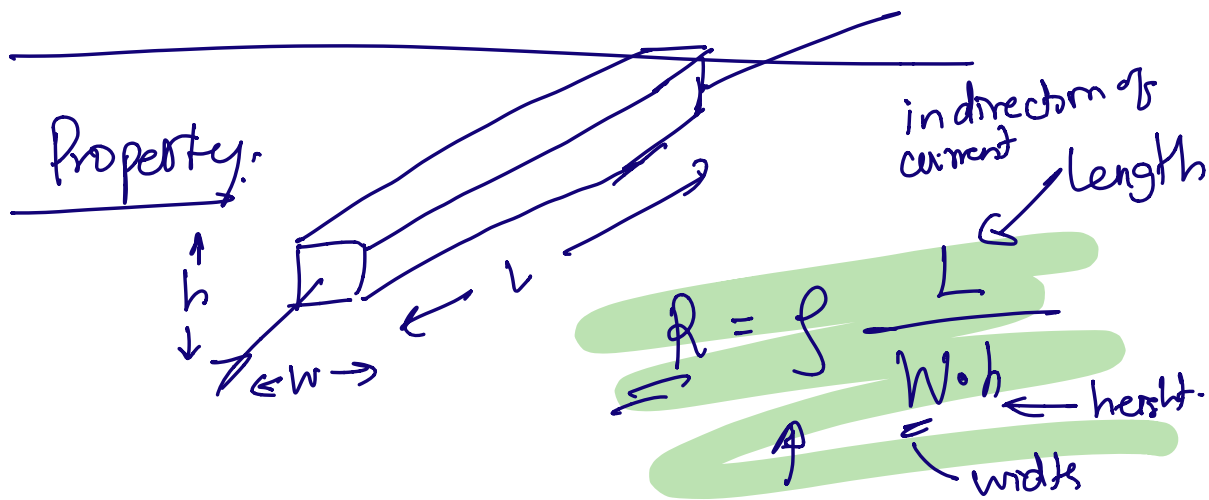

$$R = \rho \frac{L}{w \cdot h}$$

Labels: ρ is resistivity, L is length, $w \cdot h$ is width.

ρ : resistivity

"rho"


Units: $[\Omega m]$

resistivity.

Resistance is resistivity $\times \frac{L}{w \cdot h}$

Resistor length : L .

Break @ length x

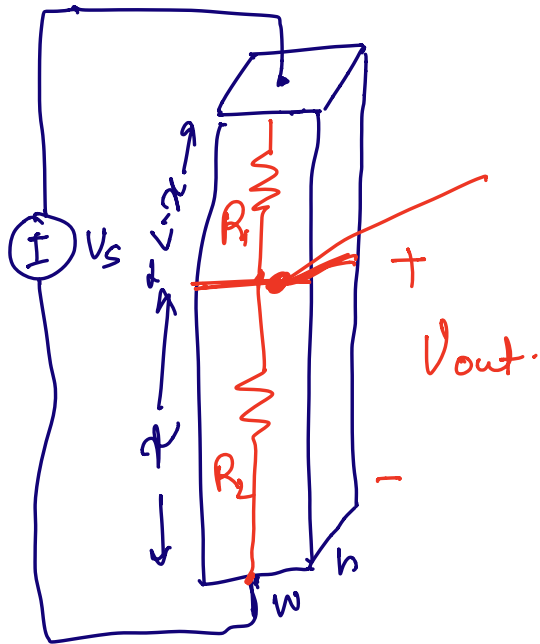

$$V_{out} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

$$R_2 = \rho \cdot \frac{x}{w \cdot h}$$

$$R_1 = \rho \cdot \frac{(L-x)}{w \cdot h}$$

$$V_{out} = V_s \cdot \frac{\rho \cdot x}{w \cdot h}$$

$$\frac{\rho \cdot \frac{L-x}{w \cdot h} + \rho \cdot \frac{x}{w \cdot h}}$$

$$V_{out} = V_s \cdot \frac{x}{L}$$

Solve for x :


$$x = \frac{L \cdot V_{out}}{V_s}$$

x is the distance of the point at which I touch!

1D touchscreen.

① Voltage V_{out} is proportional to the resistance R_2 .

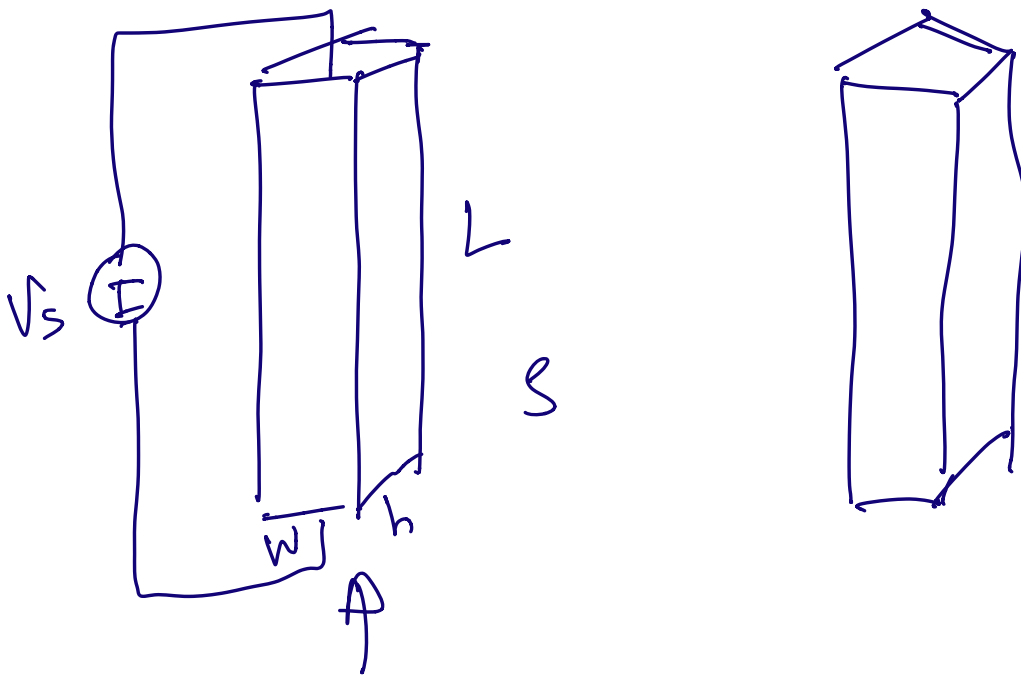
② Resistance R_2 is proportional to the length of the resistor. (x)



Resistance of block?

$$R = \rho \cdot \frac{L}{w \cdot h}$$

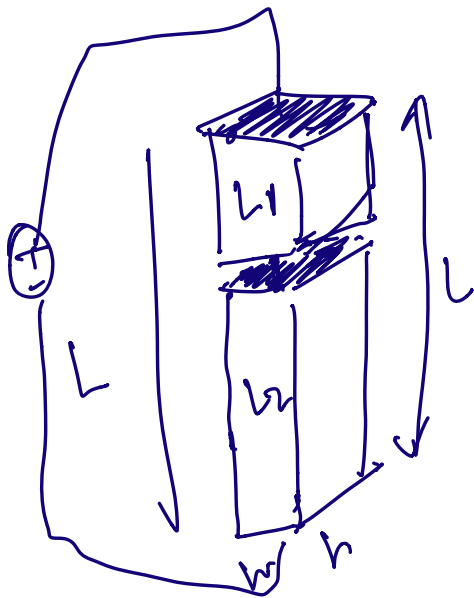Block 1: resistivity ρ
 Block 2: re ... ρ




~~$R = \rho \cdot \frac{L}{w \cdot h}$~~

$$R = \frac{\rho \cdot L}{w \cdot h}$$

$$= R_1 \text{ (top block)}$$

$$= \frac{\rho \cdot L_1}{w \cdot h}$$

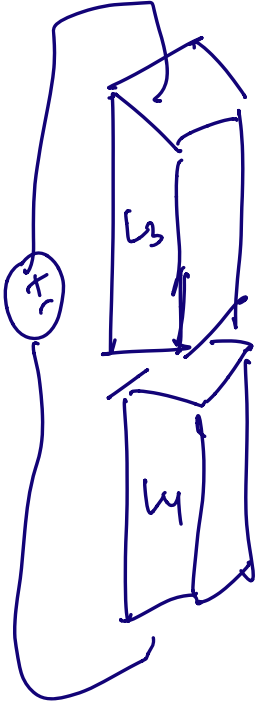

$$B_2 = \frac{P \cdot L_2}{W \cdot h}$$

$$L_3 + L_4 = L$$