

EECS16A Module 2, Lecture 3

Today.


- ID Touchscreen -
- Power

Logistics: ^② Trivia night (Sat)

① Call me maybe

→ Advising. - Help w/
Oct 15th. choosing
• HWG course.

Last time ① Voltage Divider

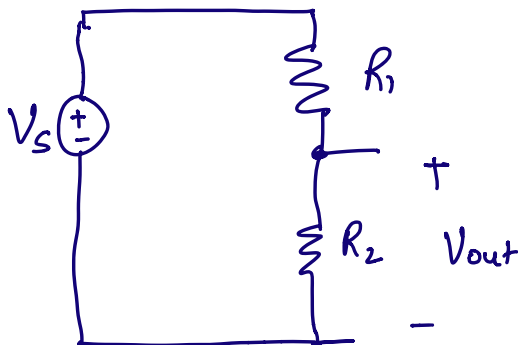

$$V_{out} = \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_s$$

3V, 5V

$$(5V) \times \frac{3}{5} = 3V$$

Node Voltage Analysis

① Labeling all currents, voltages.

② ~~Setting~~ Setting up and solving a system of linear equations

② Resistivity: Property of a material.

(ρ) rho.


Copper: $1.7 \times 10^{-8} \Omega \cdot m$ ←

aluminum: $2.7 \times 10^{-8} \Omega \cdot m$


Silicon: $2.3 \times 10^3 \Omega \cdot m$ ←

(R) Resistance = $\rho \cdot \frac{L}{W \cdot h}$

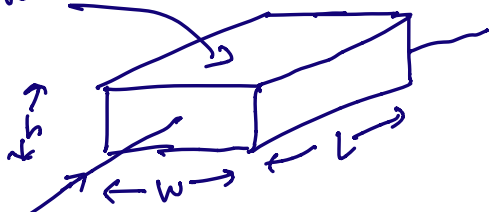ρ resistivity = (resistivity) $\times \frac{\text{Length}}{(\text{Width}) \cdot (\text{Height})}$



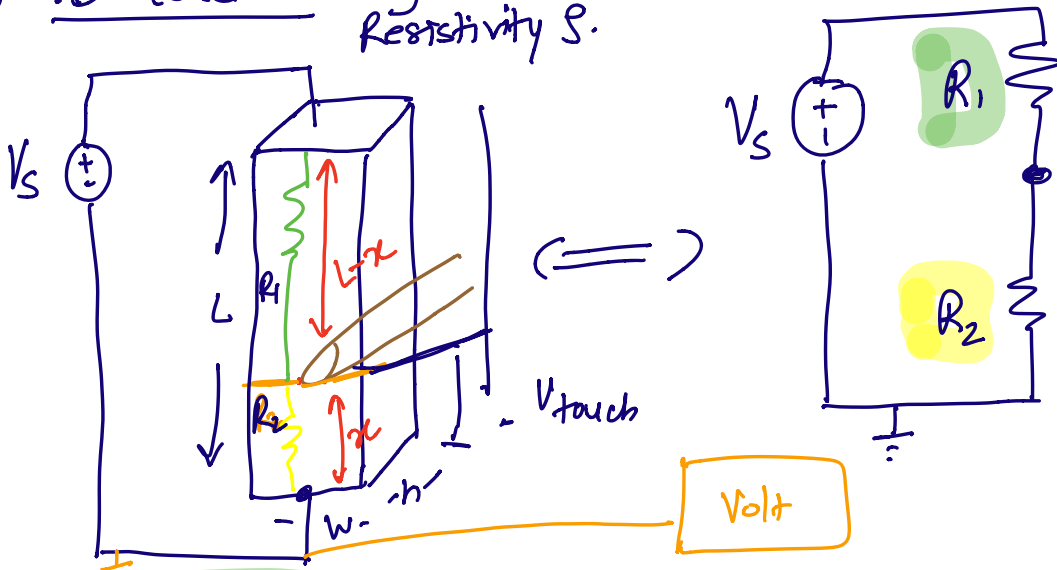③ 1D Touch. Long Resistor Resistivity ρ .




$$R_1 = \frac{\rho(L-x)}{w \cdot h}$$

$$R_2 = \frac{\rho \cdot x}{w \cdot h}$$


$$V_{\text{touch}} = V_s \cdot \left(\frac{R_2}{R_1 + R_2} \right)$$
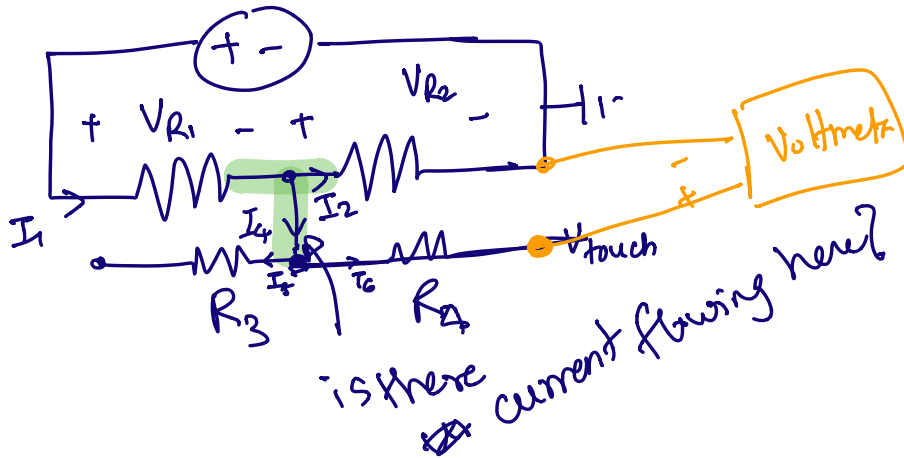
$$x = \frac{V_{\text{touch}} \cdot L}{V_s}$$



"Dangling resistor"


How do we measure voltage?

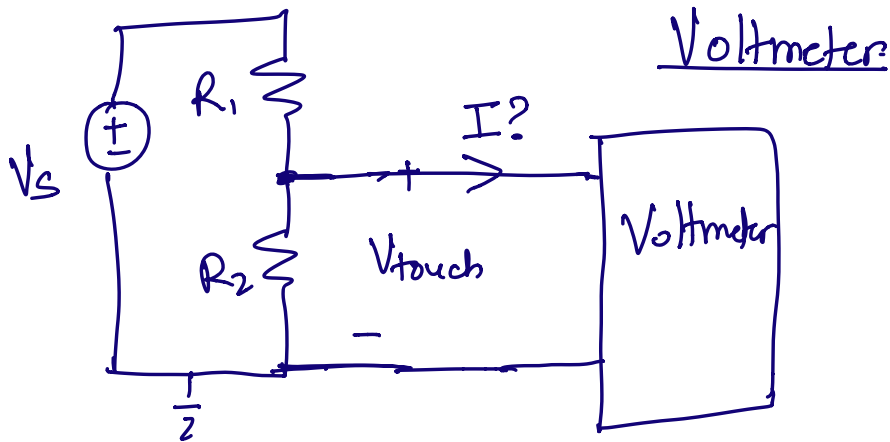

For $I = 0$, you need very high resistance for the voltmeter.
 "Open circuit"

How to measure current?

"Ammeter"

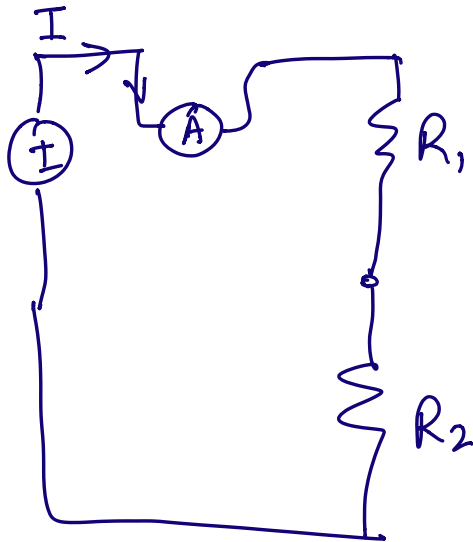

"Short circuit"
 $R = 0$ for the
ammeter

Energy and Power in a circuit

Good measurement: does not draw power.

• Charge : Positive or Negative

Units of Coulomb.

Symbol: Q .

• Current: Amount of charge crossing per unit time.

$$I = \frac{dQ}{dt}$$

- Voltage : Energy required to move a unit charge from point A. to B.

$$V_{AB} = \frac{dE_{AB}}{dq}$$

- Power: Change in energy per unit time

$$P = \frac{dE}{dt} \quad (\text{Energy per time}).$$

Unit: Power : Watts

Energy : Joules.

Light bulb: 10W , 1 hour

$$E = \text{Power} \times \text{time}$$

$$= 10W \times 1 \text{ hour} = 10 \text{ Watt-hours}$$

$$= 10 \text{ W} \times 3600 \text{ seconds}$$

$$= 36,000 \text{ Ws (Joule)}$$

$$= 36 \text{ kilojoules}$$

How do we think about power in circuits?

$$V = \frac{dE}{dq}$$


energy / charge

$$I = \frac{dq}{dt}$$

charge / time.

$$\begin{aligned} \text{Power (P)} &= \text{Energy per time} = \frac{dE}{dt} \\ &= \frac{dE}{dq} \cdot \frac{dq}{dt} = V \cdot I \end{aligned}$$


Passive sign convention

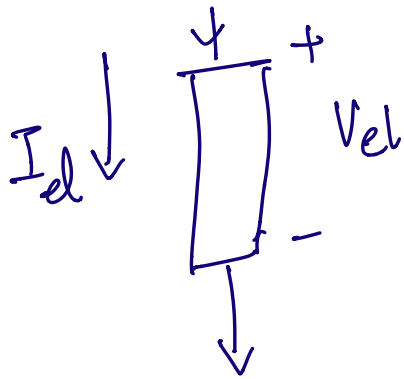

Power dissipated by the element:

$$P_{el} = V_{el} \cdot I_{el}$$

Example:

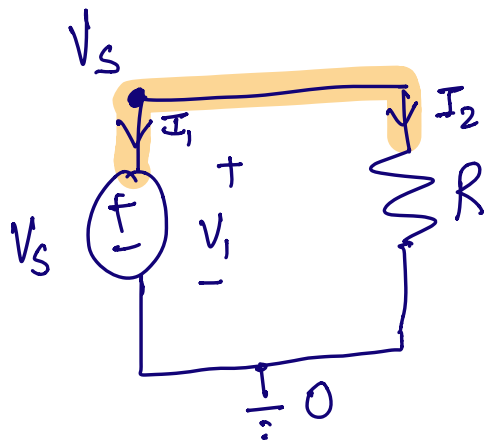

$$+ V_R$$
$$-$$

$$V_S = 5V$$

$$R = 1\Omega$$

$$V_1 = V_R = V_S$$

$$V_R = I_2 \cdot R$$

$$I_2 ?$$

$$I_2 = \frac{V_R}{R} = \frac{V_S}{R}$$

$$\begin{aligned} \text{Power dissipated by } R &= V_R \cdot I_2 = V_S \cdot \frac{V_S}{R} \\ (R) &= V_S^2 / R \end{aligned}$$

$$\begin{aligned} \underline{\text{KCL:}} \quad I_1 + I_2 &= 0 & = \frac{25 \text{ (V)(V)}}{1 \Omega} \\ I_1 &= -I_2. \end{aligned}$$

Power dissipated by the voltage source:


$$= I_1 \cdot V_1 = -I_2 \cdot V_s \quad (P_{Vs})$$

$$= -\frac{V_s}{R} \cdot V_s = -\frac{V_s^2}{R}$$

$$P_{Vs} + P_R = 0$$

Voltage source delivers power.

Short circuit?

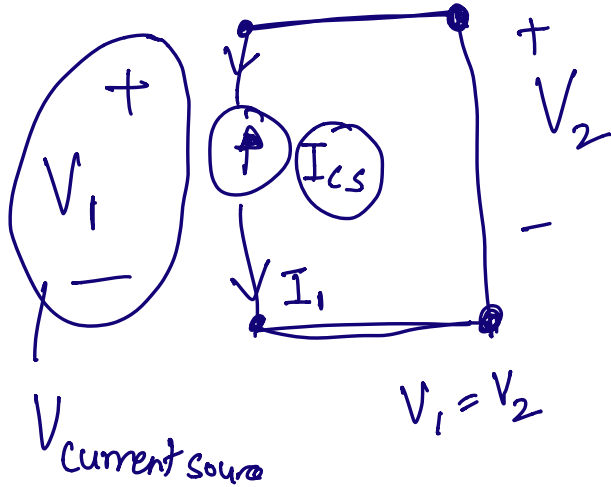


$V_{\text{current source}} = V_{\text{short circuit}} = 0$

$V_2 = 0$

Power: $V_2 \cdot I_1$




$\Rightarrow 0$

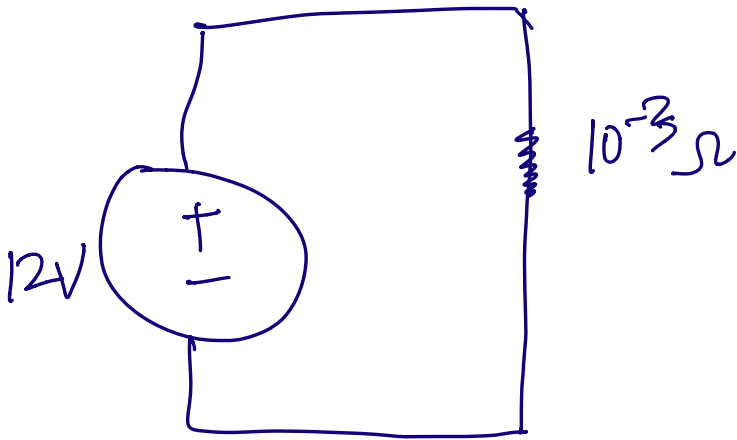


$I = \frac{V}{R} = \frac{12V}{10^{-3} \Omega} = 12,000 \text{ Amp}$

Power: $= V \cdot I$

Office Hours

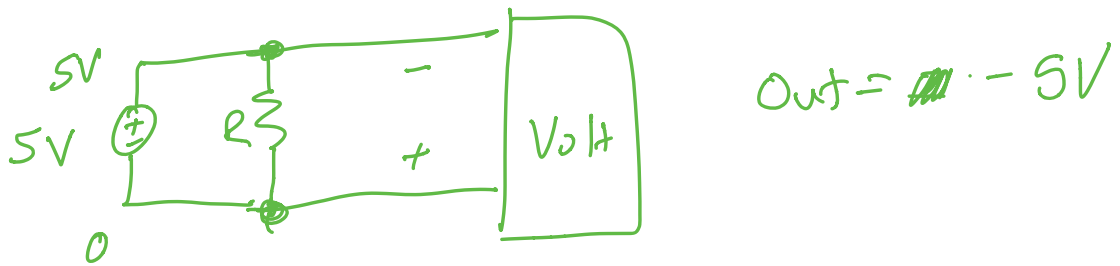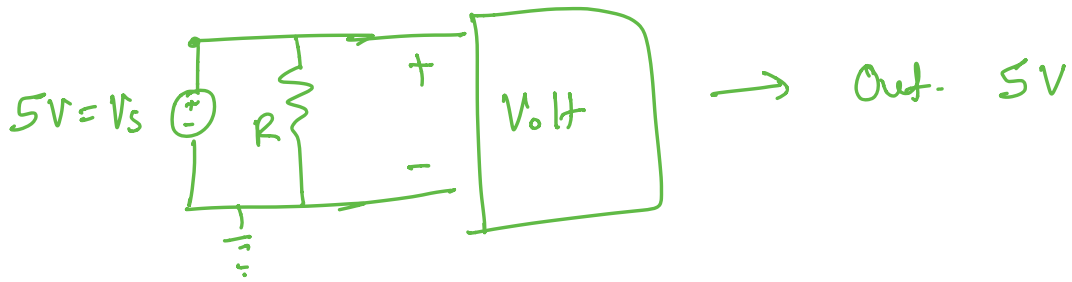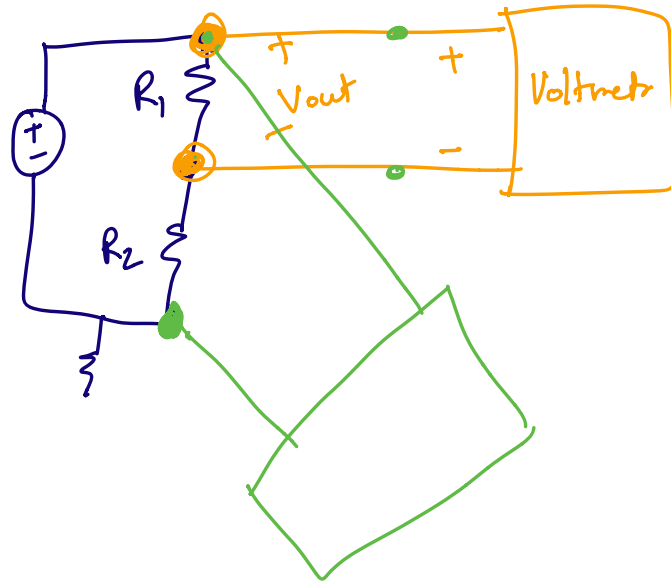

Dangling Resistor

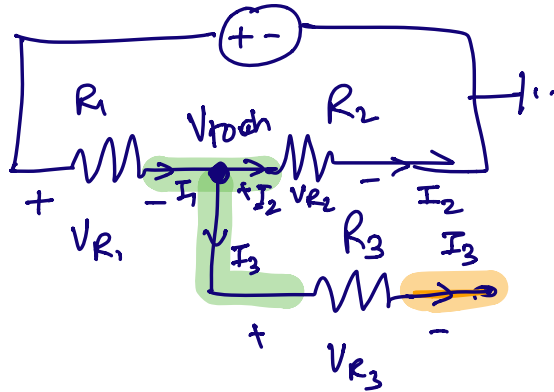

KCL: $I_1 = I_2 + I_3$

$\Rightarrow I_1 = I_2$

KCL: $I_3 = 0$