

Module 2, Lecture 4

Last time:

- 1D Touchscreen
- Power


Logistics

- Advising Oct 15.
- How are you doing?
 - ↳ Message from your colleges
- Zoom update
- Check video permissions.

Today:

- 2D touchscreen
- Equivalence

An interesting circuit

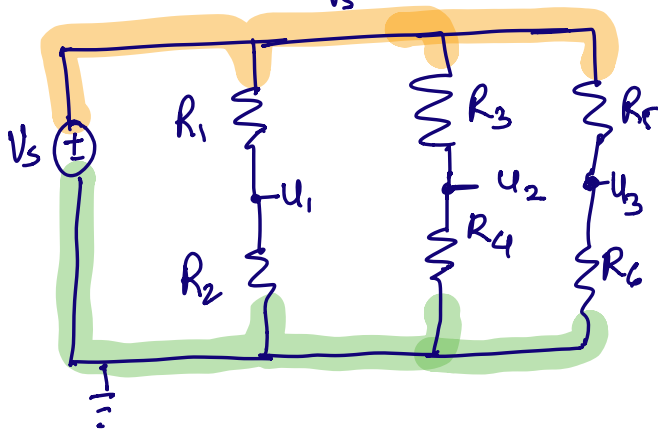


$$u_1 = \frac{R_2}{R_1 + R_2} \cdot V_s$$

$$u_2 = \frac{R_4}{R_3 + R_4} \cdot V_s$$

$$u_3 = \frac{R_6}{R_5 + R_6} \cdot V_s$$

k is a scalar, e.g. $k=2$

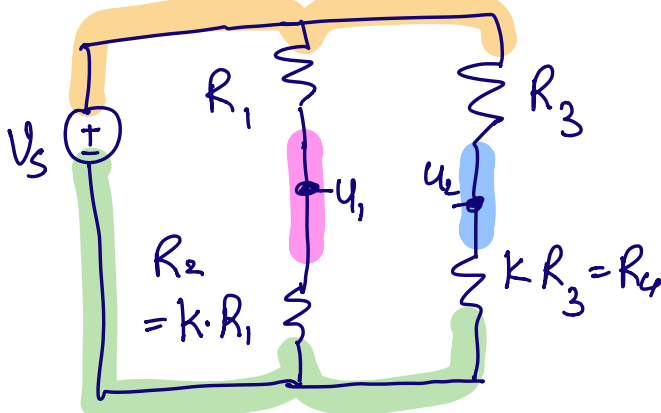

$$u_1 = \frac{k R_1}{R_1 + k R_1} \cdot V_s$$
$$= \frac{k}{1+k} \cdot V_s$$


Ratio of the resistors is $\underline{\underline{k}}$

$$u_2 = \frac{k R_3 \cdot V_s}{R_3 + k R_3} = \frac{k}{1+k} \cdot V_s$$

$R_1 = R_1$
 $R_2 = k \cdot R_1$

Ratio between R_1 and R_2 is k

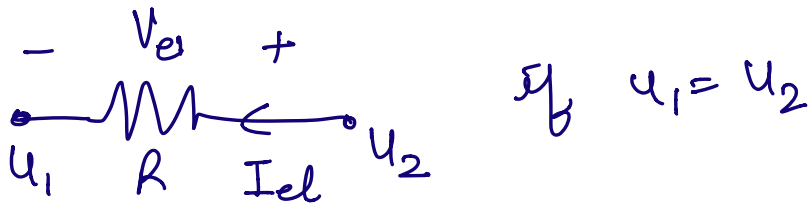
Turns out: $u_1 = u_2$ if $R_1 : R_2 = R_3 : R_4$.




If there is no voltage drop across a resistor, then there is no current flowing through it!

$$u_1 = \frac{R_2}{R_1 + R_2} \cdot V_s = \frac{k R_1}{(1+k) R_1} \cdot V_s$$

$$= \frac{k}{1+k} V_s$$

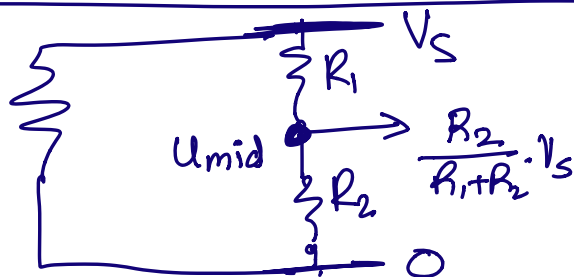

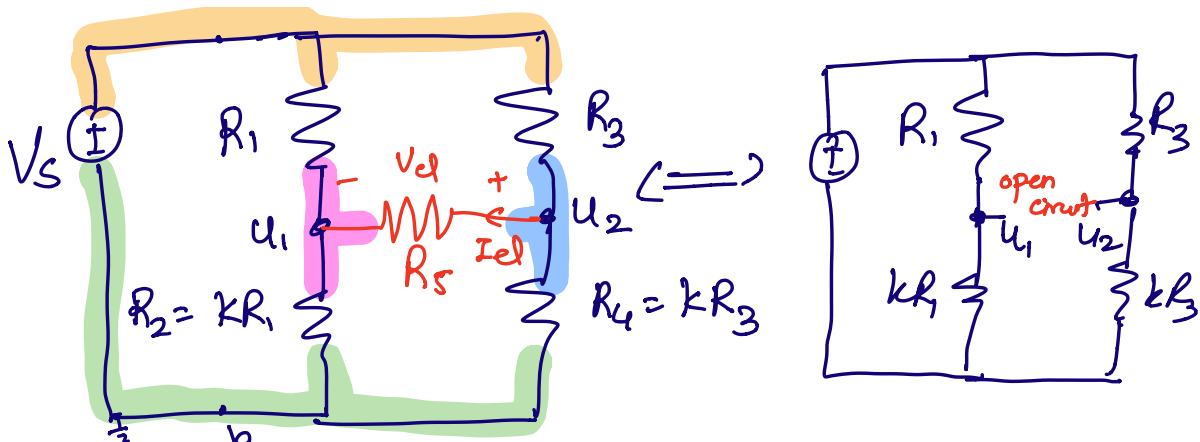

$$R_1 + R_2 = R_1 + kR_1 = (1+k)R_1$$


Question: What is the current through R_5 ?

Answer: There is no current.

Another way: Node Voltage Analysis.


Building on this:
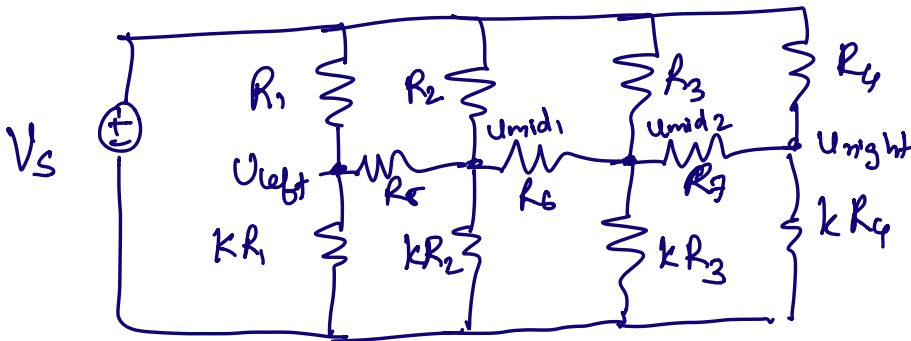
$$U_{\text{left}} = U_{\text{mid}_1} = U_{\text{mid}_2} = U_{\text{right}}$$



R_5, R_6, R_7 will have no current flowing through.

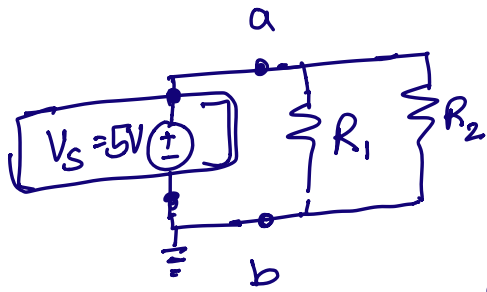Grid of Resistors: Good model for a "resistive sheet"




Diff between (a-b)

$$b=0, \Rightarrow a=5V$$


Even with R_2 , diff between

$$a-b = 5V.$$

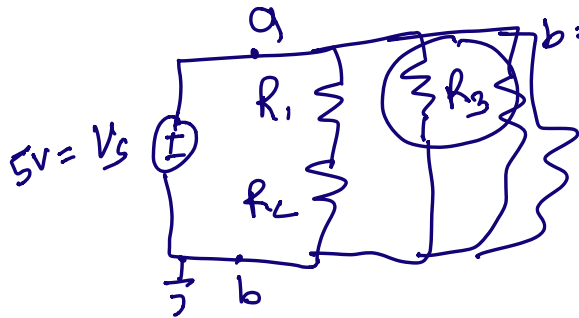


$$b=0, a=5V.$$

1D Touchscreens

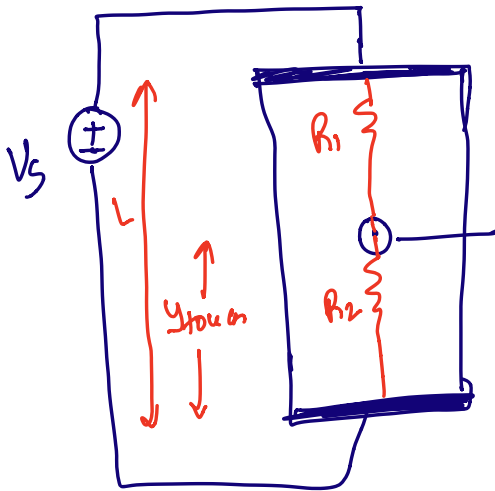


touch-
 V_{touch} .

Voltage
Divider

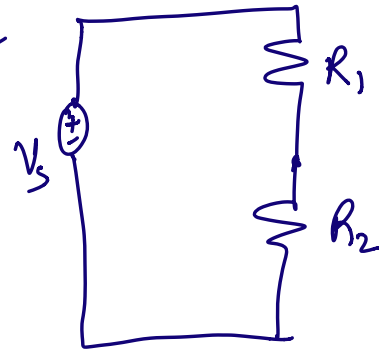

$$V_{touch} = \frac{Y_{touch} \cdot V_s}{L}$$


Another model: Grid-based model.

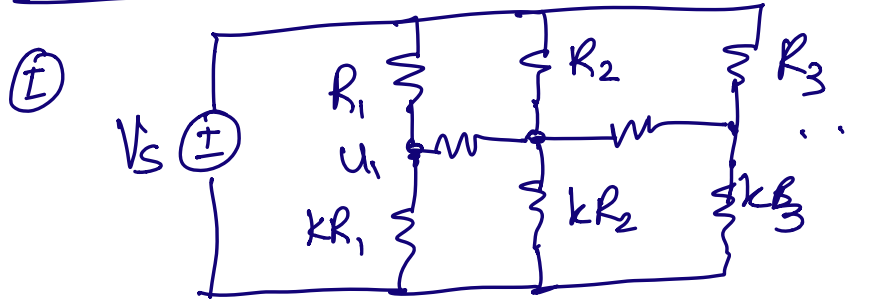



Vertical position ✓

Horizontal position ?


Recap: :

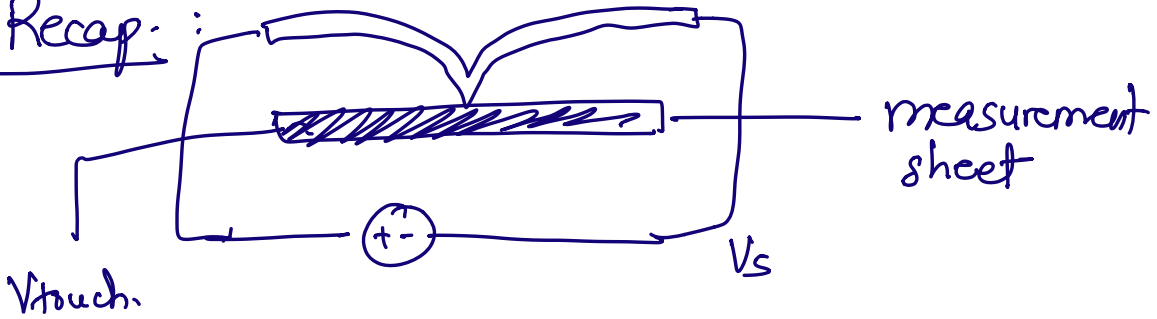

2D touch screen: Consider:

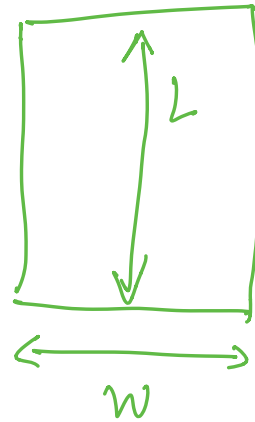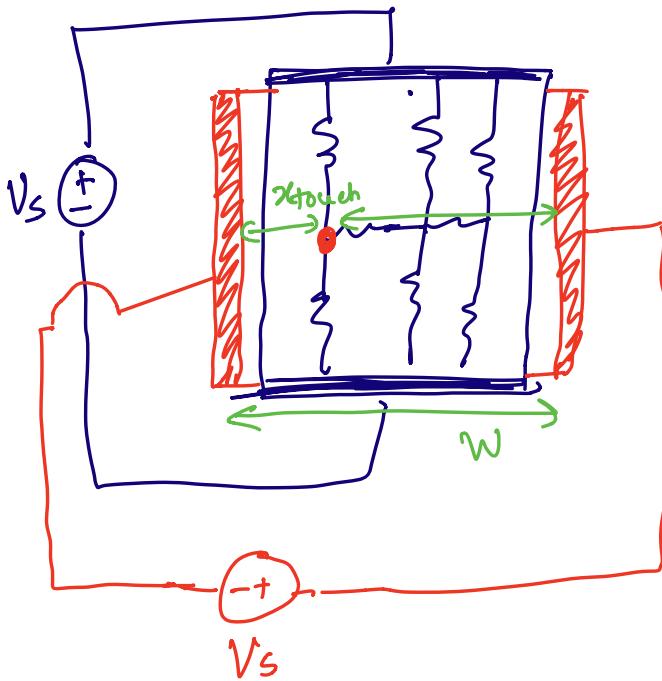

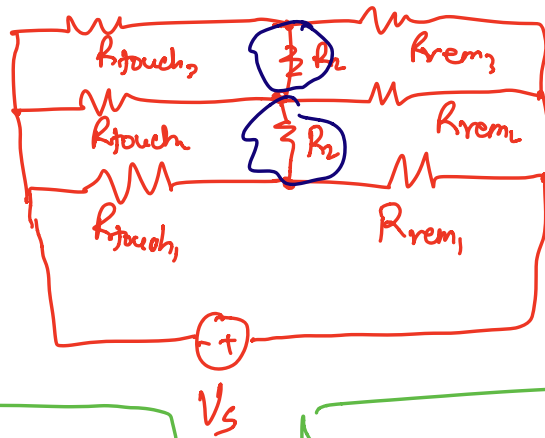
$$R = \frac{\rho \cdot \text{length}}{\text{width} \times \text{thickness}}$$




$$R_{touch,} = \frac{\rho \cdot x_{touch}}{L \cdot h}$$


$$R_{rem,} = \frac{\rho \cdot (W - x_{touch})}{L \cdot h}$$

Switches

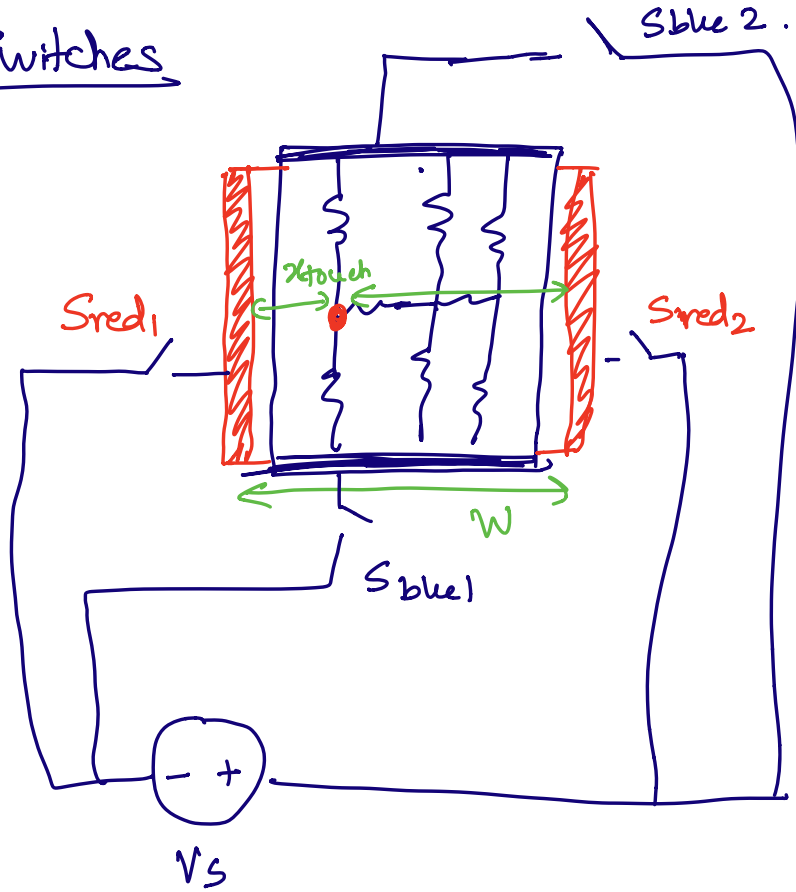


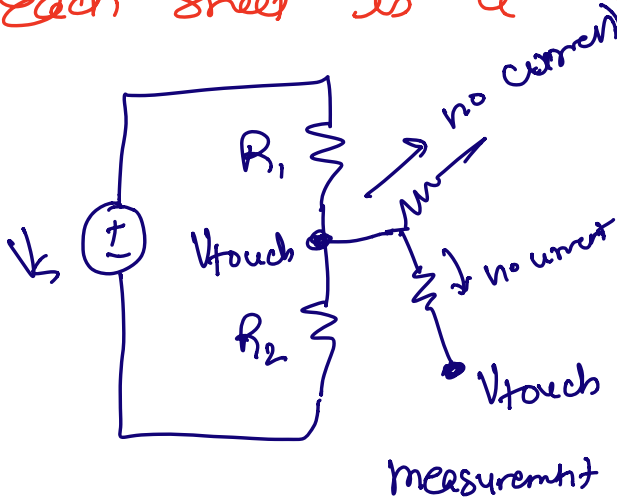Each sheet is a measurement ^{sheet} ~~for the~~ for the other sheets



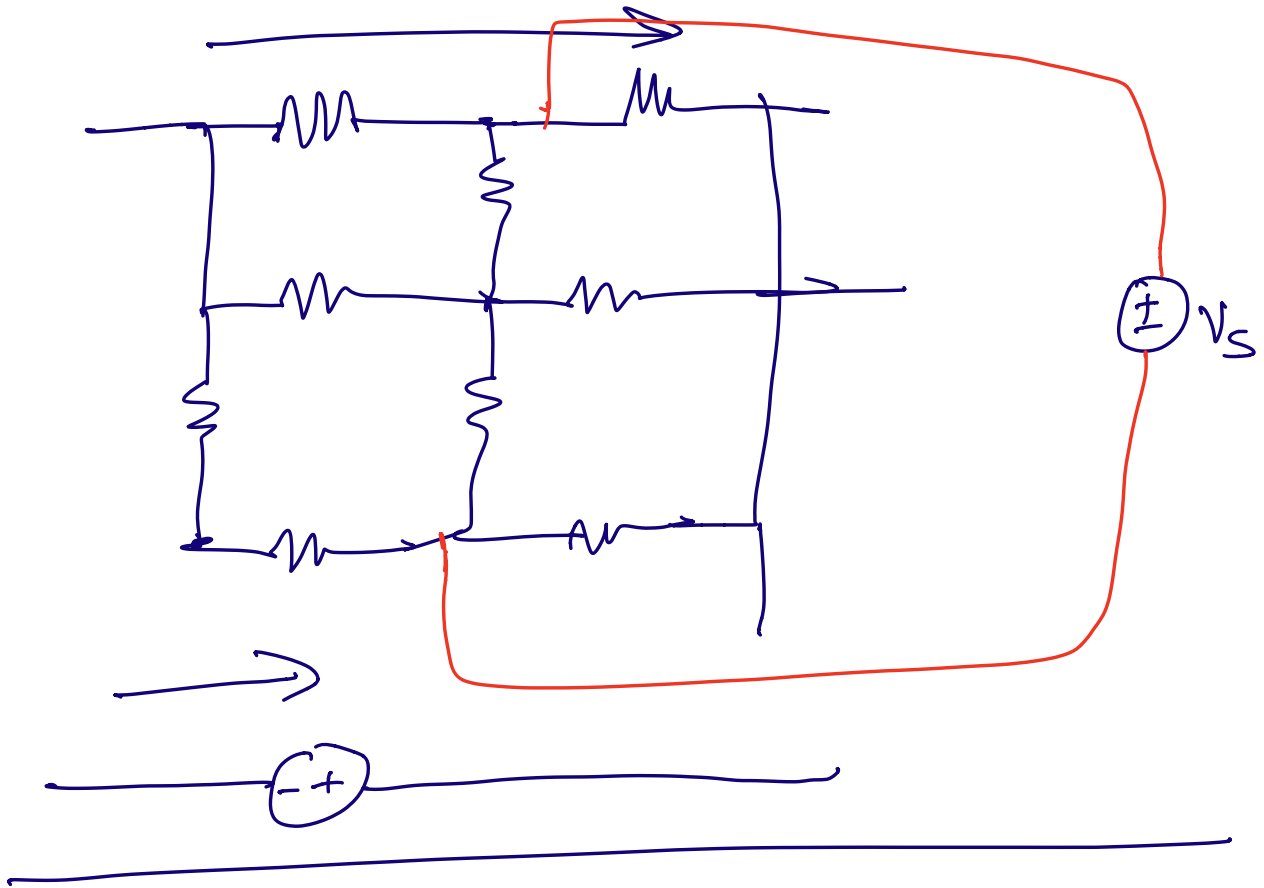

Take aways.

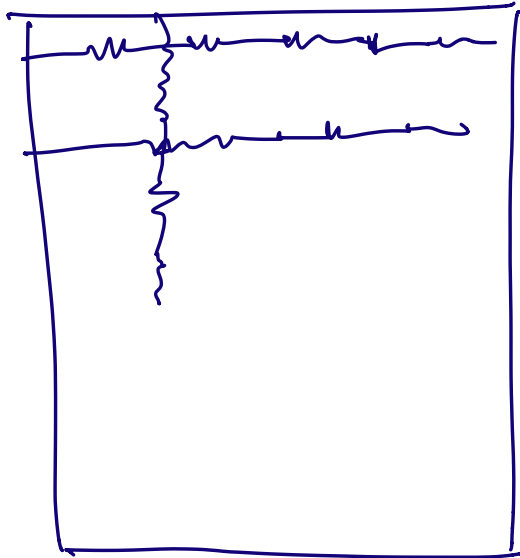

Office hours

