

EECS 16A Lecture 6


• Superposition: Linear Algebra tricks for circuits.

• Capacitors

Logistics

• Extended circuits review.

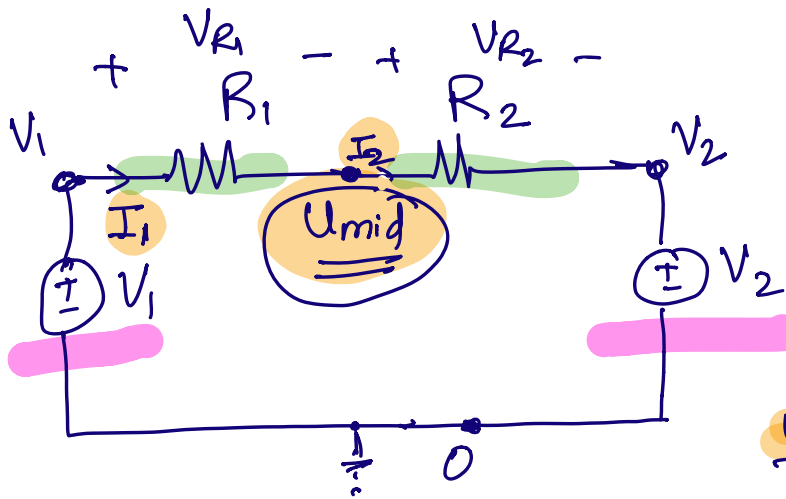Superposition : Power of the linearity of circuits



NVA

Unknowns:

U_{mid} , I_1

Knowns: V_1, V_2, R_1, R_2

KCL:

$$I_1 = I_2$$

Element eqⁿs: $V_{R_1} = I_1 R_1$, $V_{R_2} = I_2 R_2$

Substitue:

$$V_{R_1} = V_1 - U_{mid} = I_1 R_1 \quad (1)$$

$$V_{R_2} = U_{mid} - V_2 = I_2 R_2 = I_1 R_2 \quad (2)$$

(1) \Rightarrow

$$U_{mid} + I_1 R_2 = V_1$$

(2)

$$U_{mid} - I_1 R_2 = V_2$$

$$I_1 = \frac{V_1 - V_2}{R_1 + R_2}$$

$$U_{mid} = \frac{R_1 V_2 + R_2 V_1}{R_1 + R_2}$$

$$\vec{x} = \begin{bmatrix} U_{mid} \\ I_1 \end{bmatrix}$$

$$\underbrace{\begin{bmatrix} 1 & R_1 \\ 1 & -R_2 \end{bmatrix}}_A \underbrace{\begin{bmatrix} U_{mid} \\ I_1 \end{bmatrix}}_{\vec{x}} = \underbrace{\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}}_{\vec{b}}$$

$$\vec{x} = A^{-1} \vec{b}$$

$$A\vec{x} = \vec{b}$$


Check: Is A invertible?

$$A = \begin{bmatrix} 1 & R_1 \\ 1 & -R_2 \end{bmatrix}$$

$$\begin{bmatrix} R_1 \\ -R_2 \end{bmatrix} = \alpha \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

Is this possible?

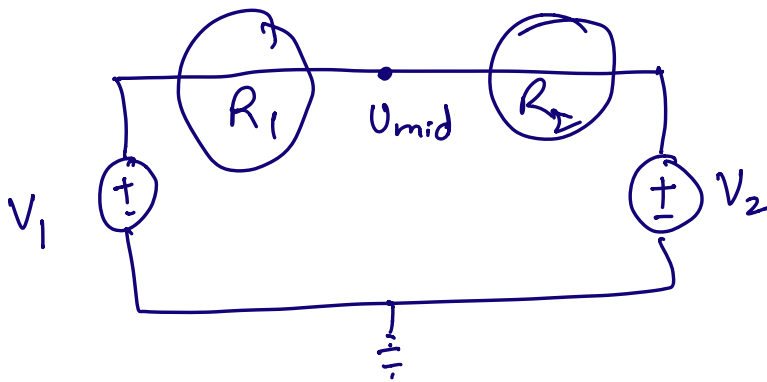\Rightarrow A is always invertible,
except when $R_1 = R_2 = 0$



① If math breaks \Rightarrow physical world is also probably unhappy ;)

$$\underbrace{\begin{bmatrix} 1 & R_1 \\ 1 & -R_2 \end{bmatrix}}_A \underbrace{\begin{bmatrix} \text{Umid} \\ \text{I} \end{bmatrix}}_{\vec{x}} = \underbrace{\begin{bmatrix} v_1 \\ v_2 \end{bmatrix}}_{\vec{b}}$$

$$\vec{x} = A^{-1} \vec{b}$$

$$\begin{aligned} \vec{b} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} &= \begin{bmatrix} v_1 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ v_2 \end{bmatrix} \\ &= \vec{b}_1 + \vec{b}_2 \end{aligned}$$

$$\vec{x} = A^{-1} \vec{b}$$

$$= A^{-1} (\vec{b}_1 + \vec{b}_2)$$


$$= A^{-1} \vec{b}_1 + A^{-1} \vec{b}_2$$

$$= A^{-1} \begin{bmatrix} v_1 \\ 0 \end{bmatrix} + A^{-1} \begin{bmatrix} 0 \\ v_2 \end{bmatrix}.$$

$A^{-1} \begin{bmatrix} V_1 \\ 0 \end{bmatrix}$: what does this represent?


↳ Solution to
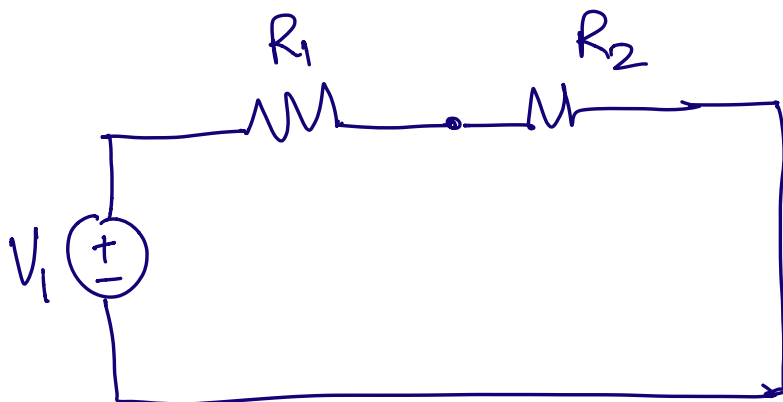
$$A \vec{x}_1 = \begin{bmatrix} V_1 \\ 0 \end{bmatrix} \quad \text{ie. our original circuit but } V_2 = 0$$



↳ $A \vec{x} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

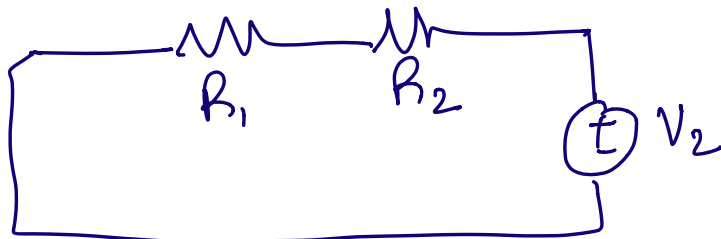Now: $A \vec{x}_1 = \begin{bmatrix} V_1 \\ 0 \end{bmatrix}$



What does $A^{-1} \begin{bmatrix} 0 \\ V_2 \end{bmatrix}$?


I can solve the circuit by breaking it up into two parts:

① with only V_1 , $V_2 = 0$

② with only V_2 but $V_1 = 0$.


$$\vec{x} = \begin{bmatrix} u_{mid} \\ I_1 \end{bmatrix} = A^{-1} \vec{b}$$
$$= A^{-1} \begin{bmatrix} V_1 \\ 0 \end{bmatrix} + A^{-1} \begin{bmatrix} 0 \\ V_2 \end{bmatrix}$$

Superposition

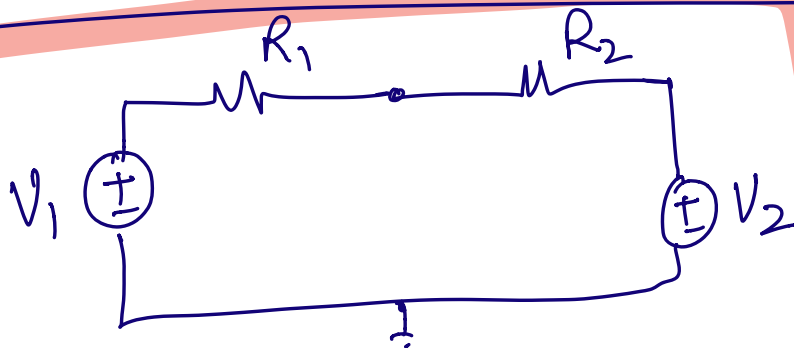


Voltage
summer
if
 $R_1 = R_2$

① Zero out the first voltage.

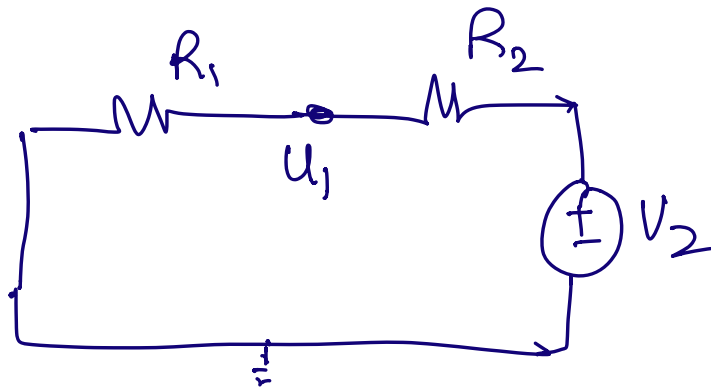

$$u_1 = \frac{R_1}{R_1 + R_2} \cdot V_2$$

② Zero out the second voltage.

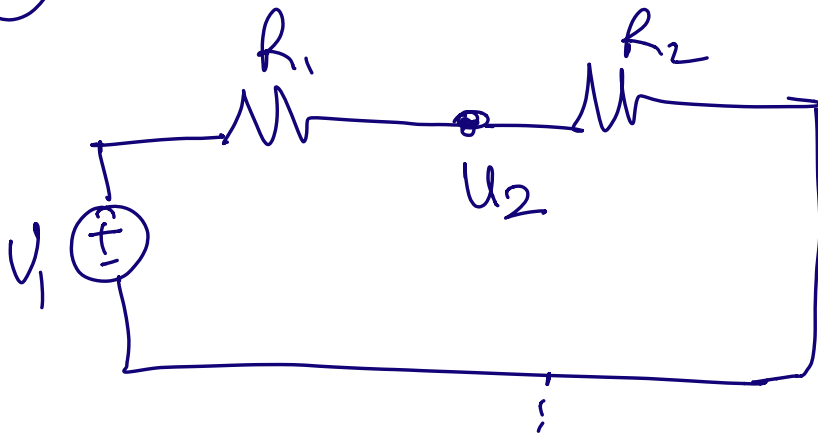

$$u_2 = \frac{R_2}{R_1 + R_2} \cdot V_1$$

③ Combining:

$$U_{\text{mid}} = U_1 + U_2$$

$$= \frac{R_1}{R_1 + R_2} V_2 + \frac{R_2}{R_1 + R_2} \cdot V_1$$

Two things:

① If $R_1 = R_2 = R$

$$U_{\text{mid}} = \frac{R (V_1 + V_2)}{2R}$$

$$= \frac{1}{2} (V_1 + V_2)$$

~~1~~ "Physical Meaning" of
2 Superposition

Setup 1

$$\begin{bmatrix} 1 & R_1 \\ 1 & -R_2 \end{bmatrix} \begin{bmatrix} u_{mid} \\ I_1 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

\xrightarrow{x}


Instead of this if I had:

Setup 2

$$\begin{bmatrix} 1 & R_1 \\ 1 & -R_2 \end{bmatrix} \begin{bmatrix} u_{mid} \\ I_1 \end{bmatrix} = \begin{bmatrix} 2V_1 \\ 2V_2 \end{bmatrix}$$

$\xrightarrow{2x}$


Example 2

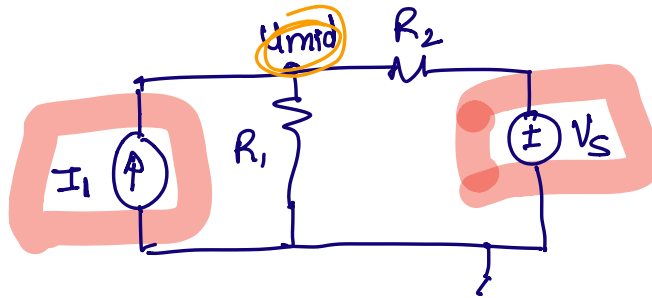

What does it mean to zero out a current source?




① Zero out the current source.

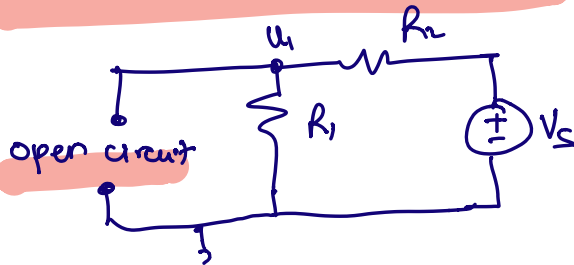

$$U_1 = \frac{R_1}{R_1 + R_2} \cdot V_S$$

② Zero out the voltage source.

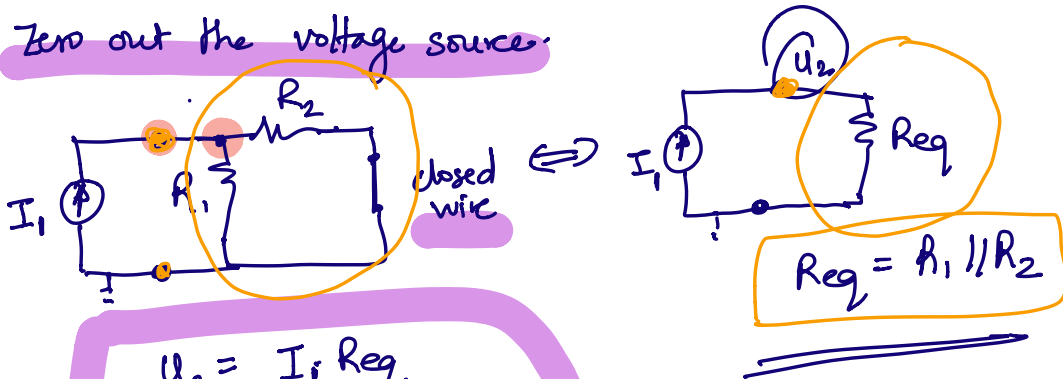


$$R_{eq} = R_1 \parallel R_2$$

$$U_2 = I_1 R_{eq} = I_1 \cdot \frac{R_1 R_2}{R_1 + R_2}$$

③ Combine:

$$U_{mid} = U_1 + U_2 = \frac{R_1 V_S}{R_1 + R_2} + I_1 \frac{R_1 R_2}{R_1 + R_2}$$

Capacitors What are they?

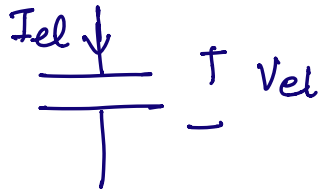

"I-V" relationship for
a capacitor:

$$Q = C \cdot V$$

Charge = Capacitance \cdot Voltage

[C]

[F]

[V]


Coulombs

Farads

voltage


$$I \text{ current: } = \frac{dQ}{dt}$$

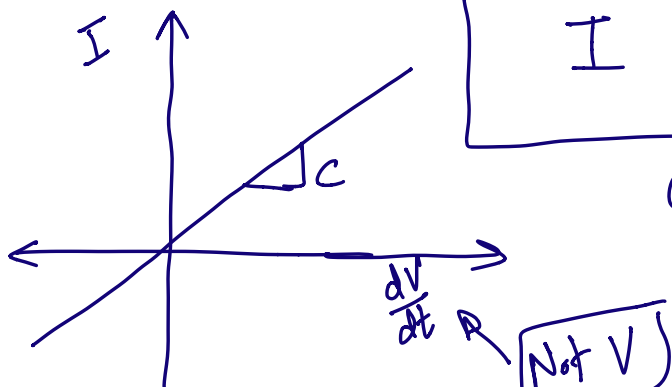Taking derivatives: $I = \frac{dQ}{dt} = \frac{d(CV)}{dt}$



$$I = C \cdot \frac{dV}{dt}$$

C is a constant.

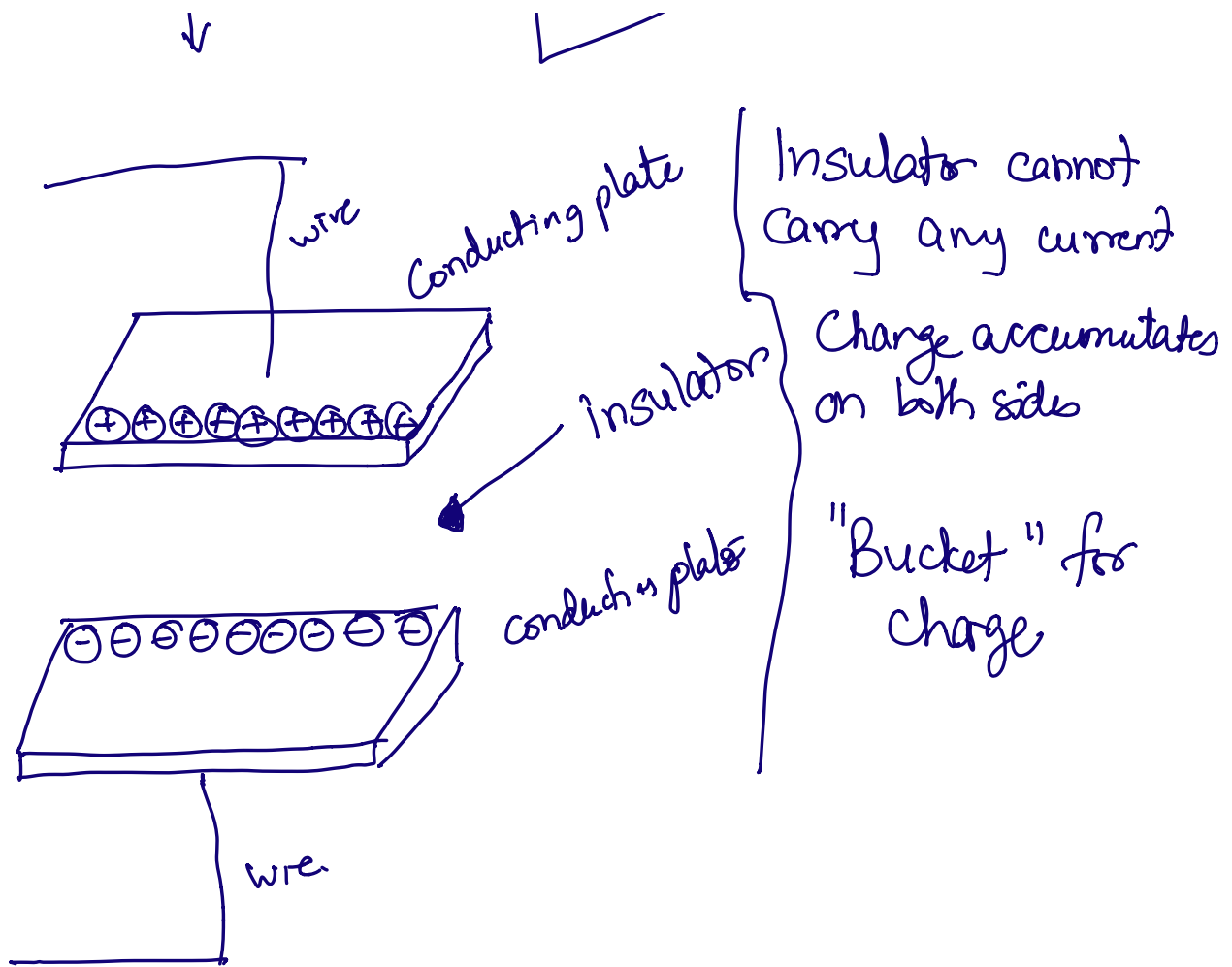

$$Q_{el} = C \cdot V_{el} \Rightarrow$$

$$V_{el} = \frac{Q_{el}}{C} \quad \otimes$$

Voltage \leftrightarrow energy?

$$V_{el} = \frac{dE_{el}}{dQ_{el}} \quad \otimes$$

$$\Rightarrow \frac{dE_{el}}{dQ_{el}} = \frac{Q_{el}}{C}$$

⇒


$$E_{el} = \int_0^Q \frac{1}{C} \cdot Q_{el} \, dQ_{el}$$

$$= \frac{1}{2} \frac{Q^2}{C}$$

$$= \frac{1}{2} \frac{C \cdot V^2}{C} = \frac{1}{2} C V^2$$

Energy stored on a capacitor: $\frac{1}{2} C \cdot V^2$

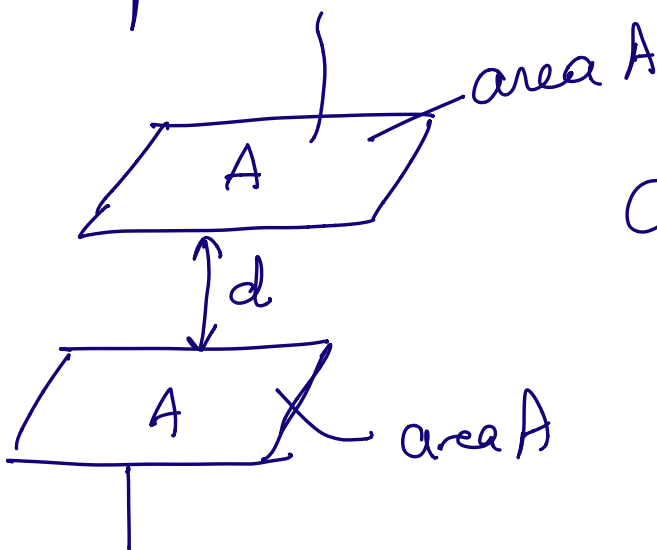How do the physical properties of a capacitor matter?



Two plates of a capacitor.

Capacitance

$$C = \epsilon \cdot \frac{A}{d}$$

$$\epsilon = \text{permittivity} \cdot \left[\frac{F}{m} \right]$$

$$\epsilon_0 = 8.85 \text{ pF/m} \quad \text{" permittivity of free space "}$$

$$= 8.85 \times 10^{-12} \text{ F/m}$$