

EECS 16A Lecture 7

- Review your study groups.

Last time:


Capacitors: buckets for charge -
store energy.

Current:
 $I = C \frac{dV}{dt}$

Charge:
 $Q = CV$

Energy
 $E = \frac{1}{2} CV^2$

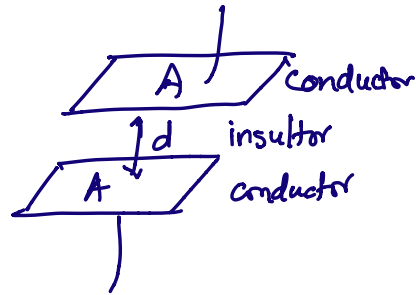Capacitance
 $C = \epsilon \cdot \frac{A}{d}$




Today: ① Circuits with capacitors.

② Capacitor equivalence

③ Capacitive touchscreen. (Charge sharing)

Example 1:

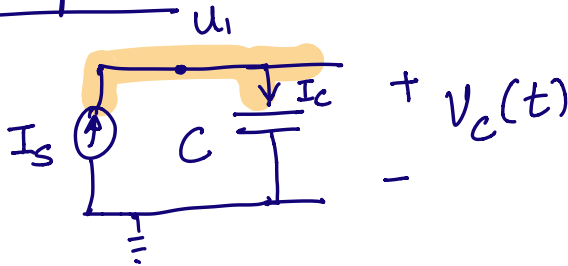

KCL: $I_s = I_c$

$I_c = C \cdot \frac{dV_c}{dt}$ (Element equation)

Integration:
 $\int_a^b f(x) dx = F(b) - F(a)$

$\int f(x) = F(x)$

$$I_s = C \cdot \frac{dV_c}{dt}$$

$V_c(0)$: initial voltage
across capacitor at
time 0.
 $V_c(t)$: volt. @ time t

Integrate


$$\int_0^t I_s dt = \int_0^t C \cdot \frac{dV_c}{dt} dt$$

Constant


$$I_s \cdot t = C [V_c(t) - V_c(0)]$$

$$V_c(t) = \frac{I_s \cdot t}{C} + V_c(0)$$

$$\begin{aligned} & \int_0^t \frac{dV_c(t)}{dt} dt \\ &= V_c(t) \Big|_0^t \\ &= V_c(t) - V_c(0) \end{aligned}$$

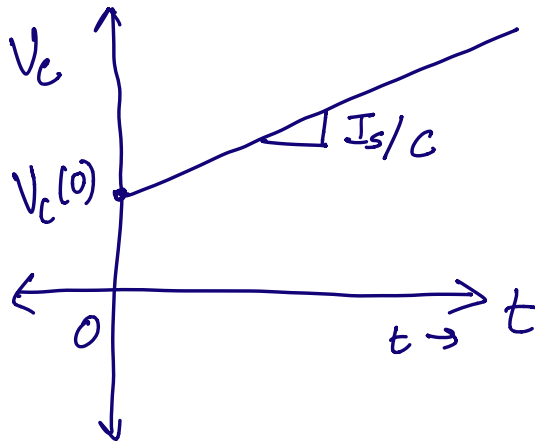

Example 2:

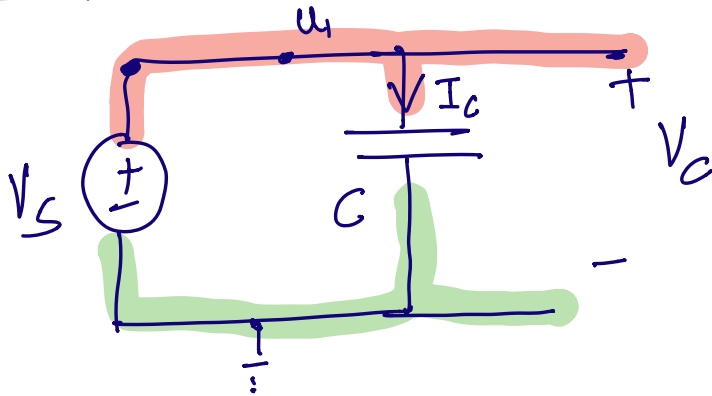


$$V_C = u_1$$

$$I_C = C \frac{dV_C}{dt}$$


$$\frac{dV_C}{dt} = \frac{dV_S}{dt} = 0$$

$$I_C = C \cdot 0 = 0$$

Example 2a:

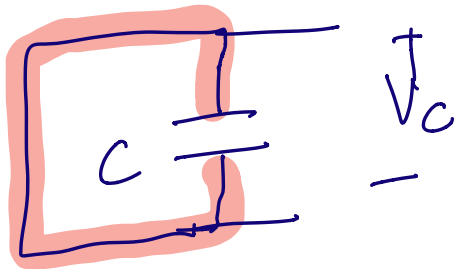


$$V_C = 0$$

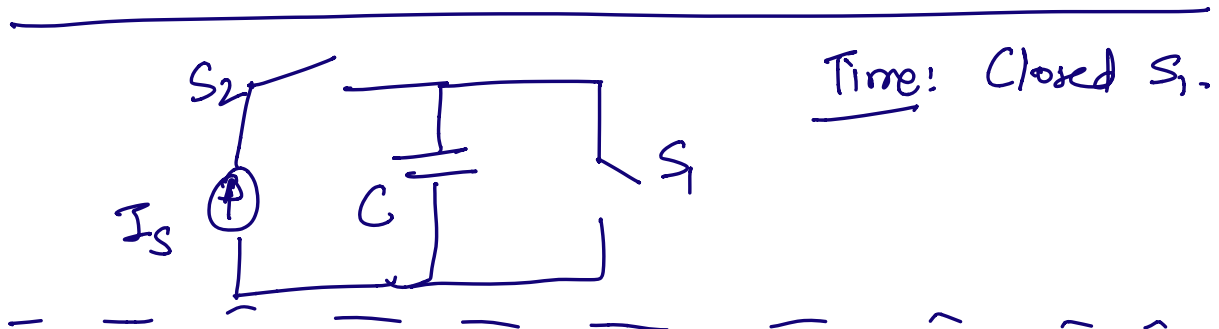

Time! Closed S_1 .

Open S_2 , S_2 close S_1

(1)

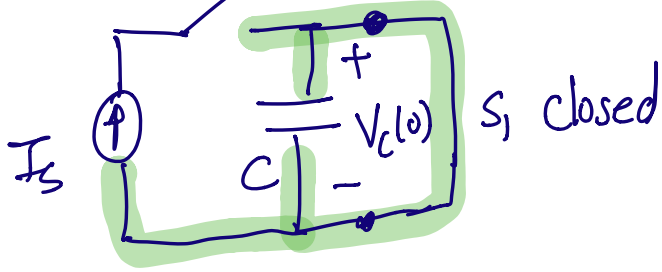


Set initial condition
of capacitor

$$V_c(0) = 0 \quad \text{Set the initial condition}$$


Then: Open S_1 , close S_2 .

(2)

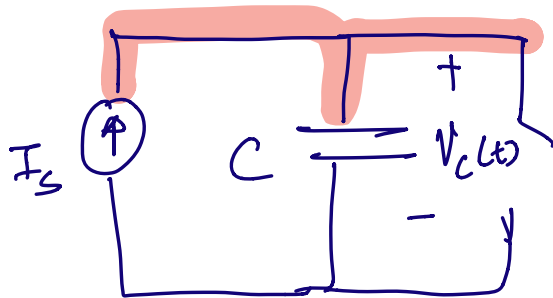

$$\begin{aligned} V_c(t) &= \frac{I_s \cdot t}{C} + V_c(0) \\ &= \frac{I_s t}{C} + 0 \end{aligned}$$

Example 3 :

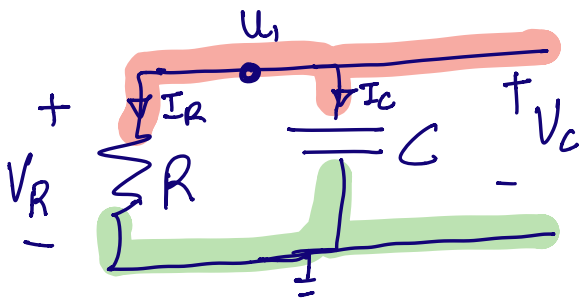

$$V_C(0) = 0$$

$$\textcircled{1} I_R = \frac{V_R}{R}$$

$$\underline{\text{KCL}}: I_R + I_C = 0 \quad *$$

$$\textcircled{2} I_C = C \frac{dV_C}{dt}$$

$$V_R = V_C$$

$$\frac{V_R}{R} + C \frac{dV_C}{dt} = 0$$

$$\frac{V_C}{R} + C \frac{dV_C}{dt} = 0$$

$$\Rightarrow \frac{dV_C}{dt} = -\frac{V_C}{RC} \quad (*)$$

What does steady state mean?

⇒ The state where nothing is changing.

$$V_C(t) = V_C(t + \Delta t)$$

$$\Rightarrow \frac{dV_C}{dt} = 0$$





"change over time"

"Steady State" $\Rightarrow \frac{dV_c}{dt} = 0$ By defⁿ of steady state



$\Rightarrow (*) \quad 0 = -\frac{V_c}{RC}$ at steady state

$\Rightarrow V_c = 0$ at steady state

Equivalence of Capacitors

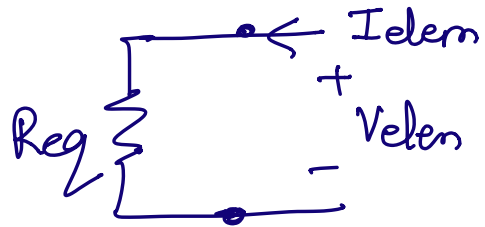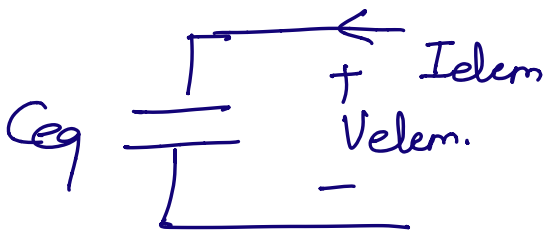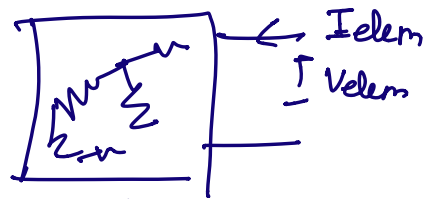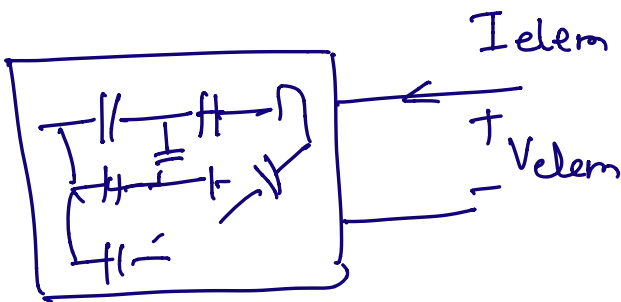

Example: Capacitors in parallel.

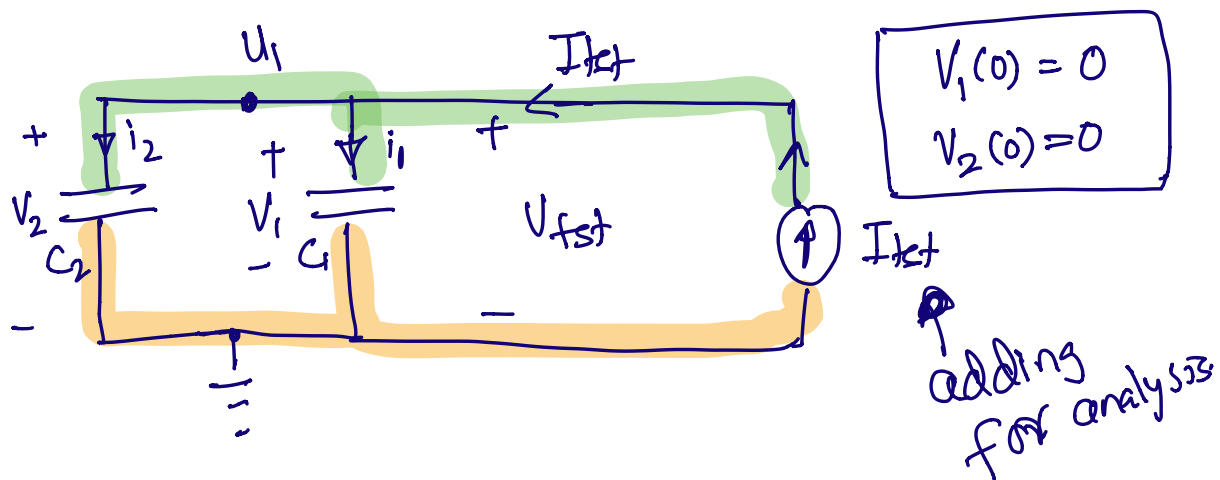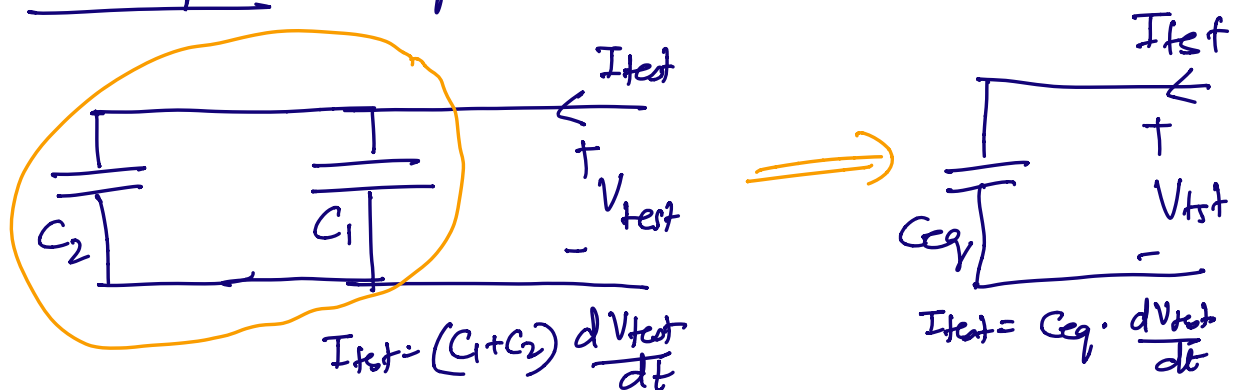

KCL: $I_{test} = i_1 + i_2$ $V_1 = V_2 = V_{test}$

$$i_1 = C_1 \cdot \frac{dV_1}{dt} \qquad i_2 = C_2 \cdot \frac{dV_2}{dt} = C_2 \cdot \frac{dV_1}{dt}$$



$$I_{test} = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt} = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_1}{dt}$$

$$I_{test} = (C_1 + C_2) \frac{dV_1}{dt} = (C_1 + C_2) \frac{dV_{test}}{dt}$$

$$I_{\text{test}} = (G + C_2) \frac{dV_{\text{test}}}{dt}$$


$$\Rightarrow C_{\text{eq}} = G + C_2$$

Capacitors in series

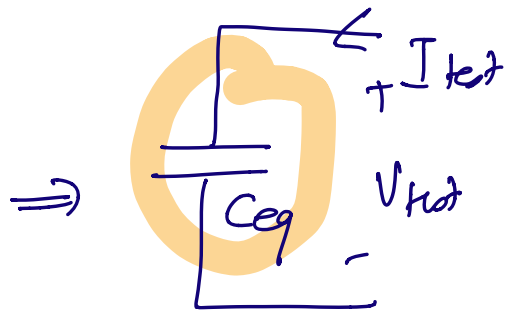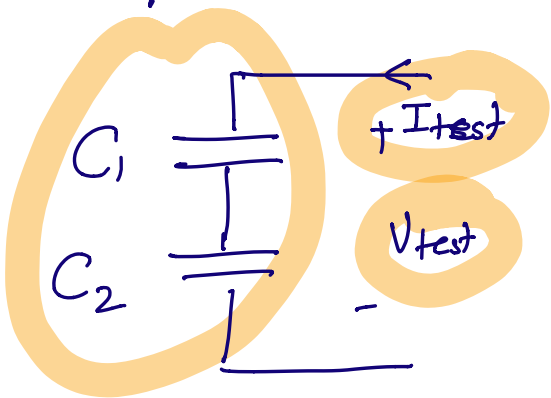

$$C_{\text{eq}} = \frac{C_1 C_2}{G + C_2}$$

Connect a current source I_{test}

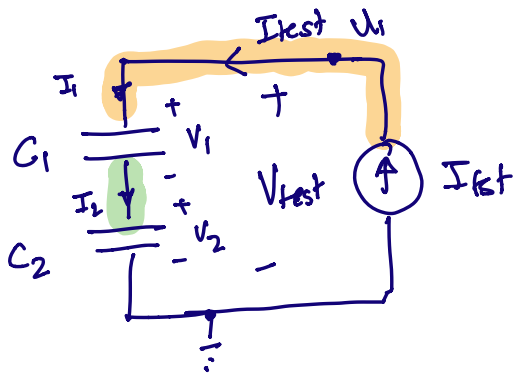

• KCL: $I_1 = I_{\text{test}}$
 $I_1 = I_2 = I_{\text{test}}$

• KVL: $V_{\text{test}} = V_1 + V_2$

$$I_1 = C_1 \frac{dV_1}{dt}$$

$$I_2 = C_2 \frac{dV_2}{dt}$$

$$\frac{dV_{\text{test}}}{dt} = \frac{dV_1}{dt} + \frac{dV_2}{dt}$$

$$\Rightarrow \frac{dV_2}{dt} = \frac{dV_{\text{test}}}{dt} - \frac{dV_1}{dt}$$



Since $I_1 = I_2$,

$$\begin{aligned} C_1 \frac{dV_1}{dt} &= C_2 \frac{dV_2}{dt} \\ &= C_2 \left(\frac{dV_{\text{test}}}{dt} - \frac{dV_1}{dt} \right) \end{aligned}$$

$$\Rightarrow (C_1 + C_2) \frac{dV_1}{dt} = C_2 \frac{dV_{\text{test}}}{dt}$$

$$\frac{dV_1}{dt} = \frac{I_1}{C_1} = \frac{I_{\text{test}}}{C_1}$$


$$\Rightarrow (C_1 + C_2) \cdot \frac{I_{\text{test}}}{C_1} = C_2 \cdot \frac{dV_{\text{test}}}{dt}$$

$$\Rightarrow I_{\text{test}} \left(\frac{C_1 + C_2}{C_1 C_2} \right) = \frac{dV_{\text{test}}}{dt}$$


$$\rightarrow I_{\text{test}} = \left(\frac{C_1 C_2}{C_1 + C_2} \right) \frac{dV_{\text{test}}}{dt}$$

$$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{C_1 \parallel C_2}{\text{notations}}$$

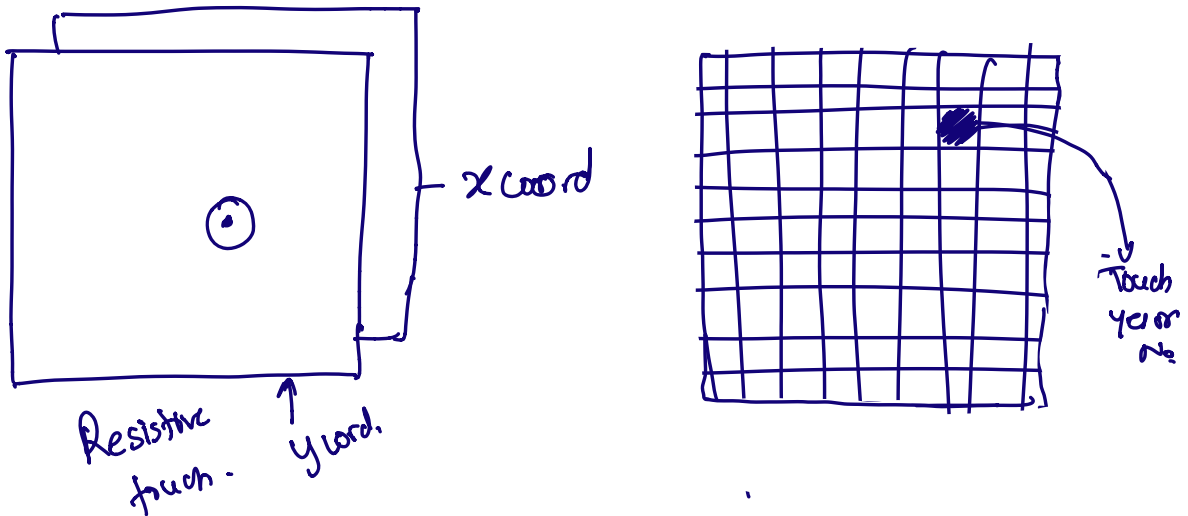
Finally: Building a capacitive touchscreen



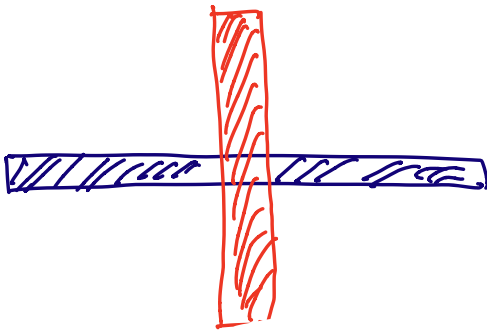How to detect touch for one pixel.
Top view



Side view:

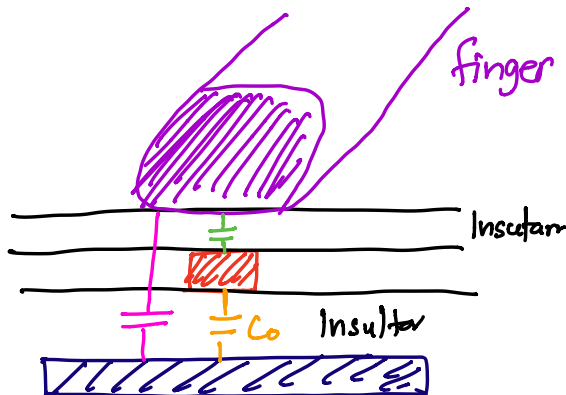

Office hours:

$$\int_0^t \frac{dV_c}{dt} \cdot dt = \int_{V_c(0)}^{V_c(t)} dV_c$$