

# EECS 16A


## Today

- More charge sharing  
"stuck in the middle with you"
- Comparators
- Op-amps.

## Logistics

- Midterm, Monday Nov 2nd.
- Clobber
- +2 points on MT1.

## Charge sharing

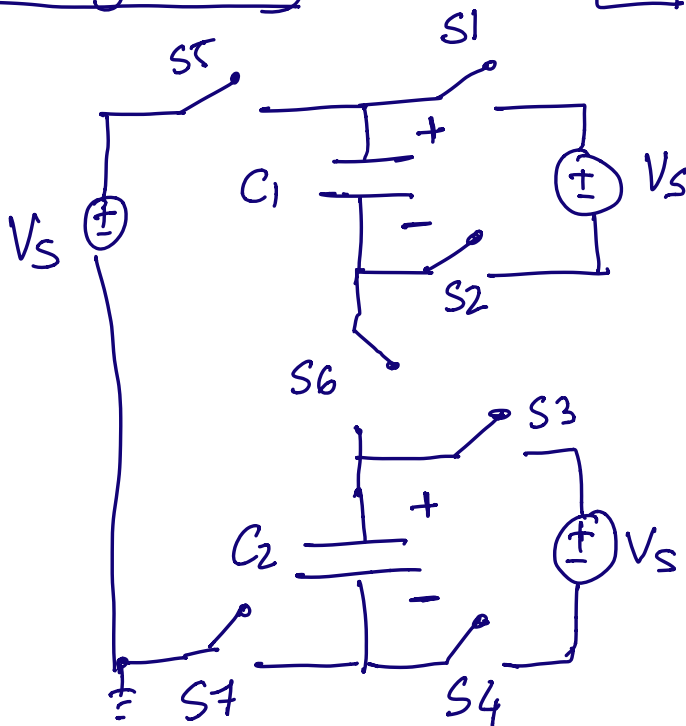

$V_S$   $C_1$   $C_2$  Initial charges 0. Last time.

Phases: 1, 2

Phase 1:

$S_1, S_2, S_3, S_4$   
closed

$S_5, S_6, S_7$   
open



Phase 2:

$S_1 - S_4$  open

$S_5 - S_7$  are closed

Question: Steady state, after Phase 2,  
what is the charge  $q_1, q_2, V_1, V_2$

Phase 1:


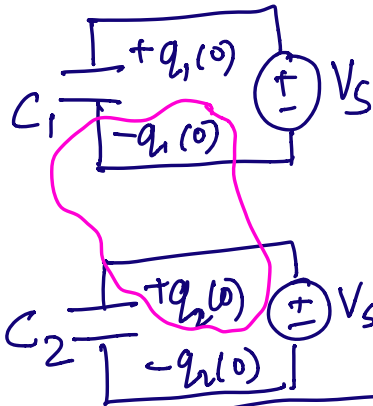
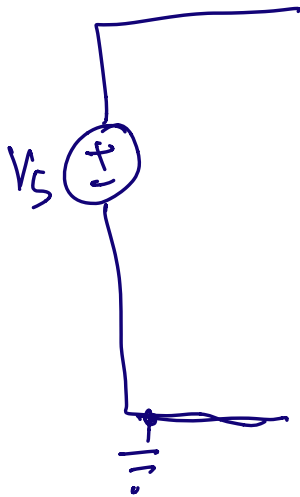


$$q_1(0) = V_S \cdot C_1$$

$$q_2(0) = V_S \cdot C_2$$

Total charge on "floating" node  
in Phase 1:  
= charge on  $C_1$  bottom plate  
+  $C_2$  top plate  
=  $-q_1(0) + q_2(0)$

Phase 2:

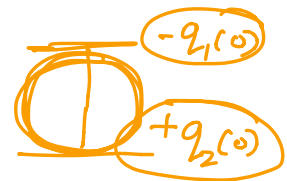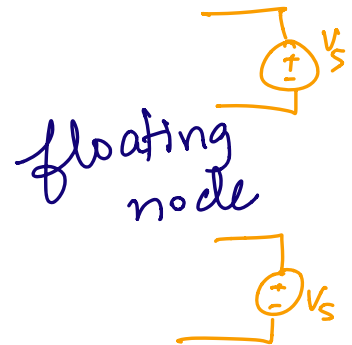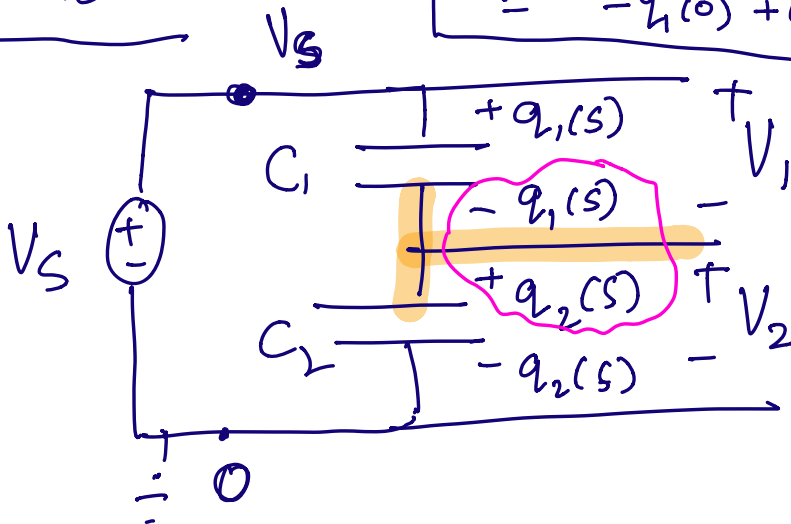

Phase 2: ①  $q_1(s) = C_1 V_1$

②  $q_2(s) = C_2 V_2$

$$\text{KVL: } V_1 + V_2 = V_s \quad (3)$$

Goals:

$$\begin{bmatrix} q_1(s) \\ q_2(s) \\ V_1 \\ V_2 \end{bmatrix}$$

Charge on bottom plate of  $C_1 = -q_1(s)$

Charge on top plate of  $C_2 = +q_2(s)$

Total charge on the floating node:  
 $-q_1(s) + q_2(s)$

Charge is conserved

$$\Rightarrow -q_1(s) + q_2(s) = -q_1(0) + q_2(0)$$

$$\boxed{-q_1(s) + q_2(s) = -V_s C_1 + V_s C_2} \quad (4)$$

$$\textcircled{1} \quad q_1(s) = C_1 V_1$$

$$\textcircled{2} \quad q_2(s) = C_2 V_2$$

$$V_1 + V_2 = V_s \quad \textcircled{3}$$


---

$$\begin{bmatrix} 1 & 0 & -C_1 & 0 \\ 0 & 1 & 0 & -C_2 \\ 0 & 0 & 1 & 1 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} q_1(s) \\ q_2(s) \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ V_s \\ -V_s C_1 + V_s C_2 \end{bmatrix}$$

---

Going back to the capacitive touch screen.
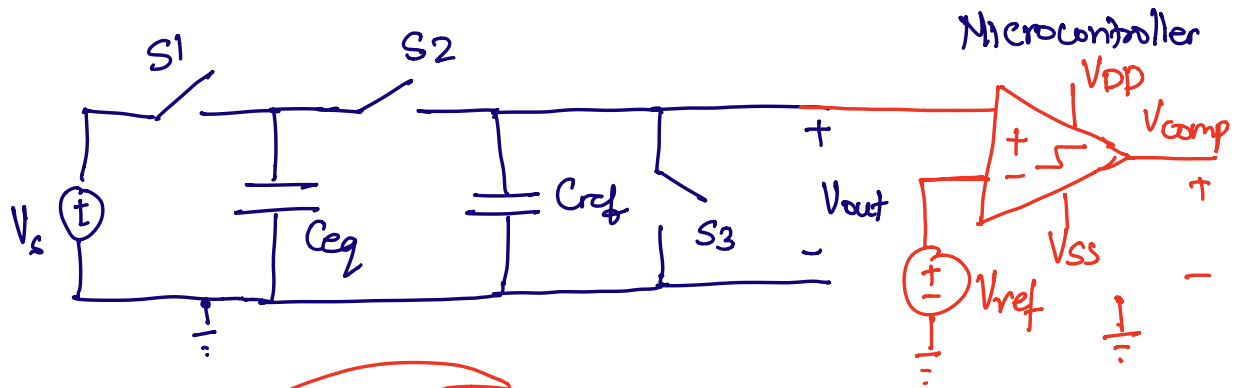
$$C_{eq} = \begin{cases} C_0 & \text{if no touch} \\ C_0 + C_\Delta & \text{if touch.} \end{cases}$$




$$V_{out} = \begin{cases} \frac{(C_0 + C_A) V_s}{C_0 + C_A + C_{ref}} & \text{touch} \\ \frac{C_0 V_s}{C_0 + C_{ref}} & \text{No touch.} \end{cases}$$

(midpoint of touch + no touch)


Comparator: Compare two voltages.

Op-Amps (Operational amplifiers)

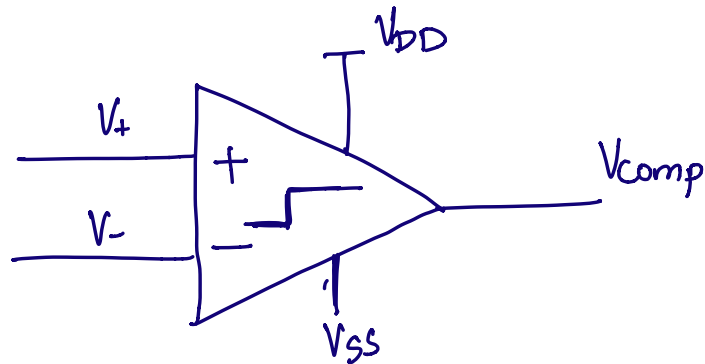

If  $V_+ > V_-$  then  $V_{comp} = V_{DD}$

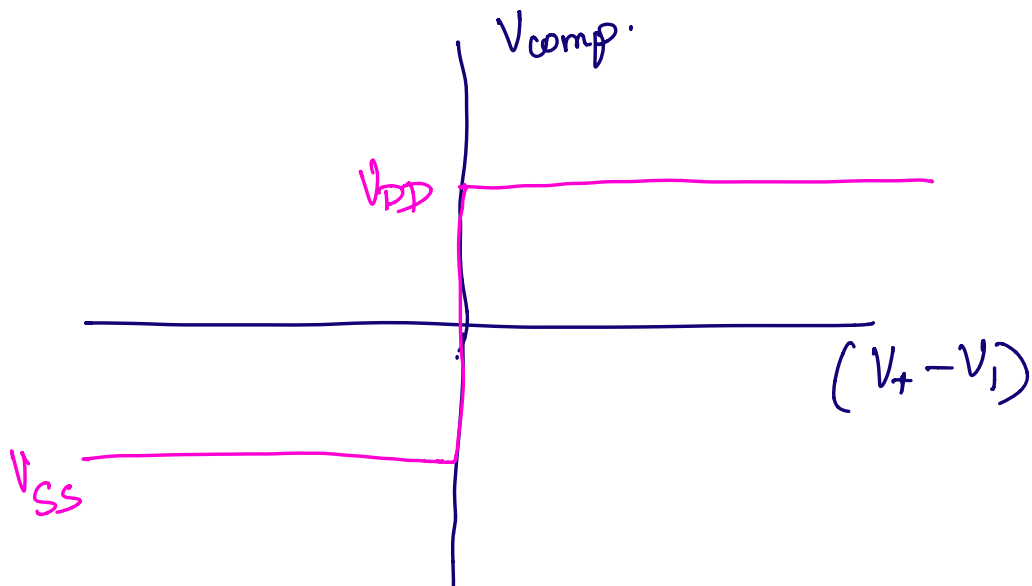If  $V_- > V_+$  then  $V_{comp} = V_{SS}$




## Operational Amplifiers

"Amplify signals"

"isolate circuits" to avoid "loading effect"


Negative feedback.

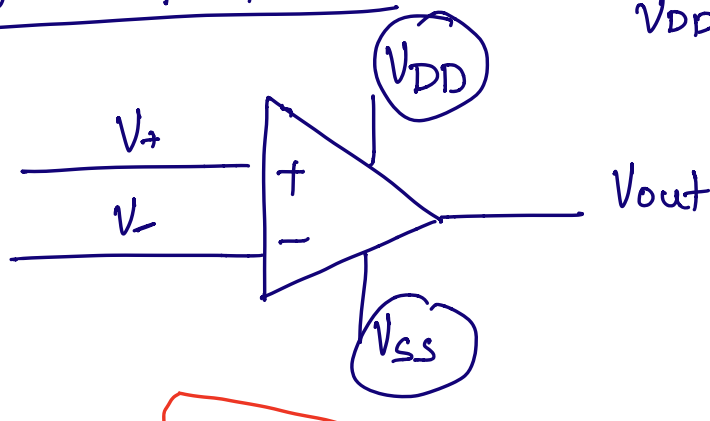

References:

$V_{DD}, V_{SS}$

Midpoint:  $\frac{V_{DD} + V_{SS}}{2}$

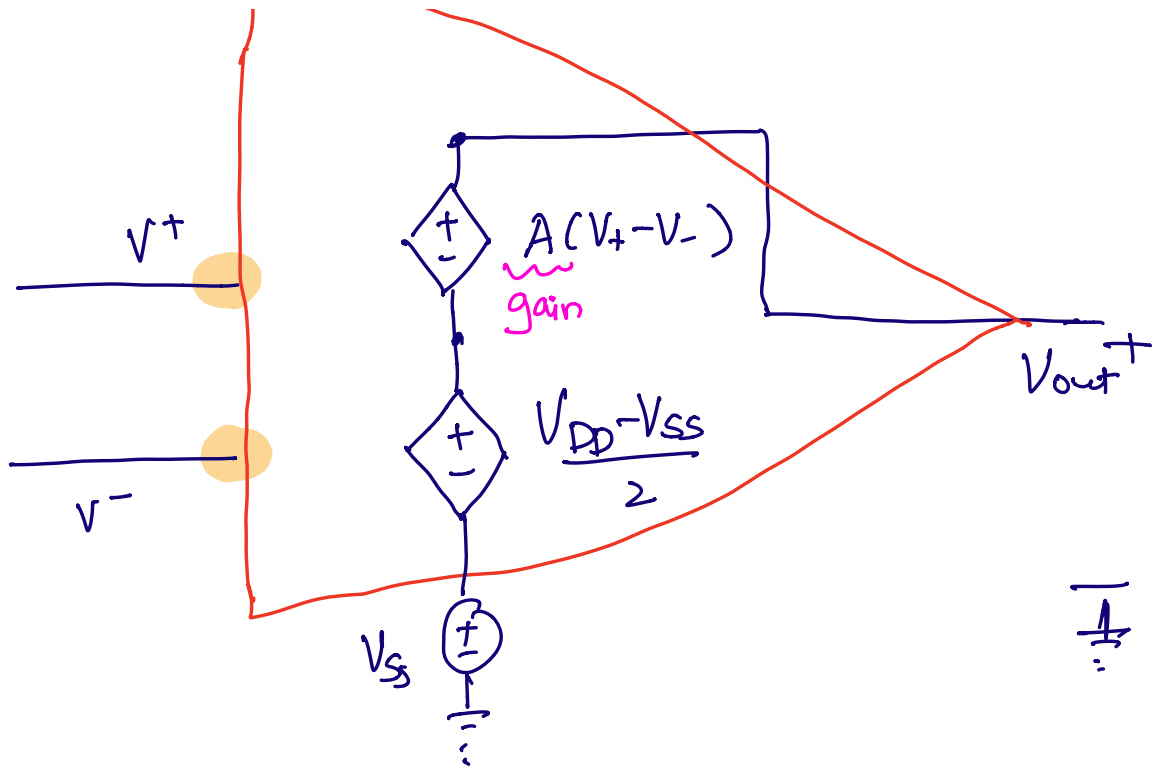

$$V_{out} = V_{SS} + \frac{V_{DD} - V_{SS}}{2} + A(V^+ - V^-)$$


$$= \frac{2V_{SS} + V_{DD} - V_{SS}}{2} + A(V^+ - V^-)$$


$$V_{out} = \frac{V_{DD} + V_{SS}}{2} + A(V^+ - V^-)$$

Caveat - Max value of  $V_{out} = V_{DD}$

Min value of  $V_{out} = V_{SS}$

---

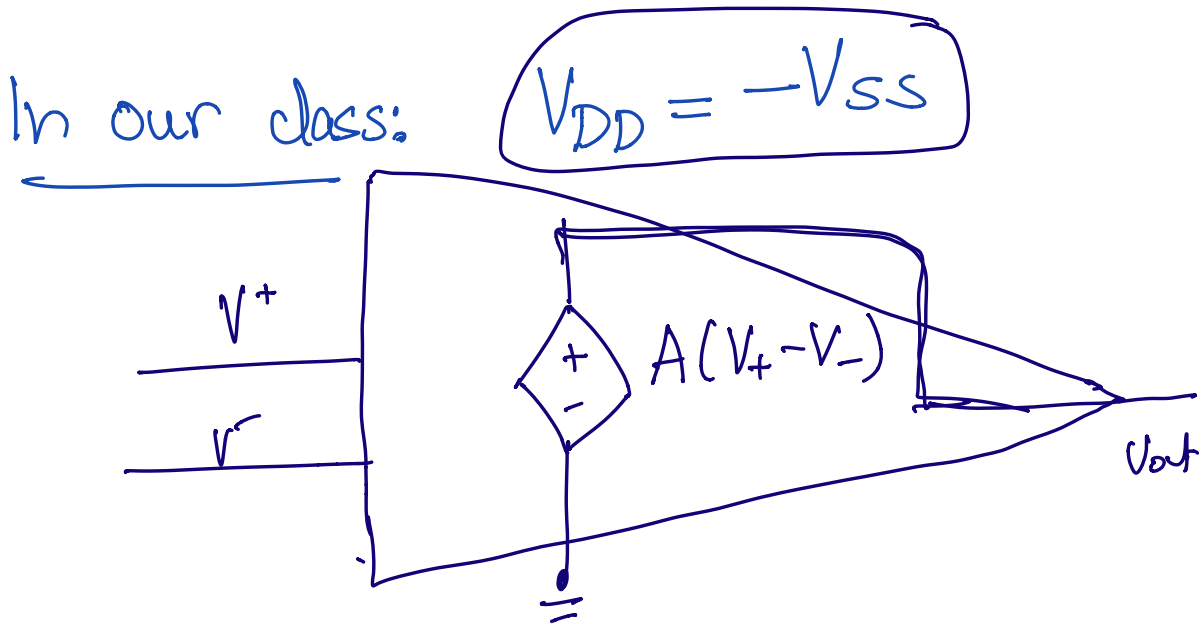
 Voltage  
 :  $\hookrightarrow$  Dependent Voltage source.



$$V_{out} = \frac{V_{DD} + V_{SS}}{2} + A(V^+ - V^-)$$

$$= 0 + \overset{\text{Scalar}}{\downarrow} A(V^+ - V^-)$$

$$V_{out} = \underset{\uparrow \text{Scalar.}}{A}(V^+ - V^-)$$

$$V_{DD} = V_{SS}$$




What happens as  $A \rightarrow \infty$  ?

$$V_{out} = \begin{cases} V_{DD} & \text{if } V_+ > V_- \\ V_{SS} & \text{if } V_- > V_+ \end{cases}$$

Capacitive touchscreen completed with comparator.

Negative feedback

Block diagram:

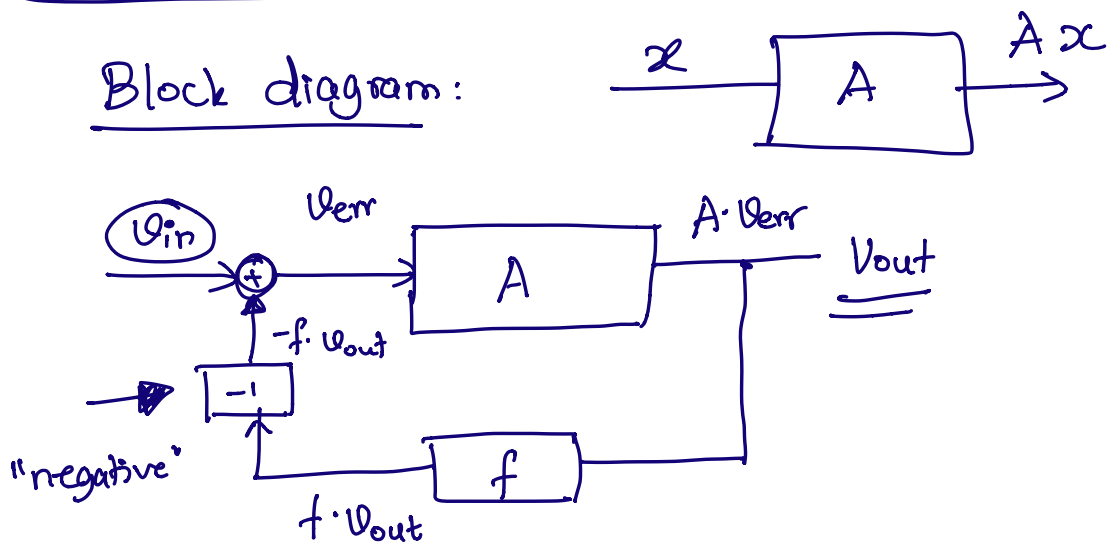

$$\rightarrow V_{out} = A \cdot V_{err}$$

$$\rightarrow V_{err} = V_{in} - f \cdot V_{out}$$

$$\Rightarrow V_{out} = A (V_{in} - f \cdot V_{out})$$

$$\Rightarrow V_{out} + A \cdot f \cdot V_{out} = A \cdot V_{in}$$

$$\Rightarrow \boxed{V_{out} = \frac{A}{1 + Af} \cdot V_{in}}$$

$A \rightarrow$  very large .  $A \rightarrow \infty$

$$\frac{A}{1 + Af} = \frac{A/A}{\frac{1 + Af}{A}} = \frac{1}{\frac{1}{A} + f}$$

$$\lim_{A \rightarrow \infty} \frac{1}{\frac{1}{A} + f} = \frac{1}{f}$$