



**3. Cover Your Basis (7 points)**

Consider the set  $S = \left\{ \left[ \begin{array}{c} \alpha - \beta \\ \alpha + 2\beta \\ -2\alpha + \beta \end{array} \right] \mid \alpha, \beta \in \mathbb{R} \right\}$ . You are told that  $S$ , alongside the traditional vector addition and scalar vector multiplication, constitutes a vector space.

(a) (2 points) **Find a basis** for the vector space  $S$ .

**Solution:**

$$\begin{bmatrix} \alpha - \beta \\ \alpha + 2\beta \\ -2\alpha + \beta \end{bmatrix} = \alpha \begin{bmatrix} 1 \\ 1 \\ -2 \end{bmatrix} + \beta \begin{bmatrix} -1 \\ 2 \\ 1 \end{bmatrix}$$

$$\mathcal{B}_S = \left\{ \begin{bmatrix} 1 \\ 1 \\ -2 \end{bmatrix}, \begin{bmatrix} -1 \\ 2 \\ 1 \end{bmatrix} \right\}$$

(b) (1 point) What is the **dimension** of the vector space  $S$ ?

**Solution:**

$$\dim(S) = 2$$

(c) (4 points) Consider a **new** vector space  $S_{\text{new}} \subset \mathbb{R}^3$  with its basis being the columns of the matrix

$$\mathbf{B} = \begin{bmatrix} -1 & 1 \\ -2 & 1 \\ 1 & -3 \end{bmatrix}.$$

**Write the coordinates** of the vector  $\vec{x} = \begin{bmatrix} 5 \\ 9 \\ -7 \end{bmatrix}$  in the basis  $\mathbf{B}$ . That is, calculate  $[\vec{x}]_{\mathbf{B}}$ .

*Hint:*  $[\vec{x}]_{\mathbf{B}}$  is a vector in  $\mathbb{R}^2$ .

**Solution:**


$$\left[ \begin{array}{cc|c} -1 & 1 & 5 \\ -2 & 1 & 9 \\ 1 & -3 & -7 \end{array} \right] \sim \left[ \begin{array}{cc|c} -1 & 1 & 5 \\ 0 & 1 & 1 \\ 0 & -2 & -2 \end{array} \right] \sim \left[ \begin{array}{cc|c} 1 & 0 & -4 \\ 0 & 1 & 1 \\ 0 & 0 & 0 \end{array} \right]$$

$$[\vec{x}]_{\mathbf{B}} = \begin{bmatrix} -4 \\ 1 \end{bmatrix}$$

PRINT your name and student ID: \_\_\_\_\_

#### 4. Mechanical Circuits (15 points)

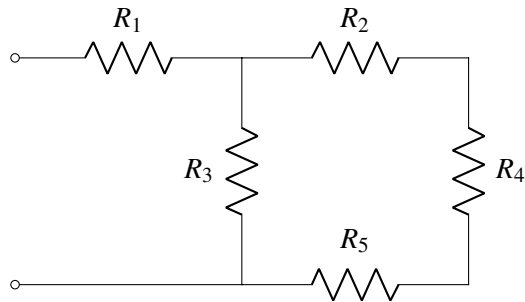- (a) (3 points) Find the equivalent resistance  $R_{eq}$  between the two terminals if  $R_1 = 12.5 \Omega$ ,  $R_2 = 5 \Omega$ ,  $R_3 = 15 \Omega$ ,  $R_4 = 5 \Omega$ , and  $R_5 = 5 \Omega$ .




**Solution:**

$$\begin{aligned} R_{eq} &= R_1 + R_3 \parallel (R_2 + R_4 + R_5) \\ &= 12.5 \Omega + 15 \Omega \parallel 15 \Omega \\ &= 12.5 \Omega + 7.5 \Omega \\ &= 20 \Omega \end{aligned}$$

PRINT your name and student ID: \_\_\_\_\_

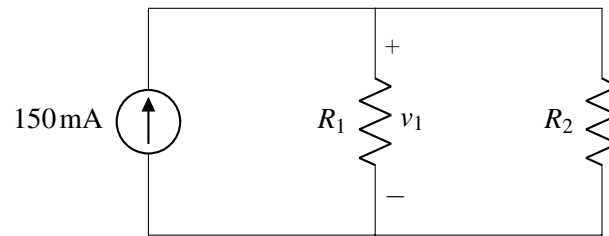(b) (4 points) Consider the following circuit below:



i. Find the voltage  $v_1$  across  $R_1$  if  $R_1 = 10\Omega$  and  $R_2 = 20\Omega$ .

**Solution:**

Using the current divider formula, we get:

$$i_1 = \frac{20\Omega}{10\Omega + 20\Omega} \cdot 150\text{mA} = 100\text{mA}$$

Using Ohm's law, we get:

$$v_1 = 100\text{mA} \cdot 10\Omega = 1\text{V}$$

ii. Calculate the power  $P_1$  dissipated by  $R_1$  if  $R_1 = 10\Omega$  and  $R_2 = 20\Omega$ .


**Solution:**

From part (b)i., we know that  $i_1 = 100\text{mA}$  and that  $v_1 = 1\text{V}$ .


$$P_1 = i_1 v_1 = 100\text{mA} \cdot 1\text{V} = 100\text{mW}$$

PRINT your name and student ID: \_\_\_\_\_

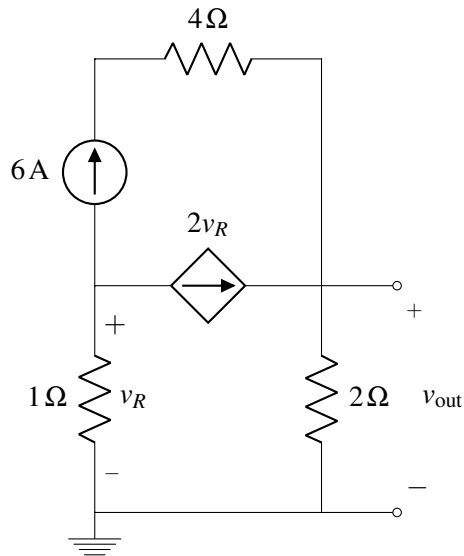(c) (8 points) Use nodal analysis to **find the voltage**  $v_{\text{out}}$  in the following circuit below.



**Solution:**

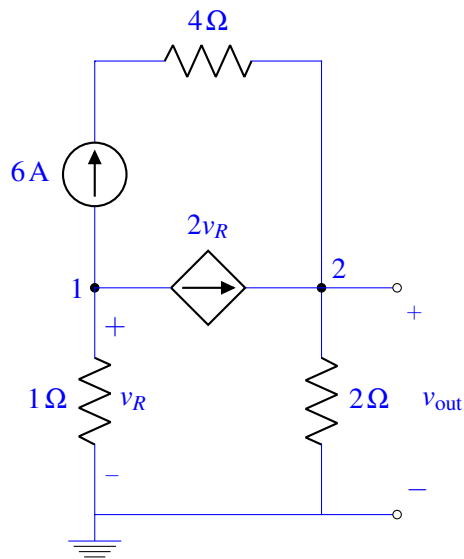

We first apply KCL at node 1.

$$\frac{v_R}{1} + 6 + 2v_R = 0$$
$$3v_R = -6 \implies v_R = -2$$


We then apply KCL at node 2.

$$-6 - 2v_R + \frac{v_{\text{out}}}{2} = 0$$
$$\frac{v_{\text{out}}}{2} = 6 - 4 = 2 \implies v_{\text{out}} = 4 \text{ V}$$

PRINT your name and student ID: \_\_\_\_\_

**5. Taking the Super-L (12 points)**

Consider the following circuit below:

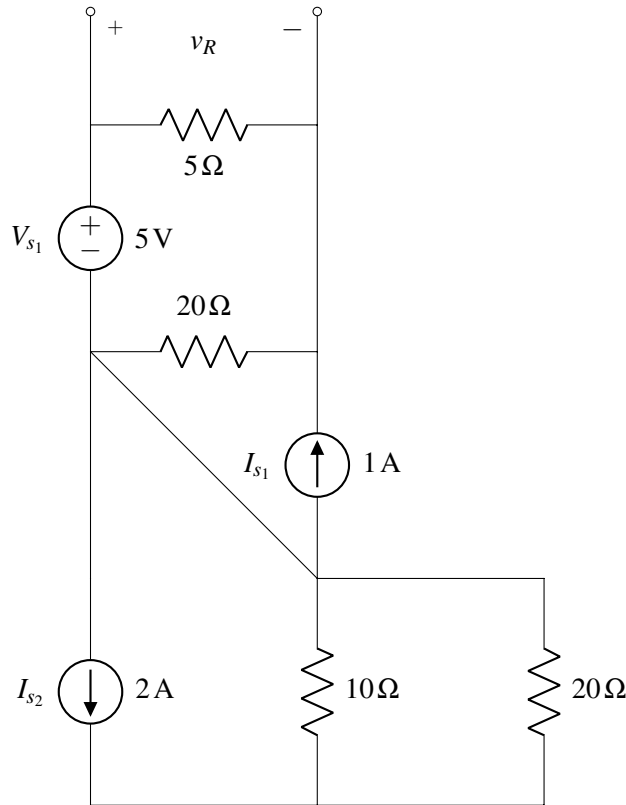


In this problem, you will use *superposition* to find the voltage  $v_R$  across the  $5\ \Omega$  resistor.

- (a) (3 points) First, turn off all sources *except*  $V_{s1}$ . Find  $v_{R1}$ , the voltage across the  $5\ \Omega$  resistor, if all sources *except*  $V_{s1}$  are turned off.

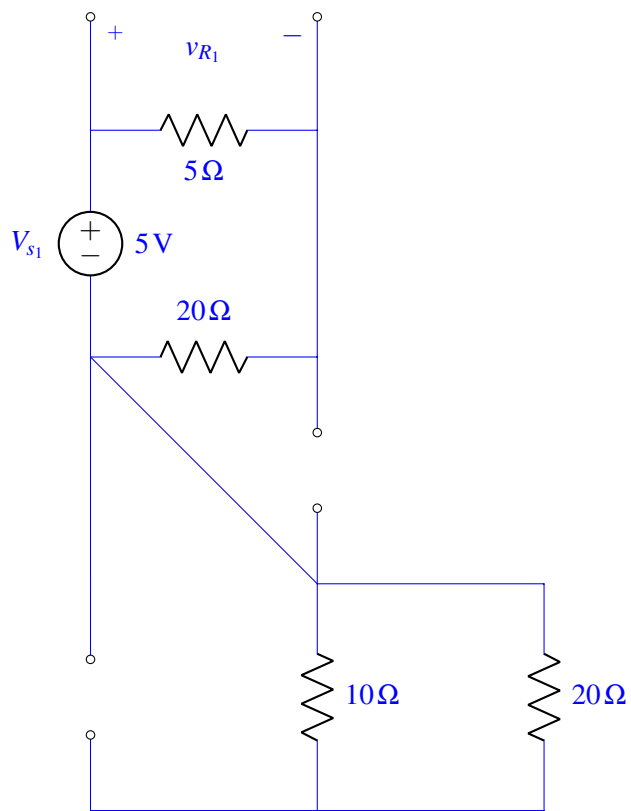**Solution:**


We turn off all sources except  $V_{s1}$  to get the following circuit:



Since the  $5\Omega$  and the  $20\Omega$  resistors are in series, we can use the voltage divider formula to find the voltage  $v_{R1}$  across the  $5\Omega$  resistor.

$$v_{R1} = \frac{5\Omega}{5\Omega + 20\Omega} \cdot 5\text{V} = 1\text{V}$$

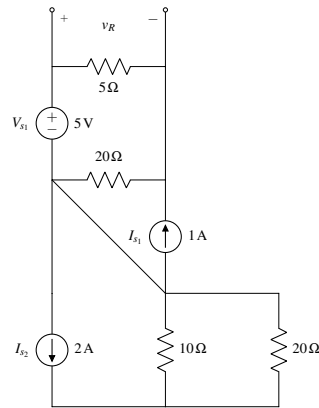PRINT your name and student ID: \_\_\_\_\_




A copy of the circuit for reference:

- (b) (3 points) Now turn off all sources *except*  $I_{s1}$ . Find  $v_{R2}$ , the voltage across the  $5\ \Omega$  resistor, if all sources *except*  $I_{s1}$  are turned off.

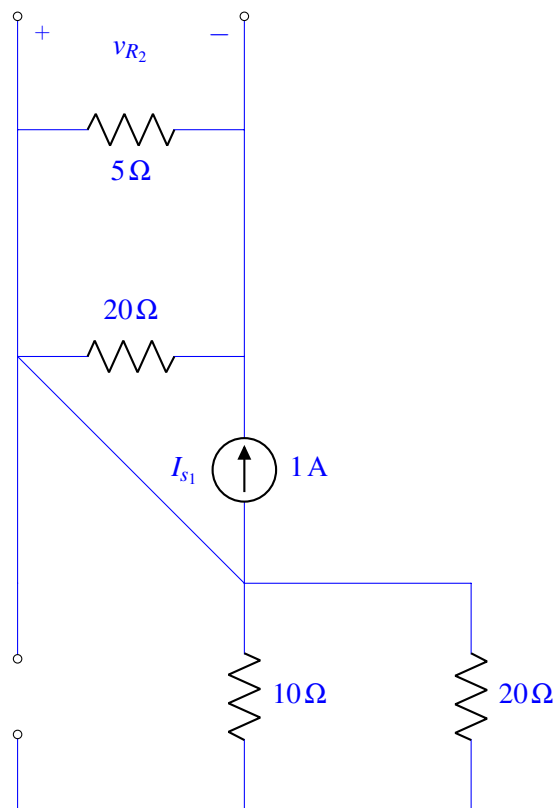**Solution:**

We turn off all sources *except*  $I_{s1}$  to get the following circuit:




Since the  $20\ \Omega$  and the  $5\ \Omega$  resistors are in parallel, we can use the current divider formula to find the current  $i_{R2}$  through the  $5\ \Omega$  resistor.

$$i_{R2} = -\frac{20\ \Omega}{20\ \Omega + 5\ \Omega} \cdot 1\ \text{A} = -0.8\ \text{A}$$

$$v_{R2} = -0.8\ \text{A} \cdot 5\ \Omega = -4\ \text{V}$$



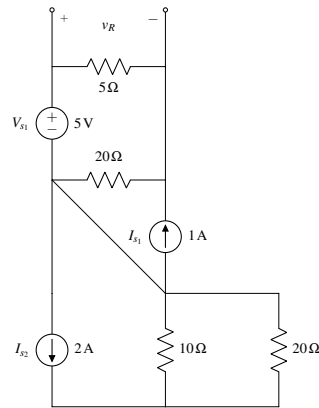PRINT your name and student ID: \_\_\_\_\_




A copy of the circuit for reference:

- (c) (3 points) Now turn off all sources *except*  $I_{s2}$ . Find  $v_{R3}$ , the voltage across the  $5\ \Omega$  resistor, if all sources *except*  $I_{s2}$  are turned off.

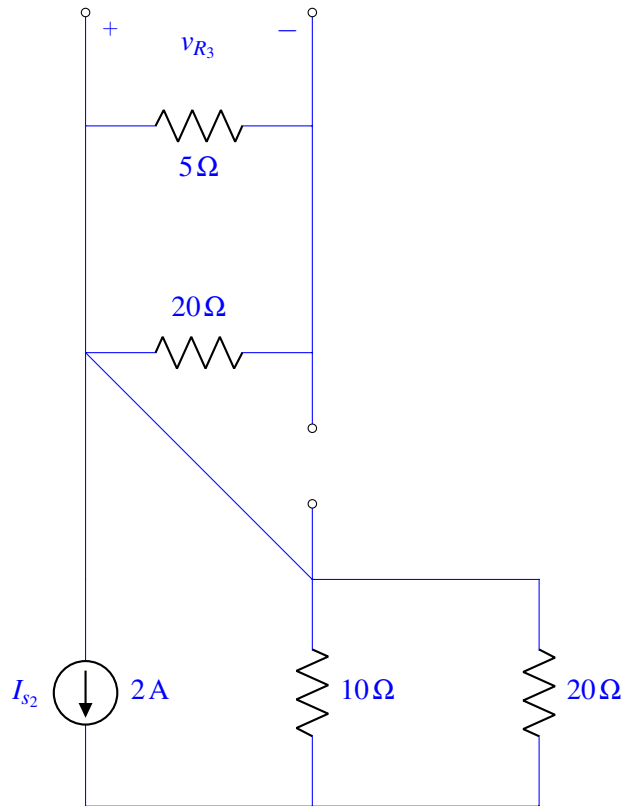**Solution:**

We turn off all sources except  $I_{s2}$  to get the following circuit:



There is no current flowing through the  $5\ \Omega$  resistor, so  $v_{R3} = 0\ \text{V}$ .

- (d) (3 points) Now **find the voltage**  $v_R$  across the  $5\ \Omega$  resistor if *all sources* are on.


**Solution:**

We add up  $v_{R1}$ ,  $v_{R2}$ , and  $v_{R3}$  to get:

$$v_R = 1\ \text{V} - 4\ \text{V} + 0\ \text{V} = -3\ \text{V}$$

**6. Golden Rules Op-Amps (14 points + 4 BONUS points)**

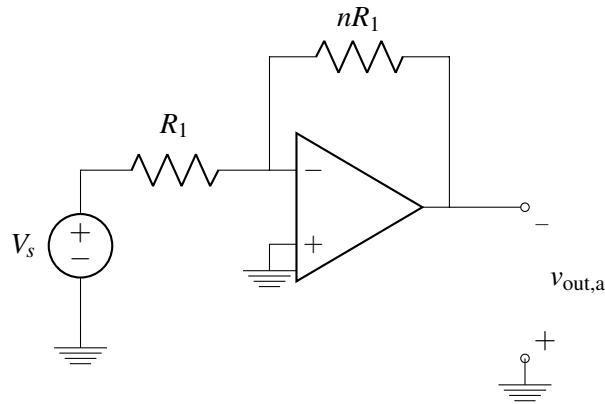
- (a) (2 points) **Find the voltage**  $v_{out,a}$  **as a function of the voltage**  $V_s$  **and**  $n$ . *Use the Golden Rules.*  
**Note:** Pay careful attention to the polarity of the voltage  $v_{out,a}$ .



**Solution:**

$$v_{out,a} = \frac{nR_1}{R_1} \cdot V_s = nV_s$$

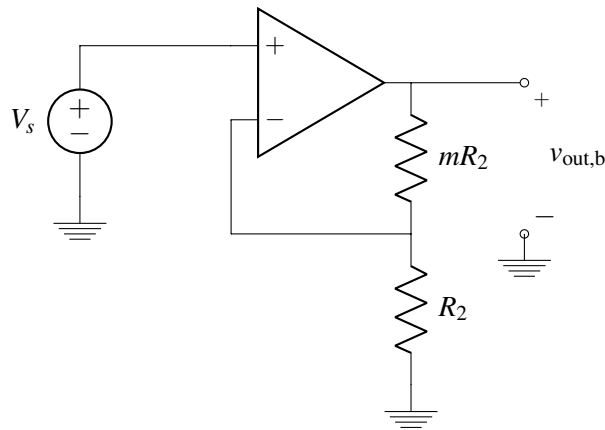- (b) (2 points) **Find the voltage**  $v_{out,b}$  **as a function of the voltage**  $V_s$  **and**  $m$ . *Use the Golden Rules.*




**Solution:**

$$v_{out,b} = \left(1 + \frac{mR_2}{R_2}\right) \cdot V_s = (1 + m)V_s$$

PRINT your name and student ID: \_\_\_\_\_

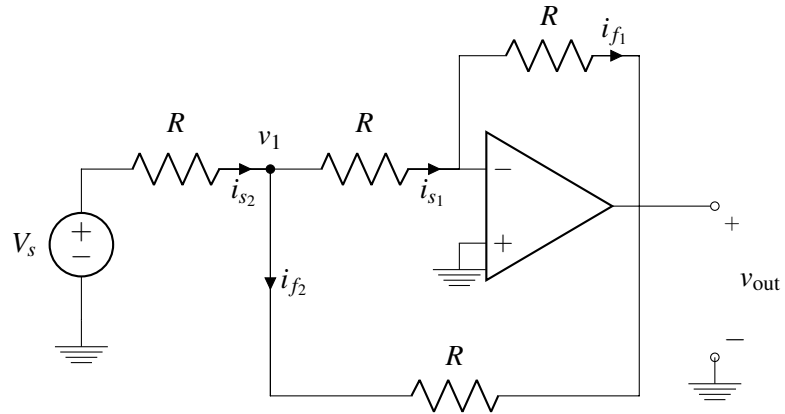(c) (10 points) **Find the currents** labeled  $i_{s1}$ ,  $i_{f1}$ ,  $i_{f2}$ , and  $i_{s2}$ , **and the voltage**  $v_{out}$ , as a function of the voltage at the node  $v_1$  **only**, **NOT** the source voltage  $V_s$ . Assume that the resistance  $R = 1\Omega$ . Show your work in the subsections provided and fill in the table at the end with your results. *Use the Golden Rules.*



i. Find  $i_{s1}$  as a function of  $v_1$ .

**Solution:**

$$i_{s1} = \frac{v_1 - 0}{R} = v_1$$

ii. Find  $i_{f1}$  as a function of  $v_1$ .

**Solution:**

$$i_{f1} = i_{s1} = v_1$$

iii. Find  $v_{out}$  as a function of  $v_1$ .

**Solution:**

$$v_{out} = 0 - i_{f1}R = -v_1$$

iv. Find  $i_{f2}$  as a function of  $v_1$ .

**Solution:**

$$i_{f2} = \frac{v_1 - v_{out}}{R} = 2v_1$$

v. Find  $i_{s2}$  as a function of  $v_1$ .

**Solution:**

$$i_{s2} = i_{s1} + i_{f2} = 3v_1$$

$i_{s1}$	$i_{f1}$	$v_{out}$	$i_{f2}$	$i_{s2}$


**Solution:**

$i_{s1}$	$i_{f1}$	$v_{out}$	$i_{f2}$	$i_{s2}$
$v_1$	$v_1$	$-v_1$	$2v_1$	$3v_1$

PRINT your name and student ID: \_\_\_\_\_

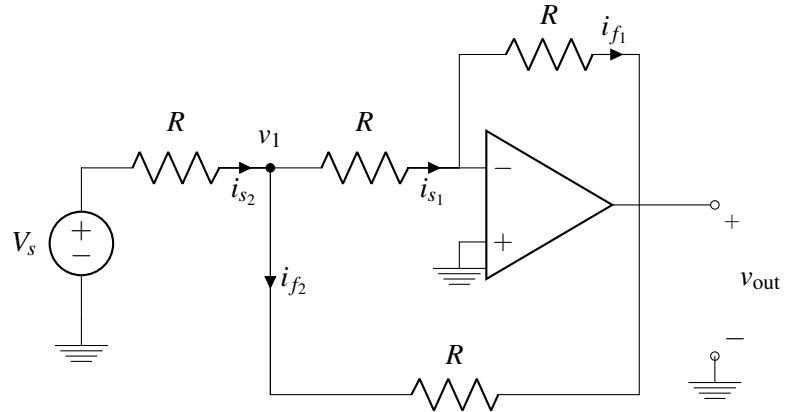- (d) (4 **BONUS** points) In the circuit, find  $v_{\text{out}}$  as a function of  $V_s$ . Assume that the resistance  $R = 1\ \Omega$ . Use the Golden Rules.

*Hint:* This is the same circuit as in part (c). You may want to use your results from part (c).



**Solution:**

From part (c), we know that  $i_{s2} = 3v_1$ . Using Ohm's law, we get:

$$\frac{V_s - v_1}{R} = 3v_1 \implies V_s - v_1 = 3v_1 \implies V_s = 4v_1$$

Furthermore, we know that  $v_{\text{out}} = -v_1$ .

$$V_s = 4v_1 = -4v_{\text{out}} \implies v_{\text{out}} = -\frac{V_s}{4}$$

**7. Thévenin Rhymes with Almost Nothing (14 points)**

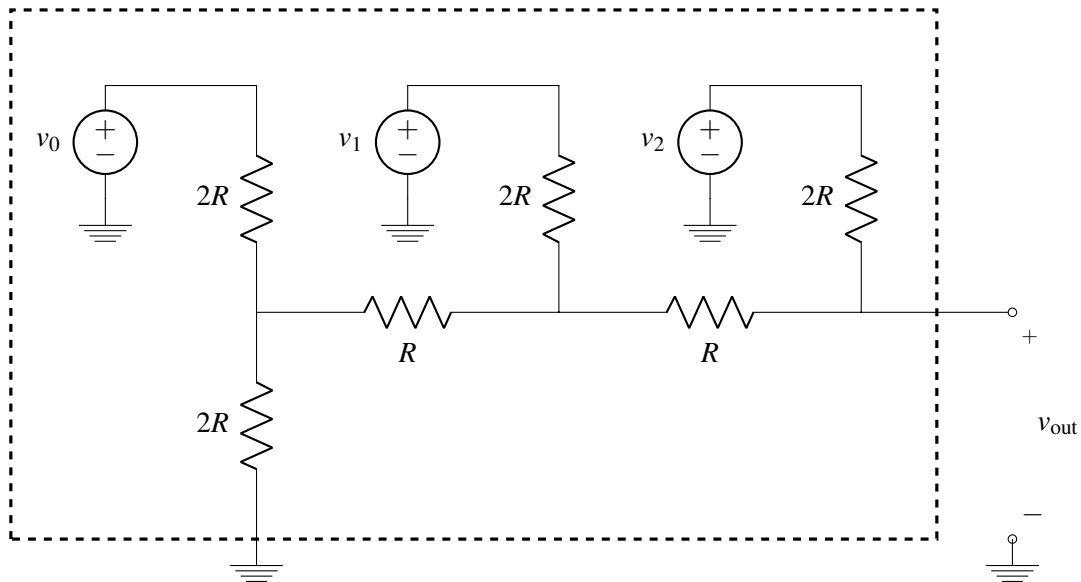



Figure 7.1: Three stage resistor ladder.


- (a) (4 points) This circuit has three sources  $v_0$ ,  $v_1$ , and  $v_2$  connected to a resistor network. What is the **Thévenin equivalent resistance**  $R_{th}$  of this circuit at the terminals labeled  $v_{out}$ ?

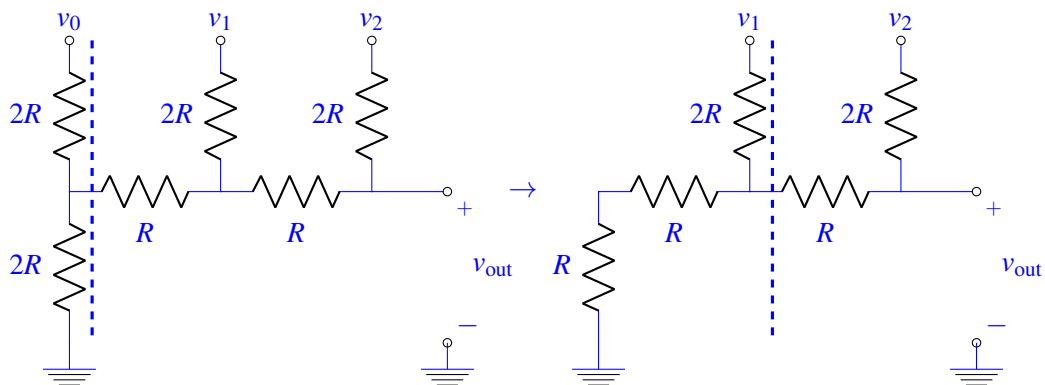**Solution:**


$$R_{th} = R$$

We can see this by redrawing the circuit and noting that at each rung of the ladder, there is a resistance of  $1R$  looking left. Simplifying the circuit, rung by rung, eventually leads to the Thévenin equivalent resistance equal to  $R$  at the output.



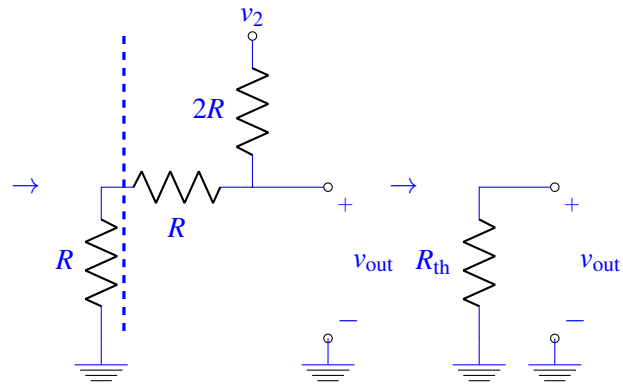

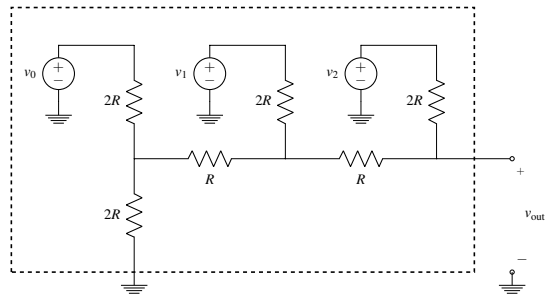PRINT your name and student ID: \_\_\_\_\_



A copy of the circuit for reference:


(b) (4 points) Find the **Thévenin equivalent voltage** ( $V_{th} = v_{out}$ ) of this circuit at the terminals labeled  $v_{out}$ . You are given the following information:

- i. The output voltage when  $v_0$  is **on** and *all other sources* are off is  $\frac{v_0}{8}$ .
- ii. The output voltage when  $v_1$  is **on** and *all other sources* are off is  $\frac{v_1}{4}$ .

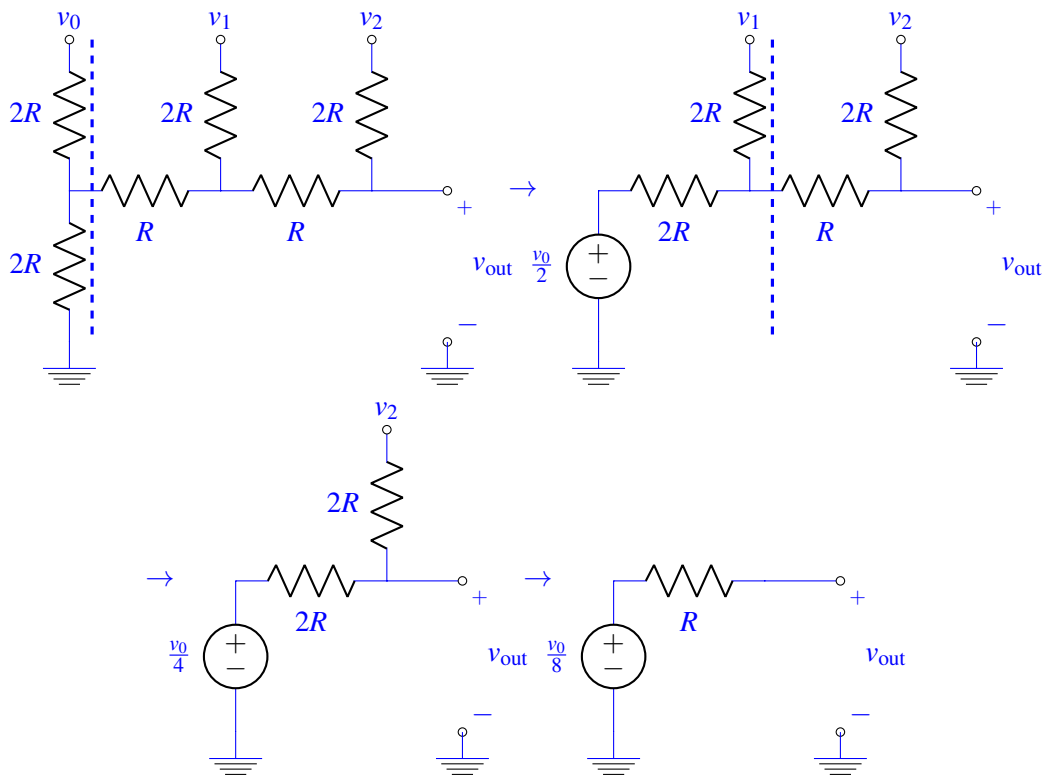**Solution:**

By a similar strategy to the solution to part (a), we can redraw the circuit and note that at each rung of the ladder, there is a resistance of  $1R$  looking left. Simplifying the circuit, rung by rung, eventually leads to the Thévenin equivalent voltage, for example, of source  $v_0$ . Likewise, by superposition we can add the voltage contributed by  $v_1$  and  $v_2$ :

$$V_{th} = \frac{v_0}{8} + \frac{v_1}{4} + \frac{v_2}{2}$$





PRINT your name and student ID: \_\_\_\_\_

- (c) (6 points) Now consider the case when we attach a resistor with resistance  $3R$  to the output of our circuit. We set the voltage inputs so that  $v_0 = 8V_{DD}$ ,  $v_1 = 4V_{DD}$ , and  $v_2 = 2V_{DD}$ . Calculate the current  $i_{out}$  through the load resistor as a function of  $V_{DD}$  and  $R$ .

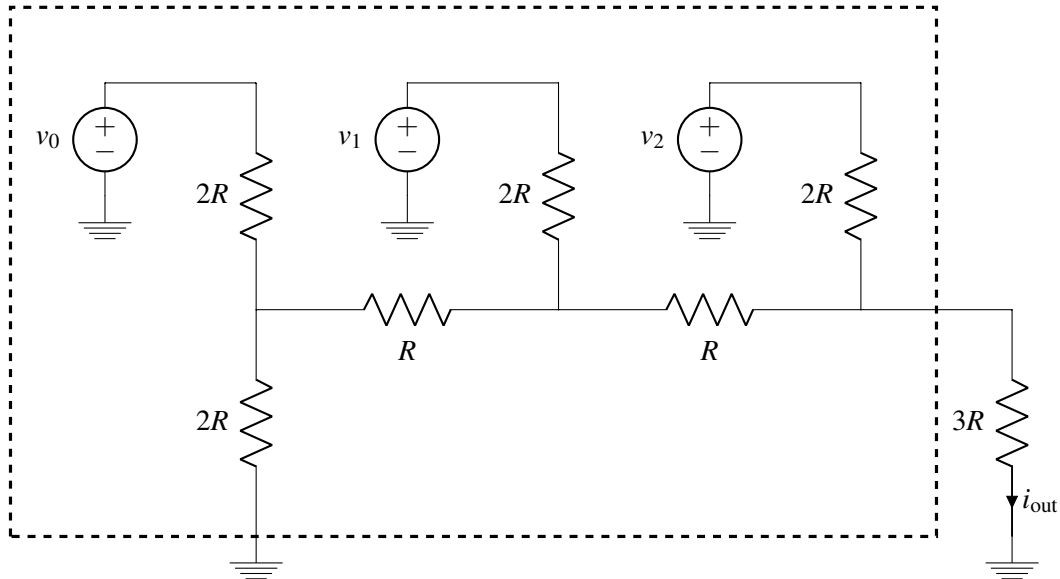


Figure 7.2: Loaded resistor ladder.

**Solution:**

Using the Thévenin equivalent calculated in part (a) and (b), we see that we can calculate the current using the sum of  $3R$  and the equivalent resistance  $R$ .

$$V_{th} = \frac{v_0}{8} + \frac{v_1}{4} + \frac{v_2}{2} = \frac{8V_{DD}}{8} + \frac{4V_{DD}}{4} + \frac{2V_{DD}}{2} = 3V_{DD}$$
$$i_{out} = \frac{V_{th}}{4R} = \frac{3}{4} \frac{V_{DD}}{R}$$

### 8. CompanEE-16A's Microcontroller (18 points)

A company in Berkeley called CompanEE-16A designs and manufactures microcontrollers for electrical engineers and hobbyists around the world. Their current microcontroller model, Version 1.6.A, is poorly documented. It's your job to find out how the microcontroller's pins behave when circuits are attached to them.


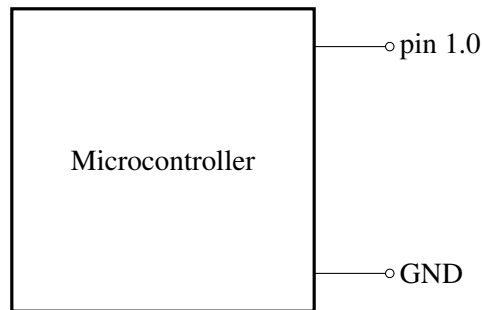


Figure 8.1: Microcontroller black box.

- (a) (4 points) First off, you need to find an *equivalent circuit* for the microcontroller's output pins. You have access to a voltmeter (an open circuit that measures the voltage across its terminals) and an ammeter (a short circuit that measures the current through it). You also have a voltage source that displays the current that it is supplying.
- Describe qualitatively how you would find the Thévenin equivalent voltage between pin 1.0 and GND.

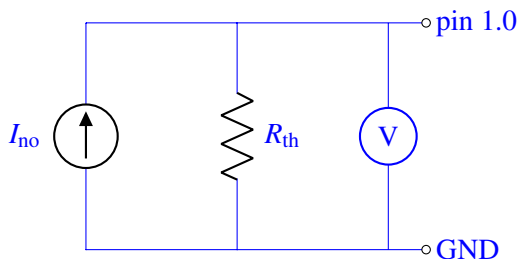**Solution:**


Measure the voltage across pin 1.0 and GND with the voltmeter.



- Describe qualitatively how you would find the Norton equivalent current between pin 1.0 and GND.

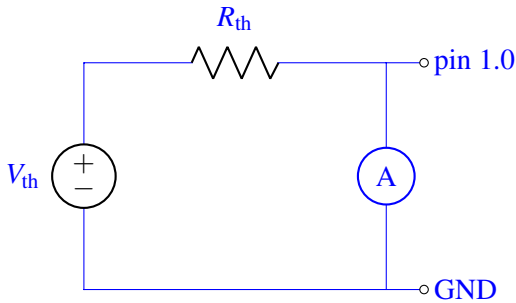**Solution:**

Measure the current across pin 1.0 and GND with the ammeter.



iii. Using these results  $V_{th}$  and  $I_{no}$ , and assuming that  $V_{th} \neq 0$  and  $I_{no} \neq 0$ , write the expression that you would use to calculate the equivalent resistance between pin 1.0 and GND.

**Solution:**

Divide  $V_{th}$  by  $I_{no}$ .

iv. Suppose that you measured  $V_{th} = 0V$  and  $I_{no} = 0A$ , describe what you would need to do to find the equivalent resistance.

**Solution:**

Apply the voltage source, measure the current, and divide the two results to find the equivalent resistance.

(b) (4 points) After taking the appropriate measurements using the methods in part (a), you find that  $V_{\text{voltmeter}} = 4V$  and  $I_{\text{ammeter}} = 2mA$ . Calculate  $V_{th}$ ,  $R_{th}$ ,  $R_{no}$ , and  $I_{no}$ .

i.  $V_{th}$

**Solution:**

$$V_{th} = 4V$$

ii.  $I_{no}$

**Solution:**

$$I_{no} = 2mA$$

iii.  $R_{th}$

**Solution:**

$$R_{th} = \frac{4V}{2mA} = 2k\Omega$$


iv.  $R_{no}$

**Solution:**

$$R_{no} = \frac{4V}{2mA} = 2k\Omega$$

PRINT your name and student ID: \_\_\_\_\_

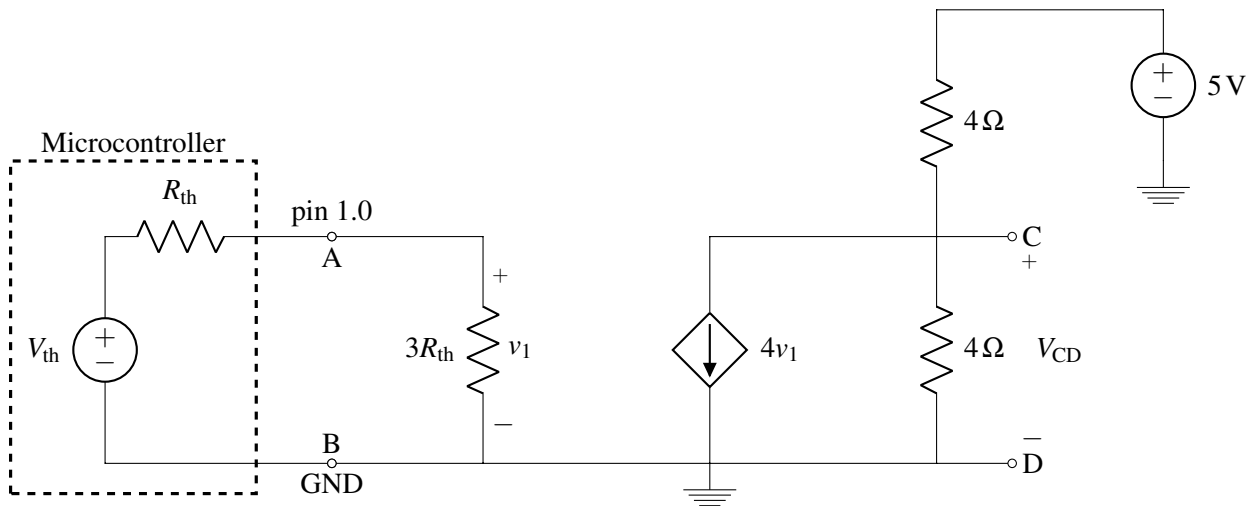- (c) (10 points) CompanEE-16A is so pleased with your work that they give you a Version 1.6.A microcontroller for free! Your friend saw your free microcontroller lying on your desk and thought that it was really interesting. He had been working on a mysterious circuit (shown below) for EE105 and wants to connect it onto your board. You connect terminal A of the mysterious circuit to pin 1.0 of the microcontroller and terminal B of the circuit to GND (shown below). **Find the voltage  $V_{CD}$**  between terminals C and D in terms of  $V_{th}$ .



**Solution:**

$$v_1 = \frac{3R_{th}}{3R_{th} + R_{th}} \cdot V_{th} = \frac{3}{4}V_{th}$$

Using KCL at node C, we get:

$$\frac{5V - V_{CD}}{4} = \frac{V_{CD}}{4} + 4v_1$$

$$5V - V_{CD} = V_{CD} + 16v_1$$


$$V_{CD} = \frac{5V - 16v_1}{2} = \frac{5V - 16 \cdot \frac{3}{4}V_{th}}{2} = \frac{5}{2}V - 6V_{th}$$

PRINT your name and student ID: \_\_\_\_\_

### 9. Touchy Currents (10 points)

In the capacitive touchscreen lab, you learned how a voltage source and a comparator can be used to determine whether a finger is touching a capacitive touchscreen. In this problem, you will explore how a current source can be used to detect touch.

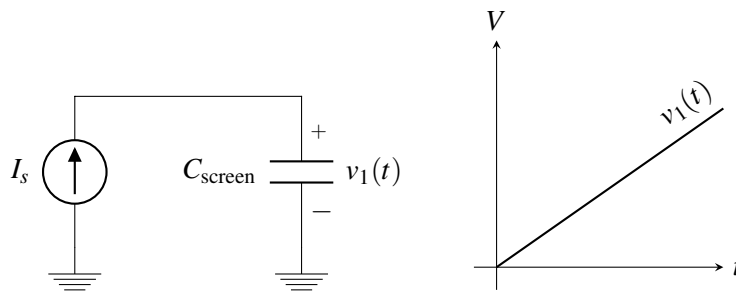- (a) (4 points) The capacitor  $C_{\text{screen}}$  is connected to a current source with a constant value  $I_s$  as shown in the circuit below. The capacitor is initially uncharged. At time  $t = 0$ , the current source switches on. For time  $t \geq 0$ , the plot of the capacitor voltage  $v_1(t)$  is a line. **Find the slope** of this line in terms of  $I_s$  and  $C_{\text{screen}}$ .




**Solution:**


$$I_s = C_{\text{screen}} \frac{dv_1(t)}{dt}$$
$$\frac{dv_1(t)}{dt} = \frac{I_s}{C_{\text{screen}}}$$

PRINT your name and student ID: \_\_\_\_\_

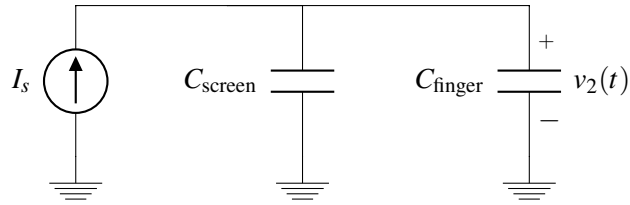- (b) (2 points) Suppose that instead, at time  $t < 0$ , a capacitor  $C_{\text{finger}} > 0$  is placed in parallel with  $C_{\text{screen}}$  as shown in the circuit below. Both capacitors are initially uncharged. At time  $t = 0$ s, the current source switches on.




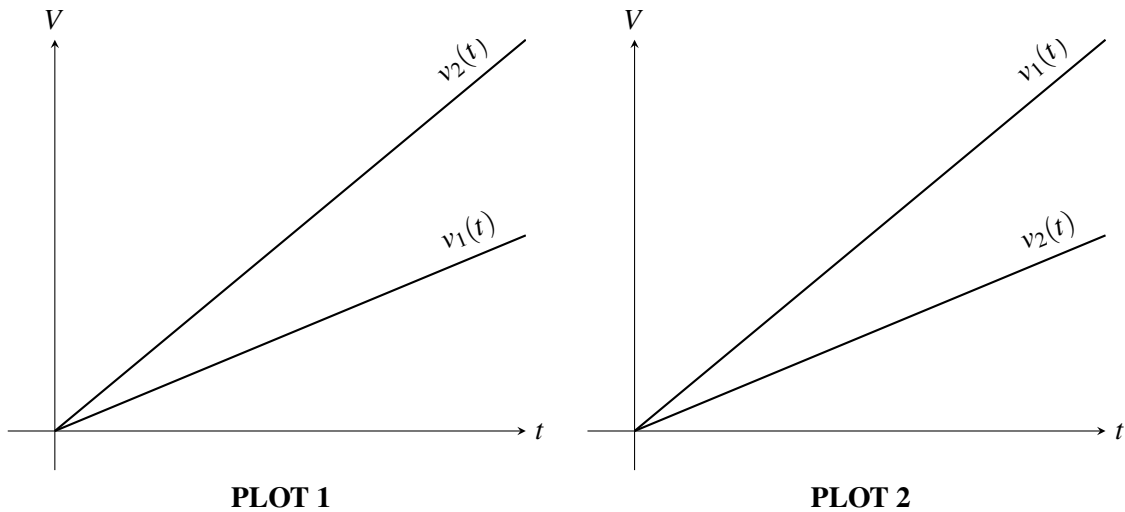Circle the correct plot of  $v_1(t)$  and  $v_2(t)$ , where  $v_1(t)$  is the voltage over time when there is no touch and  $v_2(t)$  is the voltage over time when there is touch. If the capacitive touch screen is being touched, it is being touched for the entire duration shown in the plot.



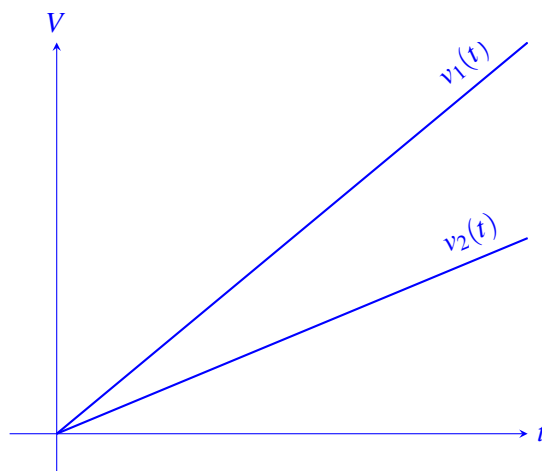
**Solution:**

The slope of  $v_2(t)$  should be smaller than the slope of  $v_1(t)$ .




PRINT your name and student ID: \_\_\_\_\_

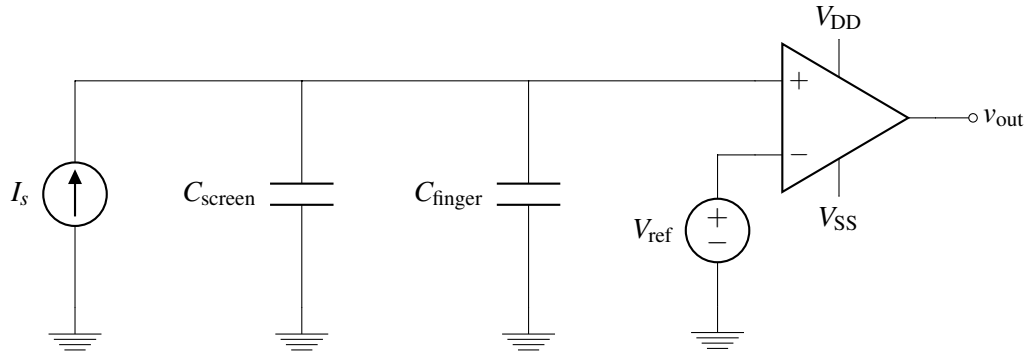(c) (4 points) You connect the circuit to a comparator, as shown here:




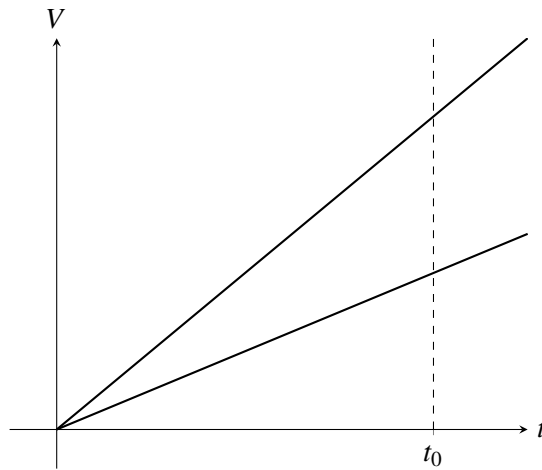On the following set of axes, **label the lines**  $v_1(t)$  and  $v_2(t)$  corresponding to the plot you chose in part (b) and **draw a horizontal line** that represents an appropriate reference voltage  $V_{ref}$  that could be used to detect the presence of a touch at a time  $t = t_0$ .



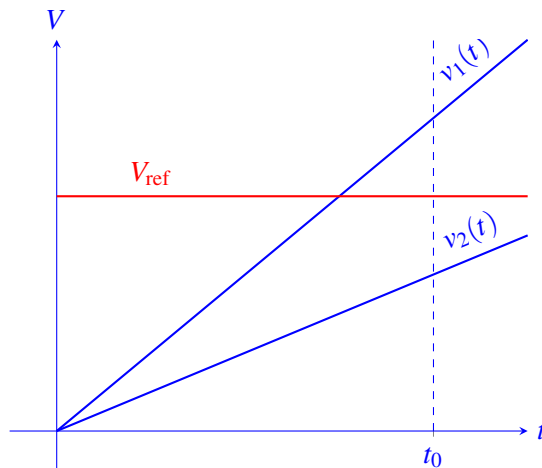**Solution:**


Any horizontal line between  $v_1(t_0)$  and  $v_2(t_0)$  for  $V_{ref}$  is acceptable.



**10. Sorry, I don't make puns free of charge. (22 points)**

Because of size constraints in modern semiconductor processes, circuit designers often use switches and capacitors instead of resistors to perform certain functions. We will investigate how charge sharing can be used to replace standard resistive circuits. In all parts of this question, assume that there is no leakage and that the capacitors reach steady state in each phase.

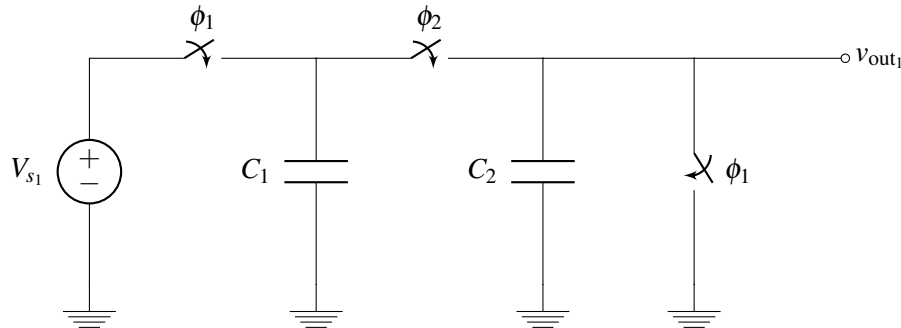(a) (4 points) Consider the following two-phase circuit switched capacitor circuit:



In phase  $\phi_1$ , find the **voltage across** and the **charge on** each capacitor  $C_1$  and  $C_2$  in terms of the input source voltage  $V_{s1}$  and the capacitances  $C_1$  and  $C_2$ .

**Solution:**

In phase  $\phi_1$ , the only capacitor connected to  $V_{s1}$  is  $C_1$ . At steady state, its voltage will be equal to  $V_{s1}$ , and its charge will be related to its capacitance  $C_1$ :

$$v_{C_1, \phi_1} = V_{s1} \quad Q_{C_1, \phi_1} = C_1 V_{s1}$$

In phase  $\phi_1$ , both of the plates of  $C_2$  are connected to ground, so:

$$v_{C_2, \phi_1} = 0 \quad Q_{C_2, \phi_1} = 0$$

(b) (4 points) Now the switches change state, and we look at what happens in phase  $\phi_2$ . Calculate the **voltage across** both capacitors  $C_1$  and  $C_2$  in terms of the input source voltage  $V_{s1}$  and the capacitances  $C_1$  and  $C_2$ .

**Solution:**

After switching from phase  $\phi_1$  to phase  $\phi_2$ , there is no additional charge added to the system, so the total charge from phase  $\phi_1$  must equal the total charge in phase  $\phi_2$ . More specifically, we can describe this using our result from part (a):

$$Q_{\phi_1} = Q_{\phi_2} \implies Q_{\phi_2} = C_1 V_{s1}$$

Since we know that charge is conserved, we can express our total charge in phase  $\phi_2$   $Q_{\phi_2}$  as a sum of the charges on each capacitor, giving us:

$$Q_{\phi_2} = Q_{C_1, \phi_2} + Q_{C_2, \phi_2}$$




We know that  $C_1$  and  $C_2$  are in parallel, so the voltage across  $C_1$  and  $C_2$  is equal to  $v_{out_1}$ .

$$Q_{\phi_2} = C_1 v_{out_1} + C_2 v_{out_1}$$

Substituting our previous expression  $Q_{\phi_2} = C_1 V_{s_1}$  into our equation, we can solve for the voltage across each capacitor.

$$C_1 V_{s_1} = C_1 v_{out_1} + C_2 v_{out_1} \implies v_{out_1} = v_{C_1, \phi_2} = v_{C_2, \phi_2} = \frac{C_1 V_{s_1}}{C_1 + C_2}$$

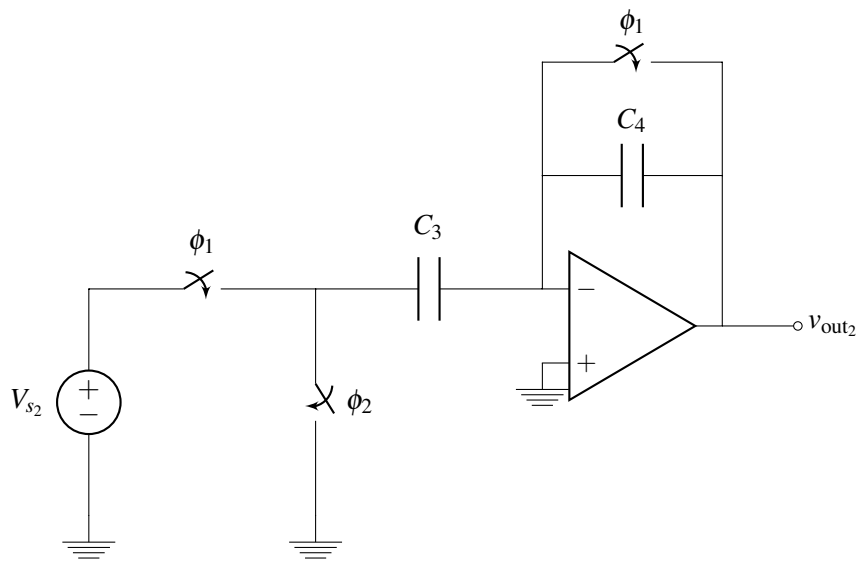- (c) (4 points) In the following circuit, first, all switches labeled  $\phi_1$  are closed, and all switches labeled  $\phi_2$  are opened. Some time after the circuit reaches steady state, all switches labeled  $\phi_2$  are closed, and all switches labeled  $\phi_1$  are opened. **Find the voltage**  $v_{out_2}$  **at steady state only in the second phase**  $\phi_2$  as a function of the input source voltage  $V_{s_2}$  and the capacitances  $C_3$  and  $C_4$ .



**Solution:**

In phase  $\phi_1$ ,  $C_3$  is connected to  $V_{s_2}$ , so its voltage will be equal to  $V_{s_2}$ , and its charge will be equal to  $Q_{C_3, \phi_1} = C_3 V_{s_2}$ .  $C_4$  is shorted, so its charge will be equal to  $Q_{C_4, \phi_1} = 0$ .


In phase  $\phi_2$ , both plates of  $C_3$  are connected to ground, so its voltage is zero. Therefore,  $Q_{C_3, \phi_2} = 0$ .

However, since charge is conserved, all of the negative charges on the right plate of  $C_3$  must have been transferred to the left plate of  $C_4$  in phase  $\phi_2$ . Therefore,

$$Q_{C_4, \phi_2} = Q_{C_3, \phi_1} = C_3 V_{s_2} \implies v_{out_2} = \frac{Q_{C_4, \phi_2}}{C_4} = \frac{C_3 V_{s_2}}{C_4}$$

PRINT your name and student ID: \_\_\_\_\_

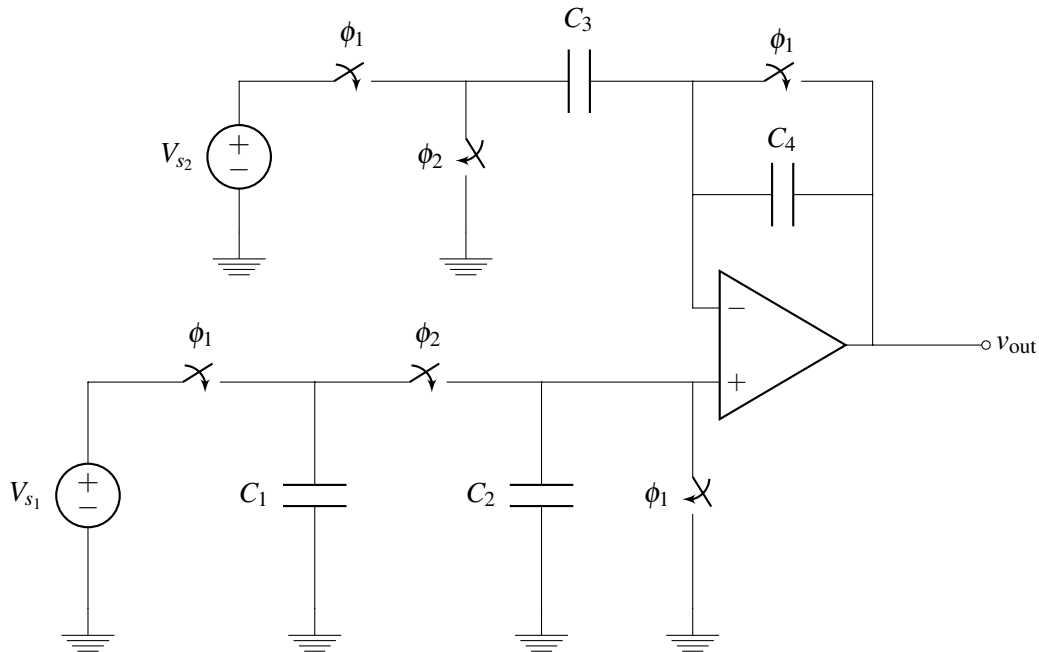- (d) (10 points) Now we combine both of the previous circuits into one. First, all switches labeled  $\phi_1$  are closed, and all switches labeled  $\phi_2$  are opened. Some time after the circuit reaches steady state, all switches labeled  $\phi_2$  are closed, and all switches labeled  $\phi_1$  are opened. **Find the voltage**  $v_{\text{out}}$  at steady state **only in the second phase**  $\phi_2$  as a function of the input source voltages  $V_{s_1}$  and  $V_{s_2}$  and the capacitances  $C_1$ ,  $C_2$ ,  $C_3$ , and  $C_4$ .



**Solution:**

In phase  $\phi_1$ , we know from part (c) that  $Q_{3,\phi_1} = C_3 V_{s_2}$ . Using the sign convention for  $C_3$  and  $C_4$  that the plates connected to the negative terminal of the op-amp are negative, we get  $Q_{3,\phi_1} = Q_{3,\phi_2} + Q_{4,\phi_2}$  since charge is conserved.

In phase  $\phi_2$ , we know from part (b) that  $V^+ = \frac{C_1 V_{s_1}}{C_1 + C_2}$ . Applying the Golden Rules, we know that  $V^- = \frac{C_1 V_{s_1}}{C_1 + C_2}$ .

$$Q_{3,\phi_2} = C_3(0 - V^-) = C_3 \left( 0 - \frac{C_1 V_{s_1}}{C_1 + C_2} \right)$$

$$Q_{4,\phi_2} = C_4(v_{\text{out}} - V^-) = C_4 \left( v_{\text{out}} - \frac{C_1 V_{s_1}}{C_1 + C_2} \right)$$

$$Q_{3,\phi_1} = Q_{3,\phi_2} + Q_{4,\phi_2}$$

$$C_3 V_{s_2} = C_3 \left( 0 - \frac{C_1 V_{s_1}}{C_1 + C_2} \right) + C_4 \left( v_{\text{out}} - \frac{C_1 V_{s_1}}{C_1 + C_2} \right)$$

$$C_3 V_{s_2} + (C_3 + C_4) \frac{C_1 V_{s_1}}{C_1 + C_2} = C_4 v_{\text{out}}$$

$$v_{\text{out}} = \frac{C_3 V_{s_2}}{C_4} + \left( 1 + \frac{C_3}{C_4} \right) \frac{C_1 V_{s_1}}{C_1 + C_2}$$

PRINT your name and student ID: \_\_\_\_\_

Extra page for scratchwork.

If you want any work on this page to be graded, please refer to this page on the problem's main page.