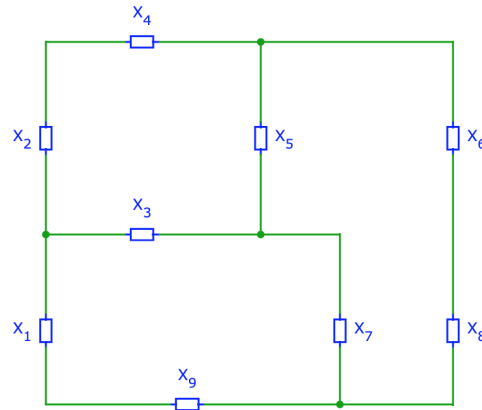


# EECS 16A    Designing Information Devices and Systems I

## Fall 2021    Discussion 5A

### 1. Label the circuit

In the circuit shown below, label all the nodes, and show one possible way of labeling all the element voltages and currents following the passive sign convention.



**Solution/Answer:** There are seven nodes.

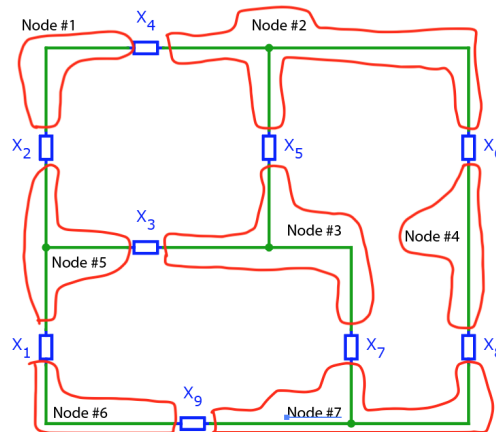


Figure 1: Labeled Nodes

Here is an example of the element voltages and currents. Note that this is not a unique solution, and any labeling following the passive sign convention is correct.


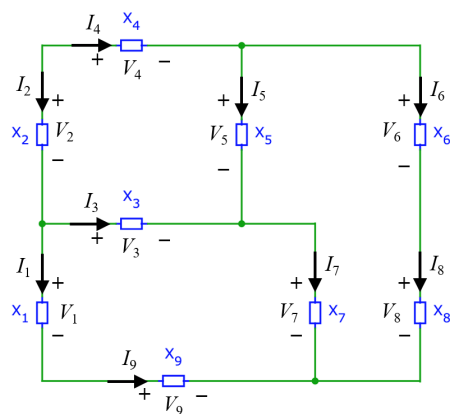


Figure 2: Labeled element voltages and currents
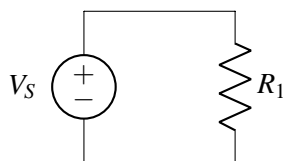
## 2. A Simple Circuit


For the circuit shown below, find the voltages across all the elements and the currents through all the elements.



- (a) In the above circuit, pick a ground node. Does your choice of ground affect the voltage across and the current through elements?

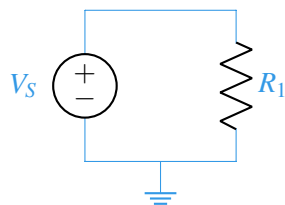**Solution/Answer:**


There are two nodes in this circuit and thus two choices for the ground node. The choice of ground does not matter. We will use the ground node shown below:



- (b) With your choice of ground, label the node potentials for every node in the circuit.

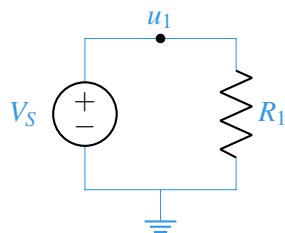**Solution/Answer:**


Since this circuit only has two nodes, there will only be one additional node potential.



- (c) Label all of the branch currents. Does the direction you pick matter?

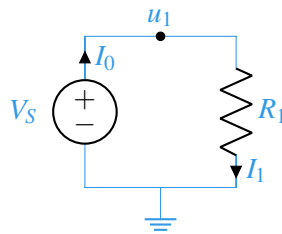**Solution/Answer:**


When labeling the currents through branches, the direction you pick does not matter.



- (d) Draw the  $+/-$  labels on every element. What convention must you follow?

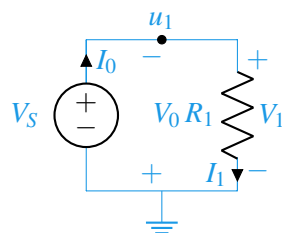**Answer:**

When drawing the  $+/-$  labels, you must follow the passive sign convention. That is, current flows into the  $+$  terminal of every element.



- (e) Use KCL to find an equation for the unknown currents.

**Solution/Answer:**

KCL gives us one equation for the node at the top, namely that  $I_0 - I_1 = 0$ .

- (f) Use KVL and Ohm's law to find two equations for the unknown node potentials and currents.

**Solution/Answer:**

We know that the difference in potentials across the voltage source must be the voltage on the voltage source, i.e.

$$-V_0 = V_S \quad (1)$$

We also know that the voltage across the resistor is equal to the current times the resistance, i.e.

$$V_1 = I_1 R_1 \quad (2)$$

Writing the equations for node potentials we have:

$$\begin{aligned} 0 - u_1 &= V_0 \\ u_1 - 0 &= V_1 \end{aligned} \quad (3)$$

Substituting expressions from Equations (1) and (2) into Equation (3), we have:

$$\begin{aligned} -u_1 &= -V_S \implies u_1 = V_S \\ V_1 &= I_1 R_1 \implies -I_1 R_1 + u_1 = 0 \end{aligned} \quad (4)$$


- (g) Solve the system of equations if  $V_S = 5\text{ V}$  and  $R_1 = 5\Omega$ .

**Solution/Answer:**

By plugging the given values into the system of equations, we get:  $I_0 = 1\text{ A}$ ,  $I_1 = 1\text{ A}$ ,  $u_1 = 5\text{ V}$ .
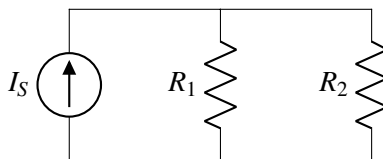
### 3. A Slightly More Complicated Circuit


For the circuit shown below, find the voltages across all the elements and the currents through all the elements.



- (a) In the above circuit, pick a ground node. Does your choice of ground matter?

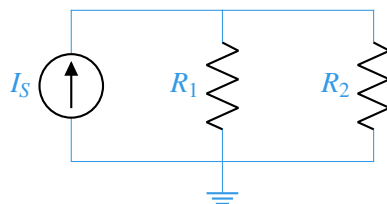**Solution/Answer:**


There are two nodes in this circuit and thus two choices for the ground node. The choice of ground does not matter. We will use the ground node shown below:



- (b) With your choice of ground, label the node potentials for every node in the circuit.

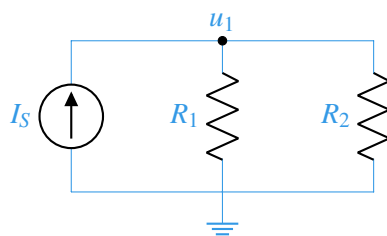**Solution/Answer:**


Since this circuit only has two nodes, there will only be one additional node potential.



- (c) Label all of the branch currents. Does the direction you pick matter?

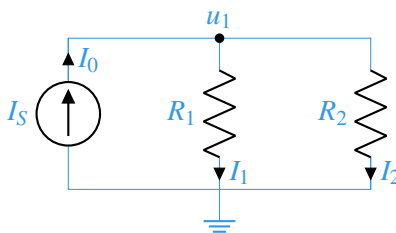**Solution/Answer:**


When labeling the currents through branches, the direction you pick does not matter.



- (d) Draw the  $+/-$  labels on every element. What convention must you follow?

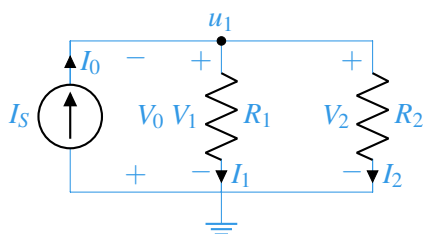**Solution/Answer:**

When drawing the  $+/-$  labels, you must follow the passive sign convention. That is, current flows into the  $+$  terminal of every element.



- (e) Set up a matrix equation in the form  $\mathbf{A}\vec{x} = \vec{b}$  to solve for the unknown node potentials and currents. What are the dimensions of the matrix  $\mathbf{A}$ ? Hint: you don't need to fill out the elements of  $\mathbf{A}$  or  $\vec{b}$  in this part of the question.

**Solution/Answer:**

$$\begin{bmatrix} ? & ? & ? & ? \\ ? & ? & ? & ? \\ ? & ? & ? & ? \\ ? & ? & ? & ? \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} ? \\ ? \\ ? \\ ? \end{bmatrix}$$

$\mathbf{A}$  will be a  $4 \times 4$  matrix since there are four unknowns in the circuit, the currents  $I_0$ ,  $I_1$ , and  $I_2$  and the one potential  $u_1$ .

- (f) Use KCL to find as many equations as you can for the matrix.

**Solution/Answer:**

KCL gives us one equation for the node at the top, namely that  $I_0 - I_1 - I_2 = 0$ . Thus, so far our matrix is as follows:

$$\begin{bmatrix} 1 & -1 & -1 & 0 \\ ? & ? & ? & ? \\ ? & ? & ? & ? \\ ? & ? & ? & ? \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} 0 \\ ? \\ ? \\ ? \end{bmatrix}$$

- (g) Use KVL and Ohm's law to find the remaining equations for the matrix.

**Solution/Answer:** We know that the current through the current source must be the value of the current source, i.e.

$$I_0 = I_S \quad (5)$$

We also know that the voltage across the resistor is equal to the current times the resistance, i.e.

$$\begin{aligned} V_1 &= I_1 R_1 \\ V_2 &= I_2 R_2 \end{aligned} \quad (6)$$

Writing the equations for node potentials we have:

$$\begin{aligned} 0 - u_1 &= V_0 \\ u_1 - 0 &= V_1 \\ u_1 - 0 &= V_2 \end{aligned} \quad (7)$$

Using Equation (5) and substituting expressions from Equation (6) into Equation (7), we have:

$$\begin{aligned}
 I_0 &= I_S \\
 V_1 = I_1 R_1 &\implies -I_1 R_1 + u_1 = 0 \\
 V_2 = I_2 R_2 &\implies -I_2 R_2 + u_1 = 0
 \end{aligned} \tag{8}$$

Our matrix is then:

$$\begin{bmatrix} 1 & -1 & -1 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & -R_1 & 0 & 1 \\ 0 & 0 & -R_2 & 1 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} 0 \\ I_S \\ 0 \\ 0 \end{bmatrix}$$

(h) Solve the system of equations if  $I_S = 5 \text{ A}$ ,  $R_1 = 5 \Omega$ , and  $R_2 = 10 \Omega$ .

**Solution/Answer:**

By plugging in the values into the system of equations, we get:

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} 5 \\ 3.33 \\ 1.67 \\ 16.67 \end{bmatrix}$$