

(a) **Speed control**

In our first circuit design, we will begin by making PetBot decrease speed as it drives towards light. **Design a motor-driving circuit that outputs a decreasing positive motor voltage as PetBot drives toward the light source.** The motor voltage should be at least 5 V when far away from the light. At this far away from the light source, the photoresistor value will be $10\text{k}\Omega$, and then drop towards 100Ω as it approaches the light.

In your design, you may use any number of resistors and op-amps. You also have access to voltage sources of 10 V and -10V . **Based on your circuit, derive an expression for the motor voltage as a function of the circuit components that you used.**


NOTE! Since the motor is a resistor, the circuit design **MUST** have a buffer so that the applied voltage to the motor does not depend on its resistance.

Follow the design procedure introduced before:

Step 1(Specification) For this problem, we specify it as "We want to design a circuit such that when the PetBot gets closer to the light, the circuit outputs an decreasing voltage."

Step 2(Strategy) As introduced in the context, the resistance of a light-sensitive resistor decrease when PetBot gets closer to the light. So we can break down the problem into: 1)Convert distance to light exposure; 2)Convert light exposure to resistance of a light-sensitive resistor; 3)Convert decreasing resistance to decreasing voltage output.

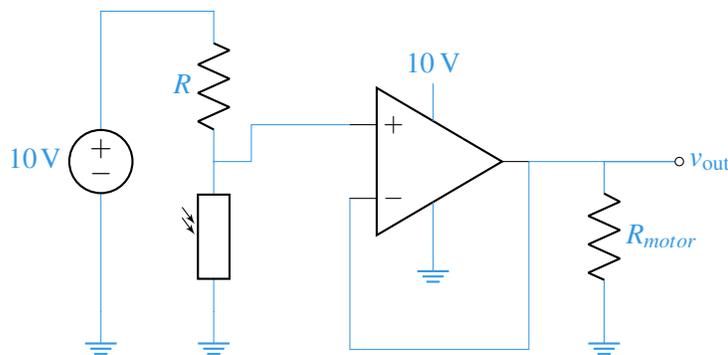Step 3(Implementation) We can use voltage divider to covert resistance to voltage output, and use an op-amp buffer circuit to drive the motor. A natural choice for our design is to combine a voltage divider with a buffer circuit, as depicted below.



Step 4(Verification) The output of the above circuit is:

$$v_{out} = \left(\frac{R_p}{R_p + R} \right) 10\text{V}$$

R_p represents the photoresistor, and $R \leq 10\text{k}\Omega$.

Since we require $v_{out} \geq 5\text{V}$ when far from light ($R_p = 10\text{k}\Omega$), the maximum allow value for R is $R = R_p$ as stated.

(b) Distance control

When the PetBot stops at a distance of 1 m away from the light, the photo-resistor has a value 1 k Ω . We would like to have the PetBot drive away when closer than 1m from the light (so for lower R_p), and drive towards the light when exceeding 1m (so for greater R_p).


Design a comparator circuit that outputs a positive motor voltage when the PetBot exceeds 1 m in distance from the flashlight (making the PetBot move toward it), and a negative voltage when PetBot is within 1 m of flashlight (making the PetBot back away from the flashlight).

In your design, you may use any number of resistors along with the comparator. You also have access to voltage sources of 10 V and -10 V.

Step 1(Specification) For this problem, we specify it as "We want to design a circuit such that when the PetBot exceeds 1 m closer from the flashlight, the circuit outputs an negative voltage."

Step 2(Strategy) As introduced in the context, the resistance of a light-sensitive resistor decrease when PetBot gets closer to the light. So we can break down the problem into: 1)Convert distance to light exposure; 2)Convert light exposure to resistance of a light-sensitive resistor; 3)Convert decreasing resistance to either positive or negative constant voltage output.

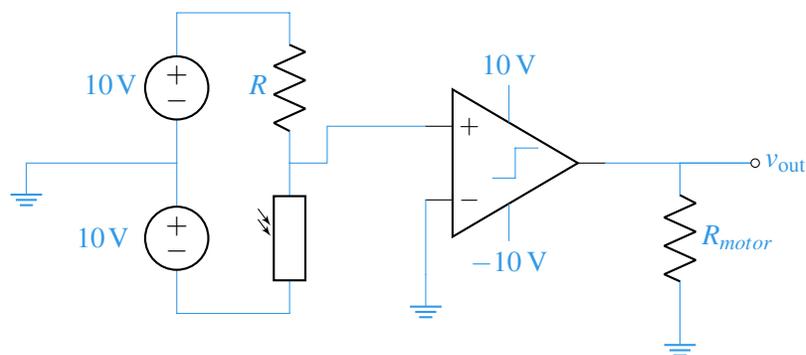Step 3(Implementation) We can combine a voltage divider and a comparator to achieve the goal. One possible comparator circuit design is shown below:



Since we have grounded the negative input terminal (and there is no feedback in the circuit), we realize the comparator rails high (positive $v_{out} = +10$ V when the input to the positive op-amp terminal has positive voltage).

Step 4(Verification) Using our voltage-divider knowledge (and recognizing this divider is analogous to a simple divider with $V_s = 20$ V and then shifted by 10V) we find the positive node voltage:


$$u_+ = 20 \left(\frac{R_p}{R_p + R} \right) - 10 = 10 \left(\frac{R_p - R}{R_p + R} \right).$$

Notice for $R_p > R$, the node u_+ has positive voltage and so $u_+ > u_-$, thus $v_{out} > 0$. Conversely when $R_p < R$, the u_+ node goes below zero and renders a negative v_{out} on the motor.


This means our circuit successfully applies positive motor voltage (drives PetBot forward) when far away from the light source with large R_p , and applies negative voltage when too close to the light. Our exact design criteria are met when $R = R_p = 1$ k Ω .

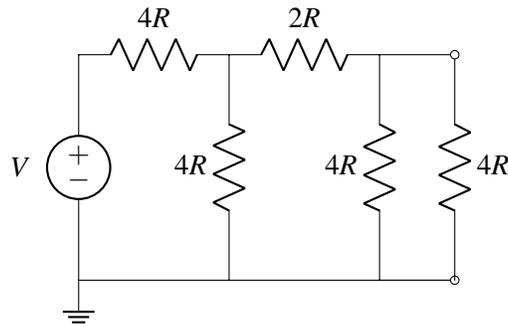2. OPTIONAL: Power to Resist (from Spring 2018 midterm 2)

Find the power dissipated by the voltage source in the circuit below. Be sure to use passive sign convention.



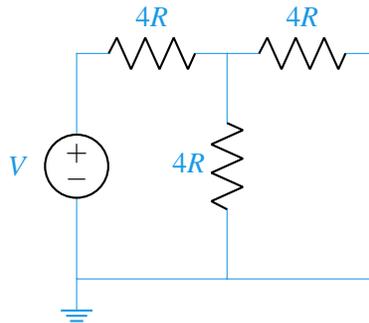Answer: We want to find the equivalent resistance across the voltage source in Figure 6.2. Start by reducing the two resistors on the right to $4R \parallel 4R = 2R$. Then combine the other $2R$ resistor with this to get a new resistor of value $4R$ as in the circuit below.



Once again we have $4R \parallel 4R = 2R$. This is finally in series with $4R$ giving us a total resistance of $4R + 2R = 6R$

$$P = VI = V \frac{-V}{6R} = -\frac{V^2}{6R}$$

The negative sign is present because the voltage source actually provides power, which can also be seen by using passive sign convention.