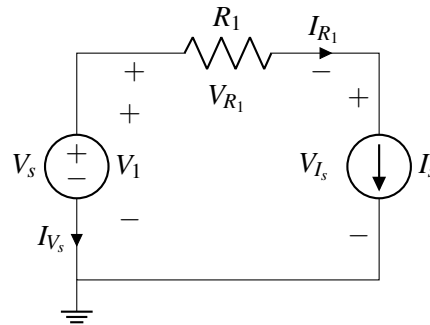


# EECS 16A    Designing Information Devices and Systems I

## Fall 2021    Discussion 7B

### 1. Passive Sign Convention and Power v 2.0

Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$ ,  $I_s = 0.5\text{ A}$  and  $R_1 = 5\ \Omega$ .



### 2. Resist the Touch

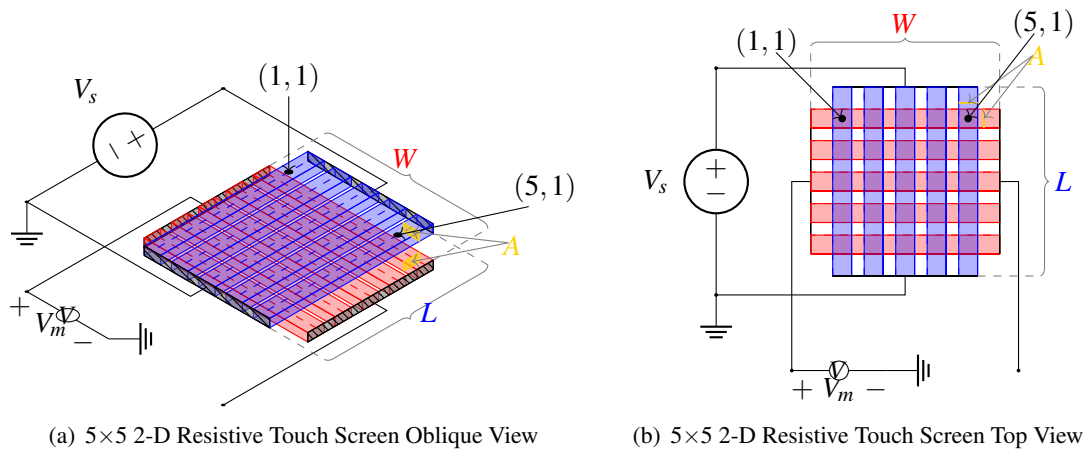
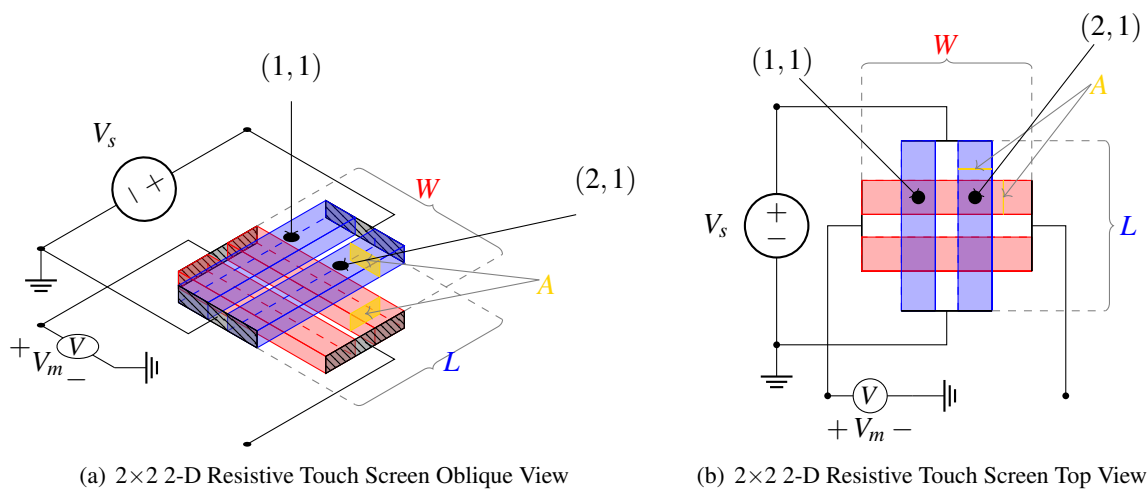


Figure 1:  $N \times N$  Resistive Touch Screen,  $N = 5$

In this question we will be re-examining the 2-dimensional resistive touchscreen. This touchscreen, is slightly different to the one shown in lecture and more like the one we will be examining in lab.

The touchscreen has length  $L$  and width  $W$  and is composed of a rigid bottom-layer and a flexible top-layer. Instead of having two continuous resistive sheets on the top and bottom layers, this is a simpler implementation with  $N$  vertical strips of conductive material in the top layer and  $N$  horizontal strips of conductive material in the bottom layer. The strips of a single layer are all connected by an ideal conducting plate on each side. All strips have resistivity,  $\rho$ , and cross-sectional area,  $A$ .

Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point in Figure 1(b) is position  $(1, 1)$ , and the upper right touch point is  $(N, 1)$ . The

Figure 2:  $2 \times 2$  Resistive Touch Screen

spacing between the strips in the top layer is  $\frac{W}{N+1}$ , and the spacing between the strips in the bottom layer is  $\frac{L}{N+1}$ .

- Find the resistance  $R_y$  for a single vertical blue strip and  $R_x$  for a single horizontal red strip, as a function of the screen dimensions  $W$  and  $L$ , the strip resistivity  $\rho$ , and the cross-sectional area  $A$ .
- Consider a  $2 \times 2$  example for the touchscreen circuit, shown in Figure 2.

Assume that we connect a voltage source  $V_s$ , between the top and bottom terminals of the blue strips, and a voltmeter  $V_m$  to one of the left or right terminals as depicted in the diagram.

If  $V_s = 3 \text{ V}$ ,  $R_x = 2000 \Omega$ , and  $R_y = 2000 \Omega$ , draw the equivalent circuit for when the point  $(2, 2)$  is pressed and solve for the measured voltage,  $V_m$ , with respect to ground.

Reminder: all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point is position  $(1, 1)$ . The spacing between the strips in the top layer is  $\frac{W}{N+1}$ , and the spacing between the strips in the bottom layer is  $\frac{L}{N+1}$ .

- Suppose a touch occurs at coordinates  $(i, j)$  for an arbitrary  $N \times N$  touchscreen, and the voltage source and meter are connected as in the figures. A  $5 \times 5$  example is shown in Figure 1(b). Find an expression for  $V_m$  as a function of  $V_s$ ,  $N$ ,  $i$ , and  $j$ . Again, the upper left corner is the coordinate  $(1, 1)$  and the upper right coordinate is  $(N, 1)$
- Optional / Fun: Experiment with the TinkerCad models below to validate the theoretical results you just derived.

TinkerCad model of  $2 \times 2$  equivalent circuit: <https://www.tinkercad.com/things/0wIXz3MkD7B>

TinkerCad model of  $3 \times 2$  equivalent circuit: <https://www.tinkercad.com/things/k5oolj2tUEN>