

Welcome to EECS 16A!

Designing Information Devices and Systems I

Ana Claudia Arias and Miki Lustig
Fall 2021

Module 2
Lecture 11

Op-amp circuit analysis (Note 19)





Last Lecture...

Toolbox

- Resistors
- Capacitors
- Open-circuits
- Voltage Dividers/Summers
- Op-Amps
- Thevenin and Norton Equivalence
- KCL/KVL
- Element Definitions
- DAC
- Negative Feedback
- Op-Amp in Negative Feedback
- "Golden Rules" for Op-Amps

$$A_V = \frac{V_{out}}{V_{in}}$$

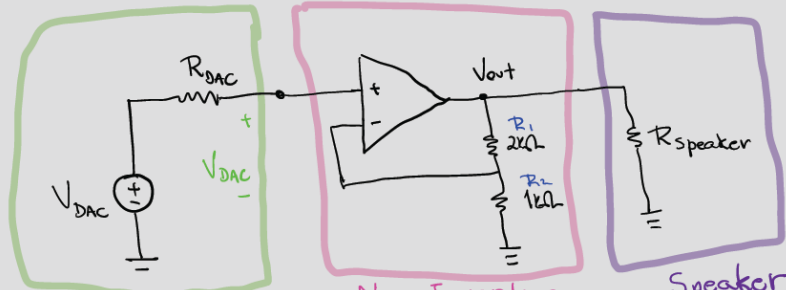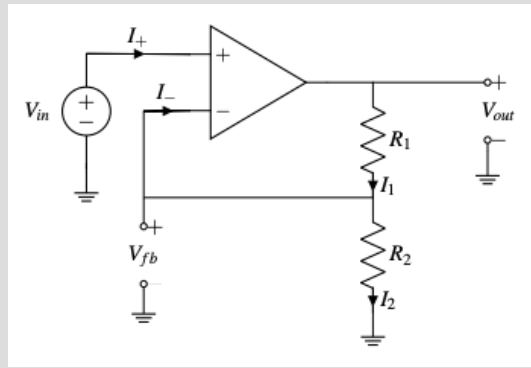


Non-Inverting Amplifier
(feedback gain = 3)
Gain = $1 + \frac{R_1}{R_2}$

Party time!
Yay!


Today

Voltage Divider

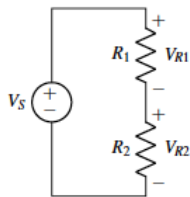


$$V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$$

Voltage Summer

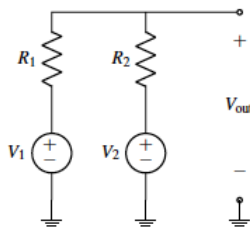


$$V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$$

Unity Gain Buffer

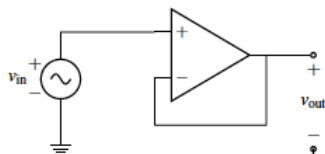


$$\frac{v_{out}}{v_{in}} = 1$$

Inverting Amplifier

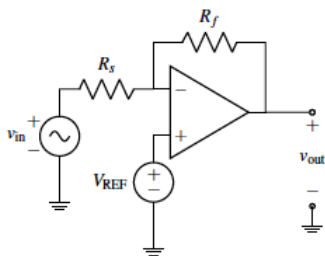


$$v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right) + V_{REF} \left(\frac{R_f}{R_s} + 1 \right)$$

Non-inverting Amplifier

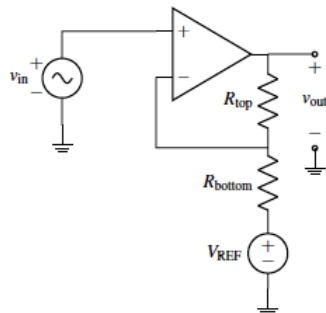

$$v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$$

Transresistance Amplifier

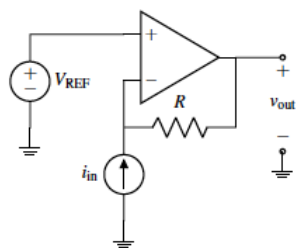

$$v_{out} = i_{in} (-R) + V_{REF}$$


Checking for Negative Feedback (Determining the polarity of NFB)

Step 1 – Zero out all independent sources : replacing voltage sources with wires and current sources with open circuits as in superposition





Step 2 – Wiggle the output and check the loop – to check how the feedback loop responds to a change.

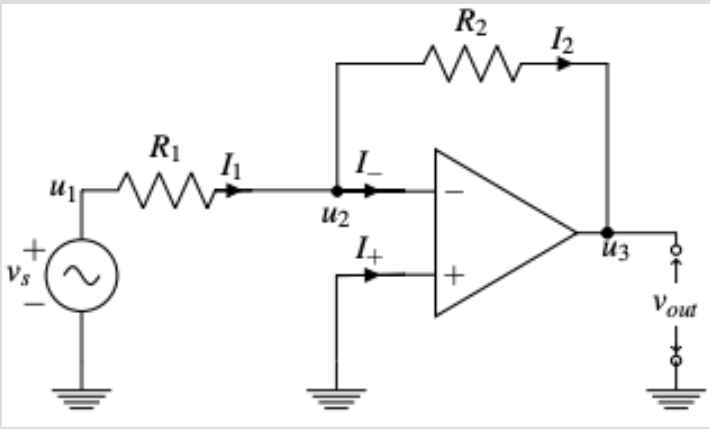- if the error signal decreases, the output must also decrease. **The circuit is in negative feedback**
- if the error signal increases, the output must also increase. **The circuit is in positive feedback**



Now lets solve it...

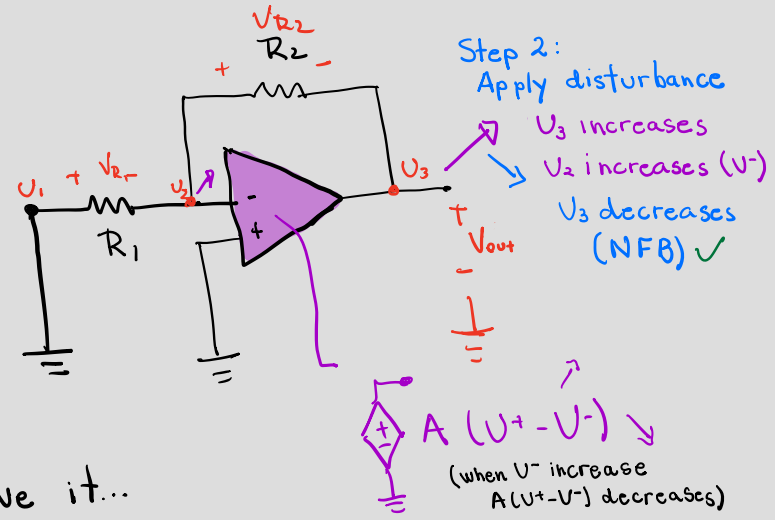

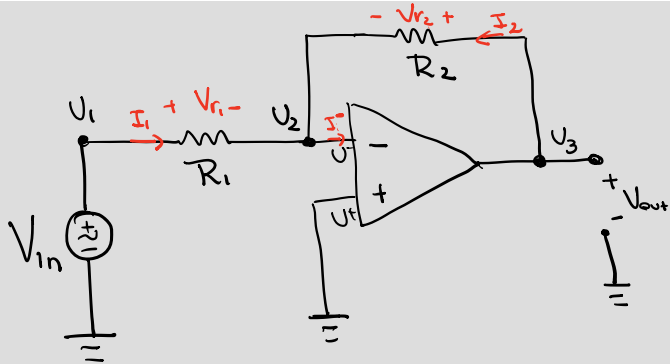

NFB \Rightarrow GR #2 applies
 $U^+ = U^-$

- ① $U_1 = V_{in}$
 $U_3 = V_{out}$
 $U_2 = 0$ (circuit in NFB \Rightarrow GR #2 applies $U^+ = U^-$)
 $\hookrightarrow U_2 = U^-$ We know $U^+ = 0 \Rightarrow U^- = 0$
 $U^- = U_2 \Rightarrow U_2 = 0$

② Element Definitions:

$V_{R1} = I_1 R_1$
 $V_{R2} = I_2 R_2$

Voltage Def:
 $V_{R1} = U_1 - U_2 = U_1 = V_{in}$
 $V_{R2} = U_3 - U_2 = U_3 = V_{out}$

③ (KCL)
 $I_1 + I_2 = I^- = 0$ (GR #1)

Inverting Amplifier

$V_{in} = U_1 = I_1 R_1$
 $V_{out} = U_3 = I_2 R_2$

$I_1 + I_2 = 0$


$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0$

$V_{out} = R_2 \cdot \left(-\frac{V_{in}}{R_1} \right)$

$V_{out} = -\frac{R_2}{R_1} \cdot V_{in}$

$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$

A faster way...

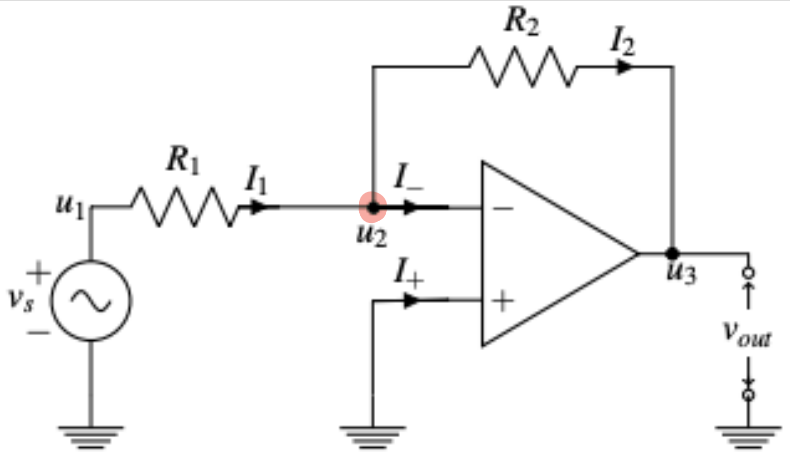

GR2: $U^+ = U^-$

$$U_2 = U^-$$

$$U^+ = 0 \Rightarrow U_2 = 0$$

GR1 + KCh ($I_1 = I_2 + I^-$)


$$\frac{U_2 - U_1}{R_1} = \frac{U_3 - U_2}{R_2} + I^-$$

$$-\frac{U_1}{R_1} = \frac{U_3}{R_2}$$


$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Example circuit 2 (trans-resistance amplifier)


$$I^+ = 0 \Rightarrow U_1 = U_2$$

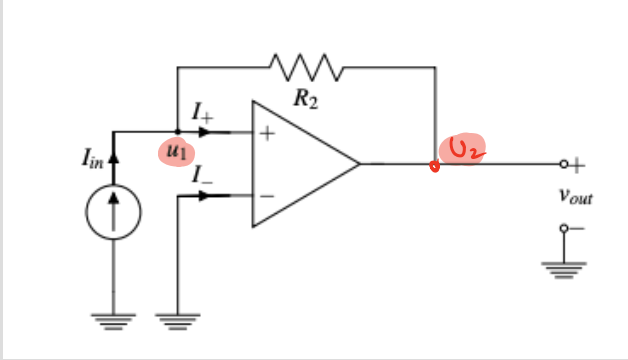

Invert polarity
⇓

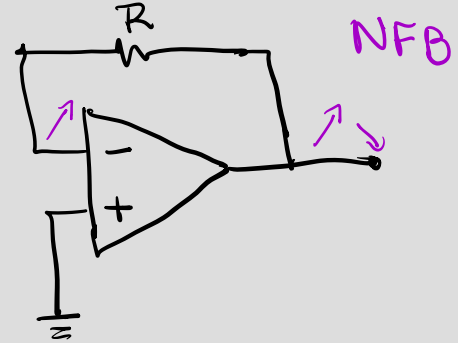


Step 1

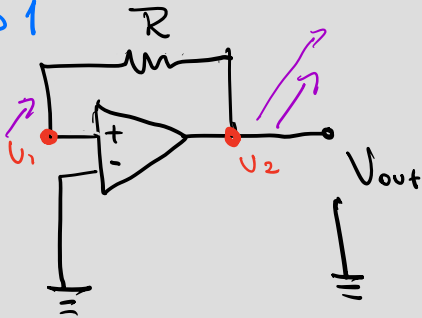

Step 2: check for NFB

Increase output →
+ moves up
output increases
by a lot

X Not in
NFB

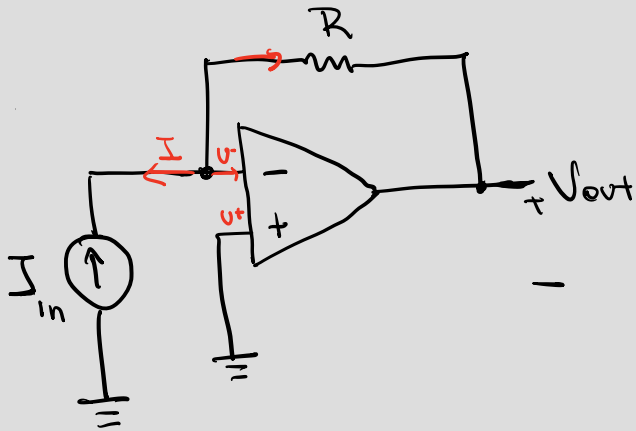

NFB : $U^+ = U^-$
 $U^+ = 0 \rightarrow U^- = 0$

GR # 2

$$\overset{GR2}{\cancel{U^-}} - \frac{V_{out}}{R} + (-I_{in}) + \overset{GR1}{\cancel{I^-}} = 0$$


$$-\frac{V_{out}}{R} = I_{in}$$

$$V_{out} = -I_{in} R$$


$$\frac{V_{out}}{I_{in}} = -R$$


The input is current ; output is voltage : we use this model in the lab for photo sensors !

Example circuit 3 -

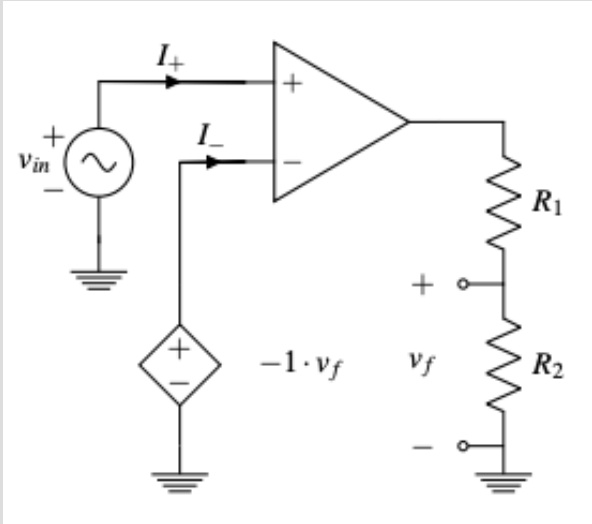

Check NFB:

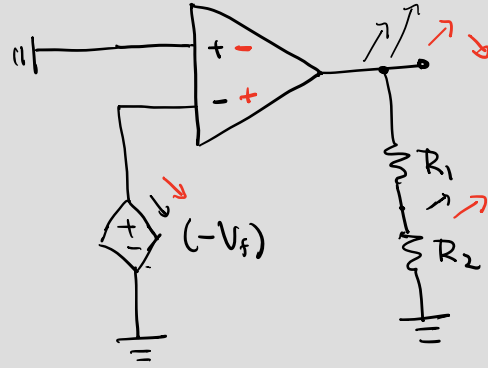

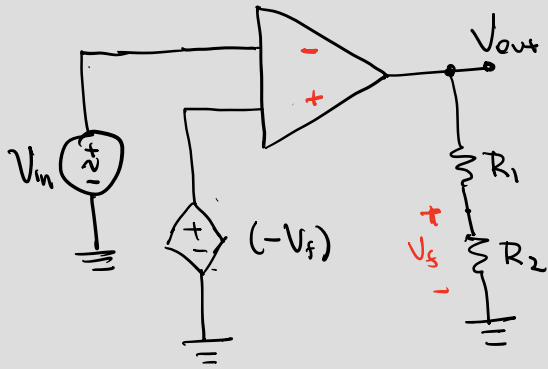

Voltage Divider

$$V_s = \frac{R_2}{R_1 + R_2} \cdot V_{out}$$

NFB (GR#2) $V^- = V^+$
 ~~$V_{in} = -V_s$~~
 V^- V^+

$$V_{in} = - \frac{R_2}{R_1 + R_2} V_{out} \Rightarrow \frac{V_{in}}{V_{out}} = - \frac{R_2}{R_1 + R_2}$$


$$A_V = \frac{V_{out}}{V_{in}} = - \frac{R_1 + R_2}{R_2} = - \left(1 + \frac{R_1}{R_2} \right)$$

Artificial Neuron

(Energy Efficient Neural Networks) — Yes we can!


- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.
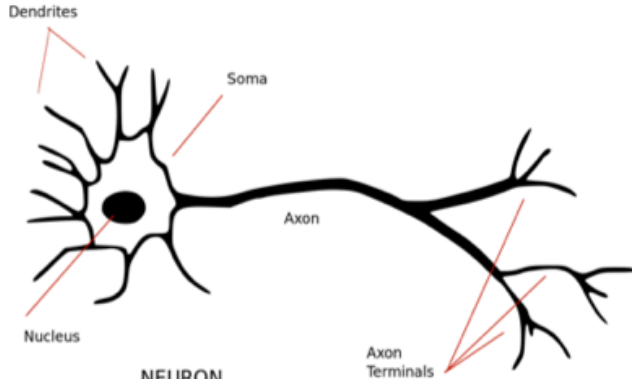
$$[a_1 \ a_2] \cdot \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = a_1 v_1 + a_2 v_2$$



NEURON

A biological Neuron

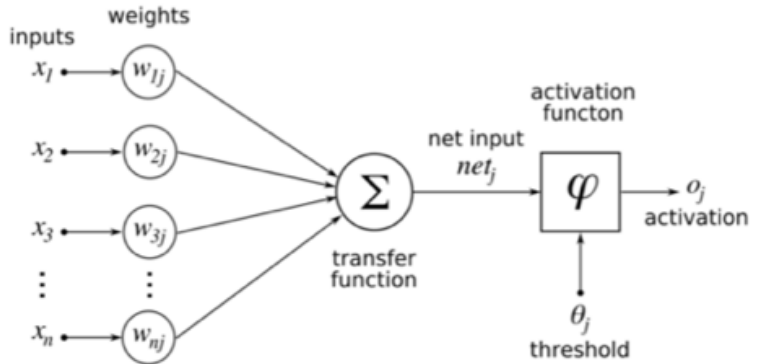


An Artificial Neuron


Artificial Neuron

- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.

Inverting summer $V_3 = V_{out} - V^-$

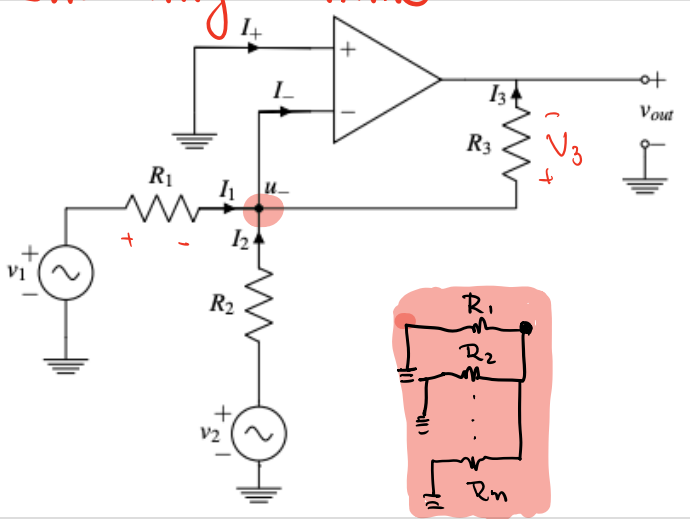

Check for NFB:

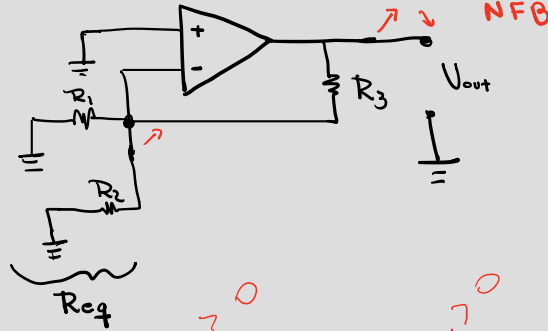

$$U^+ = U^- : \text{GRZ}$$

$$U^+ = 0 \Rightarrow U^- = 0$$

$$\text{KCh: } \frac{U^- - V_1}{R_1} + \frac{U^- - V_2}{R_2} = \frac{U^- - V_{out}}{R_3}$$

$$-\frac{V_1}{R_1} - \frac{V_2}{R_2} = \frac{V_{out}}{R_3}$$

$$V_{out} = -\frac{R_3}{R_1} V_1 + \left(-\frac{R_3}{R_2} V_2\right) + \dots + \left(-\frac{R_3}{R_N} V_N\right)$$

only negative
coef.


Weights
 $a_{11} V_1$

$a_{12} V_2$

$a_{1N} V_N$

All weights are negative: How can we make a_1 and a_2 positive?

Add another inverting amplifier circuit.

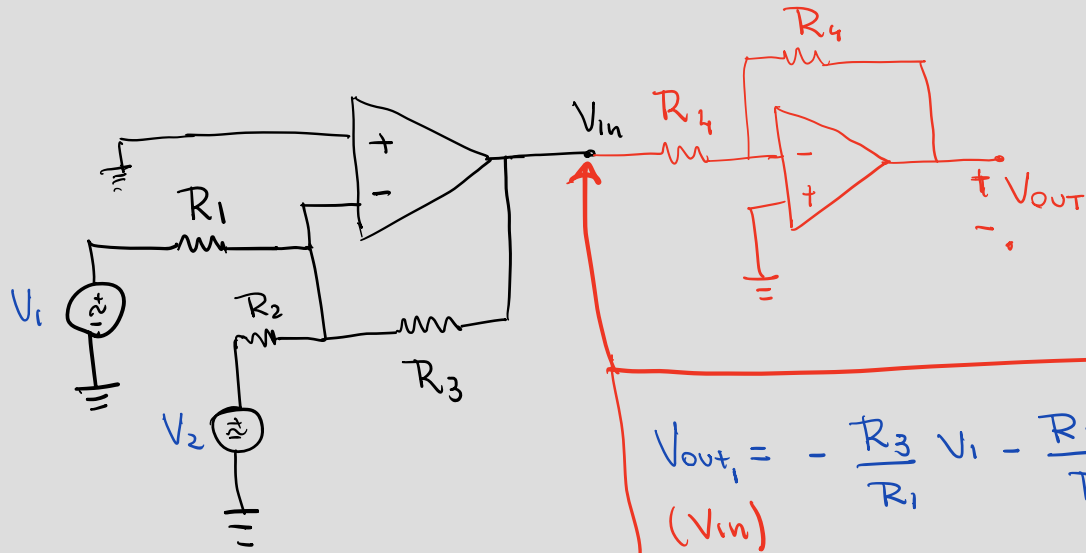

$$V_{out} = - \frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2$$

(V_{in})

$$\frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1}$$


↳ result from inverting amplifier

$$V_{out} = - \frac{R_2}{R_1} \cdot V_{in}$$

$V_{out} = - V_{in}$ (when R_1 and R_2 are the same)

Unity Gain Buffer

↳ Allows us to isolate circuits

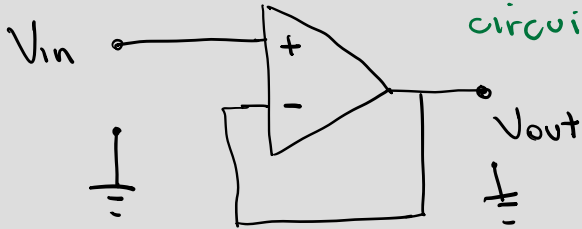

$$U^+ = V_{in}$$


$$U^- = V_{out}$$

GR2

$$U^+ = U^-$$


$$V_{in} = V_{out}$$

Speaker Design

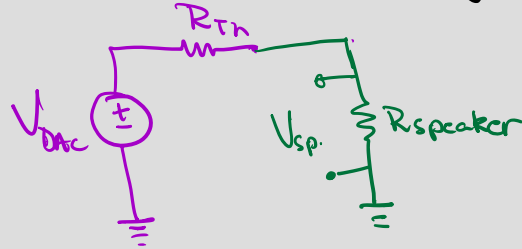

$$V_{speaker} = \frac{V_{DAC}}{126}$$

loading

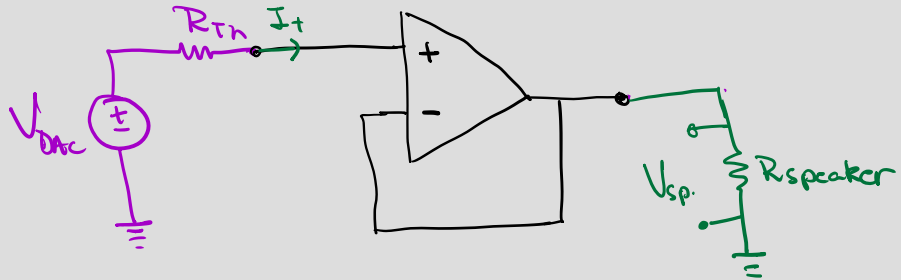

$$I^+ = 0 \Rightarrow U^+ = V_{DAC}$$

$$V_{out} = V_{speaker} = U^-$$

$$V_{DAC} = V_{speaker}$$

$$\Rightarrow U^+ = U^-$$

