

# Welcome to EECS 16A!





## Designing Information Devices and Systems I

Ana Claudia Arias and Miki Lustig  
Fall 2021

Module 2  
Lecture 10  
Negative Feedback (Note 18)



# Last Lecture...

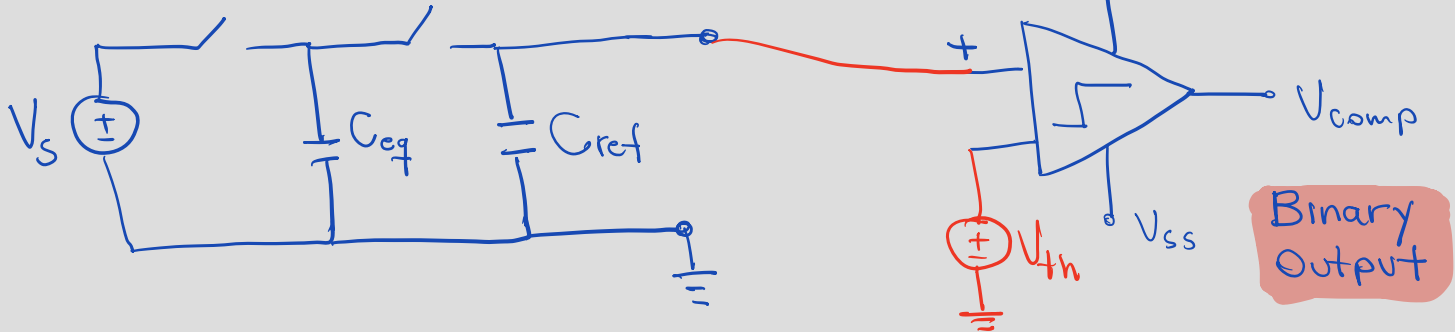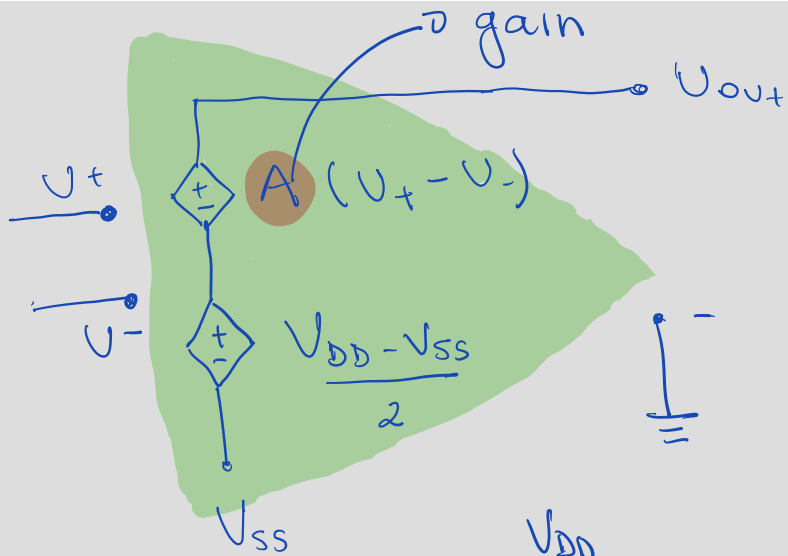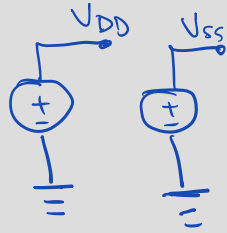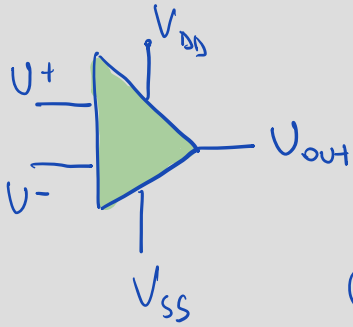

# New Design – Let's play music

## Problem

- We want to play music loud!
- Music is stored as digital signal
- Speakers are analog

## Tools

- Resistors
- Capacitors
- Open-circuits
- Voltage Dividers
- Op-Amps
- Thevenin Equivalence
- Norton Equivalence
- KCL / KVL
- Element Def.


## Specs

- Speaker takes 0-10V ✓
- Need to go from digital to analog. ?


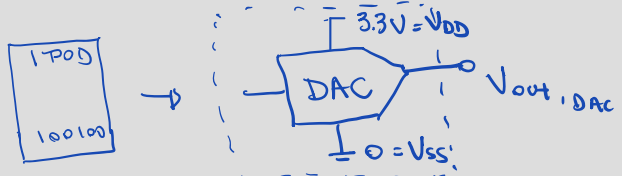
# New Design – Let's play music

\* Want to play music LOUD


↳ Music is stored as digital signal  
Digital → Analog



Digital-to-analog converter

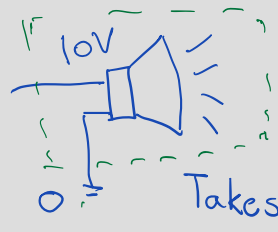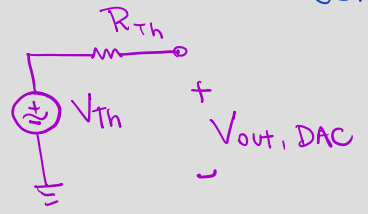




Takes Voltage and turns into sound

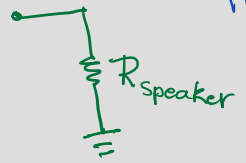


Dance!




# Digital to Analog Converter - DAC

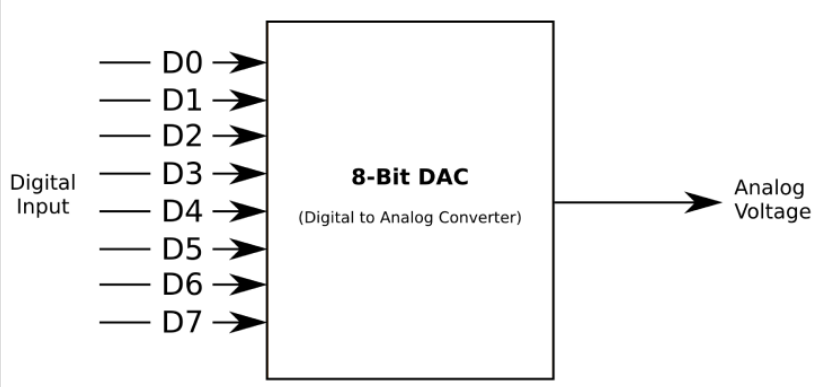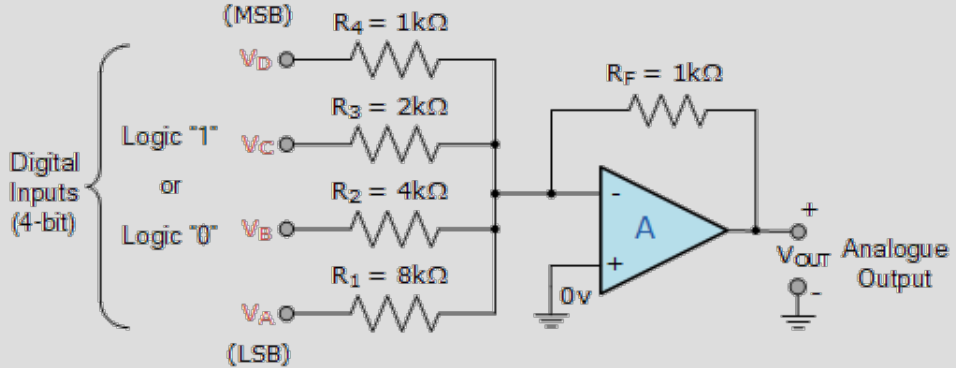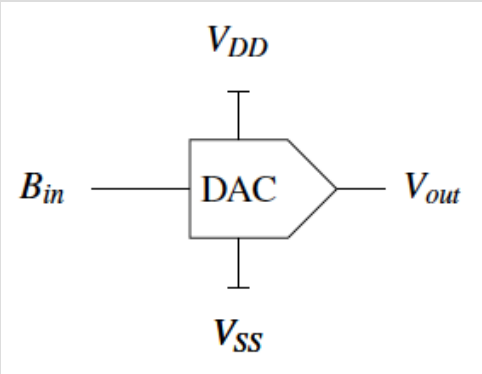

# Equivalence comes in handy again

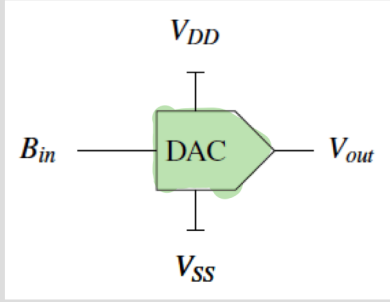

Speaker

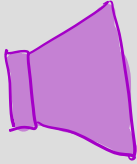


$$V_{\text{speaker}} = \frac{R_{\text{speaker}}}{R_{\text{th}} + R_{\text{speaker}}} \cdot V_{\text{th}}$$

*Handwritten annotations:  $8\Omega$  above  $R_{\text{speaker}}$ ,  $1000\Omega$  above  $R_{\text{th}}$ , and  $8\Omega$  above  $R_{\text{speaker}}$  in the denominator.*

$$V_{\text{speaker}} = \frac{V_{\text{th}}}{126}$$




Not loud!

loading Effect

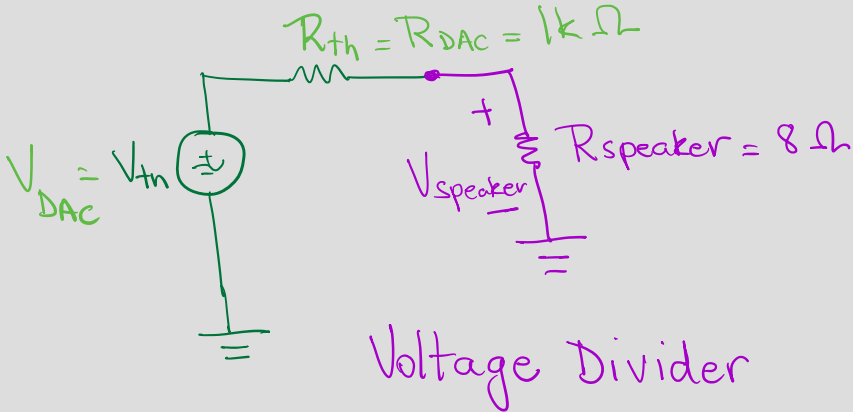

- Need to increase  $V_{\text{out}}$
- Speaker needs 0-10V
- DAC 0-3.3V
- Tool ?

# Digital to Analog Converter - DAC

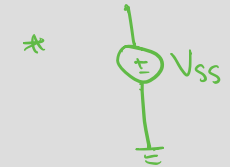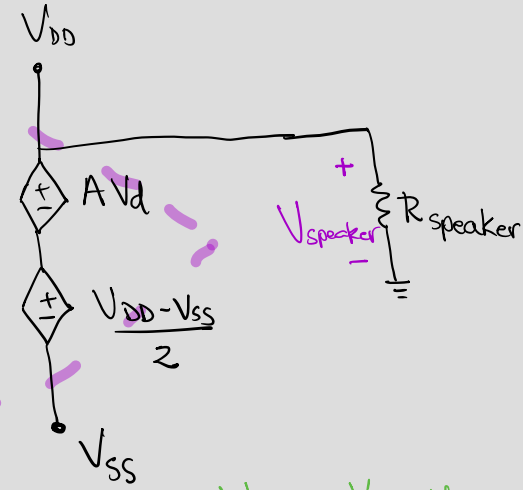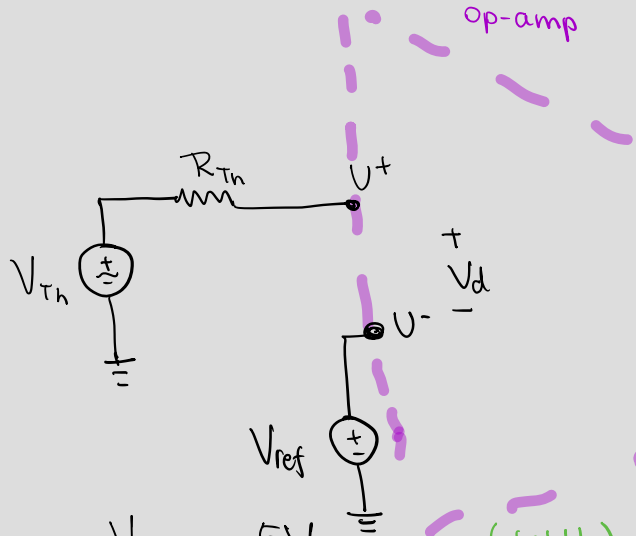

$V_{DD} = -V_{SS} = 5V$

10V output  
(Input)

(KUL)

$V_{speaker} = V_{SS} + \frac{V_{DD} - V_{SS}}{2} + A_{Vd} = A_{Vd}$



when:

$\frac{V_{DD} + V_{SS}}{2} = 0$

$V_{SS} < A_{Vd} < V_{DD}$

$V_d = U^+ - U^- = V_{Th} - V_{ref}$



# Digital to Analog Converter - DAC

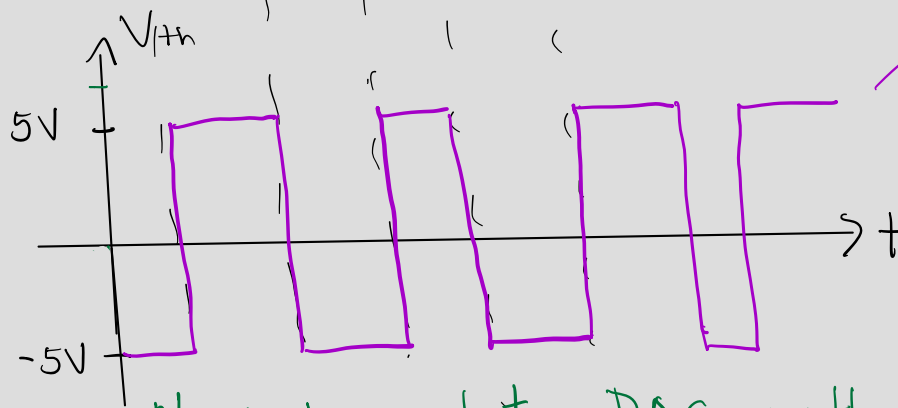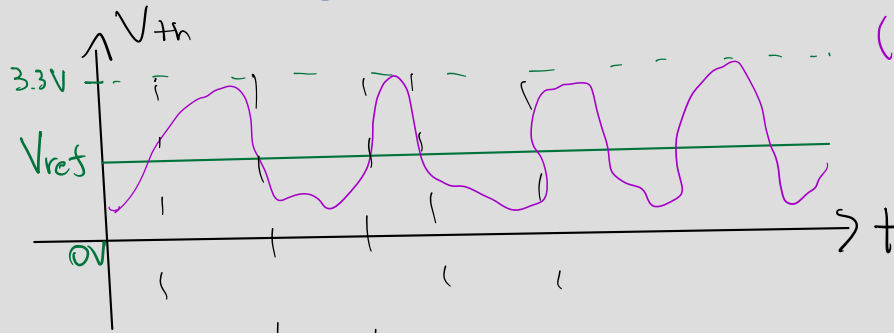

Need to isolate DAC with controllable gain!  
e.g.  $3x$



# Music output with design #1

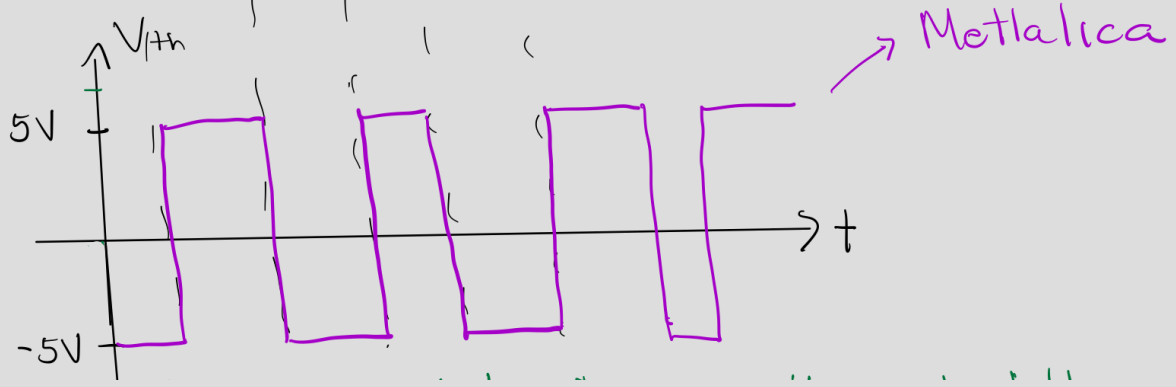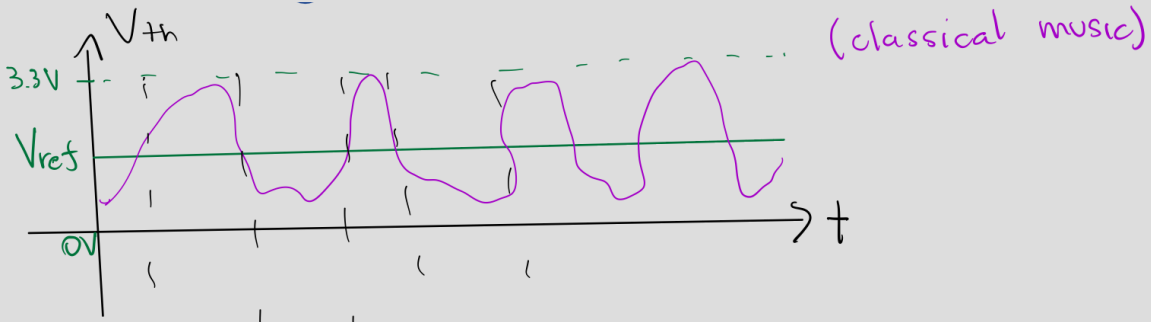

Need adjustments to our music output and gain of 3 – need more “tools” in the system

$$S_{err} = S_{in} - S_{fb}$$


$$S_{out} = A \cdot S_{err}$$

$$S_{fb} = f \cdot S_{out}$$

$$\frac{S_{out}}{A} = S_{in} - S_{fb}$$

$$S_{out} \left( \frac{1}{A} + f \right) = S_{in}$$
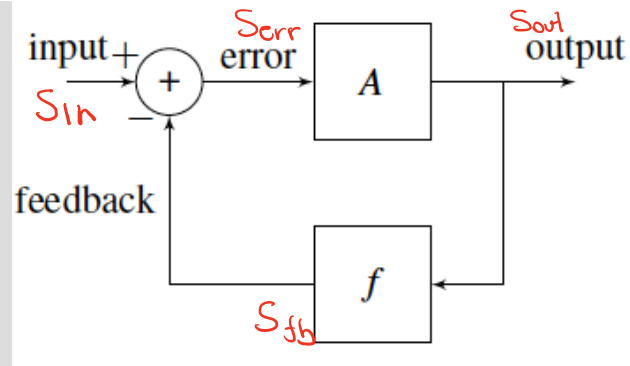
$$\frac{S_{out}}{S_{in}} = \frac{1}{\frac{1}{A} + f} = \frac{A}{1 + Af}$$



- Making small adjustments to correct output on the fly
- Basis of control theory
- Many examples in daily life:

- Biology

- Self-driving car
- Human driving car
- Hand-eye coordination

- ...

# Negative Feedback

$$\frac{S_{out}}{S_{in}} = \frac{A}{1 + A f}$$

- Describes the behaviour of the system - transfer function.
- How  $S_{out}$  depends on  $S_{in}$

$$\frac{S_{out}}{S_{in}} \underset{A \rightarrow \infty}{=} \frac{1}{f}$$


↳ We control the output via block  $f$ !

So  $V_{out} = \frac{1}{f} V_{in}$  for very large gain.


↳ we can set  $f$  to get any output.

(Beautiful result): 😊
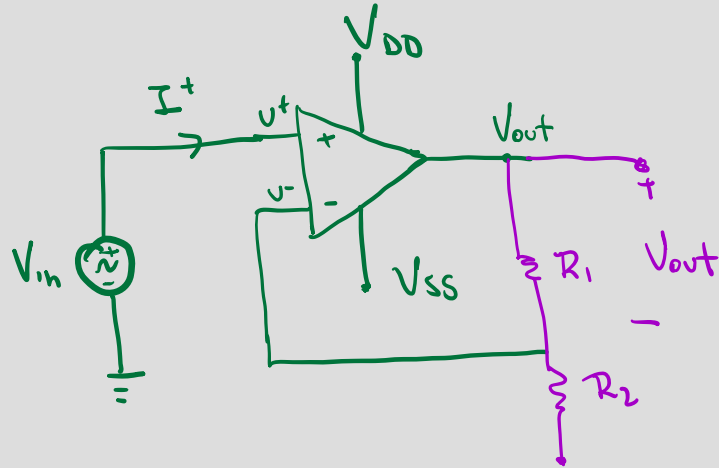
# Need to isolate the DAC from speaker – OP-Amp with NFB



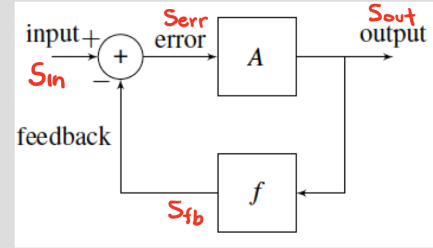
- We want to measure  $V_{out}$ , take a portion of the signal and feedback as  $V^-$




$$\begin{aligned}U^+ &= S_{in} \\V_{out} &= S_{out} \\U^- &= S_{fb} \\U^+ - U^- &= S_{err}\end{aligned}$$

# Op-Amp in negative feedback

Non-inverting op-amp

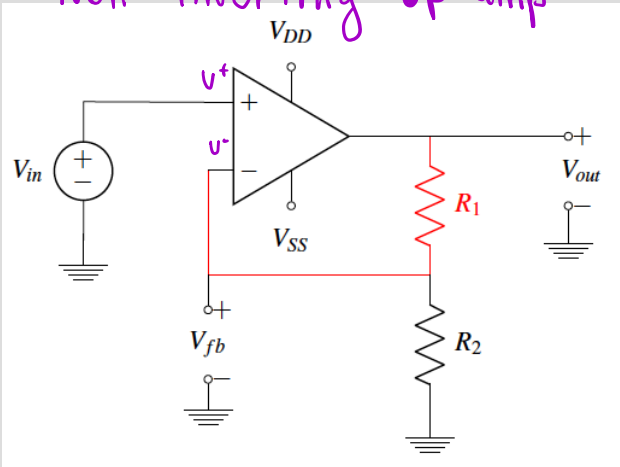


Model :

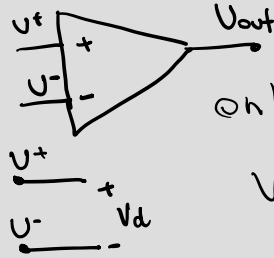

only for

$$V_{SS} < V_{ot} < V_{DD}$$

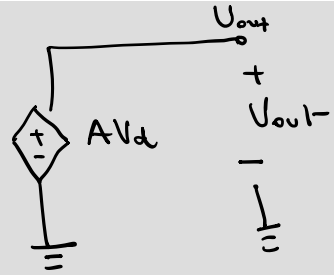

Simpler model as the second source is not "needed".

$$(1) \quad V_d = U^+ - U^- = V_{in} - V_{sb}$$

$$(2) \quad V_{out} = A V_d$$

$$(3) \quad V_{sb} = \frac{R_2}{R_1 + R_2} \cdot V_{out}$$

"BUFFER circuit"

$\hookrightarrow f$

$$V_{out} = A (V_{in} - f \cdot V_{out})$$

$$V_{out} (1 + Af) = A V_{in}$$

$$A_v = \text{Gain} = \frac{V_{out}}{V_{in}} = \frac{A}{1 + Af}$$

$$A_v = \frac{1}{f} \hookrightarrow \frac{R_1 + R_2}{R_2} = \frac{1 + \frac{R_1}{R_2}}{\frac{R_1}{R_2}}$$

# Golden Rules of Op-Amps

For our design we want  $A = 3$


$$V_d = \frac{V_{out}}{A} \quad \text{if } A \rightarrow \infty$$

$$V_d = \frac{1}{A} \cdot \frac{A}{1+A\beta} V_{in} = \frac{V_{in}}{1+A\beta} = 0$$


In NFB:  $V^+ = V^-$  and  $A \rightarrow \infty$

Rules: (Golden Rules)

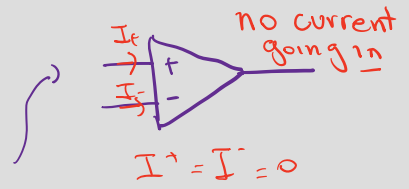- (1)  $I^+ = I^- = 0$  (always true)
- (2)  $V^+ = V^-$  (only in NFB &  $A \rightarrow \infty$ )



# Let's go back to playing music

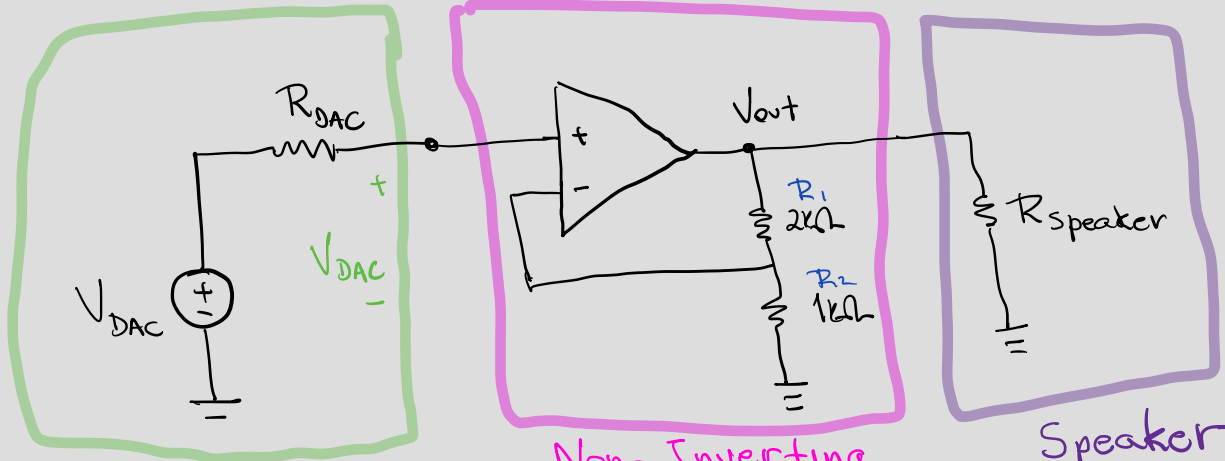

DAC

Non-Inverting Amplifier  
(feedback gain = 3)

$$\text{Gain} = 1 + \frac{R_1}{R_2}$$

Party time!  
Yay!

# New Design – Let's play music

## Problem

- We want to play music loud!
- Music is stored as digital signal
- Speakers are analog

## Tools

- Resistors
- Capacitors
- Open-circuits
- Voltage Dividers
- Op-Amps
- Thevenin Equivalence
- Norton Equivalence
- KCL / KVL
- Element Def.

## Specs

- Speaker takes 0-10V ✓
- Need to go from digital to analog. ?
- DAC ✓
- Op-amp in Negative Feedback (NFB) ✓
- Gain of 3. ✓





