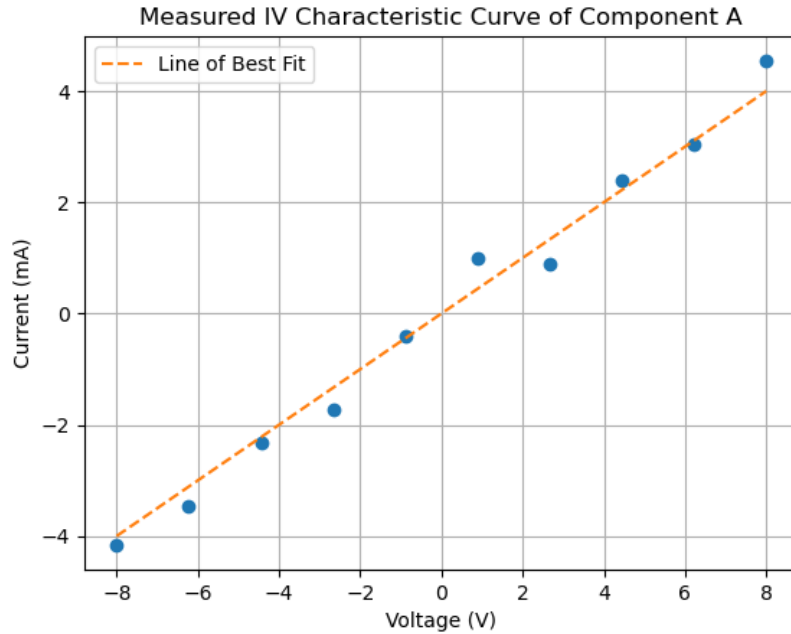


PRINT your student ID: _____

2. Characterizing Components (13 Points)

Your lab TA has been exploring the 16A lab and discovered a bin of unlabeled components. She has collected some data about these mysterious components, and needs your help to interpret them.

- (a) (3 points) She begins with a mysterious two-terminal component and labels it 'Component A'. After connecting it to one of the signal generators in the lab, she measures many voltage and current points forming an approximate I-V curve.




- i. Which circuit element best describes Component A?

- | | |
|--------------------------------------|--------------------------------------|
| <input type="radio"/> Resistor | <input type="radio"/> Capacitor |
| <input type="radio"/> Voltage Source | <input type="radio"/> Current Source |
| <input type="radio"/> Open Circuit | <input type="radio"/> Short Circuit |

- ii. Paying careful attention to the measured units of current and voltage, express both the numeric value of the circuit element and its corresponding units (from the options provided).


- | |
|---|
| <input type="radio"/> Volts (V) |
| <input type="radio"/> Amps (A) |
| <input type="radio"/> Ohms (Ω) |
| <input type="radio"/> Farads (F) |

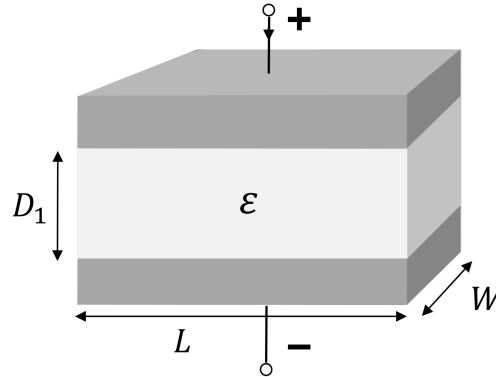- (b) (2 points) Your TA picks a different component out of the bin and labels it 'Component B'. She finds a corresponding datasheet which provides information on its structure and properties. It states that Component B is a *parallel plate capacitor*, which is physically modeled with three layers as follows:




Write an expression for the capacitance of Component B as a function of dielectric permittivity ϵ and dimensions D_1 , L , and W .

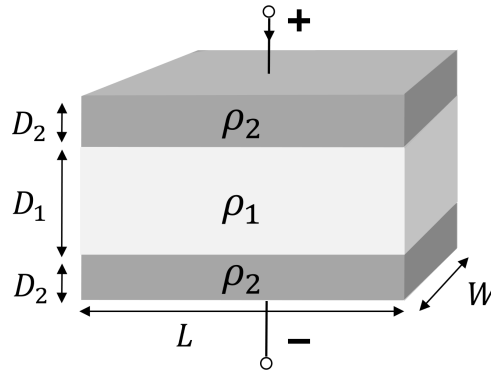- (c) (3 points) In the course of testing, your TA connected a large voltage source and put too much power through the capacitor. This resulted in the dielectric (the middle layer) breaking down, so that the entire three-layer device *behaves like a resistor*. After degradation, the device can be modeled as:



Write an expression for the *resistance* of Component B as a function of D_1 , D_2 , L , W , and resistivities ρ_1 and ρ_2 .

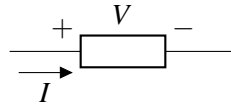- (d) (5 points) Your lab TA decides to try characterizing one final component and labels it ‘Component C’. She connects Component C to a circuit and measures the voltage across it and current through it as shown



From her measurement she finds that $I = -5\mu\text{A}$ and $V = 0.2\text{V}$.

- i. Is Component C labeled according to passive sign convention?

Yes

No

- ii. What is the power *dissipated* by Component C?

μW

- iii. Is Component C consuming or generating power?

Consuming

Generating

- iv. Regardless of your answers to the previous parts, assume Component C generates a constant $10\mu\text{W}$ of power and is connected to a 1mWh battery (a ‘Wh’ or ‘watt-hour’ is a unit of energy). How long will it take to charge the battery from 0 to 100% capacity?


hours

PRINT your student ID: _____

3. Can You Divide a Divider? (16 Points)

For all parts please give your **answer in terms of the labeled circuit quantities**. When expressing your answers, you are free to use the parallel (\parallel) operator.

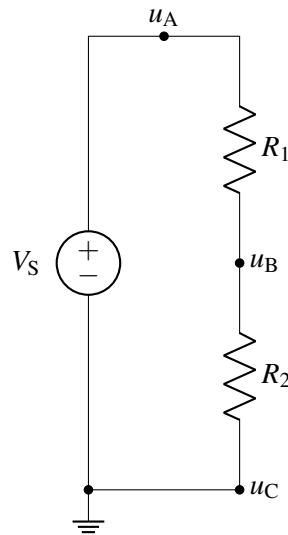(a) (4 points) Consider the circuit below.




i. Find the voltage at node u_B as a function of V_S , R_1 , and R_2 .

ii. How would you attach a voltmeter to check your answer for node voltage u_B ? Indicate the **nodes** (i.e., u_A , u_B , or u_C) you would connect to each voltmeter terminal.

positive voltmeter terminal:

negative voltmeter terminal:

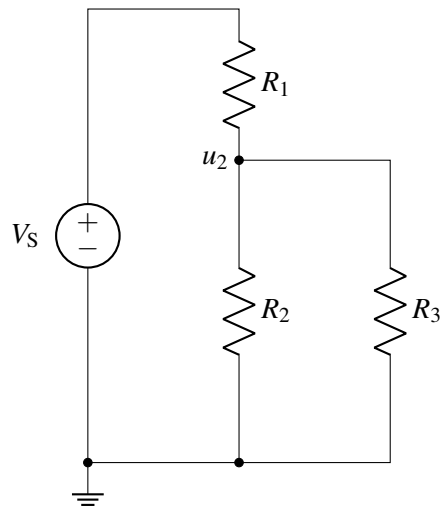(b) (4 points) Now consider a new circuit.



i. Find the voltage at node u_2 as a function of V_S , R_1 , R_2 , and R_3 .


ii. How does the node voltage u_2 compare to the node voltage u_B in part (a)? Using 1-2 sentences, provide a conceptual reason for your answer.

$u_2 > u_B$

$u_2 = u_B$

$u_2 < u_B$

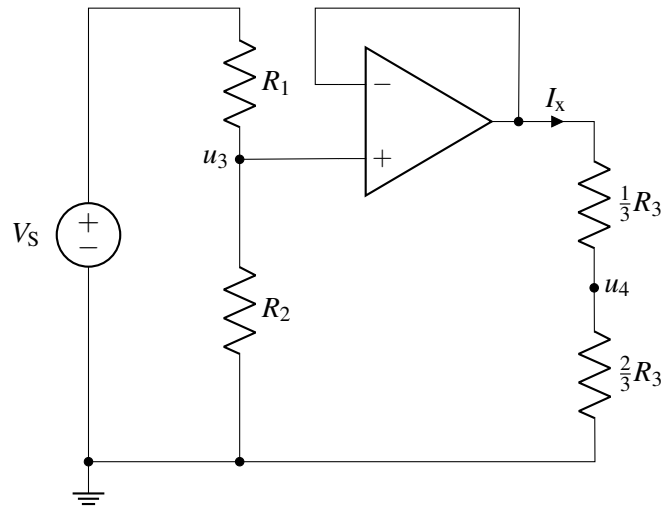- (c) (8 points) Now consider a new circuit shown below. Assume the op-amp is ideal and in negative feedback.




- i. Find an expression for the voltage at u_3 as a function of V_S , R_1 , R_2 , and R_3 .

- ii. How does the node voltage u_3 compare to the node voltage u_2 in part (b)? Using 1-2 sentences, provide a conceptual reason for your answer.

$u_3 > u_2$

$u_3 = u_2$

$u_3 < u_2$

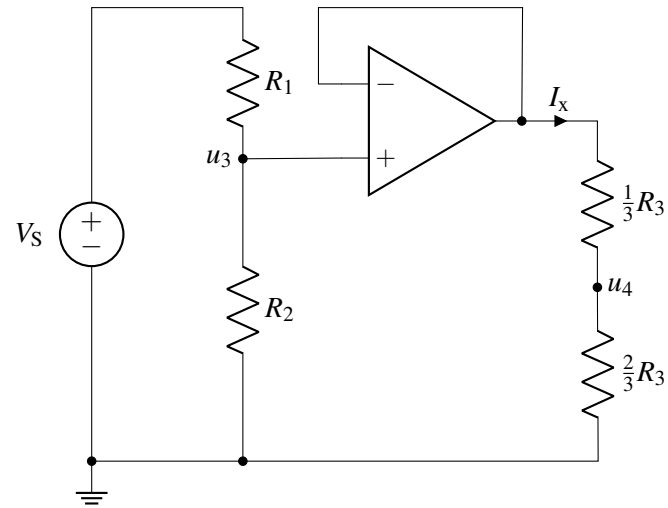


- iii. Find an expression for the voltage at u_4 as a function of V_S , R_1 , R_2 , and R_3 . Your answer should NOT include any node voltages (i.e., u_3)

- iv. Find an expression for the current I_x as a function of V_S , R_1 , R_2 , and R_3 . Your answer should NOT include any node voltages (i.e., u_3).


PRINT your student ID: _____

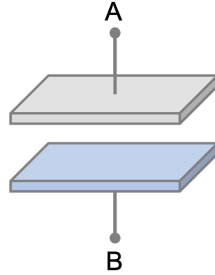4. Stacked Capacitors (11 points)

The parallel plate capacitor shown below is made up of two identical perfectly overlapping plates. The plates have length l , width w , are separated by distance d , and the dielectric material between the plates has permittivity ϵ . The capacitance formed by the two plates between nodes **A** and **B** is C_0 .



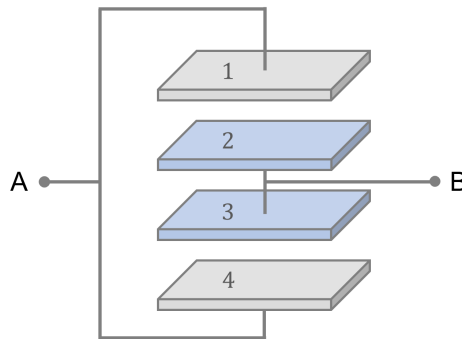- (a) (3 points) Now assuming these same specifications, we stack 4 plates on top of each other. The plates are perfectly aligned vertically and the spacing between each plate is d . We connect node **A** to the top and bottom plates and node **B** to the middle two plates.




- i. Is there capacitance formed between the 2nd and 3rd plates?

Yes


No

- ii. Draw an equivalent capacitor circuit representing this physical arrangement of plates. Label nodes **A** and **B**.

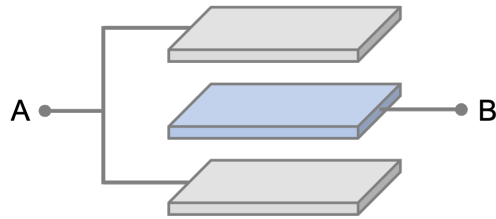
- (b) (2 points) From the capacitor configuration in part (a), we combine the two middle plates into a single plate. Assume all other specifications are the same as in part (a). Find C_{eq} , the equivalent capacitance between nodes **A** and **B**. Express your answer in terms of C_0 (the equivalent capacitance of just two plates).



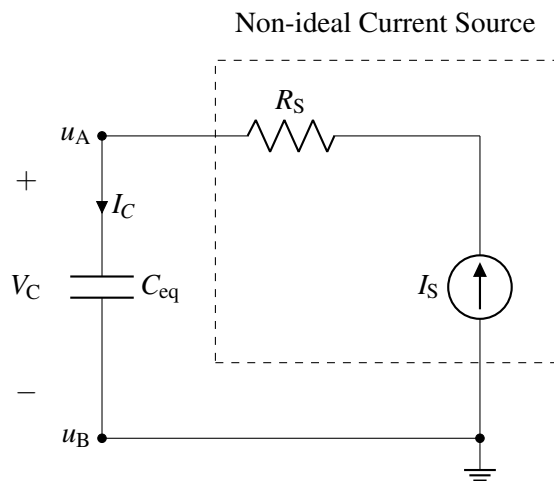- (c) (6 points) We want to charge up our stacked capacitor, C_{eq} , with a current source. Unfortunately our current source is non-ideal, and instead can be modeled by an ideal current source, I_S , and a resistor, R_S , in series. The capacitor C_{eq} is uncharged at time $t = 0$.



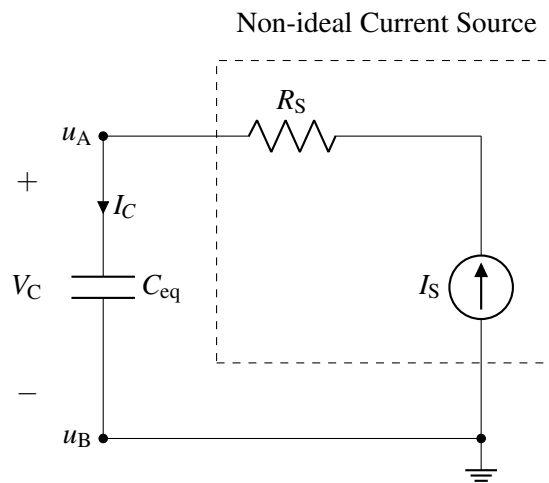- i. Find an expression for the power dissipated by resistor R_S in terms of C_{eq} , I_S , R_S , and t .




- ii. Find the node voltage $u_A(t)$ in terms of C_{eq} , I_S , R_S , and t .

- iii. Find an expression for the power delivered to the capacitor C_{eq} in terms of C_{eq} , I_S , R_S , and t . The capacitor voltage V_C and current I_C are labeled for you.

PRINT your student ID: _____


5. A Plain Circuit (16 points)

Consider the following circuit

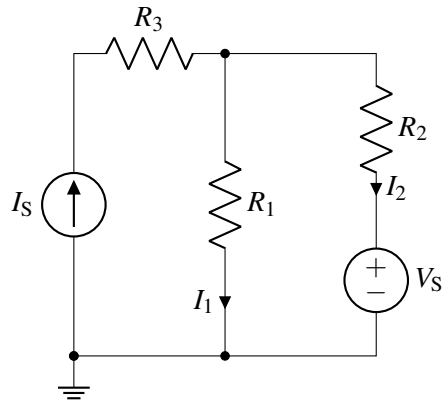

- (a) (3 points) Find the current I_1 passing through the resistor R_1 with the **current source turned on** and the **voltage source turned off**. Your answer must be *only* in terms of I_S , V_S , R_1 , R_2 , and R_3 .

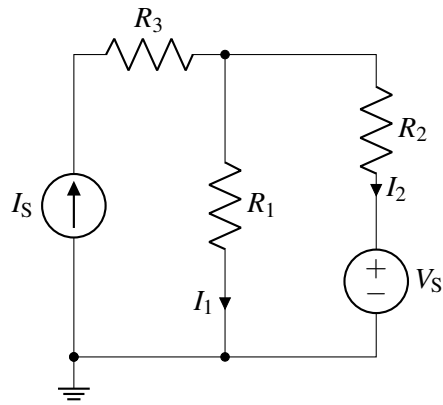
- (b) (3 points) Find the current I_1 passing through the resistor R_1 with the **current source turned off** and the **voltage source turned on**. Your answer must be *only* in terms of I_S , V_S , R_1 , R_2 , and R_3 .




- (c) (2 points) Using the principle of *superposition*, find the total current I_1 passing through the resistor R_1 when **both** the current source and voltage source are turned on. Your answer must be *only* in terms of I_S , V_S , R_1 , R_2 , and R_3 .

- (d) (2 points) Redraw the circuit but with an ammeter added to measure the current I_2 . Be sure to notate the direction of positive current for the ammeter.

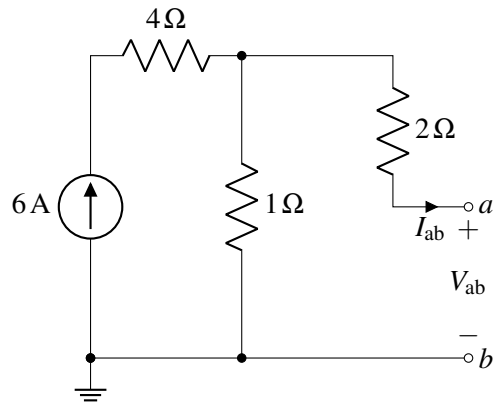- (e) (4 points) Now you want to determine the equivalent circuit seen from the voltage source V_S . You remove the voltage source from the circuit. You also now know the numerical values of the current source I_S and resistances R_1 , R_2 , and R_3 .




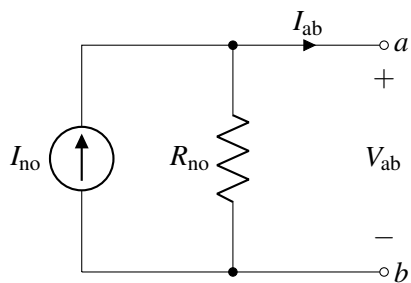
For this circuit, derive the Norton equivalent between nodes a and b . Find the Norton current, I_{no} , and the Norton resistance, R_{no} .







$$I_{no} = \boxed{} \text{ A}$$

$$R_{no} = \boxed{} \text{ } \Omega$$

 

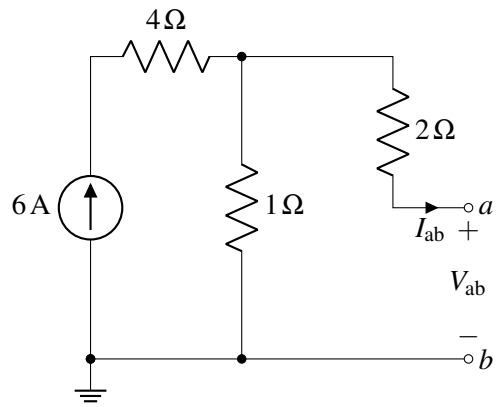

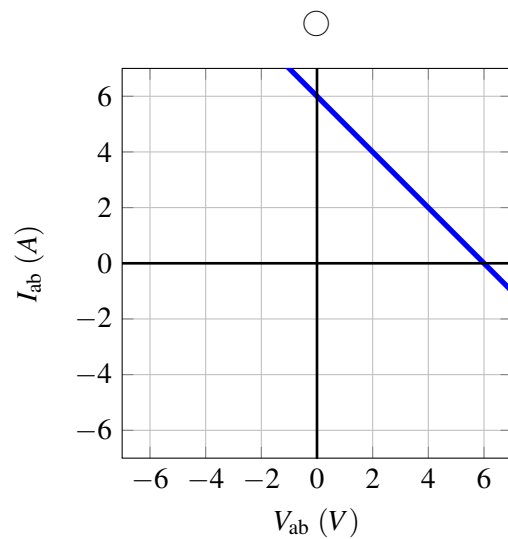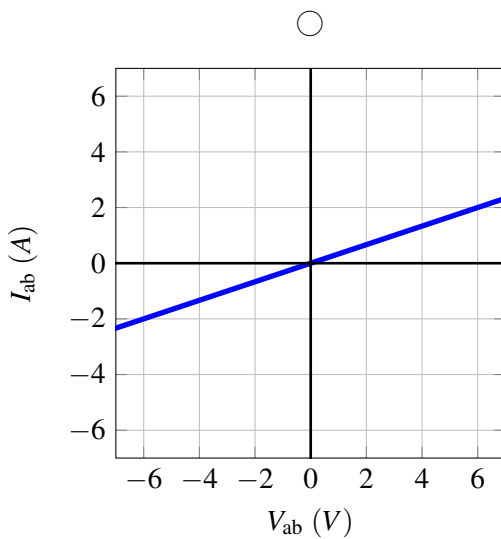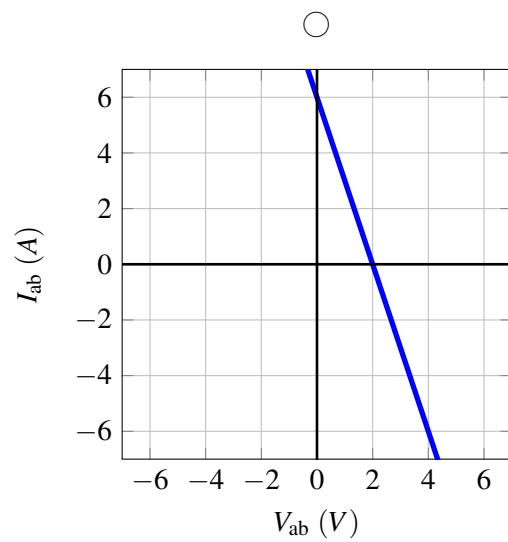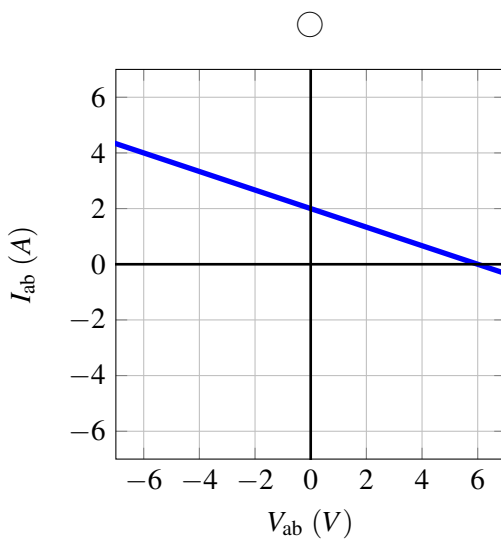
(f) (2 points) For the circuit in part (e), select the line which represents the I-V characteristic at terminals a and b (i.e., I_{ab} vs V_{ab})?



PRINT your student ID: _____

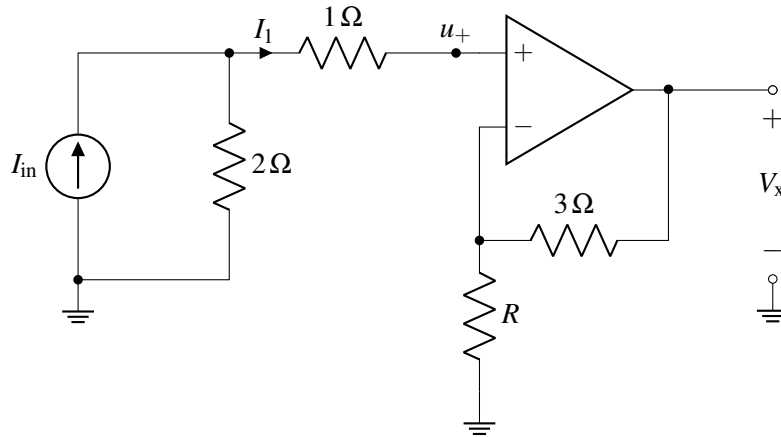6. Does The Circuit Blink? (17 points)

Consider the following circuit with an ideal op-amp



(a) (2 point) Is the op-amp configured in positive or negative feedback?

Positive feedback


Negative feedback

(b) (2 points) If $I_{in} = 1$ A, then what is value of the current I_1 ?

$$I_1 = \boxed{} \text{ A}$$

(c) (2 points) If $I_{in} = 1$ A, derive the voltage at node u_+ .


$$u_+ = \boxed{} \text{ V}$$

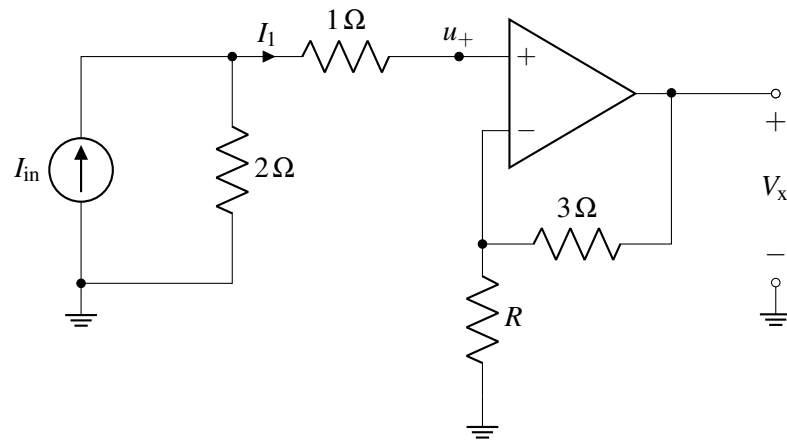



(d) (3 points) Determine the value of resistor R so that $V_x = I_{in} \cdot 5\Omega$.

$R =$ Ω

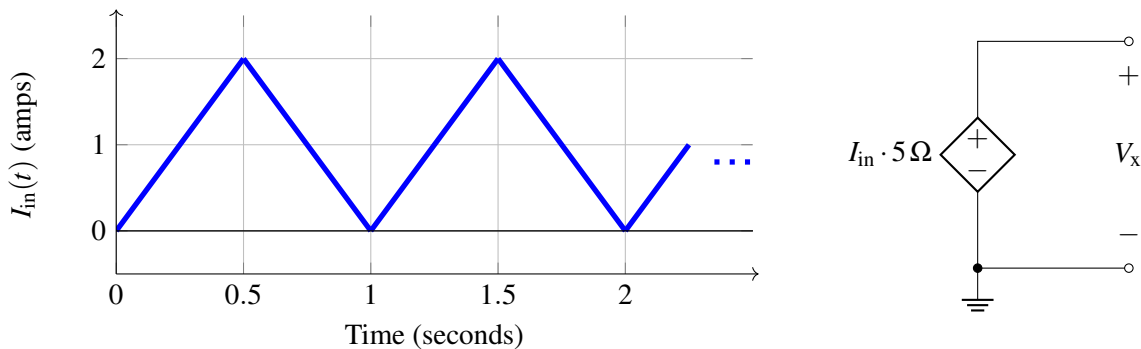(e) (8 points) Now the input current $I_{in}(t)$ has the following triangular waveform with time. Regardless of your answer to the previous parts, assume you have successfully implemented the function of the circuit: $V_x = I_{in} \cdot 5 \Omega$. Then the op-amp circuit can be represented with an equivalent circuit as shown.



Using the voltage V_x as an input, design a comparator circuit that creates an output voltage $V_{out}(t)$ alternating periodically between a low voltage $-10V$ and high voltage $+10V$ with *equal durations*. You do not have to use every element and you can use multiple of each element. **If used, also specify your chosen values of R , C , and V_{ref} for each element.** Be sure to not leave any circuit element terminals unconnected.

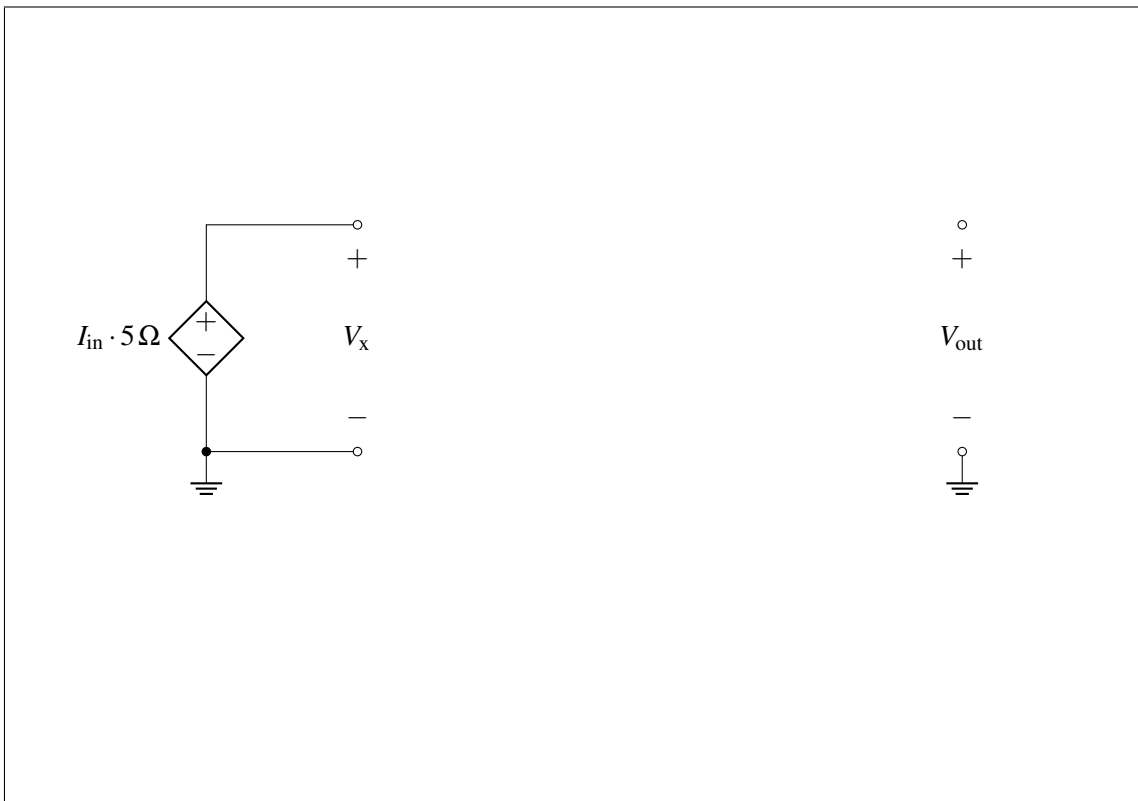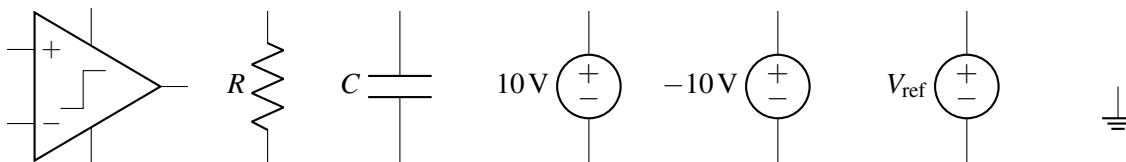

PRINT your student ID: _____

Extra page for scratchwork.
Work on this page will NOT be graded.

PRINT your student ID: _____

Extra page for scratchwork.
Work on this page will NOT be graded.

PRINT your student ID: _____

Extra page for scratchwork.
Work on this page will NOT be graded.