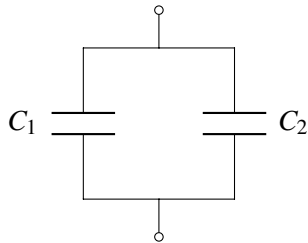



### 1. Series And Parallel Capacitors

Derive  $C_{eq}$  for the following circuits.


(a)



(b)

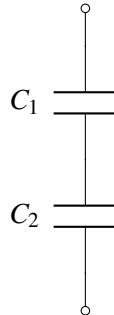

(c)

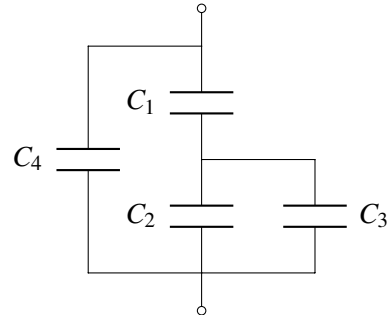

**Answer:**

(a)

$$C_{eq} = C_1 + C_2$$

We can derive this using the methods shown in lecture and in the notes. Alternatively, note that there is a more physical approach, where we consider the charges.

The total charge stored on the capacitors is  $q$  with  $q_1$  on the first capacitor and  $q_2$  on the second.

Then  $C_{eq} = \frac{q}{V} = \frac{q_1 + q_2}{V} = \frac{q_1}{V} + \frac{q_2}{V} = C_1 + C_2$ .

(b)

$$C_{eq} = C_1 \parallel C_2 = \frac{C_1 C_2}{C_1 + C_2}$$

Again, we can derive this using the methods shown in lecture and in the notes, but we will cover the more physical approach.

The voltage across the two capacitors  $V_1$  and  $V_2$  must sum to the voltage between the two terminals  $V$ . Since charge is conserved, the charge  $q$  is the same on the two capacitors. (If there is  $+q$  charge on the top plate of the top capacitor, there is  $-q$  charge on the bottom plate. To conserve charge, there is  $+q$  charge on the top plate of the bottom capacitor and thus  $-q$  charge on the bottom plate.)

Then  $\frac{1}{C_{eq}} = \frac{V}{q} = \frac{V_1 + V_2}{q} = \frac{V_1}{q} + \frac{V_2}{q} = \frac{1}{C_1} + \frac{1}{C_2}$ .


(c)

$$C_{eq} = (C_4 + (C_1 \parallel (C_2 + C_3))) = \frac{C_4(C_1 + C_2 + C_3) + C_1(C_2 + C_3)}{C_1 + C_2 + C_3}$$

### 2. Capacitance Equivalence

For the structures shown below, assume that the plates have a depth  $L$  into the page and a width  $W$  and are always a distance  $d$  apart.

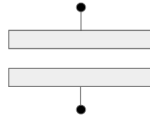
- (a) What is the capacitance of the structure shown below?



**Answer:**

The capacitance of two parallel plate conductors is given by  $C = \epsilon \frac{A}{d}$ . The cross-sectional area  $A$  is  $WL$ , so the capacitance is  $C = \epsilon \frac{WL}{d}$ .

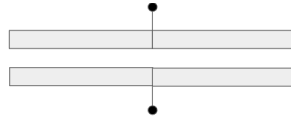
- (b) Suppose that we take two such structures and put them next to each other as shown below. What is the capacitance of this new structure?



**Answer:**

Here, we have just doubled the width of the capacitor plates. The new capacitance is  $C = \epsilon \frac{2WL}{d}$ . Notice that this is just double the capacitance from the first part.

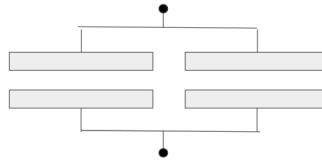
- (c) Now suppose that rather than connecting them together as shown above, we connect them with an ideal wire as shown below. What is the capacitance of this structure?



**Answer:**

Intuitively, nothing has changed here since we have just added an ideal wire between two capacitors. Thus, the answer remains  $C = \epsilon \frac{2WL}{d}$ .

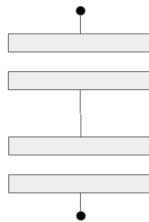
- (d) Suppose that we now take two capacitors and connect them as shown below. What is the capacitance of the structure?



**Answer:**

We know that capacitors placed in series follow the parallel rule. Thus, the overall capacitance is half the individual capacitance.

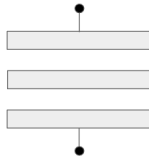- (e) What is the capacitance of the structure shown below?




**Answer:**

Notice here that we are ignoring the material in the middle. Thus, from a modeling perspective, we can think of this as the original capacitor with the distance between the plates doubled.

### 3. Current Sources And Capacitors

For the circuits given below, give an expression for  $v_{\text{out}}(t)$  in terms of  $I_s$ ,  $C_1$ ,  $C_2$ , and  $t$ . Assume that all capacitors are initially uncharged.

(a)

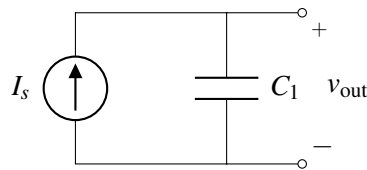


**Answer:**

$$I_s = C_1 \frac{dv_{\text{out}}(t)}{dt}$$

$$v_{\text{out}}(t) = \int \frac{I_s}{C_1} dt = \frac{I_s t}{C_1} + V_0$$

Since the capacitor is initially uncharged,  $V_0 = 0$ , so  $v_{\text{out}}(t) = \frac{I_s t}{C_1}$ .

(b)

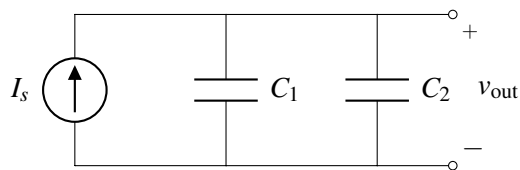


**Answer:**

We can combine the two capacitors into an equivalent capacitor with capacitance  $C_1 + C_2$ . Again,  $V_0 = 0$  because all capacitors are initially uncharged.

$$I_s = (C_1 + C_2) \frac{dv_{\text{out}}(t)}{dt}$$

$$v_{\text{out}}(t) = \frac{I_s t}{C_1 + C_2} + V_0 = \frac{I_s t}{C_1 + C_2}$$

(c)

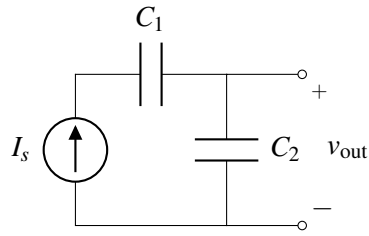


**Answer:**

By KCL, the current  $I_s$  flowing through  $C_1$  must be the current flowing through  $C_2$ .  $V_0 = 0$  because all capacitors are initially uncharged.

$$I_s = C_2 \frac{dv_{\text{out}}(t)}{dt}$$


$$v_{\text{out}}(t) = \int \frac{I_s}{C_2} dt = \frac{I_s t}{C_2} + V_0 = \frac{I_s t}{C_2}$$

(d)

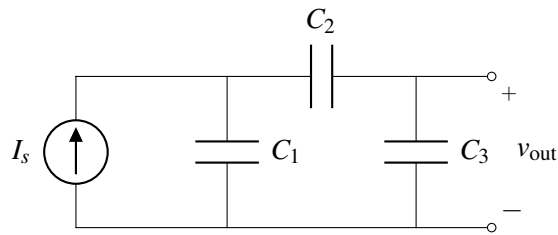


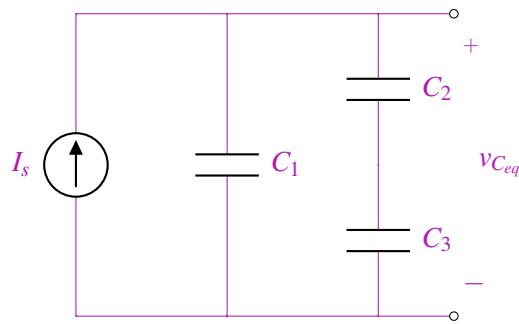**Answer:**

Instead of finding  $v_{\text{out}}$ , let's first find the voltage  $v_{C_{eq}}$  across  $C_2$  and  $C_3$ .



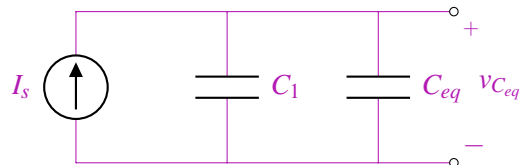To do this, we replace  $C_2$  and  $C_3$  with their equivalent capacitance  $C_{eq} = C_2 \parallel C_3 = \frac{C_2 C_3}{C_2 + C_3}$ .



From part (b), we know that to solve for  $v_{C_{eq}}$ , we can find the equivalent capacitance of  $C_1$  and  $C_{eq}$  first, which is  $C_1 + C_{eq}$ . Since the capacitors are initially uncharged,  $V_0 = 0$ .

$$v_{C_{eq}}(t) = \int \frac{I_s}{C_1 + C_{eq}} dt = \frac{I_s t}{C_1 + C_{eq}} + V_0 = \frac{I_s t}{C_1 + C_{eq}}$$

Now that we know that voltage across the equivalent capacitor  $C_{eq}$ , we can find the current flowing through the equivalent capacitor  $C_{eq}$ .

$$i_{C_{eq}}(t) = C_{eq} \frac{dv_{C_{eq}}(t)}{dt} = \frac{C_{eq}I_s}{C_1 + C_{eq}}$$

Note that the current  $i_{C_{eq}}$  is equal to the current flowing through  $C_3$  since  $C_2$  and  $C_3$  were originally connected in series.

$$i_{C_3}(t) = i_{C_{eq}}(t) = \frac{C_{eq}I_s}{C_1 + C_{eq}}$$

Since  $v_{out}$  is the voltage across the capacitor  $C_3$ , we integrate to find  $v_{out}$ . Again, since all capacitors are initially uncharged,  $V_0 = 0$ .

$$i_{C_3}(t) = C_3 \frac{dv_{out}(t)}{dt}$$

$$v_{out}(t) = \int \frac{C_{eq}I_s}{C_3(C_1 + C_{eq})} dt = \frac{C_{eq}I_s t}{C_3(C_1 + C_{eq})} + V_0 = \frac{\frac{C_2 C_3}{C_2 + C_3} I_s t}{C_3 \left( C_1 + \frac{C_2 C_3}{C_2 + C_3} \right)} = \frac{C_2 I_s t}{C_1 C_2 + C_1 C_3 + C_2 C_3}$$