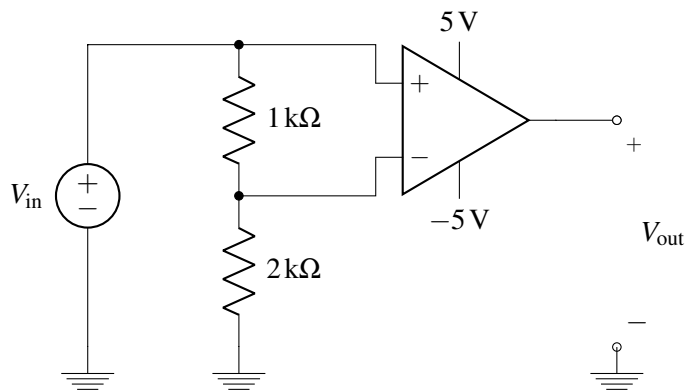


1. Op-Amps As Comparators

For each of the circuits shown below, plot V_{out} for V_{in} ranging from -10V to 10V for part (a) and from 0V to 10V for part (b). Let $A = 100$ for your plots.

(a)



Answer:

$$V_+ = V_{in}$$

$$V_- = \frac{2\text{k}\Omega}{1\text{k}\Omega + 2\text{k}\Omega} V_{in} = \frac{2}{3} V_{in}$$

$$\begin{aligned} V_{out} &= A(V_+ - V_-) + \frac{V_S^+ + V_S^-}{2} \\ &= AV_{in} \left(1 - \frac{2}{3} \right) = \frac{1}{3} AV_{in} \end{aligned}$$

The op-amp satisfies the linear relation above for $V_S^- \leq V_{out} \leq V_S^+$.

$$V_S^- \leq V_{out} \leq V_S^+$$


$$V_S^- \leq \frac{1}{3} AV_{in} \leq V_S^+$$

$$3 \frac{V_S^-}{A} \leq V_{in} \leq 3 \frac{V_S^+}{A}$$


$$3 \frac{-5\text{V}}{100} \leq V_{in} \leq 3 \frac{5\text{V}}{100}$$

$$-0.15\text{V} \leq V_{in} \leq 0.15\text{V}$$

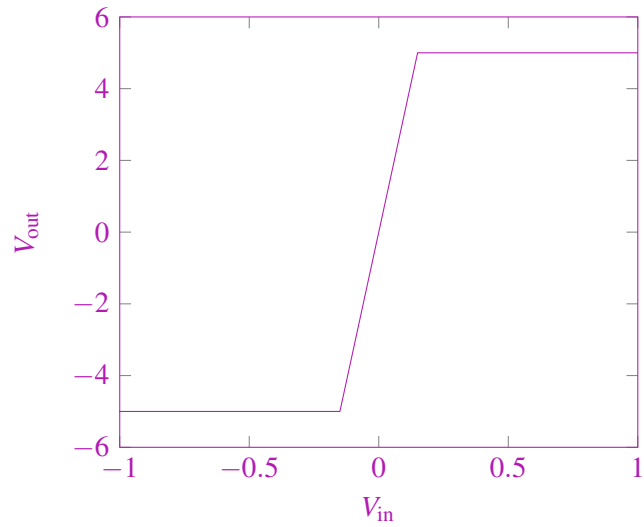The op-amp saturates outside of this range.



(b)

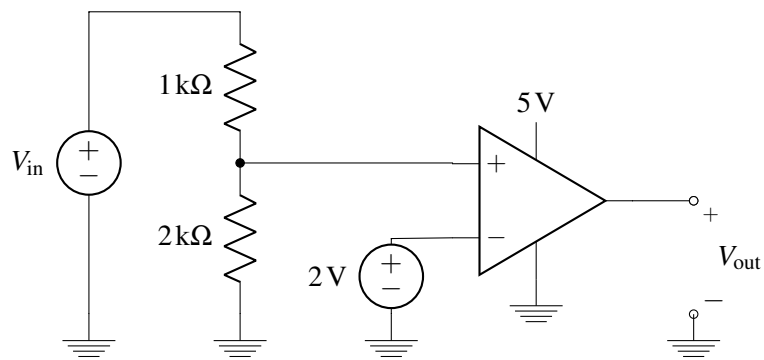

Answer:

$$V_+ = \frac{2\text{k}\Omega}{1\text{k}\Omega + 2\text{k}\Omega} V_{\text{in}} = \frac{2}{3} V_{\text{in}}$$

$$V_- = 2\text{V}$$


$$V_{\text{out}} = A(V_+ - V_-) + \frac{V_S^+ + V_S^-}{2}$$

$$= A \left(\frac{2}{3} V_{\text{in}} - 2 \right) + 2.5$$

The op-amp satisfies the linear relation above for $V_S^- \leq V_{\text{out}} \leq V_S^+$.


$$\begin{aligned}
 V_S^- &\leq V_{\text{out}} \leq V_S^+ \\
 V_S^- &\leq A \left(\frac{2}{3} V_{\text{in}} - 2 \right) + 2.5 \leq V_S^+ \\
 \frac{3}{2} \left(\frac{V_S^- - 2.5}{A} + 2 \right) &\leq V_{\text{in}} \leq \frac{3}{2} \left(\frac{V_S^+ - 2.5}{A} + 2 \right) \\
 \frac{3}{2} \left(\frac{-2.5 \text{ V}}{100} + 2 \right) &\leq V_{\text{in}} \leq \frac{3}{2} \left(\frac{5 \text{ V} - 2.5 \text{ V}}{100} + 2 \right) \\
 2.9625 \text{ V} &\leq V_{\text{in}} \leq 3.0375 \text{ V}
 \end{aligned}$$

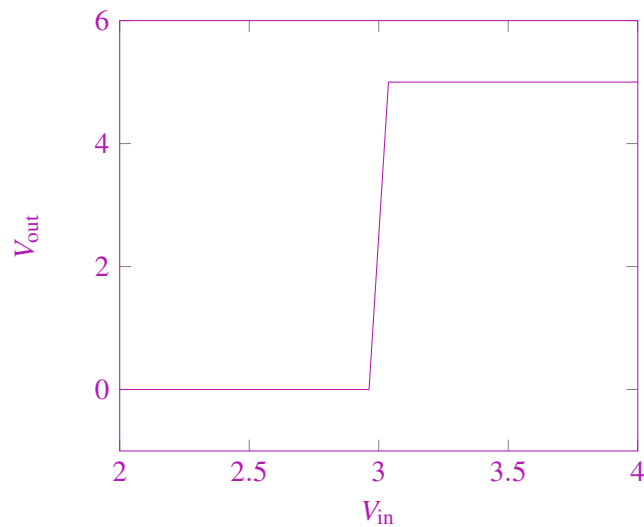The op-amp saturates outside of this range.



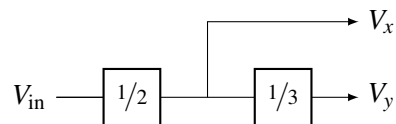2. Modular Circuits


In this problem, we will explore the design of circuits that perform a set of (arbitrary) mathematical operations. (Note that the so-called analog signal processing – where these kinds of mathematical operations are performed on continuously-valued voltages by analog circuits – is extremely common in real-world applications; without this capability, essentially none of our radios or sensors would actually work.) Specifically, let's assume that we want to implement the block diagram shown below:



In other words, we want to implement a circuit with two outputs V_x and V_y , where $V_x = \frac{1}{2} V_{\text{in}}$ and $V_y = \frac{1}{3} V_x$.


- (a) Design two voltage divider circuits that each independently would implement the two multiplications shown in the block diagram above (i.e., multiply by $\frac{1}{2}$ and multiply by $\frac{1}{3}$). Note that you do not need to include the input voltage sources in your design – you can simply define the input to each block as being at the appropriate potential (e.g., V_{in} or V_x).

Answer:

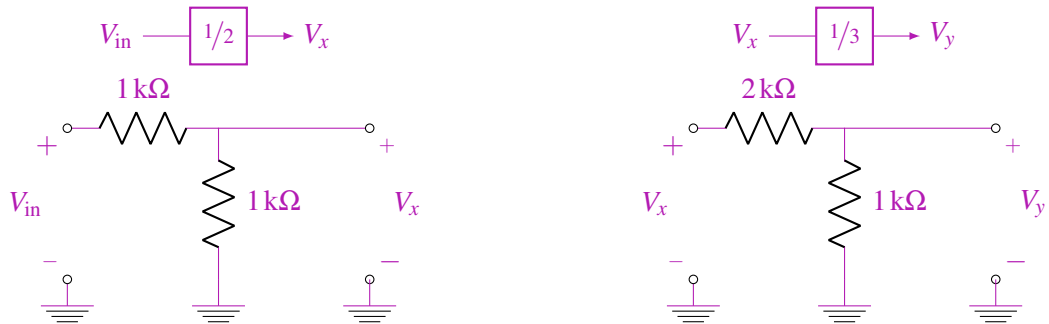

(b) Assuming that V_{in} is created by an ideal voltage source, implement the original block diagram as a circuit by directly replacing each block with the designs you came up with in part (a).

Answer:

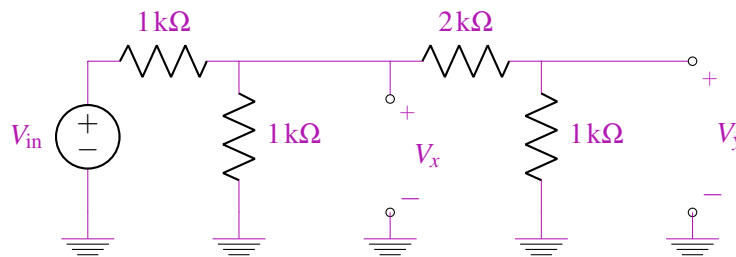

(c) For the circuit from part (b), do you get the desired relationship between V_y and V_x ? How about between V_x and V_{in} ? Be sure to explain why or why not each block retains its desired functionality.

Answer:

The relationship between V_y and V_x will be correct. The relationship between V_x and V_{in} will not be correct. The $1/3$ block will be an additional load on the $1/2$ block. Both blocks have non-zero Thevenin resistance, so the current/voltage at the load can change. Applying parallel equivalence, we get $V_x = \frac{750\Omega}{750\Omega + 1k\Omega} \cdot V_{in} = \frac{3}{7}V_{in}$.

(d) Now let's assume that we have discovered compose-able circuits that implement mathematical operations. In particular, we have these blocks that implement:


- i. $V_o = 5V_i$
- ii. $V_o = -2V_i$
- iii. $V_o = V_{i_1} + V_{i_2}$

Using just these blocks, draw the block diagram that implements:


- i. $V_o = -12V_{in_1}$
- ii. $V_o = -10V_{in_1} - 2V_{in_2}$
- iii. $V_o = -V_{in_1} + V_{in_2}$

Answer:


i.

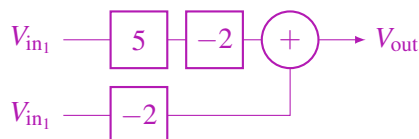

ii.

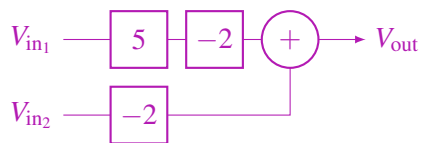


iii.

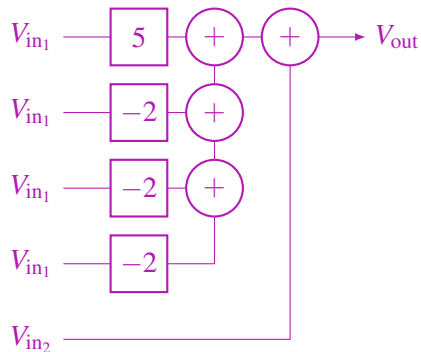

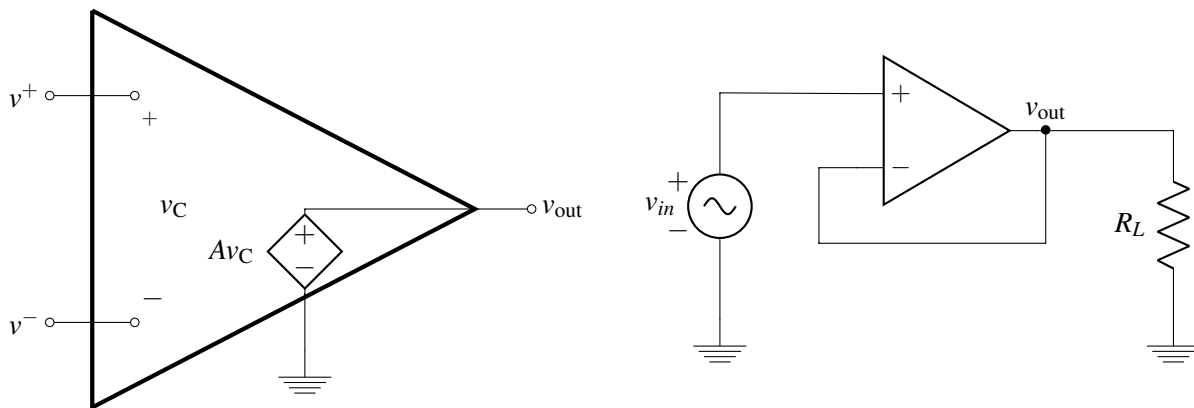3. Op-Amp Golden Rules

On the left is the equivalent circuit of an op-amp for reference.



- (a) What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are I^+ and I^-)? What are some of the advantages of your answer with respect to using an op-amp in your circuit designs?

Answer:

The v^+ and v^- terminals have no closed circuit connection between them, and therefore no current can flow into or out of them. This is very good because we can connect an op-amp to any other circuit, and the op-amp will not disturb that circuit in any way because it does not load the circuit (it is an open circuit).

- (b) Suppose we add a resistor of value R_L between v_{out} and ground. What is the value of v_{out} ? Does your answer depend on R_L ? In other words, how does R_L affect Av_C ? What are the implications of this with respect to using op-amps in circuit design?

Answer:

Notice that v_{out} is connected directly to a controlled/dependent voltage source, and therefore v_{out} (relative to ground) will always have to be equal to Av_C regardless of what R_L is connected to the op-amp. This is very advantageous because it means that the output of the op-amp can be connected to any other circuit (except a voltage source), and we will always get the desired/expected voltage out of the op-amp.

(c) Now consider the circuit on the right. Assuming that this is an ideal op-amp, what is v_{out} ?

Answer:

Recall for an ideal op-amp in negative feedback, we know from the Golden Rules that $v^+ = v^-$. In this case, $v^- = v_{\text{out}} = v^+$.

(d) Draw the equivalent circuit for this op-amp and calculate v_{out} in terms of A , v_{in} , and R_L . Does v_{out} depend on R_L ? What is v_{out} in the limit as $A \rightarrow \infty$?

Answer:

Notice that the op-amp can be modeled as a voltage-controlled voltage source. Thus, we have the following equation:

$$\begin{aligned}v_{\text{out}} &= A(v_{\text{in}} - v_{\text{out}}) \\v_{\text{out}} + Av_{\text{out}} &= Av_{\text{in}} \\v_{\text{out}} &= v_{\text{in}} \frac{A}{1+A}\end{aligned}$$

Thus, as $A \rightarrow \infty$, $v_{\text{out}} \rightarrow v_{\text{in}}$. This is the same as what we get after applying the op-amp Golden Rules.

Notice that output voltage does not depend on R . Thus, this circuit acts like a voltage source that provides the same voltage read at v^+ without drawing any current from the terminal at v^+ . This is why the circuit is often referred to as a “unity gain buffer,” “voltage follower,” or just “buffer.”