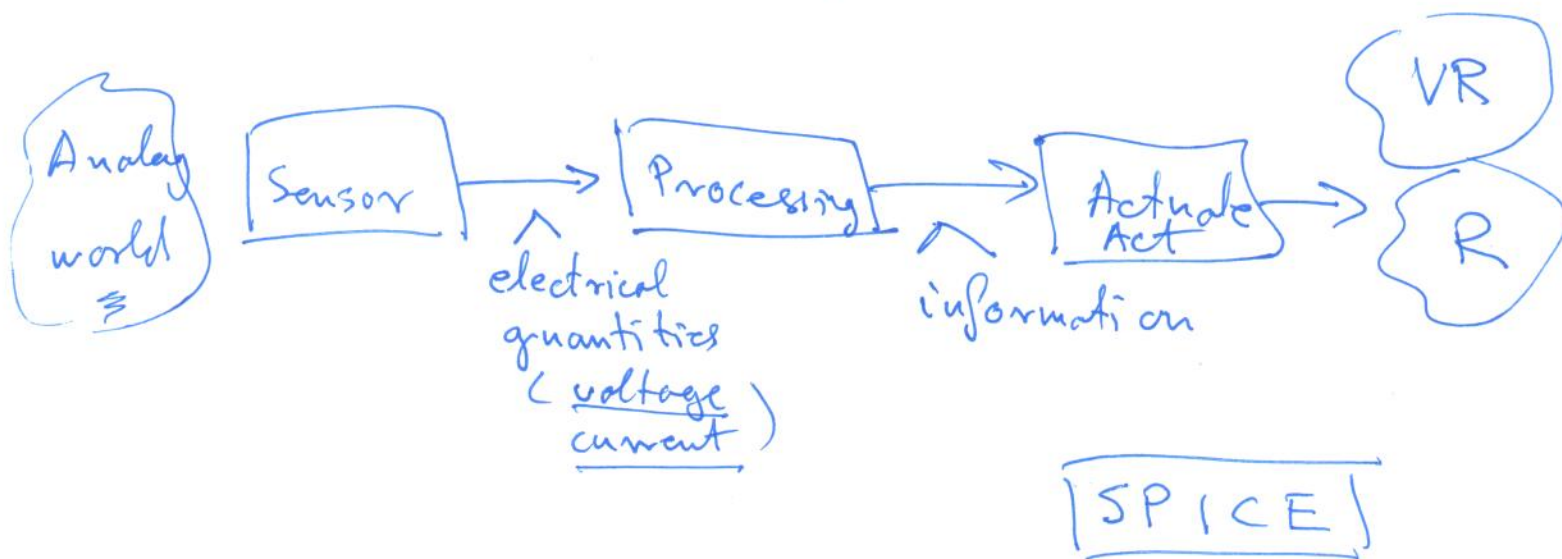


61

2/20/18 (in Lecture)

EE16A

# EE16A Module 2 - Lecture 1




## Electrical circuit analysis (tool)

<u>Quantities</u>	<u>Analytical Symbol</u>	<u>Units</u>
Voltage	V	Volts [V]
Current	I	Amps [A]
Resistance	R	Ohms [ $\Omega$ ]

Circuit diagram (collection of elements, where each element has some voltage across it and some current through it)



② Key circuit elements:

① wire

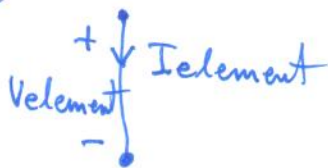


$$V_{element} = 0$$

$$I_{element} = ?$$

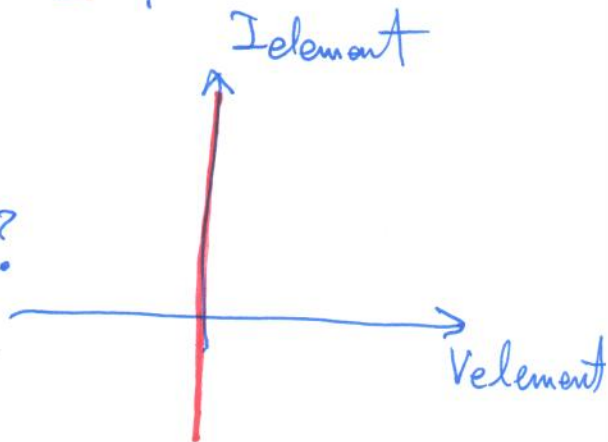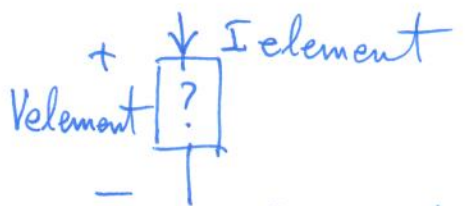


② Resistor

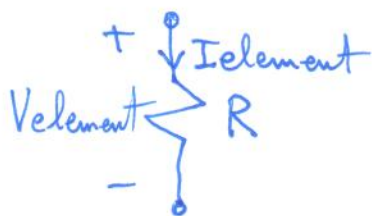


Ohm's Law

$$V_{element} = I_{element} \cdot R$$

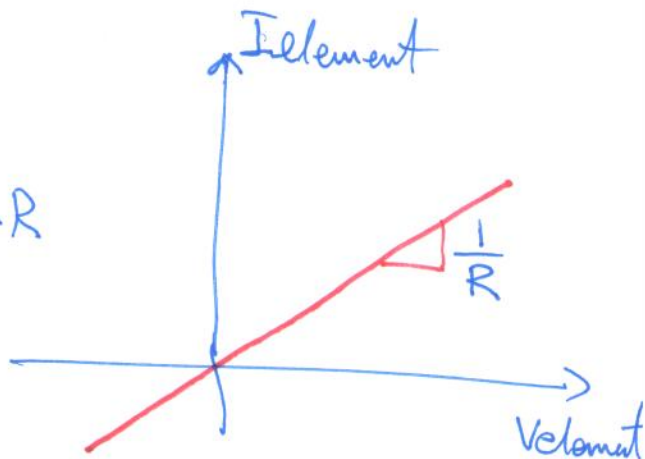


③ "open" circuit

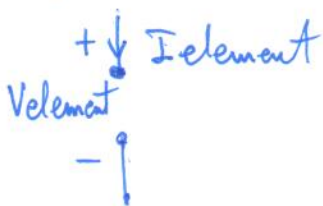


$$I_{element} = 0$$

$$V_{element} = ?$$

(set by the rest of the circuitry)

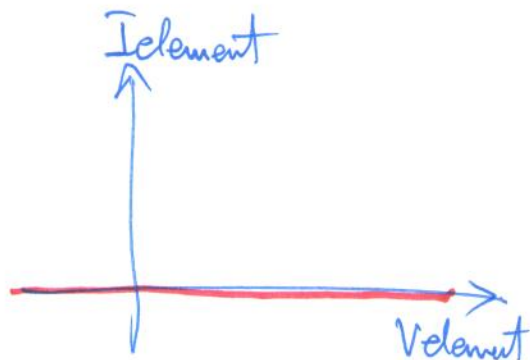


④ Voltage source:

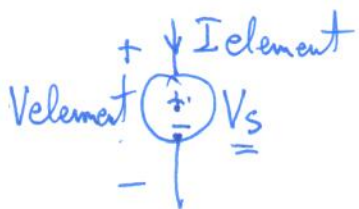

$$V_{element} = V_s$$


$$I_{element} = ?$$

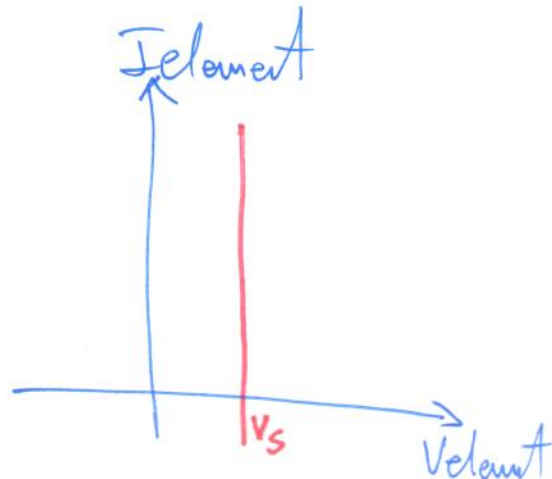

63


5

Current source:

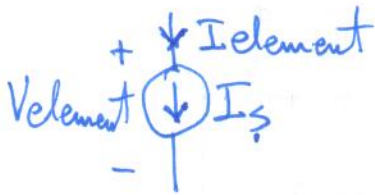

$$I_{element} = I_s$$


$$V_{element} = ?$$

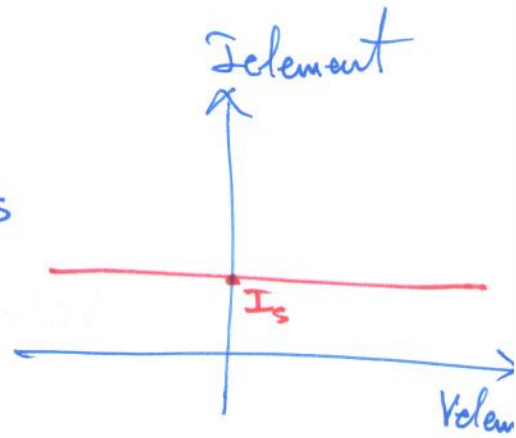

V<sub>element</sub> and I<sub>element</sub> can be positive or negative


Rules for circuit analysis:

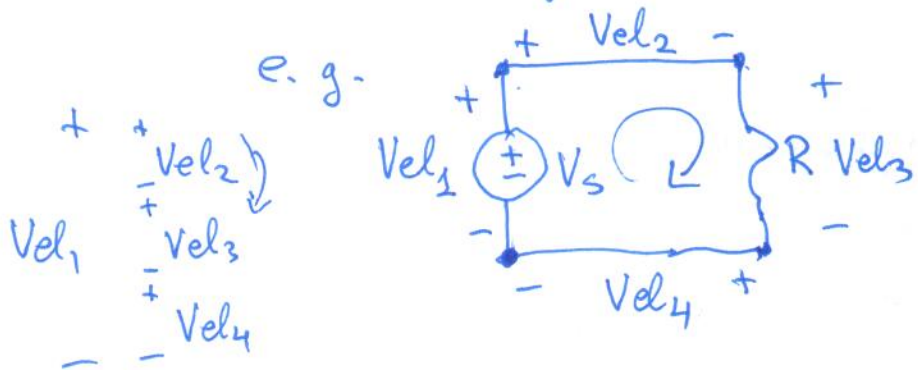① KVL: sum of voltages across the elements in a loop = 0



$$V_{el1} - V_{el2} - V_{el3} - V_{el4} = 0$$

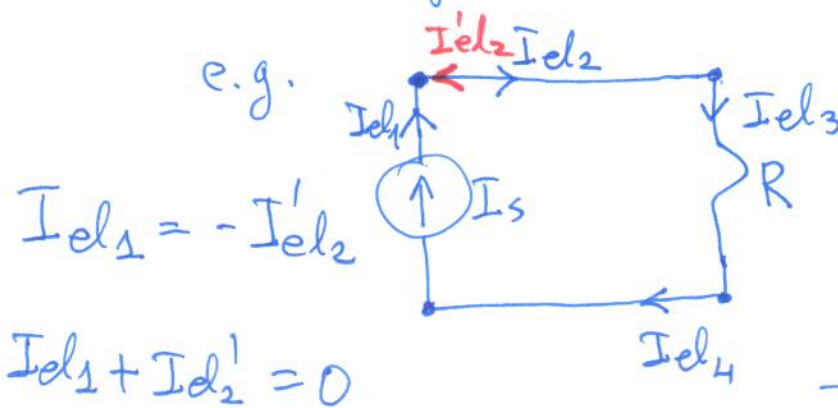② KCL: The current flowing into any junction must equal the current flowing out.



$$I_{el1} = -I'_{el2}$$

$$I_{el1} + I_{el2}' = 0$$


$$I_{el1} = I_{el2}$$

$$I_{el2} = I_{el3}$$


$$I_{el3} = I_{el4}$$

$$\rightarrow I_{el1} = I_{el4}$$

$$I_{el5} + I_{el6} = I_{el}$$

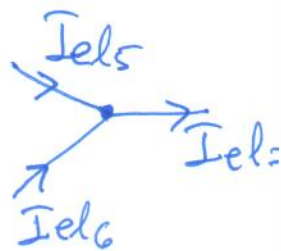


(24)

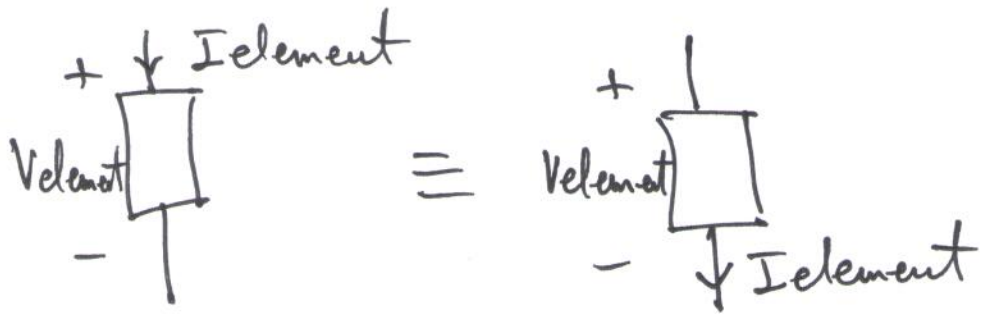

- passive sign convention

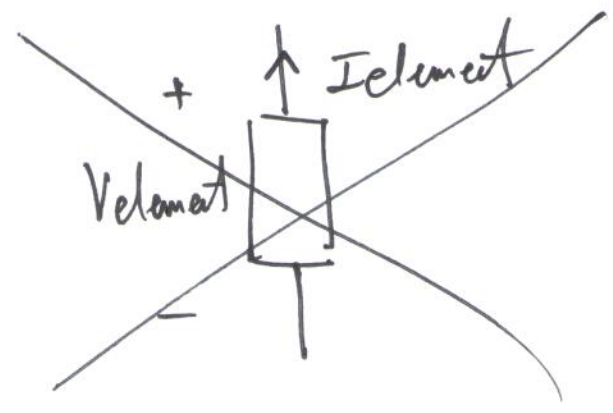
$I_{element}$  goes into a +  
or out of a - terminal





# Circuit analysis algorithm: "nodal analysis"


e.g. circuit (given)

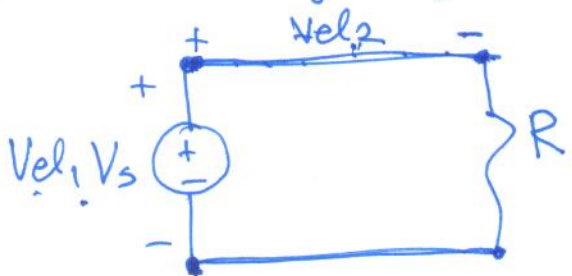

node has the same "potential"


Note 11 has a 4-element example

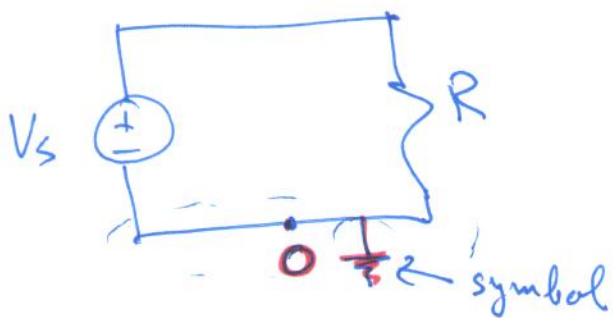Step 1: Pick a "reference" node and label it as "0". All voltages measured relative to this node.




$\frac{1}{\infty}$  "ground"

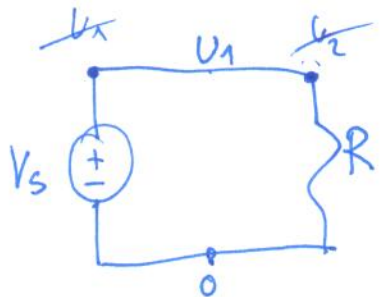Step 2: Label all remaining nodes as  $V_i$ 's [ $V_1, \dots, V_m$ ]




Step 3: Label all branch currents with  $I_m$  [ $I_1, \dots, I_k$ ]

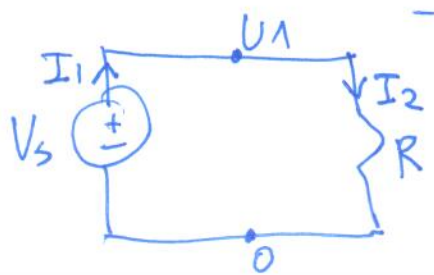- Arbitrarily pick direction of  $I_m$  ↑ unknowns



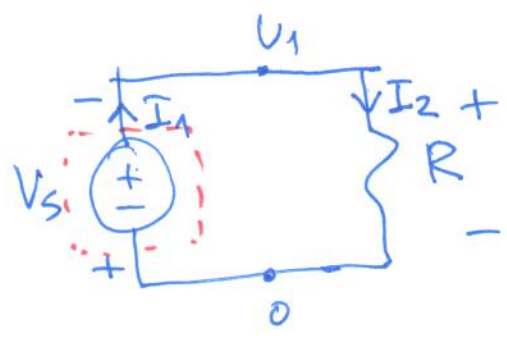66 **step 4**: Add + labels on each element following the "passive sign" convention. (independent of what is in the element)



**step 5**:

$$A \vec{x} = \vec{b}$$


$$\vec{x} = \begin{bmatrix} I_1 \\ \vdots \\ I_k \\ U_1 \\ \vdots \\ U_n \end{bmatrix}$$

$$\vec{b} = \begin{bmatrix} b_1 \\ \vdots \\ b_{k+n} \end{bmatrix}, A_{k+n \times k+n}$$

$$\vec{x} = \begin{bmatrix} I_1 \\ I_2 \\ U_1 \end{bmatrix}$$

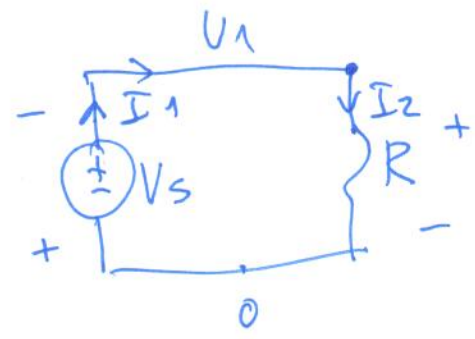**step 6**:


Use KCL to fill as many rows of A as possible (lin indep) #nodes - 1



$$I_1 = I_2$$

$$\begin{bmatrix} 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \end{bmatrix}$$

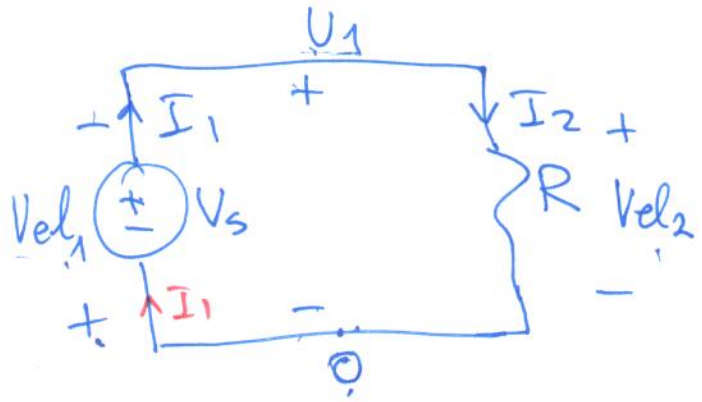step 7: Use I-V relationships for each element to fill the rest of the A matrix



Voltage source:

$Vel_1 = -V_s$        $-U_1 = -V_s$   
 $U_1 = V_s$

~~$Vel_1 = U_1 = -Vel_1$~~

Resistor:

$Vel_2 = I_2 \cdot R$     Ohm's law  
 $U_1 = Vel_2$

$\left. \begin{array}{l} U_1 = I_2 \cdot R \\ U_1 - I_2 R = 0 \end{array} \right\}$

$$\begin{bmatrix} 1 & -1 & 0 \\ 0 & 0 & 1 \\ 0 & -R & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \\ V_s \\ 0 \end{bmatrix}$$

$1 \cdot U_1 - R I_2 = 0$

$U_1 = V_s, \quad I_2 = \frac{V_s}{R}, \quad I_1 = \frac{V_s}{R}$

Note 11