




2/24/18



EE 16A Touchscreen Lecture 2

- Today:
- Review ckt analysis (voltage divider example)
 - Touchscreen construction
 - Modeling
 - Analysis + Modeling to design touchscreen
-

12

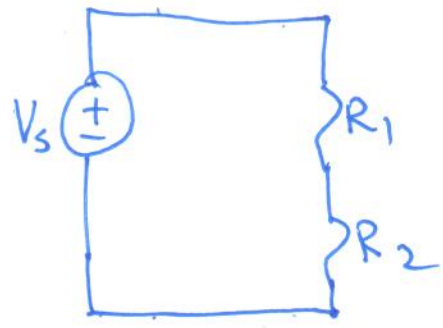

step 1

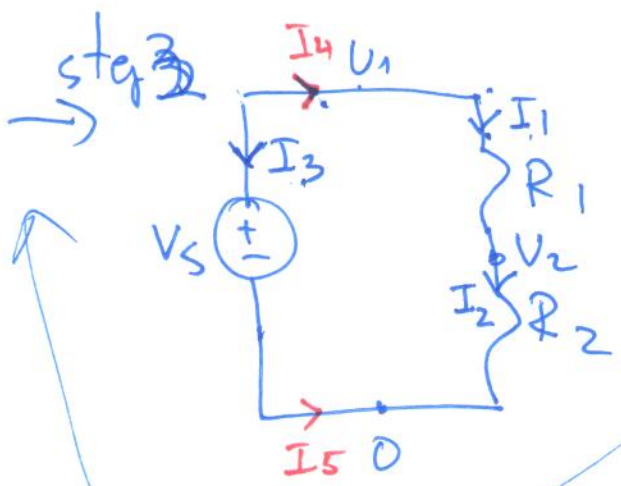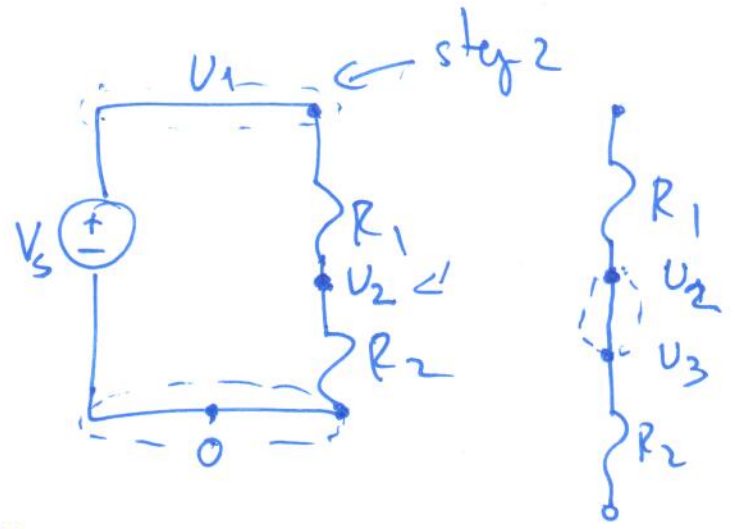


tricky
step 4

label currents in branches

label element voltages

$$I_3 + I_u = 0 \Rightarrow I_u = -I_3$$

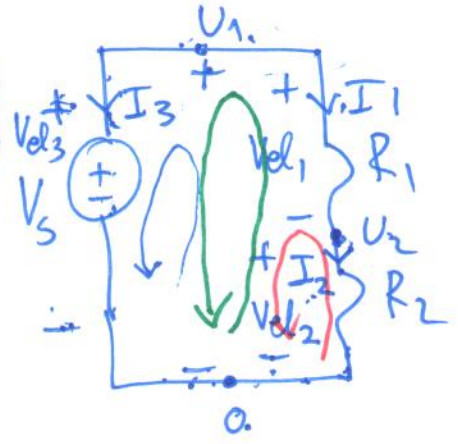

by "passive-sign" convention

step 5

$$\vec{x} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ U_1 \\ U_2 \end{bmatrix}$$

step 6

KCL

$$I_1 + I_3 = 0 \quad (1)$$

$$I_1 = I_2 \Rightarrow I_1 - I_2 = 0 \quad (2)$$

step 7

$$V_{el3} = V_s$$

$$V_{el1} = I_1 R_1 ; V_{el2} = I_2 R_2$$

$$U_1 - V_{el3} = 0 \Rightarrow U_1 = V_{el3} \Rightarrow \boxed{U_1 = V_s} \quad (3)$$

$$U_2 - V_{el2} = 0 \quad (4)$$

$$U_2 - I_2 R_2 = 0$$

②3 $V_1 \neq$

$$V_{e2} + V_{e1} - U_1 = 0$$

$$U_2 + V_{e1} - U_1 = 0$$


$$\boxed{U_2 + I_1 R_1 - U_1 = 0} \quad (5)$$

$$R_1 I_1 + 0 \cdot I_2 + 0 \cdot I_3 + (-1) \cdot U_1 + U_2 = 0$$

$$\begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & -R_2 & 0 & 0 & 1 \\ +R_1 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ V_s \\ 0 \\ 0 \end{bmatrix}$$

$$I_1 = \frac{V_s}{R_1 + R_2}, \quad I_2 = \frac{V_s}{R_1 + R_2}, \quad I_3 = -\frac{V_s}{R_1 + R_2}$$

$$U_1 = V_s$$

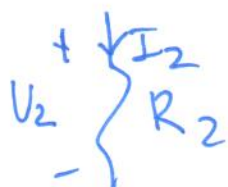

$$\boxed{U_2 = \frac{R_2}{R_1 + R_2} V_s} = \frac{V_s}{1 + \frac{R_1}{R_2}}$$

(voltage divider)

14


Resistive touchscreen:

1D

flexible conductor




not flexible conductor

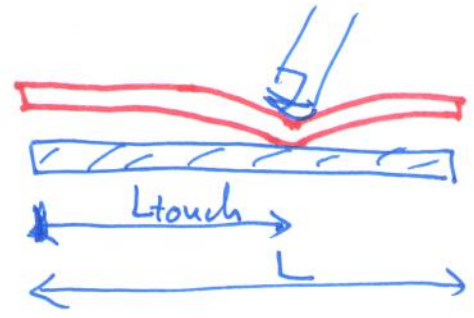

Want to measure

$$\frac{L_{touch}}{L}$$

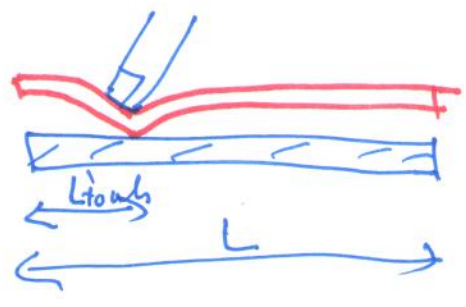

Need to convert to electrical quantities.

16A Physics

- * Charge - can be either positive or negative
basic element of electrical "stuff" (electron) flows
Unit: Coulomb [C]

* Current

Net amount of charge that passes through some cross-section area over some period of time:

$$[A] \rightarrow I = \frac{dQ}{dt} \left\{ \begin{array}{l} [C] \\ [s] \end{array} \right.$$

(25) * Voltage : Represents the energy to move a unit of charge from one point to the other

Unit of charge [C]

$$V_{AB} \quad B \rightarrow A$$


$$[V] = \frac{[J]}{[C]}$$

* Resistance : Real pieces of metal always require a certain amount of energy to be spent to allow charge to flow through

Unit [Ω]

$$V = I \cdot R$$

$$[V] = [A] \cdot [\Omega]$$

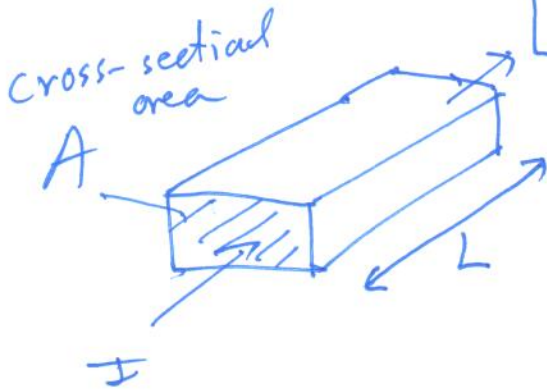

$$R = \frac{[\Omega \cdot m] [m]}{[\Omega] \cdot \frac{[m^2]}{A}}$$

↑ materials property (resistivity)

Actually :



$$R_2 = \rho \cdot \frac{L_{\text{touch}}}{A}$$


$$R_1 = \rho \cdot \frac{L_{\text{rest}}}{A}$$

Model :



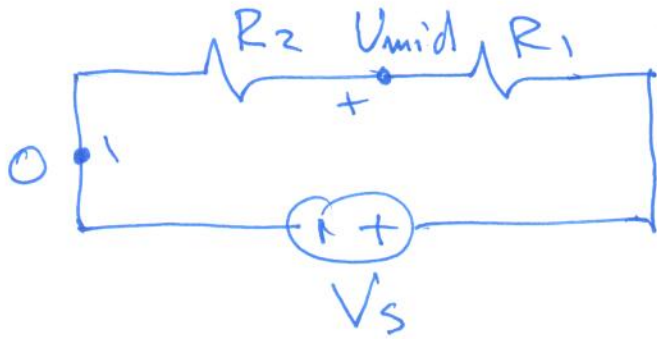(26)

Build a circuit using this model to measure $\frac{L_{touch}}{L}$ as an electrical quantity (voltage)



$$V_{mid} = \frac{R_2}{R_1 + R_2} \cdot V_s$$

$$V_{mid} = \frac{\sigma \cdot \frac{L_{touch}}{A}}{\sigma \cdot \frac{L_{rest}}{A} + \sigma \cdot \frac{L_{touch}}{A}} \cdot V_s$$

$$V_{mid} = \frac{L_{touch}}{L} \cdot V_s$$

always measure $\frac{L_{touch}}{L}$ regardless of the material

What I really have :

