

(1)

EE16A Touchscreen Module - Lecture 4

* Superposition

* Equivalence

Goal: Want to design interesting systems
→ give insight.

Reminder:

Circuit analysis objective:

Find $\vec{x} = \begin{bmatrix} I_1 \\ \vdots \\ I_m \\ U_1 \\ \vdots \\ U_k \end{bmatrix}$ for some ckt matrix A

and $\vec{b} = \begin{bmatrix} I_{s1} \\ \vdots \\ I_{sl} \\ V_{sl+1} \\ \vdots \\ V_{sm+k} \end{bmatrix}$

~~$A \cdot \vec{x} = \vec{b}$~~

$\vec{x} = A^{-1} \vec{b}$

→ and $\boxed{I_i} = \underbrace{\alpha_1 I_{s1}} + \dots + \underbrace{\alpha_l I_{sl}} + \underbrace{\alpha_{l+1} V_{sl+1}} + \dots + \underbrace{\alpha_{m+k} V_{sm+k}}$


$\underline{U_i} = \beta_1 I_{s1} + \dots + \dots + \underbrace{\beta_{m+k} V_{sm+k}}_{U_i}$

(2)


$$I_i = \underbrace{I_{i,1}}_{\alpha_1 I_{S1}} + \dots + I_{i,l} + \underbrace{I_{i,l+1}}_{\alpha_{l+1} V_S} + \underbrace{I_{i,m}}_{\alpha_m V_S}$$




$$V_S = 0 \Rightarrow$$

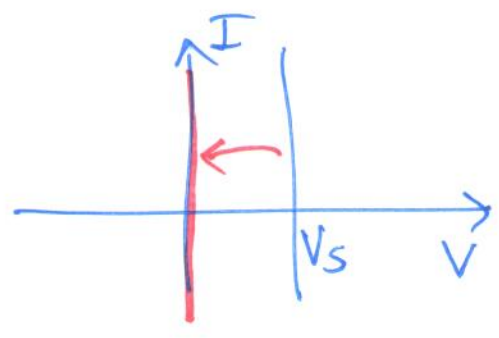


wire

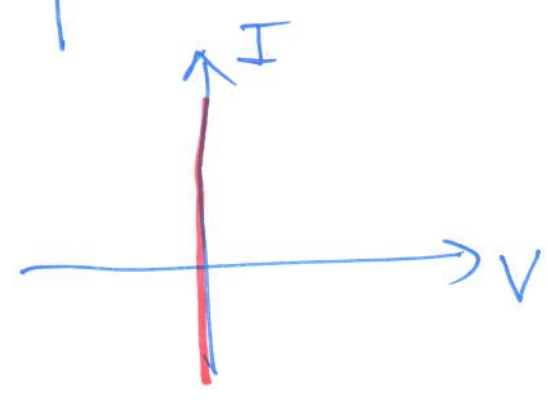

$$I_S = 0 \Rightarrow$$

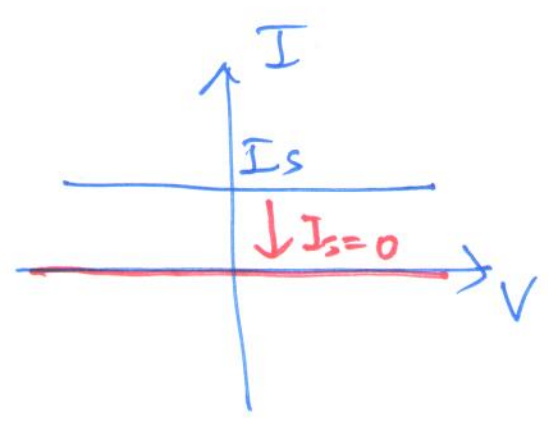


open-circuit

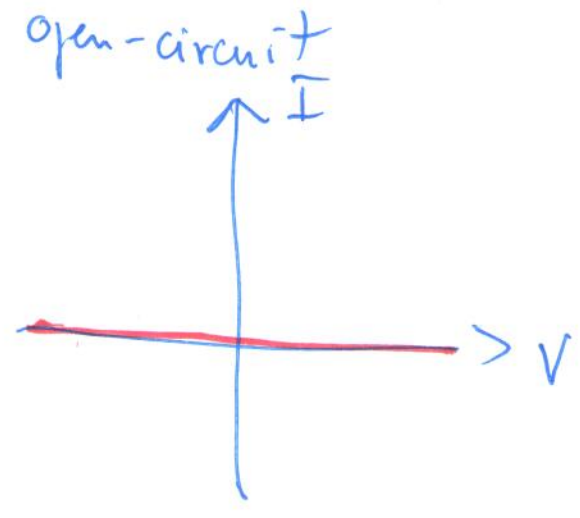


⑬ Superposition: Find I's and V's by turning on one source at a time and solving the det.

Example: voltage summer

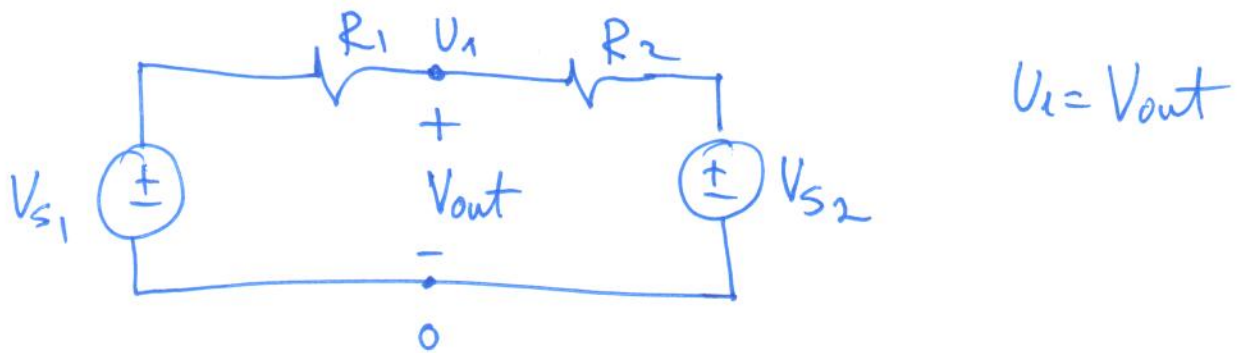

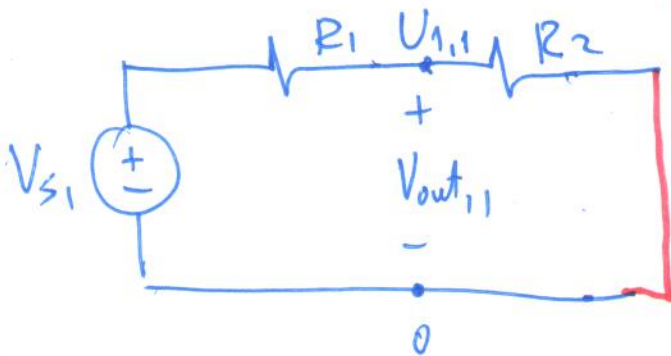
step 1: Compute a response to $V_{s1} \Rightarrow \underline{V_{s2} = 0}$



(voltage divider) 😊

$$V_{out,1,1} = \frac{R_2}{R_1 + R_2} V_{s1}$$

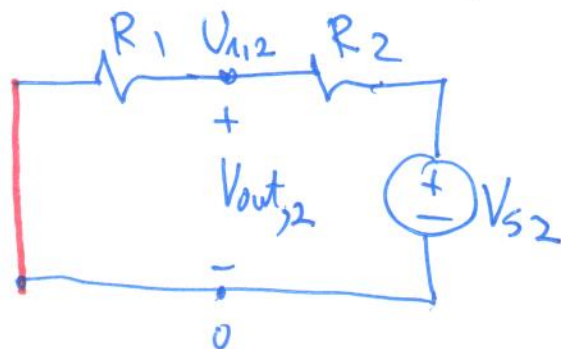step 2: Compute a response to $V_{s2} \Rightarrow \underline{V_{s1} = 0}$



voltage divider 😊


$$V_{out,2,2} = \frac{R_1}{R_1 + R_2} \cdot V_{s2}$$

(24)



$$V_{out} = V_{out,1} + V_{out,2} = \underbrace{\frac{R_2}{R_1+R_2}}_{\alpha} V_{s1} + \underbrace{\frac{R_1}{R_1+R_2}}_{\beta} V_{s2}$$

* Equivalence

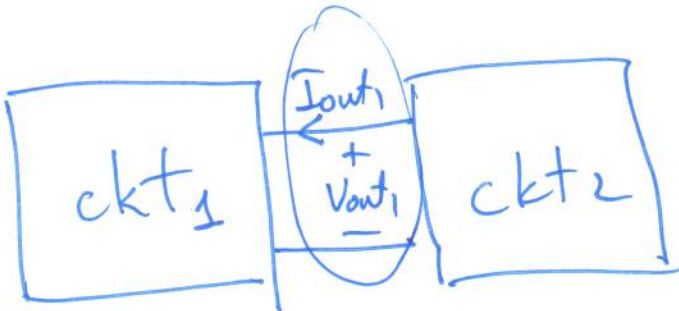
$$\frac{1}{1 + \frac{R_1}{R_2}} \quad \frac{1}{1 + \frac{R_2}{R_1}}$$



|||

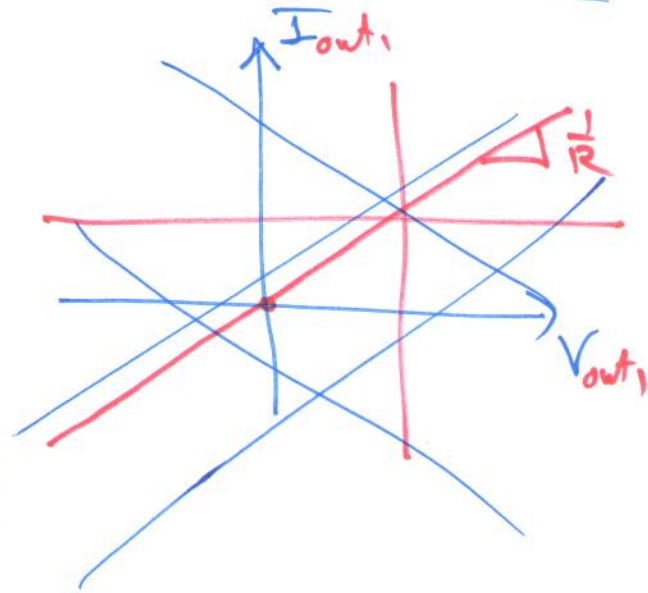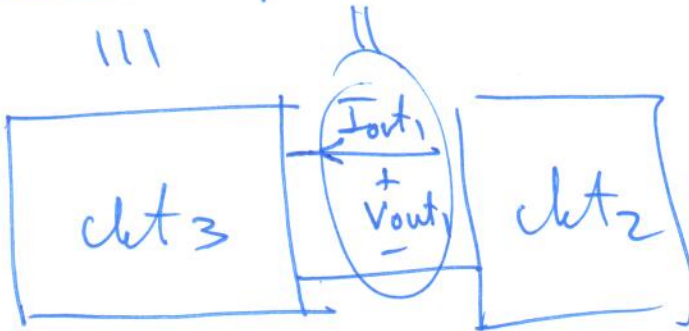



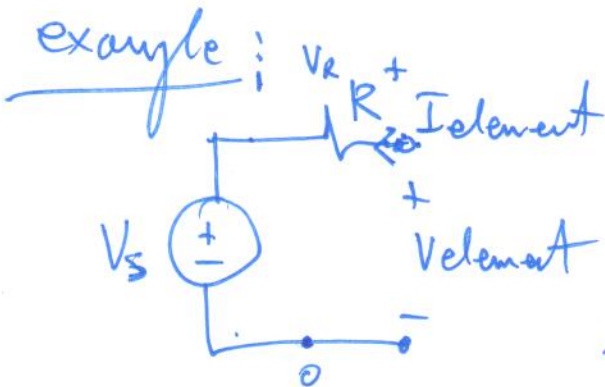
In ckt's, two elements (ckt's) are equivalent if they have the same I-V characteristic.





$$I_{element} \cdot R + V_s = V_{element}$$
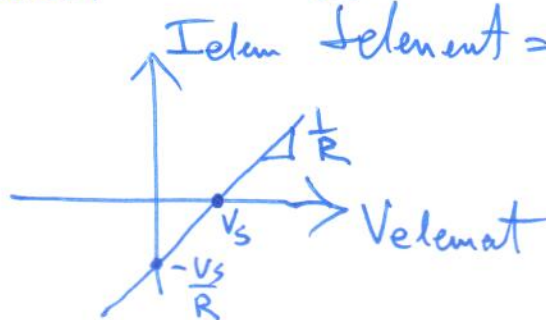
$$I_{element} = \frac{1}{R} V_{element} - \frac{V_s}{R}$$



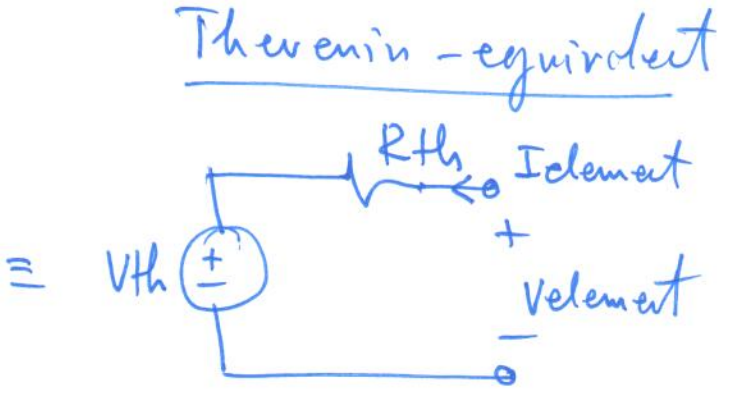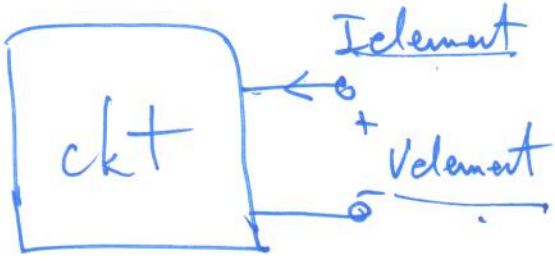

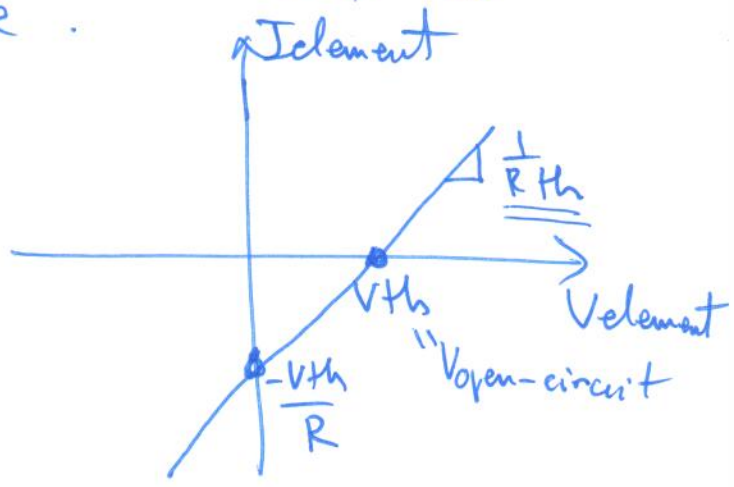
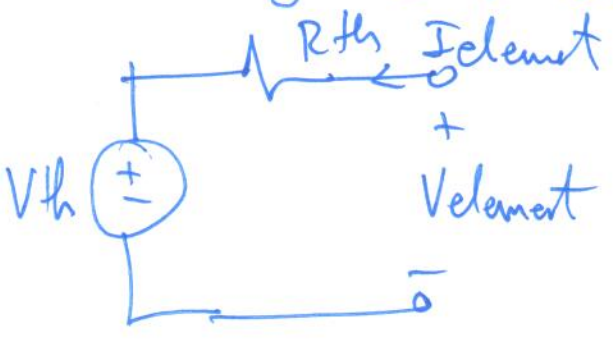
Need min of two elements (a resistor and a source) to create any I-V line.



To find V_{th} : "Connect" an "open-circuit" across two terminals and measure


$$V_{open-circ} = V_{th}$$

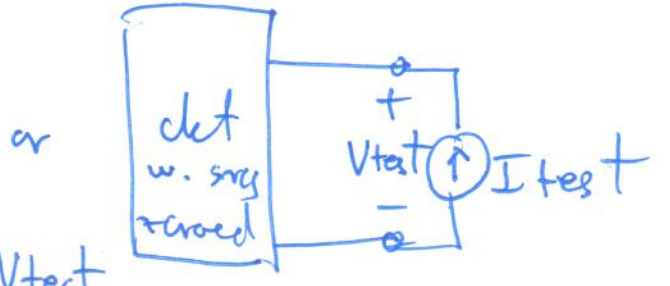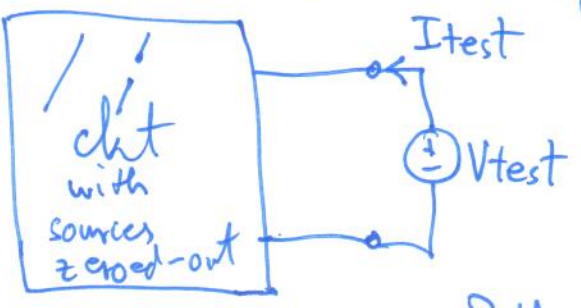To find R_{th} : Zero-out any independent sources (to find a slope)



$$R_{th} = \frac{V_{test}}{I_{test}}$$


(16)

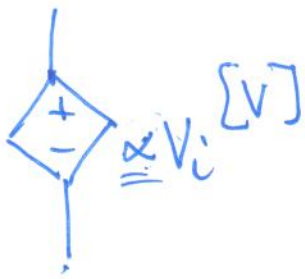

voltage-controlled voltage source



VCVS

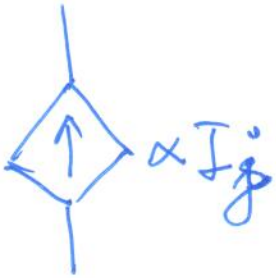


current-controlled current source

CCCS




VCCS


CCVS

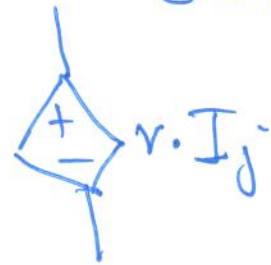


Ex 1

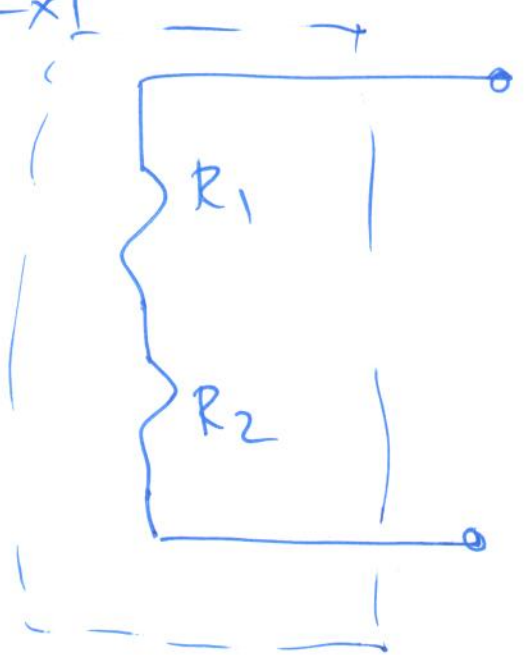

=>

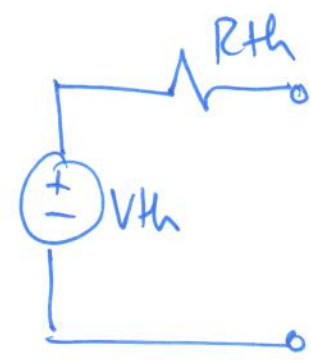


step 1:

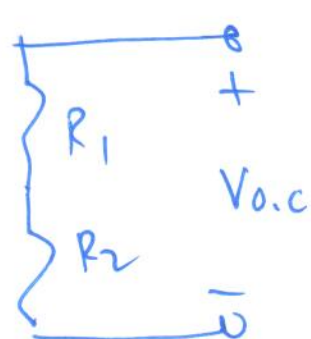

$$V_{o.c} = 0 \Rightarrow V_{th} = 0$$

step 2:

No sources =>

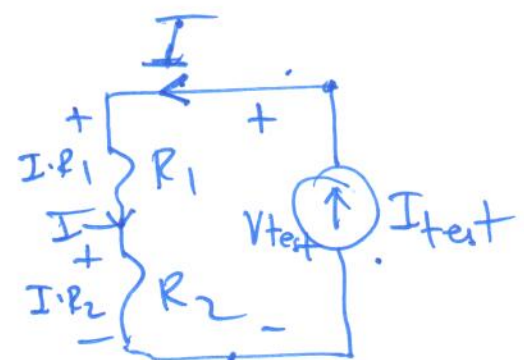



$$V_{test} = I_{test} (R_1 + R_2)$$

$$= \underbrace{I_{test}}_{I_{test}} \cdot R_1 + \underbrace{I_{test}}_{I_{test}} \cdot R_2 = I_{test} \cdot (R_1 + R_2)$$

$$R_{th} = \frac{V_{test}}{I_{test}} = R_1 + R_2$$


"in series" means that the same current flows through the elements

Q8

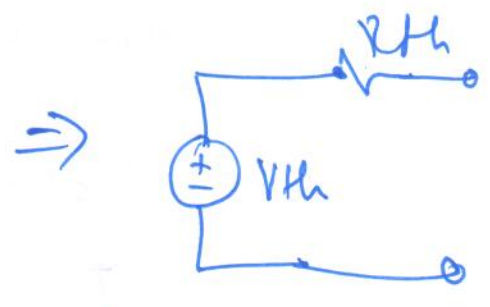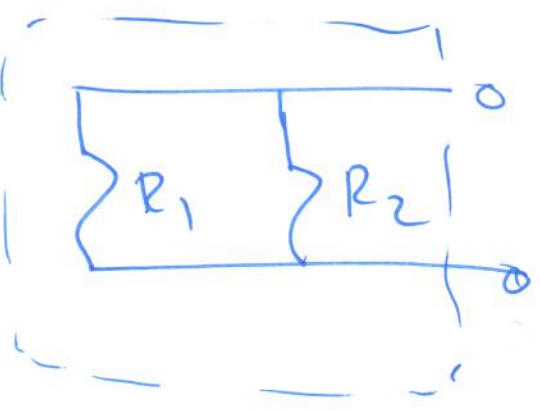

step 1: $V_{th} = 0$

step 2:

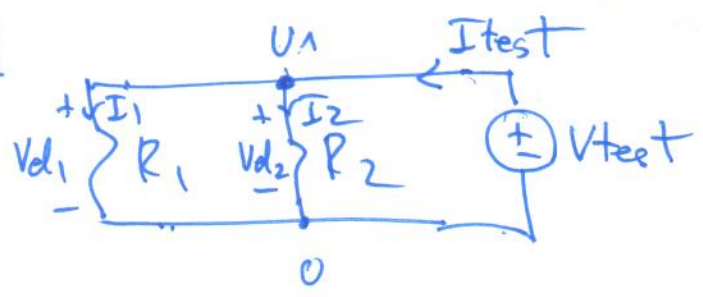

$$U_1 = V_{test}$$

$$V_{e1} = U_1 \Rightarrow I_1 = \frac{U_1}{R_1}$$


$$V_{e2} = U_1 \Rightarrow I_2 = \frac{U_1}{R_2}$$

$$I_{test} = I_1 + I_2 = \frac{V_{test}}{R_1} + \frac{V_{test}}{R_2}$$

$$= V_{test} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= V_{test} \left(\frac{R_2 + R_1}{R_1 R_2} \right)$$
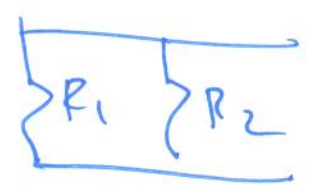
$$R_{th} = \frac{V_{test}}{I_{test}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$



parallel operator

"in parallel" means voltage across them is the same.