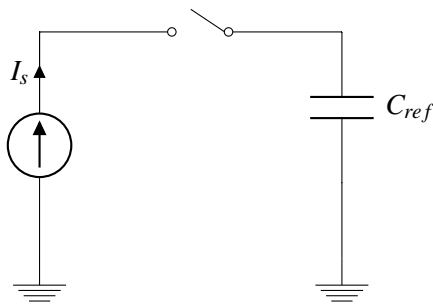


## Design Example Continued


Continuing our analysis for “countdown timer” circuit.



We know for a capacitor  $C$ :


$$I = C \frac{dV}{dt} \quad (1)$$

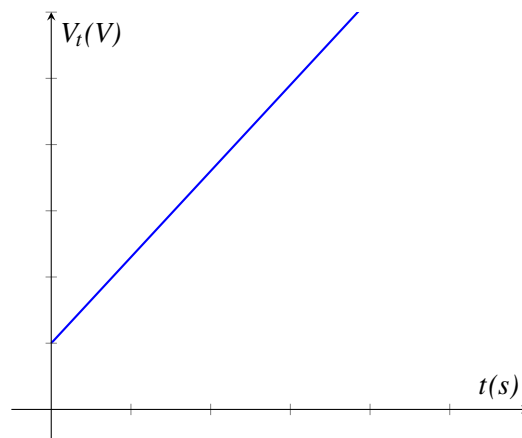There is a linear relationship between the voltage across capacitor  $V(t)$  and charging time  $t$ .




When a button is pressed, we want to turn on some circuit after 2s. Given that voltage is linearly dependent on charging time, we can use a comparator and a reference voltage  $V_{ref}$  to decide if 2s has already passed

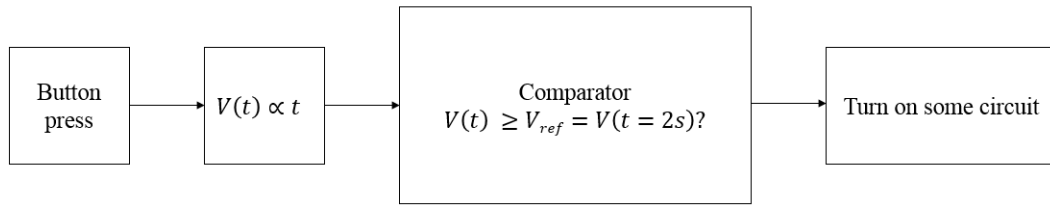after the button press to decide whether or not to turn on some circuit.




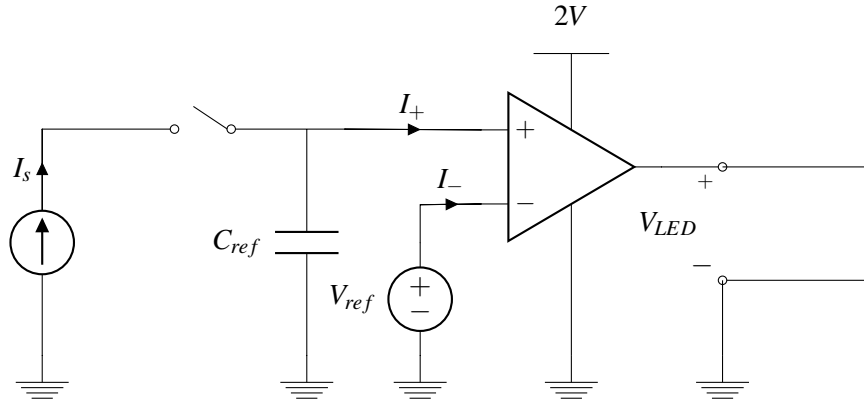Adding an op-amp comparator and a voltage source  $V_{ref}$  to the “countdown timer” circuit:



Obviously,  $V_{ref}$  should be set equal to the voltage of  $C_{ref}$  after charging for 2s. After 2s since the button is pressed, if the voltage across  $C_{ref}$  becomes higher than  $V_{ref}$ , the comparator outputs 2V to the output of the op-amp to turn on the LED.

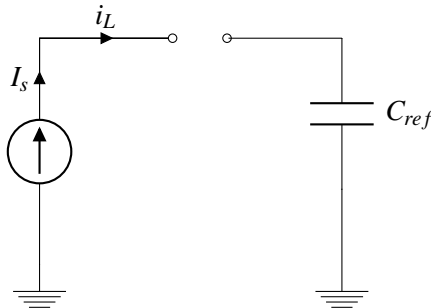
**Step 4: design verification** Now, let’s actually analyze the design completely to make sure it works. Before the button is pressed, the circuit on the current source side looks like:




According to KCL,

$$I_s = I_L \quad (2)$$

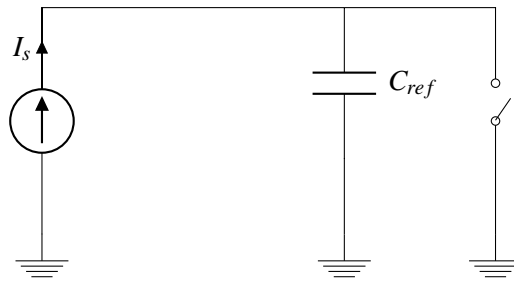
$I_s$  is the constant current supplied by the current source,  $I_L$  is the current flow into the switch. Before touch,  $I_L$  must equal 0 since there is an open circuit. However, the current source guarantees that  $I_s$  is nonzero. It is very easy to see that mathematically this is problematic, how do we solve the problem? We can add another switch in the circuit:



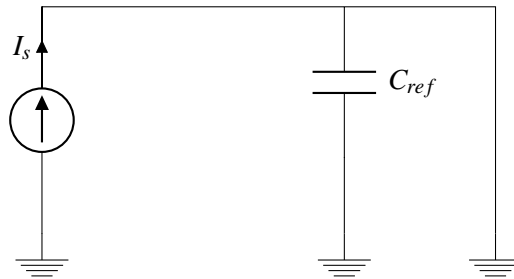Before touch, the switch is on and can be replaced by a wire:



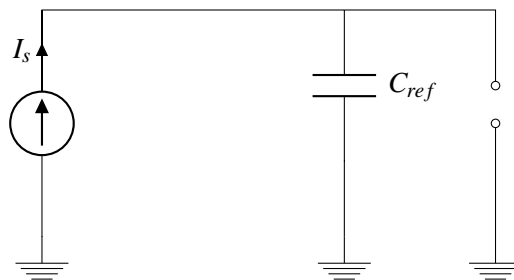After touch, the switch is off and can be replaced by an open circuit:



In either cases, there is a loop in the circuit for  $I_s$  to flow. Now, there is a remaining mystery to be answered, how do we build that current source?

## 20.1 “Almost” current source

In this section, we will use resistors, voltage sources and op amps to build a current source. We know by Ohm’s law,

$$I = \frac{V}{R} \quad (3)$$


If we have a voltage source  $V_s$ , we can scale it by a resistance value  $R$ , then we should get a constant current  $I_s$ .

Now let’s use our design procedures to build a current source.

**Step 1** restate design goal: we want to build a current source that can output constant current regardless of whatever elements we hook up to it.

**Step 2** Let's now take a voltage source and connect it to a resistor to output a current:

**Attempt #1**

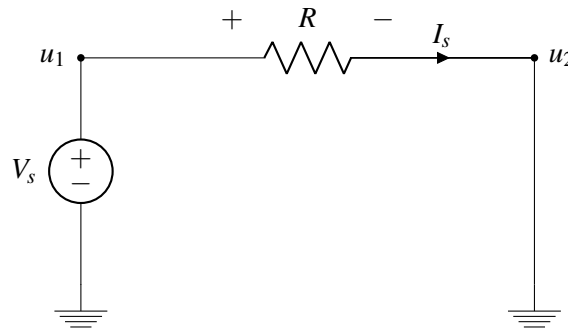


In the above circuit,

$$u_1 = V_s \quad (4)$$


$$I_s = \frac{V_s}{R} \quad (5)$$

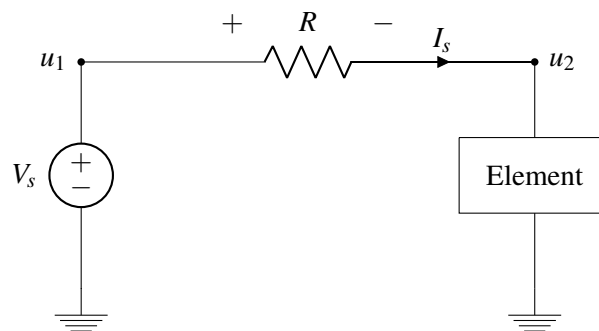However, if we hook up an element between  $u_2$  and ground, we can tell immediately that the current through  $R_s$  is no longer the constant  $I_s = \frac{V_s}{R}$ .



Recall that it is important to guarantee a constant current output from the current source regardless of the element added to the circuit.

**Attempt #2** Although our attempt 1 has failed, we have learned an important lesson: if we can somehow set  $u_2$  to  $0V$  without physically connecting it to ground. The current through  $R$  will always equal  $\frac{V_s}{R}$  ( $I_R = \frac{u_1 - u_2}{R} = \frac{V_s - 0}{R}$ )! According to golden rule #2, we can set both  $V_+$  and  $V_-$  to  $0V$  if an op amp circuit is in negative feedback. Indeed, we will now use an op amp to build a current source!

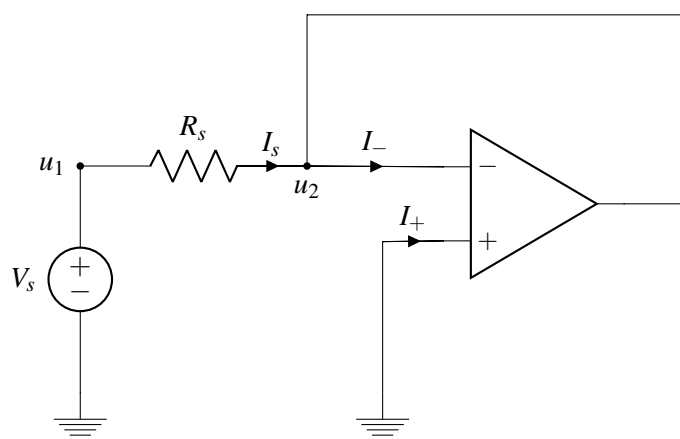

According to golden rules:

$$I_- = 0 \tag{6}$$

$$V_- = V_+ = 0V \tag{7}$$


We also know that the current across  $R$  will always be:

$$I_s = \frac{u_1 - u_2}{R} \tag{8}$$


Solving the above equations, we can get the value of  $I_s$ :

$$I_s = \frac{V}{R} \tag{9}$$

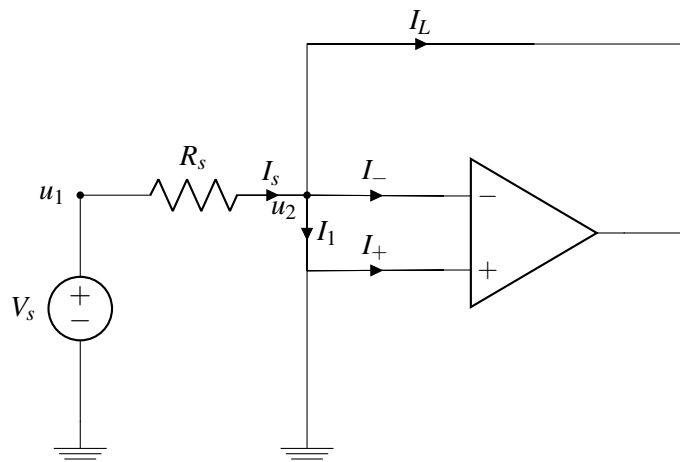By setting  $u_2$  ( $V_-$ ) to  $0V$  by using a negative feedback circuit, we have successfully built a current source! It is important to keep in mind setting  $u_2$  to  $0V$  by using a negative feedback circuit is very different from physically connecting the node of  $u_2$  to ground. If we physically connect  $u_2$  to ground by adding a wire between  $V_-$  and  $V_+$ :



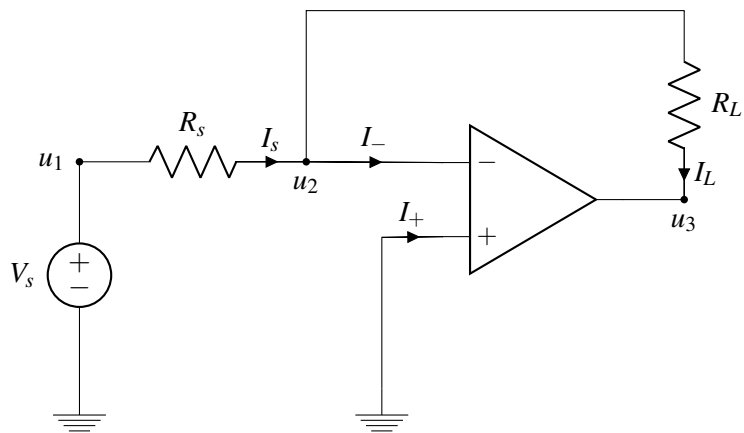If we physically connect both  $V_-$  and  $V_+$  to ground,  $I_L$  will become  $0A$  because it is shorted by the wire between  $V_-$  and  $V_+$ . Instead, now we have  $I_1 = I_s$ . So we must not physically connect  $V_-$  to ground. Let's now hook up a resistor  $R_L$  to the circuit and prove that current flow through  $R_L$  is constant:



According to KCL:


$$I_L = I_s = \frac{V}{R_s} \quad (10)$$

From  $I_L$  equation, we can see immediately that  $I_L$  is not affected by changes in  $R_L$ . How does the circuit maintain the constant current flow through  $R_L$ ?


The op-amp outputs a negative  $V_{out}$  to maintain a constant current flow through  $R_L$ . In other words, the voltage drop across  $R_L$  is always given by

$$V_{R_L} = \frac{V}{R_s} \times R_L \quad (11)$$

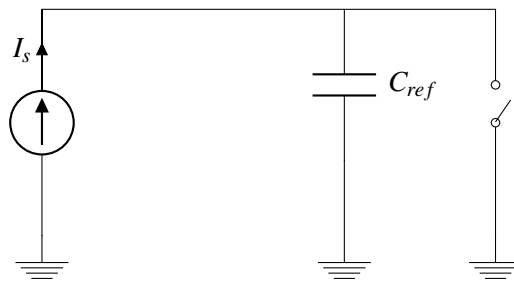Now let us plug in the current source to the following circuit:




The circuit becomes:

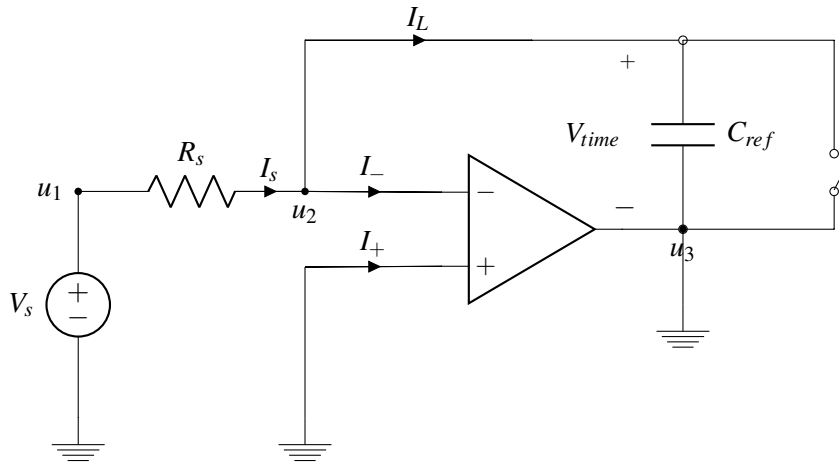

Now  $u_3$  is connected to ground. By doing this, the voltage across  $C_{ref}$  becomes:

$$V_{time} = u_2 - u_3 = 0V - 0V = 0V \quad (12)$$

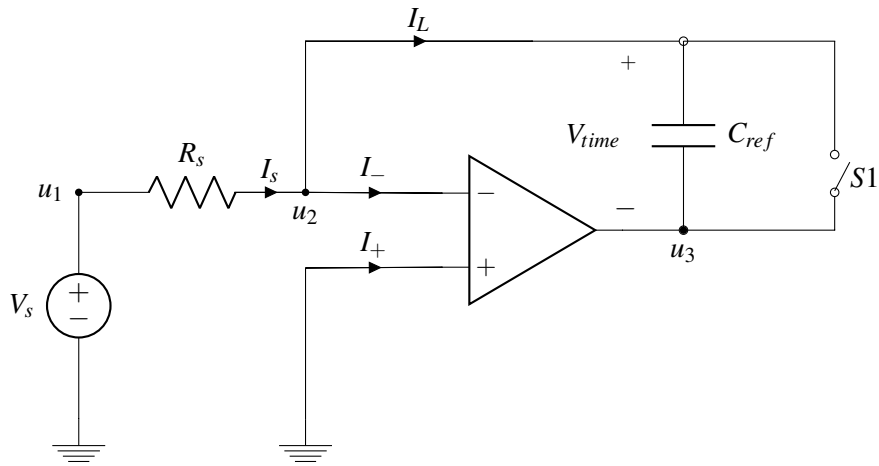There is even a worse problem, recall that there is an controlled voltage source inside the op-amp, this op-amp wants to set  $u_3$  to some nonzero value  $A \cdot V_c$  but  $u_3$  is also manually connected to  $0V$ . The fix to solve this problem is to simply get rid of the ground connection.



$$I_s = C_{ref} \frac{dV}{dt} \quad (13)$$

$$I_s = C_{ref} \frac{d(u_2 - u_3)}{dt} \quad (14)$$

According to golden rule #2,  $u_2 = 0V$ .

$$I_s = C_{ref} \frac{d(0V - u_3)}{dt} = C_{ref} \frac{d(-u_3)}{dt} \quad (15)$$

Solving the above equation:

$$u_3(t) = -\frac{I_s}{C_{ref}} \times t + u_3(t=0s) \quad (16)$$

$u_3(t)$  is associated with the initial value  $u_3(t=0s)$ . Before touch, the switch  $S1$  is on, which sets  $u_3(t=0s)$  to  $0V$ . Therefore,

$$u_3(t) = -\frac{I_s}{C_{ref}} \times t = -\frac{V_s}{R_s C_{ref}} \times t \quad (17)$$

Note there is a term  $R_s C_{ref}$  in the denominator, what is the unit of  $R_s C_{ref}$ ?

$$\text{Unit for } R_s C_{ref} = \frac{V}{A} \times CV = \frac{C}{A} = \text{second} \quad (18)$$

It is good to know that this multiplication result of  $RC$  is very useful and common in the timing analysis for circuits, this is an indicator of how fast a circuit is.

There are 2 important points to keep in mind when this current source:

- Do not connect the circuit element that we want to supply the constant current to with ground externally. Doing so may force  $V_{out}$  of the op-amp to  $0V$  and lead to nonidealities.
- The circuit element we hook up to the current source must still keep the op-amp circuit in its negative feedback state. Being in negative feedback allows us to set the node  $u_2$  to  $0V$  without physically connecting it to ground and hence allows a constant current output.